

(1)

Review of The BJT

(Bipolar Junction Transistor)

Reference: Wikipedia, Neamen (Chapter 5 and Chapter 6) 1

Learning Outcome

Able to:

- ~ Describe the general **current-voltage characteristics** for both npn and pnp bipolar transistors.
- ~ Define the four **modes of operation** of a bipolar transistor.
- ~ Describe the **small-signal hybrid- π** equivalent circuit of a bipolar transistor and determine the values of the small-signal **hybrid- π parameters**.
- ~ Understand the importance of a **multistage amplifier**.

2

1.0) Transistor

1.0.1) Introduction

~ In electronics, a **transistor** is a **semi-conductor device** commonly used to **amplify or switch electronic signals**.

~ A transistor is made of a solid piece of a semiconductor material, with **at least three terminals for connection to an external circuit**. A voltage or current applied to one pair of the transistor's terminals changes the current flowing through another pair of terminals.

~ The transistor is the **fundamental building block of modern electronic devices**, and is used in radio, telephone, computer and other electronic systems. Some transistors are packaged individually but **most are found in integrated circuits**.

From: Wikipedia 3

1.0) Transistor (Cont)


1.0.2) Importance

~ The transistor is considered by many to be **the greatest invention of the 20th-century**, or as one of the greatest. It is the key active component in practically all modern electronics.


~ Although several companies each produce over a billion individually-packaged (known as *discrete*) transistors every year, the **vast majority of transistors produced are in Integrated Circuits** (often shortened to **IC**, *microchips* or simply *chips*) along with diodes, resistors, capacitors and other electronic components to produce complete electronic circuits.

From: Wikipedia 4


1.0) Transistor (Cont)

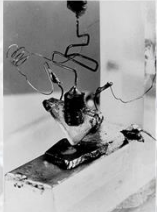

First transistor

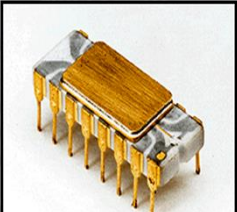

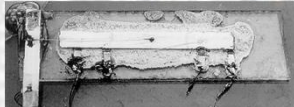The Intel 4004, it was supposed to be the brains of a calculator. Instead, it turned into a general-purpose micro-processor as powerful as ENIAC.



Integrated circuit

5

1.0) Transistor (Cont)



Intel reinvents personal computing with Ultrabooks: Ivy Bridge is built on a 22 nm (nanometer) process and has 1.48 billion 3D tri-gate transistors

From: The STAR, 15 September 2011 6

1.0) Transistor (Cont)

1.0.2) Importance (Cont)

~ A **logic gate** consists of about **twenty transistors** whereas an advanced **micro-processor**, as of **2006**, can use as many as **1.7 billion transistors** (MOSFETs). About 60 million transistors were built in 2002 ... for [every] man, woman, and child on Earth.+

~ The transistor's low cost, flexibility and reliability have made it a **ubiquitous device**.

~ Transistorized mechatronic circuits have replaced electromechanical devices in controlling appliances and machinery.

From: Wikipedia

7

1.0) Transistor (Cont)

1.0.3) Applications

~ The **bipolar junction transistor (BJT)** was the first transistor invented, and through the 1970s, was the most commonly used transistor. Even after **MOSFETs** became available, the BJT remained the transistor of choice for many **analog circuits** such as **simple amplifiers** because of **their greater linearity and ease of manufacture**.

~ Desirable properties of **MOSFETs**, such as their utility in **low-power devices**, usually in CMOS configuration, allowed them to capture nearly all market share for **digital circuits**; more recently MOSFETs have captured most analog and power applications as well, including modern clocked analog circuits, voltage regulators, amplifiers, power transmitters, motor drivers, etc.

From: Wikipedia

8

1.0) Transistor (Cont)

1.0.4) Categories

Transistors are **categorized by**:

- [1] **Semiconductor material**: germanium, silicon, gallium arsenide, silicon carbide, etc.
- [2] **Structure**: BJT, JFET, IGFET (MOSFET), IGBT, "other types".
- [3] **Polarity**: NPN, PNP (BJTs); N-channel, P-channel (FETs).
- [4] Maximum **power rating**: low, medium, and high.

From: Wikipedia

9

1.0) Transistor (Cont)

1.0.4) Categories (Cont)

Transistors are **categorized by**:

- [5] Maximum **operating frequency**: low, medium, high, radio frequency (RF), microwave
- [6] **Application**: switch, general purpose, audio, high voltage, super-beta, matched pair.
- [7] Physical **packaging**: through hole metal, through hole plastic, surface mount, ball grid array, power modules.
- [8] **Amplification factor** (transistor beta).


From: Wikipedia

10

1.0) Transistor (Cont)

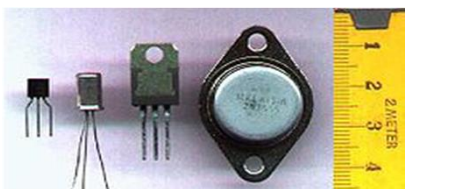1.0.4) Categories (Cont)

Thus, a particular transistor may be described as: *silicon, surface mount, BJT, NPN, low power, high frequency switch.*




From: Wikipedia

11

1.0) Transistor (Cont)

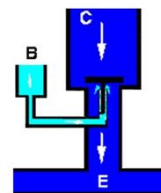1.0.5) How a transistor functions?

An illustration of BJT transistor using water rather than electricity to illustrate the way it functions:



The illustration [taken from <http://www.satcure-focus.com/tutor/page4.htm>] shows pipe work with three openings of **B (Base)**, **C (Collector)**, and **E (Emitter)**.


From <http://www.reuk.co.uk/What-is-a-Transistor.htm>

12

1.0) Transistor (Cont)

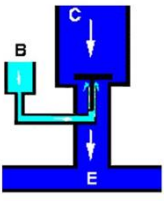1.0.5) How a transistor functions? (Cont)

An illustration of BJT transistor using water rather than electricity to illustrate the way it functions:



The reservoir of water at **C** is the *supply voltage* which is prevented from getting through to **E** by a plunger. If water is poured into **B**, it pushes up the plunger letting water to flow from **C** to **E**.


From <http://www.reuk.co.uk/What-is-a-Transistor.htm>

1.0) Transistor (Cont)

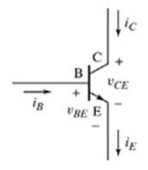1.0.5) How a transistor functions? (Cont)

If even more water is poured into **B**, the plunger moves higher, and the flow of water from **C** to **E** increases.


Therefore, for a **BJT transistor** for example, a small input current of electricity to the **Base** leads to a large flow of electricity (or current) from the **Collector** to the **Emitter**.



From <http://www.reuk.co.uk/What-is-a-Transistor.htm>

Puzzle 1:

How to make **10** from **9** sticks?



Puzzle 2:

How to make **5** from **10** sticks?

Conclusion!

Know the %secret+then you can solve the problem!

Puzzle 3:

How to make **4 inside** number **5**?

Conclusion!

Know the %secret+then you can solve the problem!

1.1) BJT Characteristics and Properties

1.1.1) Circuit Symbols and Conventions

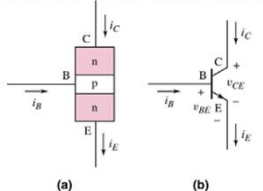


Fig 5.8: npn bipolar transistor
(a) block diagrams and (b) circuit symbols.

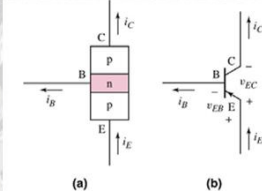



Fig 5.9: pnp bipolar transistor
(a) block diagrams and (b) circuit symbols.



Full **[more detail]** picture helps us identify somebody correctly!

→ **Correct symbol helps us identify which type of transistor correctly!**

Fast Forward...
Past Question

Question 1 [16 marks]

(a) A basic two-transistor BJT current source consists of two npn-type BJT transistors and a resistor, R_1 , to establish its reference current, I_{REF} . The reference current is established when the circuit is connected to positive and negative power source, V^+ and V^- .

(i) Let the second transistor, Q_2 , be the output transistor. Draw and label the circuit and its components clearly. [3 marks]

19

Fast Forward... (Cont)
Past Question (Cont) – Model Answer

Transistors	[1]
I_{REF}	[0.5]
R_1	[0.5]
I_O	[0.5]
Connection	[0.5]
Total	[3 marks]

20

Fast Forward... (Cont)
Past Question (Cont) – Not ALL correct answer

Question 1

i)

→ → Draw transistor with correct symbol! ← ←

21

1.1) BJT Characteristics and Properties (Cont)
1.1.2) Basic Principle of Operation

“The voltage between two terminals (B-E) controls the current through the third terminal (C)”

npn bipolar transistor

→ Transistor = a Voltage-controlled Resistor.

22

1.1) BJT Characteristics and Properties (Cont)
1.1.3) Modes of Operation

Fig 5.25: Bias conditions for the 4 modes of operations of an npn transistor.
→ Forward-active region is usually used for amplifier circuit.

23

1.1) BJT Characteristics and Properties (Cont)
1.1.3) Modes of Operation (Cont)

- 1) The transistor is biased in **Inverse-active mode** if B-E junction is **reverse biased** ($v_{BE} < 0$) and B-C junction is **forward biased** ($v_{BC} > 0$).
- 2) Transistor is in the **Saturation** if both junctions are forward biased.
- 3) Transistor is in the **Cutoff** if both junctions are zero or reverse biased.
- 4) The transistor is biased in the **Forward-active mode** if **B-E junction is forward biased** ($v_{BE} > 0$) and **B-C junction is reverse biased** ($v_{BC} < 0$).

24

1.1) BJT Characteristics and Properties (Cont)

1.1.4) Current-voltage Relationships in the Forward-active Region

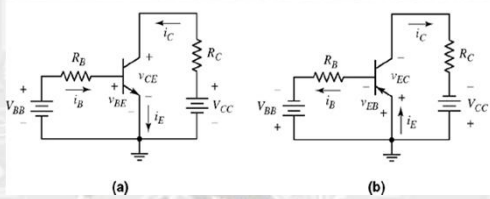


Figure 5.10: Common-emitter circuits:
 (a) with an **npn** transistor,
 and (b) with a **pnp** transistor.

25

1.1) BJT Characteristics and Properties (Cont)

Table 5.1: Summary of the bipolar current-voltage relationships in the forward active region

For npn	For pnp
$i_C = I_S e^{v_{BE}/V_T}$	$i_C = I_S e^{v_{EB}/V_T}$
$i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{BE}/V_T}$	$i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{EB}/V_T}$
$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{BE}/V_T}$	$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{EB}/V_T}$

I_S = Saturation current (strongly dependent on device and temperature)
 V_T = Thermal voltage
 β = Common-emitter current gain
 α = Common-base current gain

26

1.1) BJT Characteristics and Properties (Cont)

Table 5.1: Summary of the bipolar current-voltage relationships in the forward active region (Cont)

For both transistors

$$\alpha = \left(\frac{\beta}{1 + \beta} \right); \beta = \left(\frac{\alpha}{1 - \alpha} \right)$$

$$i_C = \beta i_B$$

$$i_C = \alpha i_E = \left(\frac{\beta}{1 + \beta} \right) i_E$$

$$i_E = i_B + i_C = (1 + \beta) i_B$$

β = Common-emitter current gain
 α = Common-base current gain

27

1.1) BJT Characteristics and Properties (Cont)

1.1.5) BJT Operating Curve

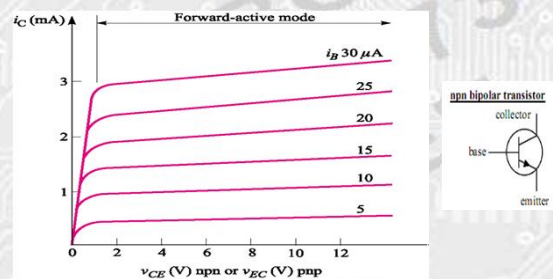


Fig 5.13: Transistor current-voltage characteristics (i_C vs v_{CE}) of the common-emitter circuit

28

1.1) BJT Characteristics and Properties (Cont)

1.1.6) Early Effect

For $V_{CE} > V_{BE(on)}$, the output curve has a finite slope due to **base-width modulation** (reduction of effective base width with increasing collector-base reverse bias).

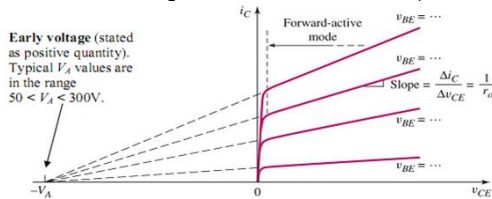


Figure 5.14: Current-voltage characteristics for the common-emitter circuit, showing **Early voltage (V_A)** and finite **output resistance, r_o** , of the transistor.

29

1.1) BJT Characteristics and Properties (Cont)

1.1.6) Early Effect (Cont)

This **Early effect** is included in the collector current equation:

$$i_C = I_S e^{v_{BE}/V_T} \Rightarrow i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A} \right) \quad (5.16)$$

$$\text{Output resistance, } r_o = \left[\frac{\partial i_C}{\partial v_{CE}} \Big|_{v_{BE}=\text{const}} \right]^{-1} \cong \frac{V_A}{I_C} \quad (5.17)$$

where I_C = quiescent collector current when v_{BE} is constant and v_{CE} is small compared to V_A .

30

1.2) DC Analysis Of Bipolar Transistor Circuits

→ DC biasing of **linear amplifiers** is required to obtain **forward-active mode** of operation

Step 1	Assume transistor is biased in the forward-active mode, i.e. $V_{BE} = V_{BE(ON)}$, $I_B > 0$ and $I_C = \beta I_B$.
Step 2	Analyze the circuit with this assumption. <ul style="list-style-type: none"> □ Perform KVL on B-E (or E-B) loop to find current I_B. □ Calculate I_C and I_E from I_B. □ Perform KVL on C-E (or E-C) loop to find voltage V_{CE}.

31

1.2) DC Analysis Of Bipolar Transistor Circuits (Cont)

→ DC biasing of **linear amplifiers** is required to obtain **forward-active mode** of operation

Step 3	Evaluate the resulting state of the transistor. If initial assumed parameters and $V_{CE} > V_{CE(sat)}$ are true, then the initial assumption is correct. However, <ul style="list-style-type: none"> □ if $I_B < 0$, then the transistor is probably cut off, and □ if $V_{CE} < 0$, the transistor is likely to be biased in saturation.
Step 4	If the initial assumption is proven incorrect, then a new assumption must be made and the new circuit must be analyzed. Step 3 must then be repeated.

32

1.2) DC Analysis Of Bipolar Transistor Circuits (Cont)

Example 5.3: DC Analysis of Common-emitter Circuit
 Calculate the base (I_B), collector (I_C), and emitter (I_E) currents and the C-E voltage (V_{CE}) for a common-emitter circuit. (Note: $V_{BE(ON)} = 0.7V$ and $\beta = 200$)

Figure 5.20: Circuit for Example 5.3

33

1.3) Transistor As Amplifier

1.3.1) Voltage Transfer Characteristics

~ Output voltage versus input voltage
 ~ Used to visualise the operation of a circuit or the state of a transistor

Figure 5.48: (a) A bipolar inverter used as an amplifier; (b) the inverter voltage transfer characteristics

34

1.3) Transistor As Amplifier (Cont)

1.3.2) Example of DC Analysis of BJT

<p>Assume: $V_{BE(ON)} = 0.7V$, $\beta = 120$, $V_{CE(sat)} = 0.2V$, $V_A = \infty$</p> <p>○ $V_i \leq 0.7V$, Q_1 = cut off: $\Rightarrow I_B = I_C = 0$, $V_o = V^+ = 5V$</p> <p>○ $V_i > 0.7V$, Q_1 = turned on (forward-active): $I_B = \frac{V_i - 0.7}{R_B}$, $I_C = \beta I_B = \frac{\beta(V_i - 0.7)}{R_B}$ and $V_o = V^+ - I_C R_C = 5 - \frac{\beta(V_i - 0.7)R_C}{R_B}$ This eq. is valid for $0.2 \leq V_o < 5V$.</p>	<p>Assume: $V_{BE(ON)} = 0.7V$, $\beta = 80$, $V_{CE(sat)} = 0.2V$, $V_A = \infty$</p> <p>○ $4.3 \leq V_i \leq 5V$, Q_1 = cut off: $\Rightarrow I_B = I_C = 0$, $V_o = 0V$</p> <p>○ $V_i < 4.3V$, Q_1 = turned on (forward-active): $I_B = \frac{(5 - 0.7) - V_i}{R_B}$, $I_C = \beta I_B = \beta \left[\frac{(5 - 0.7) - V_i}{R_B} \right]$ and $V_o = I_C R_C = \beta R_C \left[\frac{(5 - 0.7) - V_i}{R_B} \right]$ This eq. is valid for $0 \leq V_o < 4.8V$.</p>
--	---

35

1.3) Transistor As Amplifier (Cont)

1.3.2) Example of DC Analysis of BJT (Cont)

○ When $V_i = 0.2V$, Q_1 goes into saturation and V_i is found from:
 $0.2 = 5 - \frac{120(V_i - 0.7)5}{150} \Rightarrow V_i = 1.9V$

○ When $V_o = 4.8V$, Q_1 goes into saturation and V_i is found from:
 $4.8 = (80) \left[\frac{(5 - 0.7) - V_i}{R_B} \right] \Rightarrow V_i = 2.8V$

36

1.4) AC Analysis Of Bipolar Transistor Circuits

~ A BJT linear **amplifier** magnifies an ac input signal and produces an output signal that is larger in magnitude and directly proportional to the input. Therefore, ac analysis of transistor circuits is required.

~ **Superposition theory** applies, i.e. perform dc and ac analysis separately.

37

1.4) AC Analysis Of Bipolar Transistor Circuits (Cont)

- Step 1** Analyze the circuit with only dc sources present. This will give the dc or quiescent solution. The transistor must be biased in the **forward-active region** in order to produce a linear amplifier.
- Step 2** Replace each element in the circuit with its small-signal model. The **small-signal hybrid- π model** applies for the transistor.
 - To draw the small-signal model of the amplifier circuit:
 - Start with the three terminals of the transistor.
 - Then sketch the hybrid- π equivalent circuit between these terminals.
 - Connect the small-signal model of the remaining circuit elements to the transistor terminals.
- Step 3** Analyze the small-signal equivalent circuit, **setting the dc source components equal to zero**, to produce the response of the circuit to time-varying input signals only.

38

1.4) AC Analysis Of Bipolar Transistor Circuits (Cont)

1.4.1) Small-signal Hybrid- π Equivalent Circuit of npn BJT

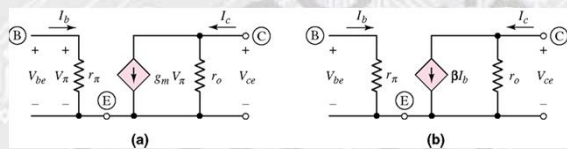


Figure 6.13: Expanded small-signal model of the **npn BJT**, including the **Early effect** when the circuit contains the (a) **voltage controlled** current source (transconductance) and (b) **current controlled** current source (current gain parameters)

39

1.4) AC Analysis Of Bipolar Transistor Circuits (Cont)

1.4.2) Small-signal Hybrid- π Equivalent Circuit of pnp BJT

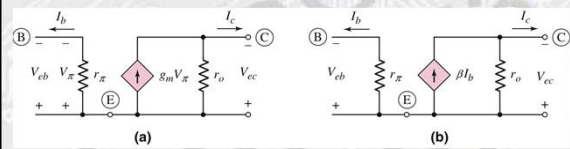


Figure 6.15: Expanded small-signal model of the **pnp BJT**, including the **Early effect** when the circuit contains the (a) **voltage controlled** current source (transconductance) and (b) **current controlled** current source (current gain parameters)

Note: The small-signal model of the **pnp BJT** is the same as in **Fig 6.13** but with all ac **voltage polarities and current directions reversed**.

40

1.4) AC Analysis Of Bipolar Transistor Circuits (Cont)

1.4.3) Small-signal Hybrid- π Equivalent Circuit of BJT (Cont)

~ AC common-emitter current gain:	$\beta = \left[\frac{\partial i_C}{\partial i_B} \right]_{Q-pt} = g_m r_\pi$
~ Transconductance:	$g_m = \left[\frac{\partial i_C}{\partial v_{BE}} \right]_{Q-pt} = \frac{I_{CQ}}{V_T}$
~ Diffusion resistance:	$r_\pi = \left[\frac{\partial i_B}{\partial v_{BE}} \right]_{Q-pt}^{-1} = \frac{\beta V_T}{I_{CQ}}$
~ Small-signal transistor output resistance:	$r_o = \left[\frac{\partial i_C}{\partial v_{CE}} \right]_{Q-pt}^{-1} = \frac{V_A}{I_{CQ}}$

41

1.4) AC Analysis Of Bipolar Transistor Circuits (Cont)


YOU NEED TO MEMORIZE THESE FORMULA

~ AC common-emitter current gain:	$\beta = g_m r_\pi$
~ Transconductance:	$g_m = \frac{I_{CQ}}{V_T}$
~ Diffusion resistance:	$r_\pi = \frac{\beta V_T}{I_{CQ}}$
~ Small-signal output resistance:	$r_o = \frac{V_A}{I_{CQ}}$

42


1.4) AC Analysis Of Bipolar Transistor Circuits (Cont)

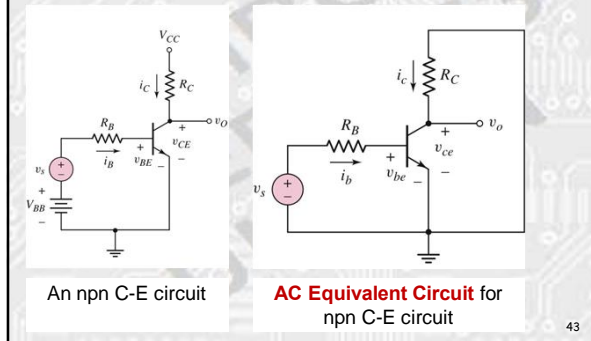1.4.4) Common-Emitter (C-E) with Time-Varying Input




1.4) AC Analysis Of Bipolar Transistor Circuits (Cont)

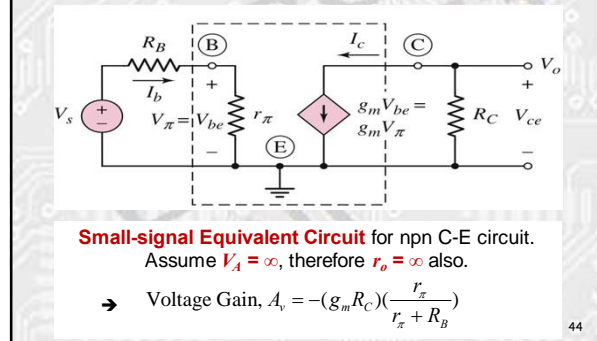1.4.4) Common-Emitter (C-E) with Time-Varying Input (Cont)




1.5) Basic Single Stage BJT Amplifiers

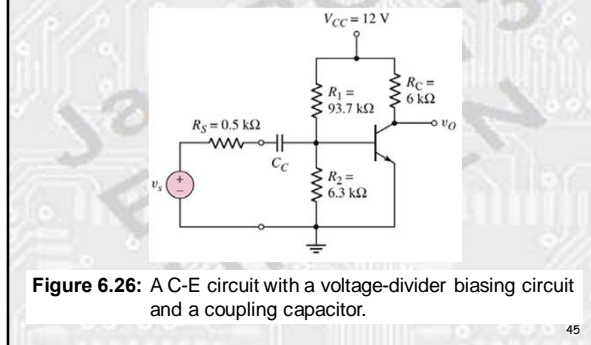
1.5.1) Basic Common-Emitter (C-E) Amplifier Circuit



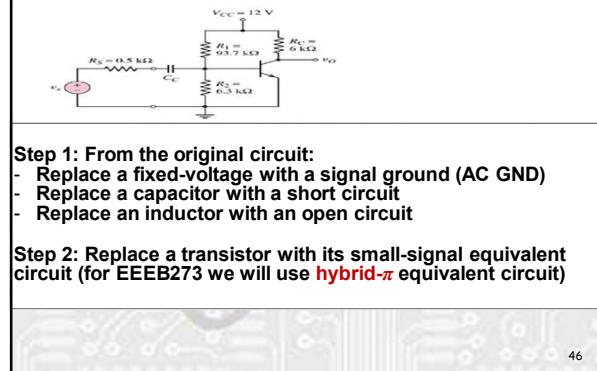
VERY IMPORTANT TO KNOW!
Steps of getting small-signal equivalent circuit from the original circuit using transistor



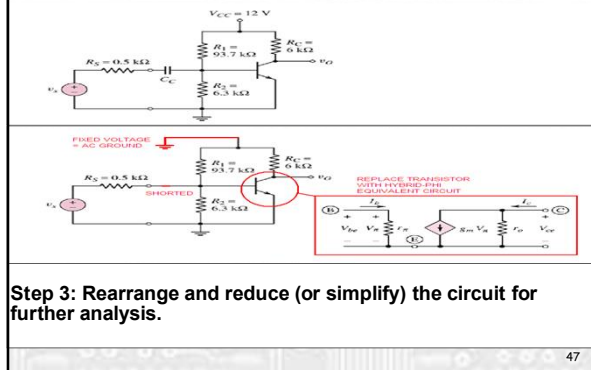VERY IMPORTANT TO KNOW!
Steps of getting small-signal equivalent circuit from the original circuit using transistor



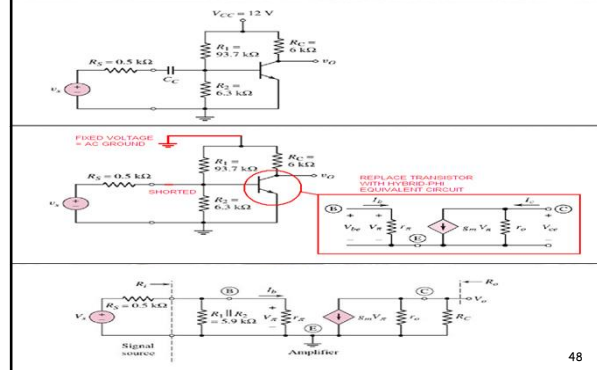VERY IMPORTANT TO KNOW!
Steps of getting small-signal equivalent circuit from the original circuit using transistor



1.5) Basic Single Stage BJT Amplifiers (Cont)

1.5.1) Basic Common-Emitter (C-E) Amplifier Circuit (Cont)

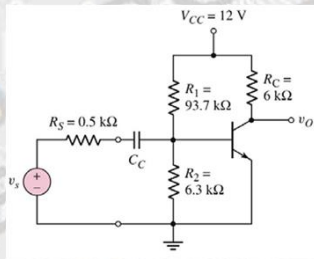


Figure 6.26: A C-E circuit with a voltage-divider biasing circuit and a coupling capacitor.

49

1.5) Basic Single Stage BJT Amplifiers (Cont)

1.5.1) Basic Common-Emitter (C-E) Amplifier Circuit (Cont)

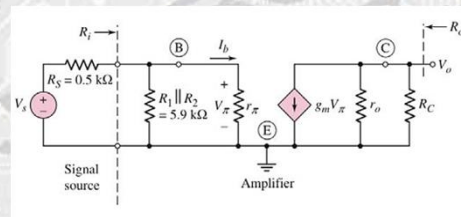


Figure 6.27: The C-E small-signal equivalent circuit, assuming the coupling capacitor is a short circuit.

50

1.5) Basic Single Stage BJT Amplifiers (Cont)

1.5.2) Common-Emitter (C-E) Amplifier with Emitter Resistor

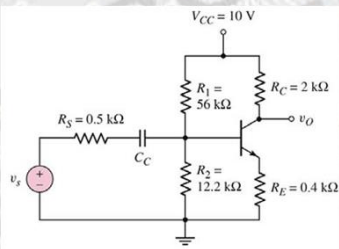


Figure 6.28: A C-E circuit with an emitter resistor, a voltage-divider biasing circuit and a coupling capacitor.

51

1.5) Basic Single Stage BJT Amplifiers (Cont)

1.5.2) C-E Amplifier with Emitter Resistor (Cont)

Assume: $V_A = \infty$. Therefore $r_o = \infty$ (an open circuit).

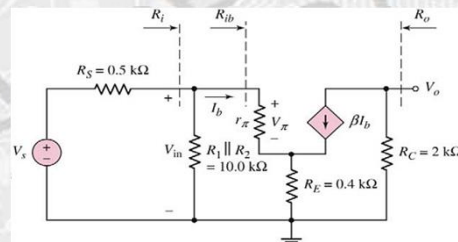


Figure 6.29: The small-signal equivalent circuit with an emitter resistor.

52

1.5) Basic Single Stage BJT Amplifiers (Cont)

1.5.2) C-E Amplifier with Emitter Resistor (Cont)

Assume: $V_A = \infty$. Therefore $r_o = \infty$ (an open circuit).

$$V_{in} = I_b r_{\pi} + (I_b + \beta I_b) R_E$$


$$R_{ib} = \frac{V_{in}}{I_b} = r_{\pi} + (1 + \beta) R_E$$

→ In the C-E configuration that includes an emitter resistance R_E , the small-signal input resistance looking into the base of the transistor (R_{ib}) is r_{π} plus the emitter resistance R_E multiplied by the factor $(1 + \beta)$. This effect is called the **Resistance Reflection Rule**.

53

1.5) Basic Single Stage BJT Amplifiers (Cont)

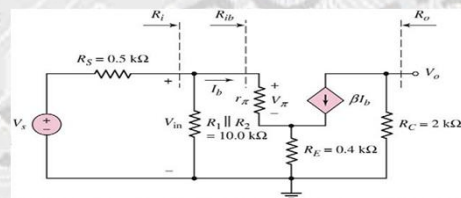1.5.2) C-E Amplifier with Emitter Resistor (Cont)



$$R_{ib} = r_{\pi} + (1 + \beta) R_E$$

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$

$$A_v = \frac{-\beta R_C}{r_{\pi} + (1 + \beta) R_E} \left(\frac{R_i}{R_i + R_S} \right)$$

54

1.5) Basic Single Stage BJT Amplifiers (Cont)

1.5.3) Common-Collector (C-C) Amplifier a.k.a Emitter Follower

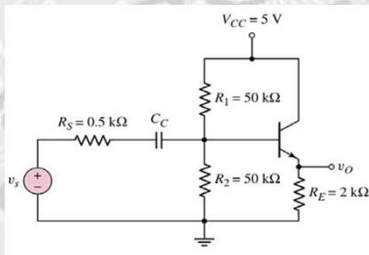


Figure 6.49: An Emitter Follower circuit.

Emitter Follower is a very important circuit for Output Stage!

1.5) Basic Single Stage BJT Amplifiers (Cont)

1.5.3) Common-Collector (C-C) Amplifier a.k.a Emitter Follower (Cont)

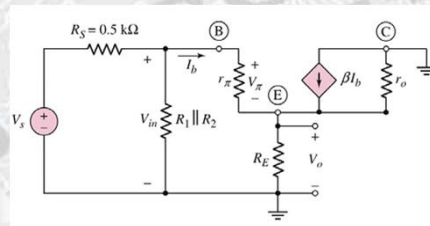


Figure 6.50: Small-signal equivalent circuit of the Emitter Follower.

1.5) Basic Single Stage BJT Amplifiers (Cont)

1.5.3) Common-Collector (C-C) Amplifier a.k.a Emitter Follower (Cont)

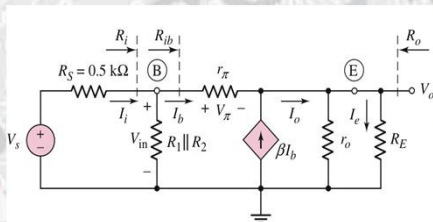


Figure 6.51: All signal grounds connected together.

$$A_v = \frac{(1 + \beta)(r_o || R_E)}{r_\pi + (1 + \beta)(r_o || R_E)} \left(\frac{R_i}{R_i + R_S} \right)$$

1.5) Basic Single Stage BJT Amplifiers (Cont)

1.5.4) Common-Base (C-B) Amplifier

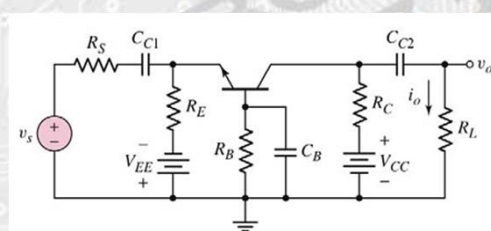


Figure 6.59: Basic Common-Base circuit.

1.5) Basic Single Stage BJT Amplifiers (Cont)

1.5.4) Common-Base (C-B) Amplifier (Cont)

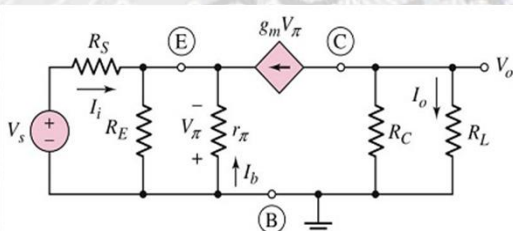


Figure 6.60(b): Small-signal equivalent circuit of the Common-Base circuit.

1.5) Basic Single Stage BJT Amplifiers (Cont)

1.5.5) Characteristics of the three BJT Amplifier configurations

Configuration	Voltage gain, Av	Current gain, Ai	Input Resistance, Ri	Output Resistance, Ro	Application
Common-Emitter (C-E)	High, Av > 1	High, Ai > 1	Moderate	Moderate to high	Power amplifier
Common-Collector (C-C)	Unity, Av ≈ 1	High, Ai > 1	High	Low	Voltage buffer
Common-Base (C-B)	High, Av > 1	Unity, Ai ≈ 1	Low	Moderate to high	Current buffer

Table 6.4

1.6) Introduction to a multistage amplifier

~ In most applications, a single-transistor amplifier (single stage) will not be able to meet the **combined specifications of a given amplification factor, input resistance, and output resistance**. For example, the required voltage gain may exceed that which can be obtained in a single stage circuit.

~ Transistor amplifier circuits can be connected in series, or **cascaded**, as shown in **Figure 6.65**. This may be done, **for example**, to increase the overall small-signal voltage gain or to **provide an overall voltage gain (A_v) greater than 1, with a very low output resistance (R_o).**

61

1.6) Introduction to a multistage amplifier (Cont)


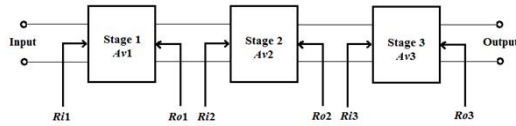


Figure 6.65: A generalized three-stage amplifier

~ The overall voltage or current gain, in general, is simply the product of the individual amplification factors. The gain of **Stage 1** is a function of the input resistance of **Stage 2**, etc. Thus, **loading effect** may have to be taken into account in gain calculations.

62

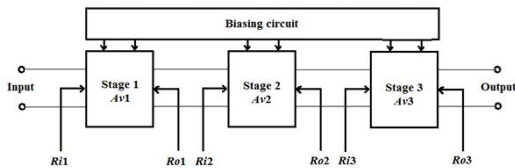
1.6) Introduction to a multistage amplifier (Cont)



~ Usually every stage in the multistage amplifier needs to be biased correctly, as shown in the figure above. In an integrated circuit (IC) design, for example in an **op-amp 741 IC**, the biasing is implemented using **constant current source**.

63

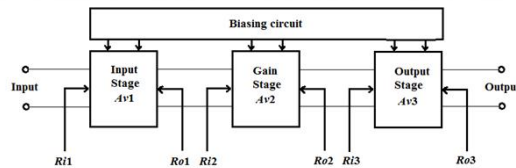
1.6) Introduction to a multistage amplifier (Cont)



~ To be more specific, every stage is given a specific name to reflect its function, such as Stage 1 is called **Input Stage**, Stage 2 becomes **Gain Stage**, and Stage 3 is named as **Output Stage**.

64

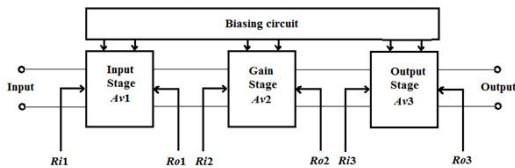1.7) Useful Equations for Resistance Calculations





~ Calculation of **loading effect** (to determine **Ri** and **Ro**) of the next stage to the gain for the previous stage may require implementation of **Resistance Reflection Rule** for the transistor used in the circuit. Equivalent resistance value depends on how it is seen from a particular transistor terminal.

65

1.7) Useful Equations for Resistance Calculations (Cont)

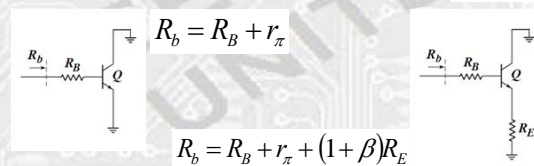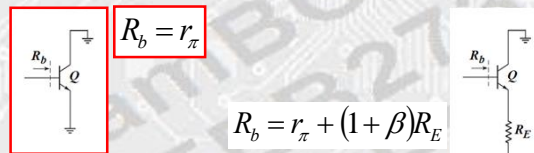1.7.1) Finding equivalent resistance seen from Base, R_b



66

Example of using Resistance Reflection Rule

Finding equivalent resistance seen from Base, R_b

Define: $R_b = \frac{V_x}{I_x}$

From circuit:

$$V_x - V_{\pi} = 0$$

$$V_x - I_x r_{\pi} = 0$$

$$\frac{V_x}{I_x} = r_{\pi}$$

Thus, $R_b = r_{\pi}$

67

1.7) Useful Equations for Resistance Calculations (Cont)

1.7.2) Finding equivalent resistance seen from Collector, R_c

$$R_c = r_o$$

$$R_c = r_o [1 + g_m (r_{\pi} \parallel R_E)]$$

68

1.7) Useful Equations for Resistance Calculations (Cont)

1.7.3) Finding equivalent resistance seen from Emitter, R_e

$$R_e = \frac{r_{\pi}}{(1 + \beta)}$$

$$R_e = \frac{r_{\pi} + R_B}{(1 + \beta)}$$

$$R_e = R_E \parallel \frac{r_{\pi} + R_B}{(1 + \beta)}$$

69

1.7) Useful Equations for Resistance Calculations (Cont)

1.7.4) Voltage Divider (or Potentiometer)

$$\frac{V_1 - V_0}{R_1} = \frac{V_2 - V_0}{R_1 + R_2}$$

$$V_1 = \frac{R_1}{R_1 + R_2} (V_2 - V_0) + V_0$$

$$V_1 = \frac{R_1}{R_1 + R_2} (V_2 - 0) + 0 = \frac{R_1}{R_1 + R_2} V_2$$

70

Past Question: A multistage amplifier!

(ii) Assuming that for all transistors: $r_{\pi} = 500 \text{ k}\Omega$, $g_m = 5 \text{ mA/V}$, $r_o = 3 \text{ k}\Omega$, $R_3 = 250 \Omega$, and $R_1 = 10 \text{ k}\Omega$. For Q_7 , the Early voltage V_A is assumed to be infinite. Calculate the small signal input impedance at the collector of Q_7 , i.e. R_{i7} , as indicated in the Figure 3b. [5 marks]

71


Introducing **LAMIRA**

Learn
Analyze
Memorize
Identify
Recognize
Answer


72

Example → **LAMIRA**
Resistance Reflection Rule

Learn
Analyze
Memorize

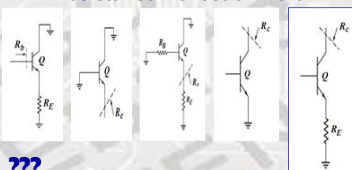

???

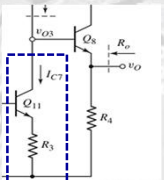

Identify
Recognize
Answer


$$R_c = r_o [1 + g_m (r_{\pi} \parallel R_E)]$$

$$R_{c11} = r_{o11} [1 + g_{m11} (r_{\pi11} \parallel R_3)]$$


73

Example → **LAMIRA**
Resistance Reflection Rule

Learn
Analyze
Memorize

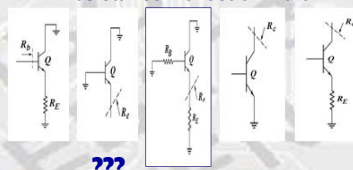

???

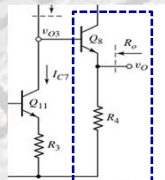

Identify
Recognize
Answer

$$R_c = R_E \parallel \frac{r_{\pi} + R_B}{(1 + \beta)}$$

$$R_o = R_4 \parallel \frac{r_{\pi 8}}{(1 + \beta)}$$

74