
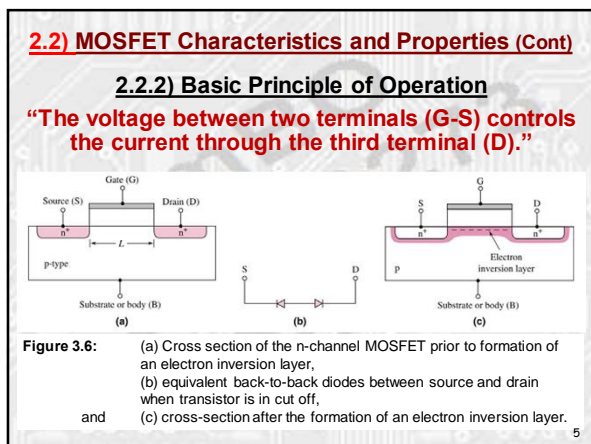
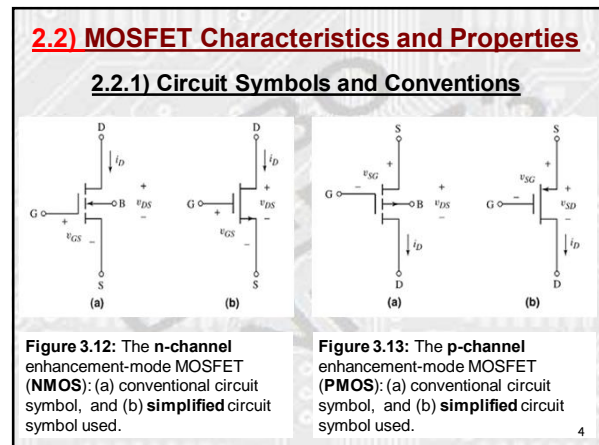


(2)
 
# Review of The MOSFET (Metal-Oxide-Semiconductor Field Effect Transistor)

Reference: Neamen, Chapter 3 and Chapter 4

- ## Learning Outcome
- Able to:**
- ~ Understand the **general operation** of n-channel and p-channel enhancement-mode MOSFETs.
  - ~ Apply the **ideal current-voltage relations** in the dc analysis and design of various MOSFET circuits.
  - ~ Describe the **small-signal equivalent circuit of the MOSFET** and able to determine the values of the small-signal parameters.



- ### 2.2) MOSFET Characteristics and Properties (Cont)
- #### 2.2.2) Basic Principle of Operation (Cont)
- a) Operation of NMOS:**
- ~ **+ve voltage applied to GATE (G)** creates an electric field in the underlying p-type substrate. This forces holes down into the substrate and attracts electrons towards the surface.
  - ~ For **zero or small  $V_{GS}$** , the **SOURCE (S)** and **DRAIN (D)** terminals are separated by the p-region (like two back-to-back diodes). Hence, **no current can flow** between S and D.
  - ~ For **larger  $V_{GS}$** , the region near the surface becomes inverted (i.e. changes from p-type to n-type) and an **n-channel inversion layer is created** between the S and D terminals. This provides **current flow from D to S**.
  - ~ Appreciable channel conduction occurs only when  $V_{GS}$  exceeds **Threshold voltage,  $V_{TN}$** .

**2.2) MOSFET Characteristics and Properties (Cont)**

**2.2.2) Basic Principle of Operation (Cont)**

**b) Operation of PMOS:**

The operation of **p-channel device** is the same except:  
 ~ The **hole is the carrier** rather than the electron.  
 ~ **Negative gate bias** is required to induce an inversion layer of holes (because substrate is of **n-type**).  
 ~ **Current flows from S to D**.  
 ~ **Threshold voltage** for p-channel device is denoted as  $V_{TP}$ .

In both types of MOSFET (i.e. **NMOS and PMOS**), the **GATE is electrically isolated** from the channel by the oxide layer,

**hence  $I_G = 0$  (No gate current!)**

7

**2.2) MOSFET Characteristics and Properties (Cont)**

**2.2.3) Modes of Operation**

There are **3 modes** of operation:

Region	NMOS	PMOS
<b>Cut off</b>	$0 < v_{GS} < V_{TN}$ $i_D = 0$	$0 < v_{SG} < V_{TP}$ $i_D = 0$
<b>Non-saturation</b>	$v_{GS} > V_{TN}$ $v_{DS} < v_{GS} - V_{TN}$ $i_D \neq 0$	$v_{SG} > V_{TP}$ $v_{SD} < v_{SG} + V_{TP}$ $i_D \neq 0$
<b>Saturation</b>	$v_{GS} > V_{TN}$ $v_{DS} \geq v_{GS} - V_{TN}$ $i_D \neq 0$	$v_{SG} > V_{TP}$ $v_{SD} \geq v_{SG} + V_{TP}$ $i_D \neq 0$

**Saturation region is usually used for amplifier circuits.** 8

**2.2) MOSFET Characteristics and Properties (Cont)**

**2.2.4) Current-voltage Relationships**

Region	NMOS	PMOS
<b>Non-saturation</b>	$v_{DS} < v_{DS}(\text{sat})$ $i_D = K_n [2(v_{GS} - V_{TN})v_{DS} - v_{DS}^2]$	$v_{SD} < v_{SD}(\text{sat})$ $i_D = K_p [2(v_{SG} + V_{TP})v_{SD} - v_{SD}^2]$
<b>Saturation</b>	$v_{DS} \geq v_{DS}(\text{sat})$ $i_D = K_n (v_{GS} - V_{TN})^2$	$v_{SD} \geq v_{SD}(\text{sat})$ $i_D = K_p (v_{SG} + V_{TP})^2$
<b>Transition Point</b>	$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$	$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$
<b>Enhancement Mode</b>	$V_{TN} > 0 \text{ V}$	$V_{TP} < 0 \text{ V}$
<b>Depletion Mode</b>	$V_{TN} < 0 \text{ V}$	$V_{TP} > 0 \text{ V}$

9

**2.2) MOSFET Characteristics and Properties (Cont)**

**2.2.5) Conduction Parameters,  $K_n$  and  $K_p$**

~ NMOSFET: 
$$K_n = \frac{W\mu_n C_{ox}}{2L} = \frac{k'_n \cdot W}{2L}$$

~ PMOSFET: 
$$K_p = \frac{W\mu_p C_{ox}}{2L} = \frac{k'_p \cdot W}{2L}$$

where: 
$$C_{ox} = \epsilon_{ox} / t_{ox}$$

is the oxide capacitance per unit area

10

**2.2) MOSFET Characteristics and Properties (Cont)**

**2.2.5) Conduction Parameters,  $K_n$  and  $K_p$  (Cont)**

$\mu_n$	mobility of electrons
$\mu_p$	mobility of holes
$\epsilon_{ox}$	oxide permittivity
$t_{ox}$	oxide thickness
$W$	channel <b>Width</b>
$L$	channel <b>Length</b>
$k'_n = \mu_n C_{ox}$	process conduction parameter (provided by manufacturer for a particular process)

→ The channel geometry, i.e. **width-to-length ratio ( $W/L$ )**, is a variable in the design of MOSFETs that can be utilized to produce specific current-voltage characteristics in MOSFET circuits.

11

**2.2) MOSFET Characteristics and Properties (Cont)**

**2.2.5) Conduction Parameters,  $K_n$  and  $K_p$  (Cont)**

Schematic of **n-Channel Enhancement Mode MOSFET**

 


Figure 3.5

12

**2.2) MOSFET Characteristics and Properties (Cont)**

**2.2.6) Voltage Relationships**

$$V_D = V_S + V_{DS(sat)}$$

$$V_{DS(sat)} = V_{GS} - V_{TN}$$

$$V_{GS} = V_{DS(sat)} + V_{TN}$$

$$V_G = V_S + V_{GS}$$

Useful relationships → **DO NOT FORGET!**

**2.2) MOSFET Characteristics and Properties (Cont)**

**2.2.7) MOSFET Operating Curve**

**Figure 3.15: Family of  $i_D$  versus  $v_{DS}$  curves for NMOS**

**2.2) MOSFET Characteristics and Properties (Cont)**

**2.2.8) Finite Output Resistance**

In an actual MOSFET, the output curve has a finite slope beyond the saturation point due to **channel length modulation** (as  $v_{DS} > v_{DS(sat)}$ ), the point of inversion zero charge moves away from D terminal causing a reduction of channel length).

$\lambda$  is a positive quantity called **channel length modulation parameter**

**Figure 3.20: Effect of channel length modulation, resulting in a finite output resistance**

**2.2) MOSFET Characteristics and Properties (Cont)**

**2.2.8) Finite Output Resistance (Cont)**

The effect of Finite Output Resistance ( $r_o$ ) is included in the **drain current** equation:

$$i_D = K_n [v_{GS} - V_{TN}]^2 \rightarrow i_D = K_n [(v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})]$$

**Output resistance:**

$$r_o = \left[ \frac{\partial v_{DS}}{\partial i_D} \right]_{v_{GS} = const} \cong \frac{1}{\lambda I_{DQ}}$$

where  $I_{DQ}$  = quiescent drain current.

**2.3) DC Analysis Of MOSFET Circuits**

→ DC biasing of MOSFET amplifiers is required to obtain **saturation mode** of operation

<b>Step 1</b>	Assume transistor is biased in the saturation region, i.e. $V_{GS} > V_{TN}$ , $I_D > 0$ and $V_{DS} \geq V_{DS(sat)}$ .
<b>Step 2</b>	Analyze the circuit using the saturation current-voltage relations. <ul style="list-style-type: none"> <li>□ Calculate <math>V_G</math> and <math>V_{GS}</math> from the biasing circuit.</li> <li>□ Calculate <math>I_D</math>.</li> <li>□ Perform KVL on D-S (or S-D) loop to find <math>V_{DS}</math> (or <math>V_{SD}</math>).</li> </ul>


**2.3) DC Analysis Of MOSFET Circuits (Cont)**

→ DC biasing of MOSFET amplifiers is required to obtain **saturation mode** of operation

<b>Step 3</b>	Evaluate the resulting bias condition of the transistor. If the assumed parameter values in step 1 are valid, then the initial assumption is correct. However, <ul style="list-style-type: none"> <li>□ if <math>V_{GS} &lt; V_{TN}</math>, then the transistor is probably cut off, and</li> <li>□ if <math>V_{DS} &lt; V_{DS(sat)}</math>, the transistor is likely to be biased in non-saturation.</li> </ul>
<b>Step 4</b>	If the initial assumption is proven incorrect, then a new assumption must be made and the circuit reanalyzed. <b>Step 3</b> must then be repeated.

**2.3 DC Analysis Of MOSFET Circuits (Cont)**

**Example of a Common-Source Circuit**

 

**Fig 3.25:** (a) An NMOS common-source circuit and (b) the NMOS circuit for Example 3.3

**Example 3.3:** Calculate the  $I_D$  and  $V_{DS}$   
(Note:  $V_{TN} = 1V$  and  $K_n = 0.1mA/V^2$ )


**2.4 AC Analysis Of MOSFET Circuits**

~ In the MOSFET amplifier analysis, superposition theory applies, i.e. perform dc and ac analysis separately.


<b>Step 1</b>	Analyze with only dc sources present to give the dc or quiescent solution. The transistor must be <b>biased in the saturation region</b> in order to produce a linear amplifier.
<b>Step 2</b>	Replace each element in the circuit with its small-signal model, including replacing the transistor by its small-signal equivalent model.  <b>To draw the small-signal model of the amplifier circuit:</b> <input type="checkbox"/> Start with the three terminals of the transistor. <input type="checkbox"/> Then sketch equivalent circuit between these terminals. <input type="checkbox"/> Connect the small-signal model of the remaining circuit elements to the transistor terminals.
<b>Step 3</b>	Analyze the small-signal equivalent circuit, setting the dc source components equal to zero, to produce the response of the circuit to time-varying input signals only.

**2.4 AC Analysis Of MOSFET Circuits (Cont)**

**2.4.1 Small-signal Hybrid- $\pi$  Equivalent Circuit of MOSFET**

 

**Figure 4.6:** Expanded small-signal equivalent circuit, including output resistance ( $r_o$ ), for NMOS transistor.

 

**Figure 6.13:** NPN BJT

**2.4 AC Analysis Of MOSFET Circuits (Cont)**

**2.4.1 Small-signal Hybrid- $\pi$  Equivalent Circuit of MOSFET (Cont)**

~ **Transconductance:**

$$g_m = \frac{\partial i_D}{\partial v_{GS}} \Big|_{v_{GS}=V_{GSQ}=const} = 2K_n(V_{GSQ} - V_{TN}) = 2\sqrt{K_n I_{DQ}}$$


~ **Small-signal transistor output resistance:**

$$r_o = \left[ \frac{\partial v_{DS}}{\partial i_D} \right]_{v_{GS}=V_{GSQ}=const} = \frac{1}{\lambda K_n (V_{GSQ} - V_{TN})^2} \cong \frac{1}{\lambda I_{DQ}}$$

Note: The small-signal model of a PMOS transistor is the same as in **Figure 4.6** but with all ac voltage polarities and current directions reversed. All the parameter equations **stated above** still apply for the PMOS transistor.

**2.5 Basic Single Stage MOSFET Amplifiers**


**2.5.1 Basic Common-Source (CS) Amplifier Circuit**

 

**Figure 4.14:** Common-source circuit with voltage-divider biasing and coupling capacitor.

**2.5 Basic Single Stage MOSFET Amplifiers (Cont)**

**2.5.1 Basic Common-Source (CS) Amplifier Circuit (Cont)**

 


**Figure 4.15:** Small-signal equivalent circuit, assuming the coupling capacitor is a short circuit.



**2.5) Basic Single Stage MOSFET Amplifiers (Cont)**

**2.5.2) Common-Source (CS) Amplifier with Source Resistor**

 


**Figure 4.19:** Common-source circuit with source resistor and positive and negative supply.

25

**2.5) Basic Single Stage MOSFET Amplifiers (Cont)**

**2.5.2) CS Amplifier with Source Resistor (Cont)**

 


**Figure 4.20:** Small-signal equivalent circuit of NMOS common-source amplifier with source resistor.

26

**2.5) Basic Single Stage MOSFET Amplifiers (Cont)**

**2.5.3) Common-Drain (CD) Amplifier a.k.a Source Follower**

 


**Figure 4.26:** NMOS source-follower or common-drain amplifier.

27

**2.5) Basic Single Stage MOSFET Amplifiers (Cont)**

**2.5.3) Common-Drain (CD) Amplifier a.k.a Source Follower (Cont)**

 


**Figure 4.27:** (a) Small-signal equivalent circuit of NMOS source-follower and (b) Small-signal equivalent circuit of NMOS source-follower with all signal grounds at a common point

28

**2.5) Basic Single Stage MOSFET Amplifiers (Cont)**

**2.5.4) Common-Gate (CG) Amplifier**

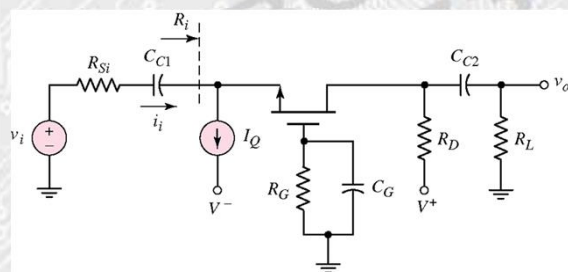


**Figure 4.32:** Common-gate circuit.

29

**2.5) Basic Single Stage MOSFET Amplifiers (Cont)**

**2.5.4) Common-Gate (CG) Amplifier (Cont)**

 

**Figure 4.33:** Small-signal equivalent circuit of common-gate amplifier.

30