

(6) MOSFET Differential Pair


Reference: Neamen, Chapter 11

- ### Learning Outcome
- Able to:**
- Describe the mechanism by which a differential-mode signal and common-mode signal are produced in a MOSFET differential-amplifier.
 - Describe the dc transfer characteristics of a MOSFET differential-amplifier.

6.0) Essential Formulas

Region	NMOS	PMOS
Saturation	$v_{DS} \geq v_{DS}(\text{sat})$ $i_D = K_n [v_{GS} - V_{TN}]^2$	$v_{SD} \geq v_{SD}(\text{sat})$ $i_D = K_p [v_{SG} + V_{TP}]^2$
Transition Point	$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$	$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$

$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$	μ_n, μ_p	Mobility of electrons, holes
$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$	ϵ_{ox}	Oxide permittivity
$C_{ox} = \epsilon_{ox} / t_{ox}$	t_{ox}	Oxide thickness
	W, L	Channel Width, Length
	$k'_n = \mu_n C_{ox}$ $k'_p = \mu_p C_{ox}$	Process conduction parameter (provided by manufacturer)

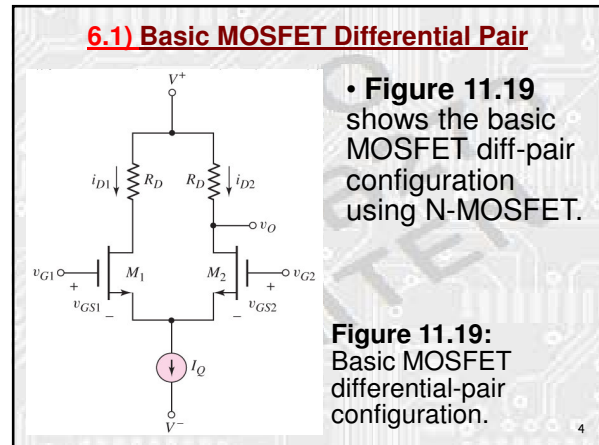

6.1) Basic MOSFET Differential Pair (Cont)

• **Two identical transistor M_1 and M_2** , whose sources are connected together, are biased by a constant current source I_Q which is connected to a negative supply V^- .

• The drains of M_1 and M_2 are connected through R_D to a positive supply V^+ .

• Assume that **M_1 and M_2 are always biased in the saturation region.** Even with $v_{G1} = v_{G2} = 0$, the M_1 and M_2 can be biased in saturation region by the current source I_Q .

Figure 11.19: Basic MOSFET differential-pair configuration.

6.1) Basic MOSFET Differential Pair (Cont)

Example 11.8

Objective: Calculate the dc characteristics of a MOSFET diff-amp.

Consider the diff-amp shown in **Figure 11.20**. The transistor parameters are:

$$K_{n1} = K_{n2} = 0.1 \text{ mA/V}^2,$$

$$K_{n3} = K_{n4} = 0.3 \text{ mA/V}^2,$$

and for all transistors $\lambda = 0$ and $V_{TN} = 1 \text{ V}$.

Determine the maximum range of common-mode input voltage, i.e. find $v_{CM}(\text{max})$ and $v_{CM}(\text{min})$.

6.1) Basic MOSFET Differential Pair (Cont)

Example 11.8 (Cont)

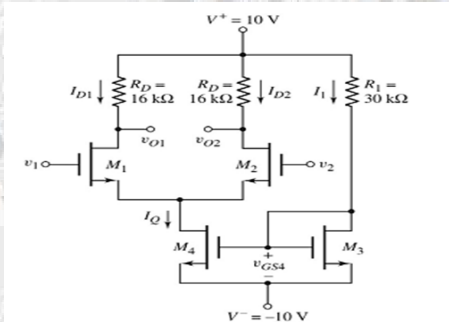


Figure 11.20: MOSFET diff amp for Example 11.8

7

6.1) Basic MOSFET Differential Pair (Cont)

Example 11.8 (Cont)

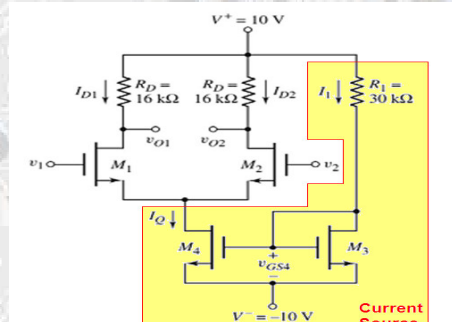


Figure 11.20: MOSFET diff amp for Example 11.8

8

6.1) Basic MOSFET Differential Pair (Cont)

Example 11.8 (Cont)

Solution:

The reference current can be determined from:

$$I_1 = \frac{V^+ - V^- - V_{GS4}}{R_1} = \frac{20 - V_{GS4}}{R_1}$$

and from $I_1 = K_{n3}(V_{GS4} - V_{TN})^2$

Thus $9V_{GS4}^2 - 17V_{GS4} - 11 = 0$ $\frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$

Yields $V_{GS4} = 2.40V$

and $I_1 = 0.587mA$

9

6.1) Basic MOSFET Differential Pair (Cont)

Example 11.8 (Cont)

The quiescent drain currents in M_1 and M_2 :

$$I_{D1} = I_{D2} = I_Q / 2 \approx 0.293 \text{ mA}$$

The gate-to-source voltages are then

$$V_{GS1} = V_{GS2} = \sqrt{\frac{I_{D1}}{K_{n1}}} + V_{TN} = \sqrt{\frac{0.293}{0.1}} + 1 = 2.71V$$


The quiescent values of v_{O1} and v_{O2} are

$$v_{O1} = v_{O2} = V^+ - I_{D1} R_D / 2 = 10 - (0.293m)(16k)/2 = 5.31 \text{ V}$$

10

6.1) Basic MOSFET Differential Pair (Cont)

Example 11.8 (Cont)

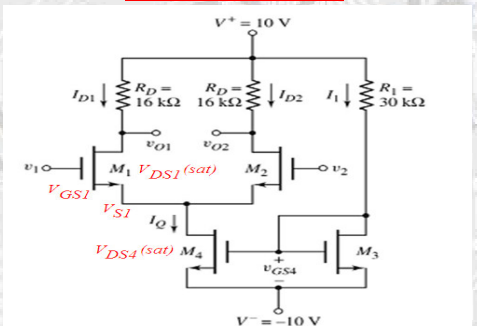

11

6.1) Basic MOSFET Differential Pair (Cont)

Example 11.8 (Cont)

The maximum common-mode input voltage is the value when M_1 and M_2 reach the transition point

$$v_{CM}(\text{max}) = V_{S1}(\text{max}) + V_{GS1} = (v_{O1} - V_{DS1}(\text{sat})) + V_{GS1}$$

The minimum common-mode input voltage is the value when M_4 reaches the transition point

$$v_{CM}(\text{min}) = V_{S1}(\text{min}) + V_{GS1} = (V^- + V_{DS4}(\text{sat})) + V_{GS1}$$

12

6.1) Basic MOSFET Differential Pair (Cont)

Example 11.8 (Cont)

The maximum common-mode input voltage is the value when M_1 and M_2 reach the transition point,

$$V_{DS1} = V_{DS2} = V_{DS1}(\text{sat}) = V_{GS1} - V_{TN}$$

$$V_{DS1} = 2.71 - 1 = 1.71 \text{ V}$$

Therefore,

$$v_{CM}(\text{max}) = v_{O1} - V_{DS1}(\text{sat}) + V_{GS1}$$

$$= 5.31 - 1.71 + 2.71 = 6.31 \text{ V}$$

The minimum common-mode input voltage is the value when M_4 reaches the transition point,

$$V_{DS4} = V_{DS4}(\text{sat}) = V_{GS4} - V_{TN} = 2.4 - 1 = 1.4 \text{ V}$$

Therefore,

$$v_{CM}(\text{min}) = V^- + V_{DS4}(\text{sat}) + V_{GS1}$$

$$= (-10) + 1.4 + 2.71 = -5.89 \text{ V}$$

13

6.2) DC Transfer characteristics

• Use circuit in **Figure 11.19**. Assume M_1 and M_2 are matched and neglecting their output resistances:

$$i_{D1} = K_n (v_{GS1} - V_{TN})^2 \quad (11.60(a))$$

$$i_{D2} = K_n (v_{GS2} - V_{TN})^2 \quad (11.60(b))$$

Taking square roots and subtracting

$$\sqrt{i_{D1}} - \sqrt{i_{D2}} = \sqrt{K_n} (v_{GS1} - v_{GS2}) = \sqrt{K_n} \cdot v_d$$

where $v_d = v_{G1} - v_{G2} = v_{GS1} - v_{GS2} \quad (11.61)$

is the **differential-mode input voltage**.

14

6.2) DC Transfer characteristics (Cont)

- If $v_d > 0$, then $v_{G1} > v_{G2}$ and $v_{GS1} > v_{GS2}$ which implies that $i_{D1} > i_{D2}$

• Since $i_{D1} + i_{D2} = I_Q \quad (11.62)$

$$(\sqrt{i_{D1}} - \sqrt{I_Q - i_{D1}})^2 = (\sqrt{K_n} \cdot v_d)^2 = K_n v_d^2$$

$$\sqrt{i_{D1}}(I_Q - i_{D1}) = \frac{1}{2}(I_Q - K_n v_d^2)$$

$$i_{D1}^2 - I_Q i_{D1} + \frac{1}{4}(I_Q - K_n v_d^2)^2 = 0$$

15

6.2) DC Transfer characteristics (Cont)

• Applying the **quadratic formula**, rearranging terms, and noting that $i_{D1} > I_Q/2$ and $v_d > 0$, can obtain

$$i_{D1} = \frac{I_Q}{2} + \sqrt{\frac{K_n I_Q}{2}} \cdot v_d \sqrt{1 - \left(\frac{K_n}{2I_Q}\right) v_d^2} \quad (11.66)$$

• Using Equation (11.62) can also obtain

$$i_{D2} = \frac{I_Q}{2} - \sqrt{\frac{K_n I_Q}{2}} \cdot v_d \sqrt{1 - \left(\frac{K_n}{2I_Q}\right) v_d^2} \quad (11.67)$$

$$\frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

16

6.2) DC Transfer characteristics (Cont)

• The normalized drain currents are

$$\frac{i_{D1}}{I_Q} = \frac{1}{2} + \sqrt{\frac{K_n}{2I_Q}} \cdot v_d \sqrt{1 - \left(\frac{K_n}{2I_Q}\right) v_d^2} \quad (11.68)$$

and $\frac{i_{D2}}{I_Q} = \frac{1}{2} - \sqrt{\frac{K_n}{2I_Q}} \cdot v_d \sqrt{1 - \left(\frac{K_n}{2I_Q}\right) v_d^2} \quad (11.69)$

→ These equations describe the dc transfer characteristics for the circuit. They are plotted in **Figure 11.21** as a function of normalized differential input voltage $v_d / \sqrt{2I_Q / K_n}$

17

6.2) DC Transfer characteristics (Cont)

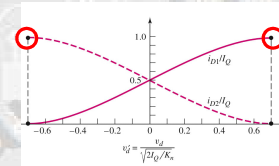


Fig 11.21: Normalized dc transfer characteristics for MOSFET differential amp.

• From (11.68) and (11.69), at a specific differential input voltage, bias current I_Q is switched entirely to one transistor or the other.

→ This occurs when $|v_d|_{\text{max}} = \sqrt{I_Q / K_n} \quad (11.70)$

18

6.2) DC Transfer characteristics (Cont)

- Forward transconductance = the slope of the dc transfer characteristics for the i_{D1} curve.
- From **Figure 11.21**, maximum forward transconductance occurs at $v_d = 0$, so that

$$g_f(\text{max}) = \left. \frac{di_{D1}}{dv_d} \right|_{v_d=0} \quad (11.71)$$

- Using (11.66),

$$g_f(\text{max}) = \sqrt{\frac{K_n I_Q}{2}} = \frac{g_m}{2} \quad (11.72)$$

where g_m is each transistor's transconductance.

19

6.2) DC Transfer characteristics (Cont)

- The slope of i_{D2} characteristic curve at $v_d = 0$ is the same, except negative.

Note:

- Similar to BJT diff-amp, the differential-mode **input voltage must be held within a small range of voltages so as to remain linear.**

- However, the $v_d(\text{max})$ for the MOSFET diff-amp is much larger than $v_d(\text{max})$ for the BJT diff-amp. **Why?** Because the gain of the MOSFET diff-amp is much smaller than the gain of the bipolar (BJT) diff-amp.

Next

20

6.3) AC equivalent circuit

- **Figure 11.22** is AC equivalent circuit of diff-amp configuration, showing only diff voltage and signal currents as a function g_m . Assume output resistance looking into the current source is infinite.


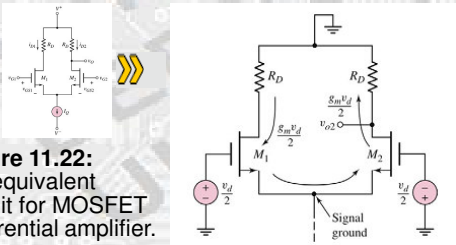


Figure 11.22: AC equivalent circuit for MOSFET differential amplifier.

21

6.3) AC equivalent circuit (Cont)

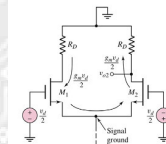

- Using this equivalent circuit, the **One-sided output** voltage at v_{o2} is

$$v_{o2} \equiv v_o = + \frac{g_m v_d}{2} R_D \quad (11.73)$$

Figure 11.22: AC equivalent circuit for MOSFET differential amplifier.

- Then the differential voltage gain is

$$A_d = \frac{v_o}{v_d} = \frac{g_m R_D}{2} = \sqrt{\frac{K_n I_Q}{2}} R_D \quad (11.74)$$

22

6.4) Differential- and Common-Mode Input Impedances

- At low frequencies, input impedance of a MOSFET is essentially infinite.

→ This means that both the differential- and common-mode input resistances of a MOSFET diff-amp are **infinite**.

23

6.5) Small-signal Equivalent Circuit Analysis

- Can determine basic relationships for differential-mode gain, common-mode gain, and **CMRR** from an analysis of **the small-signal equivalent circuit.**

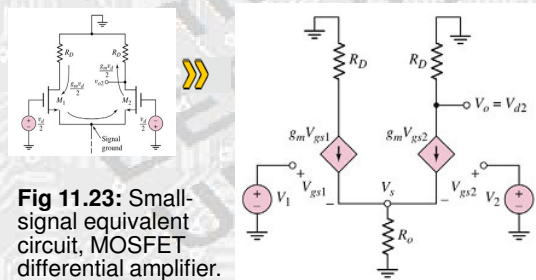


Fig 11.23: Small-signal equivalent circuit, MOSFET differential amplifier.

24

6.5) Small-signal Equivalent Circuit Analysis (Cont)

- Assume that transistors are matched, with $\lambda = 0$ for each transistor, and that constant-current source is represented by a **finite output resistance** ($R_o \neq \infty$).
- Two transistors are biased at the same quiescent current, and $g_{m1} = g_{m2} \equiv g_m$

• KCL equation at **node** V_s

$$g_m V_{gs1} + g_m V_{gs2} = \frac{V_s}{R_o}$$

From the circuit, $V_{gs1} = V_1 - V_s$ and $V_{gs2} = V_2 - V_s$

Then,
$$g_m (V_1 + V_2 - 2V_s) = \frac{V_s}{R_o} \quad (11.76)$$

6.5) Small-signal Equivalent Circuit Analysis (Cont)

- Solving for V_s

$$V_s = \frac{V_1 + V_2}{2 + \frac{1}{g_m R_o}} \quad (11.77)$$

- For a **one-sided output** at the drain of M_2

$$V_o = V_{d2} = -(g_m V_{gs2}) R_D = -(g_m R_D)(V_2 - V_s)$$

- Substitute (11.77) and rearranging terms yields

$$V_o = -g_m R_D \left[\frac{V_2 \left(1 + \frac{1}{g_m R_o} \right) - V_1}{2 + \frac{1}{g_m R_o}} \right] \quad (11.79)$$

6.5) Small-signal Equivalent Circuit Analysis (Cont)

- Based on relationships between input voltages V_1 and V_2 and differential- and common-mode voltages, as given by **Equation (11.29)**, Equation (11.79) can be written

$$V_o = \frac{g_m R_D}{2} V_d - \frac{g_m R_D}{1 + 2g_m R_o} V_{cm} \quad (11.80)$$

- The output voltage, in general form, is

$$V_o = A_d V_d + A_{cm} V_{cm}$$

- The transconductance g_m of the MOSFET is

$$g_m = 2\sqrt{K_n I_{DQ}} = \sqrt{2K_n I_Q}$$

$$V_1 = V_{cm} + \frac{V_d}{2}$$

$$V_2 = V_{cm} - \frac{V_d}{2}$$

27

6.5) Small-signal Equivalent Circuit Analysis (Cont)

6.5.1) Differential- and Common-mode Gains

- Therefore:

→ **Differential-mode gain** is

$$A_d = \frac{g_m R_D}{2} = \sqrt{2K_n I_Q} \left(\frac{R_D}{2} \right) = \sqrt{\frac{K_n I_Q}{2}} \cdot R_D \quad (11.82(a))$$

→ **Common-mode gain** is

$$A_{cm} = \frac{-g_m R_D}{1 + 2g_m R_o} = \frac{-\sqrt{2K_n I_Q} \cdot R_D}{1 + 2\sqrt{2K_n I_Q} \cdot R_o} \quad (11.82(b))$$

For an ideal current source, $R_o = \infty$, so $A_{cm} = 0$.

28

6.5) Small-signal Equivalent Circuit Analysis (Cont)

6.5.2) Common-Mode Rejection Ratio

→ **Common-mode rejection ratio (CMRR)** is

$$CMRR = \frac{1}{2} \left[1 + 2\sqrt{2K_n I_Q} \cdot R_o \right] \quad (11.83)$$

This demonstrate that the **CMRR** for the MOSFET diff-amp is also a **strong function of the output resistance** of the constant-current source.

→ The value of **CMRR** can be increased by increasing the output resistance of the current source. The increase can be accomplished by using a more sophisticated current source circuit, such as **the MOSFET cascode current mirror**.

29

6.5) Small-signal Equivalent Circuit Analysis (Cont)

Example 11.9

Objective:

Determine the differential-mode voltage gain, common-mode voltage gain, and CMRR for a MOSFET diff-amp.

Consider a MOSFET diff-amp with the configuration in **Figure 11.20**. Assume the same transistor **parameters as given in Example 11.8 except** assume $\lambda = 0.01 \text{ V}^{-1}$ for M_4 .

30

6.5) Small-signal Equivalent Circuit Analysis (Cont)

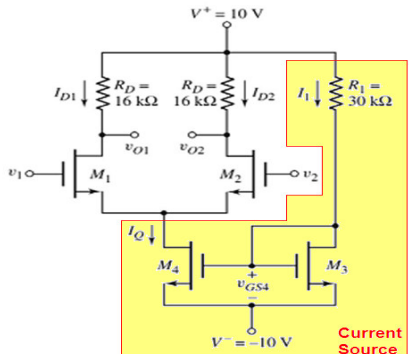


Figure 11.20: MOSFET diff amp for Example 11.8

31

6.5) Small-signal Equivalent Circuit Analysis (Cont)

Example 11.9 (Cont)

Solution:

From Example 11.8, bias current is $I_Q = 0.587 \text{ mA}$.

The output resistance of the current source is then

$$R_o = 1 / (\lambda I_Q) = 1 / (0.01 \times 0.587 \text{ m}) = 170 \text{ k}\Omega$$

The differential-mode voltage gain is

$$A_d = \sqrt{\frac{K_n I_Q}{2}} \cdot R_D = \sqrt{\frac{(1)(0.587 \text{ m})}{2}} \cdot (16 \text{ k})$$

→ $A_d = 8.67$

32

6.5) Small-signal Equivalent Circuit Analysis (Cont)

Example 11.9 (Cont)

Solution: (Cont)

and the common-mode voltage gain is

$$A_{cm} = \frac{-\sqrt{2K_n I_Q} \cdot R_D}{1 + 2\sqrt{2K_n I_Q} \cdot R_o} = \frac{-\sqrt{2(1)(0.587 \text{ m})} \cdot (16 \text{ k})}{1 + 2\sqrt{2(1)(0.587 \text{ m})} \cdot (170 \text{ k})}$$

→ $A_{cm} = -0.0469$

The common-mode rejection ratio is then

$$CMRR_{dB} = 20 \log_{10}(8.67/0.0469) = 45.3 \text{ dB}$$

33

6.6) Two-Sided Output

• For an ideal MOSFET op-amp, with the **two-sided output** defined as with $V_o = V_{d2} - V_{d1}$, then

$$V_o = g_m R_D (V_{gs1} - V_{gs2}) = g_m R_D (V_1 - V_2)$$

With: $V_1 = V_{cm} + V_d/2$ and $V_2 = V_{cm} - V_d/2$

→ **Differential-mode voltage gain is**

$$A_d = g_m R_D \tag{11.84(a)}$$

→ **Common-mode voltage gain is**

$$A_{cm} = 0 \tag{11.84(b)}$$

$A_{cm} = 0$ is a consequence of using matched devices and elements in the diff-amp circuit.

34

6.6) Two-Sided Output (Cont)

6.6.1) Effect of R_D and g_m mismatches

	R_D mismatch $R_{D1} = R_D + \Delta R_D$ $R_{D2} = R_D - \Delta R_D$ $V_o = g_m (R_{D1} V_{gs1} - R_{D2} V_{gs2})$	g_m mismatch $g_{m1} = g_m + \Delta g_m$ $g_{m2} = g_m - \Delta g_m$ $V_o = R_D (g_{m1} V_{gs1} - g_{m2} V_{gs2})$
A_d	$g_m R_D$	$g_m R_D$
A_{cm}	$\cong \frac{\Delta R_D}{R_D}$	$\frac{R_D (2\Delta g_m)}{1 + 2R_D g_m}$
$CMRR = \frac{ A_d }{ A_{cm} }$	$\frac{g_m R_D}{(\Delta R_D / R_D)}$	$\frac{1 + 2R_D g_m}{2(\Delta g_m / g_m)}$

Note: CMRR of mismatched elements in MOSFET diff-amp is identical with the results of mismatched elements in the BJT diff-amp.

Next

35

Larger circuits

36

6.1) Basic MOSFET Differential Pair

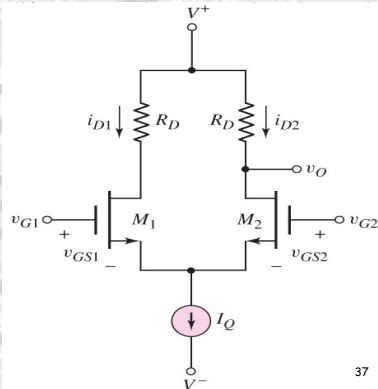


Figure 11.19: Basic MOSFET differential-pair configuration.

37

6.1) Basic MOSFET Differential Pair (Cont)

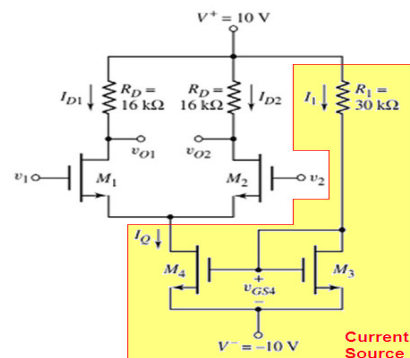


Figure 11.20: MOSFET diff amp for Example 11.8

38

6.2) DC Transfer characteristics (Cont)

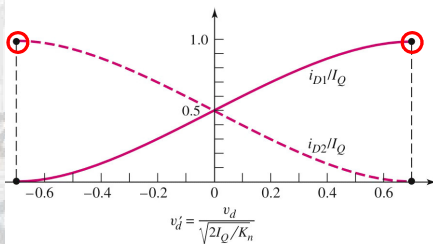


Fig 11.21: Normalized dc transfer characteristics for MOSFET differential amp.

→ This occurs when $|v_d|_{\max} = \sqrt{I_Q / K_n}$ (11.70)

39

6.3) AC equivalent circuit

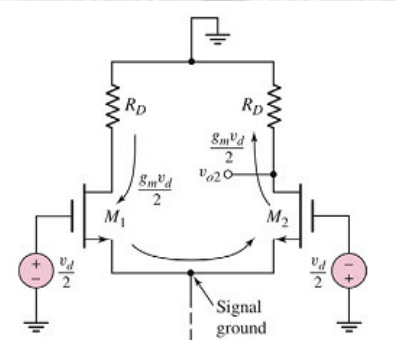


Figure 11.22: AC equivalent circuit for MOSFET diff-amp.

40

6.5) Small-signal Equivalent Circuit Analysis

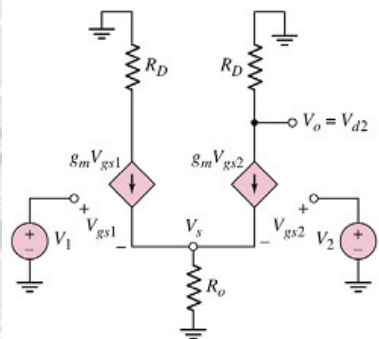


Fig 11.23: Small-signal equivalent circuit, MOSFET diff-amp.

41