

(7) Differential Amplifier with Active Load

Reference: Neamen, Chapter 11

Learning Outcome

Able to:

- Describe active loads.
- Design a diff-amp with an active load to yield a specified differential-mode voltage gain.

7.0) Active Loads

- **Active loads** are essentially **transistor current sources used in place of the resistive loads** in the diff-amp circuits **to increase differential-mode gain**.
- BJTs {MOSFETs} in the active load circuit are biased at Q-point in forward-active {saturation} mode.
- Diff-pair induces a change in I_C { I_D }, which in turn, produces a change in V_{EC} { V_{SD} }.

→ Refer to **Figure 11.27** for BJT.

7.0) Active Loads (Cont)

Figure 11.27: Current-voltage characteristics of active load device using BJT.

- ΔV_{EC} { ΔV_{SD} } **is proportional to r_o** (small-signal output resistance) of the transistor.
- Value of r_o **is much larger than resistive loads**, so the small-signal **voltage gain will be larger** with the active load.

5.2) Basic BJT Differential Pair

- **Figure 11.2** shows the basic BJT differential-pair configuration using npn transistors.

REMEMBER...

Figure 11.2: Basic BJT differential-pair **using npn transistors**.


7.1) BJT Diff-Amp with Active Load

- **Figure 11.28** shows a diff-amp with active load.

Figure 11.28: BJT diff-amp with active load.

Figure 11.2

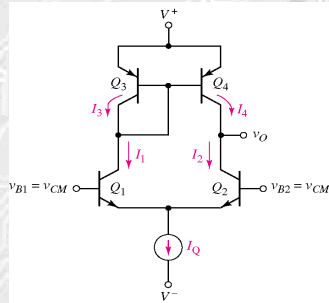7.1) BJT Diff-Amp with Active Load (Cont)



• Q_1 and Q_2 are diff pair biased with a constant current I_Q , and Q_3 and Q_4 form the load circuit.

• From the collectors of Q_2 and Q_4 , obtain a **one-sided output** v_O .

Figure 11.28: BJT diff-amp with active load.

7

7.1) BJT Diff-Amp with Active Load (Cont)

IDEAL CASE:


- All Q_s are matched:
 - $v_{B1} = v_{B2} = v_{CM}$
 - I_Q splits evenly between Q_1 and Q_2
- Neglecting base currents:
 - $I_4 = I_3$ [through current-source circuit]
 - $I_1 = I_2 = I_3 = I_4 = I_Q/2$ with no load connected at output.

ACTUAL CASE:

- Base currents are non-zero.
- A second amplifier stage is connected at the diff-amp output.

8

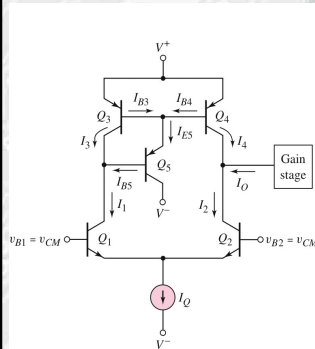7.1) BJT Diff-Amp with Active Load (Cont)




• **Figure 11.29** shows a diff-amp with an active load, corresponding to a **3-transistor current source**, as well as a second amplifying stage (**gain stage**).

Figure 11.29: BJT diff amp with 3-transistor active load and second stage gain.

9

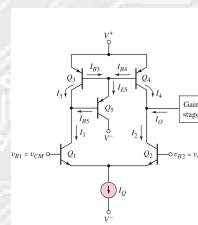7.1) BJT Diff-Amp with Active Load (Cont)



- For simplicity, assume all Q_s current gain (β) are equal.
- Current I_O is the dc bias current from the gain stage.
- Assuming all Q_s are matched and $v_{B1} = v_{B2} = v_{CM}$, current I_Q splits evenly and $I_1 = I_2$

Figure 11.29: BJT diff amp with 3-transistor active load and second stage gain.

- To ensure that Q_2 and Q_4 are biased in forward-active mode, **dc currents must be balanced, or $I_3 = I_4$**

10

7.1) BJT Diff-Amp with Active Load (Cont)

• From **Figure 11.29**

$$I_{E5} = I_{B3} + I_{B4} = \frac{I_3}{\beta} + \frac{I_4}{\beta} \quad (11.93)$$

Then
$$I_{B5} = \frac{I_{E5}}{1 + \beta} = \frac{I_3 + I_4}{\beta(1 + \beta)} \quad (11.94)$$

If base currents and I_O are small, then

$$I_3 + I_4 \cong I_Q$$

Therefore,
$$I_{B5} \cong \frac{I_Q}{\beta(1 + \beta)} \quad (11.96)$$

11

7.1) BJT Diff-Amp with Active Load (Cont)

- For the **circuit to be balanced**, i.e. for $I_1 = I_2$ and $I_3 = I_4$, must have

$$I_O = I_{B5} = \frac{I_Q}{\beta(1 + \beta)} \quad (11.97)$$

Equation (11.97) implies that 2nd amplifying stage must be **designed and biased such that the direction of the dc bias current is as shown in Figure 11.29** and its value is equal to the result of Equation (11.97).

12

7.2) Small-Signal Analysis of BJT Active Load

• **Figure 11.30** shows a differential amplifier with a 3-transistor active load circuit.

Figure 11.30: BJT diff-amplifier with 3-transistor active load, showing the signal currents.

7.2) Small-Signal Analysis of BJT Active Load (Cont)

• The resistance R_L represents small-signal input resistance of the gain stage.

• A pure diff-mode input voltage is applied as indicated.

• Signal voltage at base of Q_1 produces a signal collector current

$$i_1 = (g_m v_d) / 2$$

where g_m is transconductance for both Q_1 and Q_2

Figure 11.30: BJT diff amp with 3-transistor active load, showing the signal currents.

7.2) Small-Signal Analysis of BJT Active Load (Cont)

• Assume the **base currents are negligible**, a signal current $i_3 = i_1$ is induced in Q_3 , and the current mirror produces a signal current i_4 equal to i_3 .

• Signal voltage at the base of Q_2 produces a signal collector current $i_2 = (g_m v_d) / 2$, with direction shown.

7.2) Small-Signal Analysis of BJT Active Load (Cont)

• The two signal currents' transistors are biased at the same quiescent current, i_2 and i_4 , add to produce a signal current in the load resistance R_L .

• The discussion is a first-order evaluation of circuit operation → know the induced currents in Q_2 and Q_4
 → **To more accurately determine the output voltage**, need to consider equivalent small-signal collector-emitter output circuit of the 2 transistors.

7.2) Small-Signal Analysis of BJT Active Load (Cont)

• **Figure 11.31(a)** shows the small-signal equivalent circuit at collector nodes of Q_2 and Q_4 . The circuit can be rearranged to combine signal grounds at a common point, as in Figure 11.31(b).

Figure 11.31: (a) Small-signal equivalent circuit BJT diff amp with active load and (b) rearrangement of small-signal equivalent circuit.

7.2) Small-Signal Analysis of BJT Active Load (Cont)

• From **Figure 11.31(b)**, the **Output Voltage** is

$$v_o = 2 \left(\frac{g_m v_d}{2} \right) (r_{o2} \parallel r_{o4} \parallel R_L) \quad (11.98)$$

and the **small-signal diff-mode voltage gain** is

$$A_d = \frac{v_o}{v_d} = g_m (r_{o2} \parallel r_{o4} \parallel R_L) \quad (11.99)$$

Equation (11.99) can be rewritten in the form

$$A_d = \frac{g_m}{\frac{1}{r_{o2}} + \frac{1}{r_{o4}} + \frac{1}{R_L}} = \frac{g_m}{g_{o2} + g_{o4} + G_L} \quad (11.100)$$

7.2) Small-Signal Analysis of BJT Active Load (Cont)

- Recall that

$$g_m = I_Q / 2V_T, r_{o2} = V_{A2} / I_2, r_{o4} = V_{A4} / I_4$$

The parameters g_{m2} , g_{m4} , and G_L are the corresponding conductances. Assuming

$$I_2 = I_4 = I_Q / 2$$

Equation (11.100) can be rewritten in the form

$$A_d = \frac{\frac{I_Q}{2V_T}}{\frac{I_Q}{2V_{A2}} + \frac{I_Q}{2V_{A4}} + \frac{1}{R_L}} \quad (11.101)$$

19

7.2) Small-Signal Analysis of BJT Active Load (Cont)

- The **Output Resistance** looking back into the common collector node is

$$R_o = r_{o2} \parallel r_{o4}$$

- To minimize loading effects, need $R_L > R_o$.
- However, since R_o is generally large for active loads, this condition may not be able to be satisfied.
- The severity of the loading effect can be determined by comparing R_L and R_o .

Next

20

7.2) Small-Signal Analysis of BJT Active Load (Cont)

Example 11.10

Objective:

Determine the differential-mode gain of a diff-amp with an active load, taking loading effects into account.

Consider the diff-amp in **Figure 11.30**, biased with $I_Q = 0.20 \text{ mA}$. Assume an Early voltage of $V_A = 100 \text{ V}$ for all transistors.

Determine the open-circuit ($R_L = \infty$) differential-mode voltage gain, as well as the differential-mode voltage gain when $R_L = 100 \text{ k}\Omega$.

21

7.2) Small-Signal Analysis of BJT Active Load (Cont)

Example 11.10 (Cont)

Solution:

From Equation (11.101), the open-circuit voltage gain becomes

$$A_d = \frac{\frac{I_Q}{2V_T}}{\frac{I_Q}{2V_{A2}} + \frac{I_Q}{2V_{A4}}} = \frac{\frac{0.2\text{m}}{2(0.026)}}{\frac{0.2\text{m}}{2(100)} + \frac{0.2\text{m}}{2(100)}} = 1923$$

22

7.2) Small-Signal Analysis of BJT Active Load (Cont)

Example 11.10 (Cont)

Solution: (Cont)


When $R_L = 100 \text{ k}\Omega$, the voltage gain is

$$A_d = \frac{\frac{I_Q}{2V_T}}{\frac{I_Q}{2V_{A2}} + \frac{I_Q}{2V_{A4}} + \frac{1}{R_L}}$$

$$A_d = \frac{\frac{0.2\text{m}}{2(0.026)}}{\frac{0.2\text{m}}{2(100)} + \frac{0.2\text{m}}{2(100)} + \frac{1}{100\text{k}}} = 321$$

23

6.1) Basic MOSFET Differential Pair

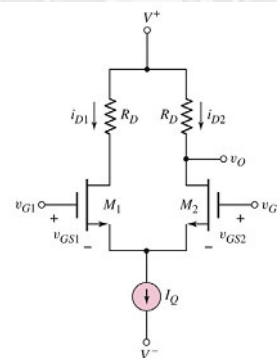


• **Figure 11.19** shows the basic MOSFET diff-pair configuration using N-MOSFET.

REMEMBER...

Figure 11.19: Basic MOSFET differential-pair configuration.

24

7.3) MOSFET Diff-Amp with Active Load

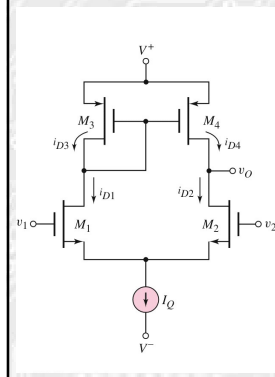

• **Figure 11.32** shows a MOSFET diff-amp with an active load.


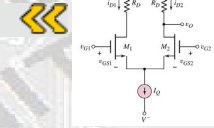


Figure 11.32: MOSFET diff-amp with active load.

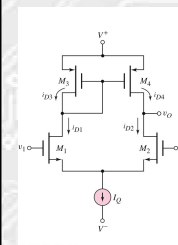7.3) MOSFET Diff-Amp with Active Load (Cont)



- M_1 and M_2 are n-channel devices and form the **diff pair biased with I_Q** .
- **The load circuit consists of M_3 and M_4** , both p-channel devices, connected in a current-mirror configuration.

Figure 11.32: MOSFET diff-amp with active load. A one-sided output v_O is taken from the common drains of M_2 and M_4 .

7.3) MOSFET Diff-Amp with Active Load (Cont)

- When a common-mode voltage

$$v_1 = v_2 = v_{CM}$$

is applied:

- the current I_Q splits evenly between transistors M_1 and M_2 ,
- and $i_{D1} = i_{D2} = I_Q / 2$.

- There are no gate currents, therefore $i_{D3} = i_{D1}$ and $i_{D4} = i_{D2}$

7.3) MOSFET Diff-Amp with Active Load (Cont)

- If a small diff-mode input voltage $v_d = v_1 - v_2$ is applied, then from (11.66) and (11.67):

$$i_{D1} = (I_Q / 2) + i_d \quad (11.102(a))$$

$$i_{D2} = (I_Q / 2) - i_d \quad (11.102(b))$$

where i_d is the signal current.

- For small values of v_d ,

$$i_d = (g_m v_d) / 2$$

7.3) MOSFET Diff-Amp with Active Load (Cont)

- Since M_1 and M_2 are in series, can be seen that

$$i_{D3} = i_{D1} = (I_Q / 2) + i_d \quad (11.103)$$

- Finally, the current mirror consisting of M_3 and M_4 produces

$$i_{D4} = i_{D3} = (I_Q / 2) + i_d \quad (11.104)$$

7.4) Small-Signal Analysis of MOSFET Active Load

- **Figure 11.33** is ac equivalent circuit of the diff-amp with active load circuit, showing the signal currents.

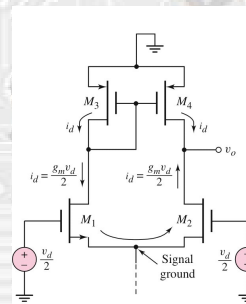


Figure 11.33: The ac equivalent circuit, MOSFET diff amp with active load.

7.4) Small-Signal Analysis of MOSFET Active Load (Cont)

- The negative sign for i_{D2} in (11.102(b)) shows up as a change in current direction in M_2 , as indicated in the figure.
- **Figure 11.34(a)** shows the small-signal equivalent circuit at drain nodes of M_2 and M_4 .
- By connecting the output to gate of **another MOSFET** (i.e. equivalent to ∞ impedance at low frequency), output terminal is effectively an open circuit.

Figure 11.33: The ac equivalent circuit, MOSFET diff amp with active load.

31

7.4) Small-Signal Analysis of MOSFET Active Load (Cont)

- Therefore, the circuit can be rearranged by combining the signal grounds at a common point, as shown in **Figure 11.34(b)**.

Figure 11.34: (a) Small-signal equivalent circuit, MOSFET diff amp with active load and (b) rearranged small-signal equivalent circuit.

32

7.4) Small-Signal Analysis of MOSFET Active Load (Cont)

- From **Figure 11.34(b)**, the **Output Voltage** is

$$v_o = 2 \left(\frac{g_m v_d}{2} \right) (r_{o2} \parallel r_{o4}) \quad (11.105)$$

and the **small-signal diff-mode voltage gain** is

$$A_d = \frac{v_o}{v_d} = g_m (r_{o2} \parallel r_{o4}) \quad (11.106)$$

Equation (11.106) can be rewritten in the form

$$A_d = \frac{g_m}{\frac{1}{r_{o2}} + \frac{1}{r_{o4}}} = \frac{g_m}{g_{o2} + g_{o4}} \quad (11.107)$$

33

7.4) Small-Signal Analysis of MOSFET Active Load (Cont)

- Recall that

$$g_m = 2\sqrt{K_n I_D} = \sqrt{2K_n I_Q}$$

$$g_{o2} = \lambda_2 I_{DQ2} = (\lambda_2 I_Q) / 2$$

$$g_{o4} = \lambda_4 I_{DQ4} = (\lambda_4 I_Q) / 2$$

then Equation (11.107) becomes

$$A_d = \frac{2\sqrt{2K_n I_Q}}{I_Q (\lambda_2 + \lambda_4)} = 2 \sqrt{\frac{2K_n}{I_Q}} \cdot \frac{1}{\lambda_2 + \lambda_4} \quad (11.108)$$

34

7.5) MOSFET Diff-Amp with Cascode Active Load

- The differential-mode voltage gain is proportional to the output resistance (R_o) looking into the active load transistor.
- The voltage gain can be increased, therefore, if R_o can be increased.
- An increase in R_o can be achieved by using, for example, a **cascode active load**.

35

7.5) MOSFET Diff-Amp with Cascode Active Load (Cont)

- **Figure 11.36** shows a MOSFET differential amplifier with cascode active load.

- R_o for the circuit, as discussed in the cascode current source, is given by

$$R_o = r_{o4} + r_{o6} (1 + g_m r_{o4})$$

$$\rightarrow R_o \approx g_m r_{o4} r_{o6} \quad (11.109)$$

- Therefore, the small-signal diff-mode voltage gain is

$$A_d = v_o / v_d$$

$$\rightarrow A_d = g_m (r_{o2} \parallel R_o) \quad (11.110)$$

Figure 11.36: MOSFET diff amp with cascode active load.

36

7.5) MOSFET Diff-Amp with Cascode Active Load (Cont)

Example 11.12

Objective:

Calculate the differential-mode gain of a MOSFET diff-amp with a cascode active load.

Consider the diff-amp in **Figure 11.36**.

Assume that NMOS devices are available with the following parameters: $V_{TN} = 0.5 \text{ V}$, $k'_n = 80 \mu\text{A/V}^2$, $\lambda_n = 0.02 \text{ V}^{-1}$, and $(W/L)_n = 10$.

Assume that PMOS devices are available with the following parameters: $V_{TP} = -1.0 \text{ V}$, $k'_p = 40 \mu\text{A/V}^2$, and $\lambda_p = 0.02 \text{ V}^{-1}$.

Choose supply voltages of $\pm 5 \text{ V}$ and choose a bias current of approximately $I_Q = 200 \mu\text{A}$.

37

7.5) MOSFET Diff-Amp with Cascode Active Load (Cont)

Example 11.12 (Cont)

Solution:

The transistor transconductance is

$$g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{\left(\frac{80\mu}{2}\right)(10)\left(\frac{200\mu}{2}\right)} = 0.40\text{mA/V}$$

The output resistance of individual transistor is

$$r_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.02)\left(\frac{200\mu}{2}\right)} = 500\text{k}\Omega$$

38

7.5) MOSFET Diff-Amp with Cascode Active Load (Cont)

Example 11.12 (Cont)

Solution: (Cont)

The output resistance of the cascode active load is then

$$R_o = r_{o4} + r_{o6}(1 + g_m r_{o4})$$

$$R_o = 500\text{k} + 500\text{k}[1 + (0.40\text{m})(500\text{k})] = 101\text{M}\Omega$$

The differential-mode voltage gain is then found to be

$$A_d = g_m (r_{o2} \parallel R_o) = (0.40\text{m})(500\text{k} \parallel 101\text{M}) = 200$$

39


7.5) MOSFET Diff-Amp with Cascode Active Load (Cont)

Ex 11.12

Do! Help yourself.

40

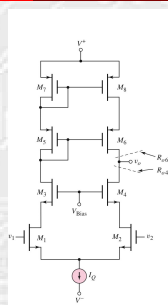7.5) MOSFET Diff-Amp with Cascode Active Load (Cont)



- The diff-mode voltage gain can be further increased by using a cascode configuration in the differential pair as well as in the active load, **Figure 11.37**.
→ M_3 and M_4 are the cascode for the differential pair M_1 and M_2

- Diff-mode voltage gain is now
 $A_d = v_o / v_d = g_m (R_{o4} \parallel R_{o6})$

where $R_{o4} \approx g_m r_{o2} r_{o4}$
and $R_{o6} \approx g_m r_{o6} r_{o8}$

- The small-signal A_d of this type of amplifier can be in the order of 10,000.

Figure 11.37: A MOSFET cascode diff amp with a cascode active load.

41

Larger circuits

42

7.1) BJT Diff-Amp with Active Load

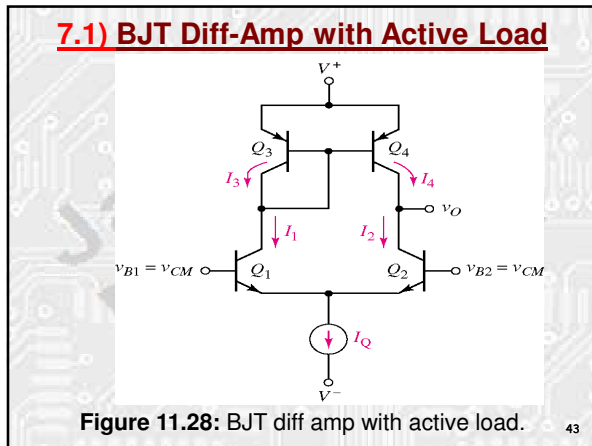


Figure 11.28: BJT diff amp with active load. 43

7.1) BJT Diff-Amp with Active Load (Cont)

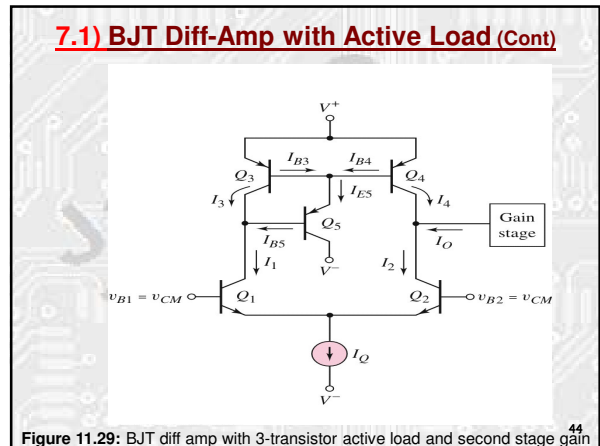


Figure 11.29: BJT diff amp with 3-transistor active load and second stage gain. 44

7.2) Small-Signal Analysis of BJT Active Load

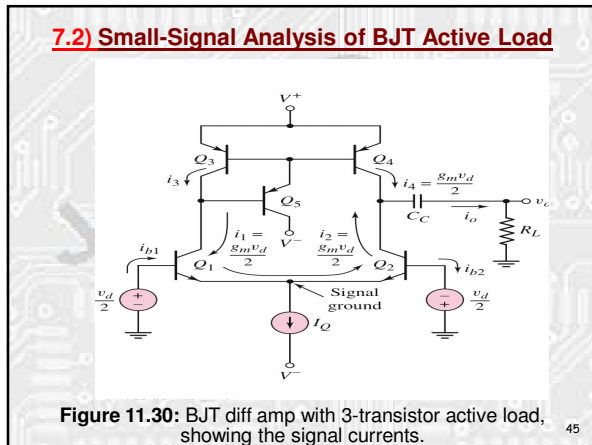


Figure 11.30: BJT diff amp with 3-transistor active load, showing the signal currents. 45

7.2) Small-Signal Analysis of BJT Active Load (Cont)

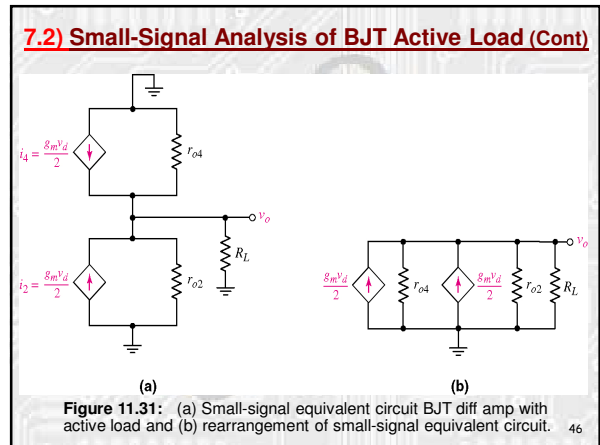


Figure 11.31: (a) Small-signal equivalent circuit BJT diff amp with active load and (b) rearrangement of small-signal equivalent circuit. 46

7.3) MOSFET Diff-Amp with Active Load

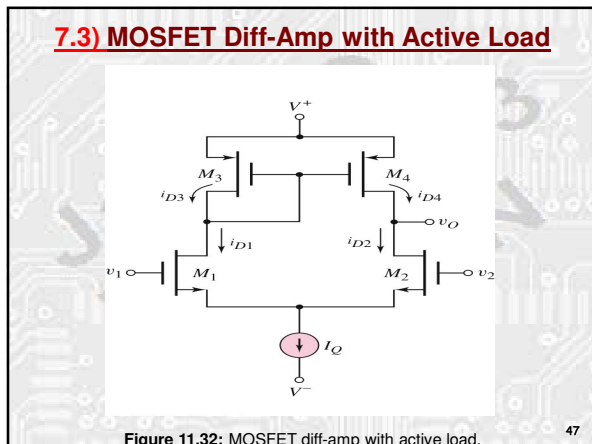


Figure 11.32: MOSFET diff-amp with active load. 47

7.4) Small-Signal Analysis of MOSFET Active Load

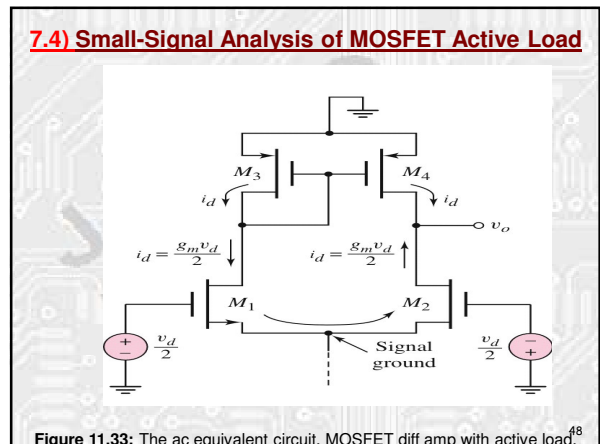


Figure 11.33: The ac equivalent circuit, MOSFET diff amp with active load. 48

7.4 Small-Signal Analysis of MOSFET Active Load (Cont)

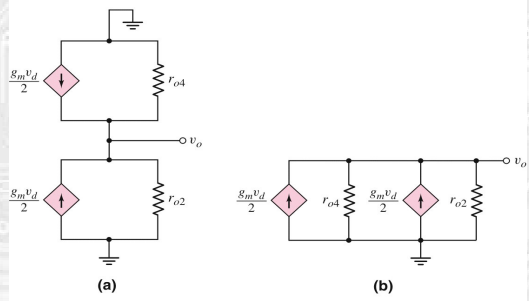


Figure 11.34: (a) Small-signal equivalent circuit, MOSFET diff amp with active load and (b) rearranged small-signal equivalent circuit.

7.5 MOSFET Diff-Amp with Cascode Active Load (Cont)

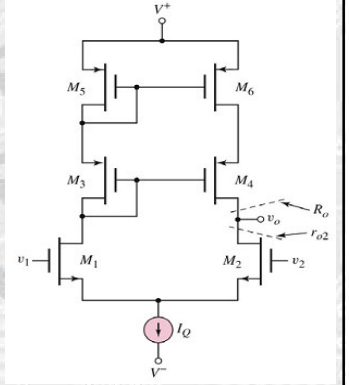


Figure 11.36: MOSFET diff amp with cascode active load.