

(8)

Gain Stage and Simple Output Stage

Reference: Neamen, Chapter 11

1

Learning Outcome

Able to:

- Analyze an example of a gain stage and output stage of a multistage amplifier.

2

8.0) Introduction

- In virtually all operational amplifiers (**op-amps**), there are **3 stages**:

- 1) First stage is **Input Stage** → Diff-amp with active load → to amplify difference between input signals v_1 and v_2 .
- 2) Second stage is **Gain Stage** → Darlington pair → to provide additional gain.
- 3) Third stage is **Output Stage** → Emitter follower → to minimize loading effect on output signal.


3

8.1) Darlington Pair and Simple Emitter-Follower Output

- Figure 11.46** shows a **BJT diff-amp** with a **3-transistor active load**, a **Darlington pair** connected to the diff-amp output, and a simple **emitter-follower output stage**.
- Diff-pair transistors (Q_1 and Q_2) are biased with a **Widlar current source** at a bias current I_Q .
- For the diff-amp currents **to be balanced**:

$$I_O = I_{B5} = \frac{I_Q}{\beta(1 + \beta)} \quad (11.118)$$

4

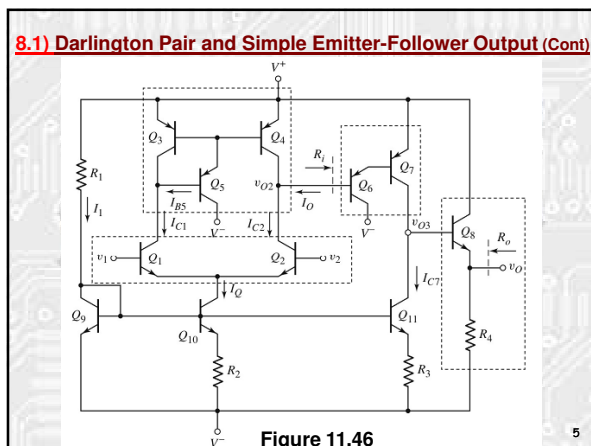

8.1) Darlington Pair and Simple Emitter-Follower Output (Cont)

- From the figure, can be seen

$$I_O = \frac{I_{E6}}{(1 + \beta)} = \frac{I_{C7}}{\beta(1 + \beta)} \quad (11.119)$$

- In order for $I_O = I_{B5}$, require that $I_{C7} = I_Q$
 → Means that emitter resistors of Q_{10} and Q_{11} should have same value (i.e. $R_2 = R_3$).
- Q_{11} also **acts as an active load** for Darlington pair gain stage.
- Q_8 and R_4 form the simple emitter-follower output stage → minimizes loading effects because its output resistance is small.

6

8.1 Darlington Pair and Simple Emitter-Follower Output (Cont)

• **Ideally:**

- When diff-amp input is a pure common-mode signal, the output $v_o = 0$.
- The combination of Q_7 and Q_{11} allows dc level to shift.
- By slightly changing bias current I_{C7}
 - V_{EC7} and V_{CE11} can be varied such that $v_o = 0$.
- This small variation in I_{C7} will not significantly change the balance between I_O and I_{B5} .

7

8.2 Darlington Pair: Input Impedance

- The input resistance of Darlington pair (Q_6 and Q_7) determines the loading effect on basic diff-amp.
- The gain of Darlington pair affects the overall gain of the op-amp circuit, and the output resistance of the emitter follower determines any loading effects on the output signal.
- **Figure 11.47(a)** is the **ac equivalent circuit** of the Darlington pair, where R_{L7} is the effective resistance connected between collector of Q_7 and signal ground.
- **Figure 11.47(b)** is the **simple hybrid- π model** of the Darlington pair Q_6 and Q_7 turned upside down.

8

8.2 Darlington Pair: Input Impedance (Cont)

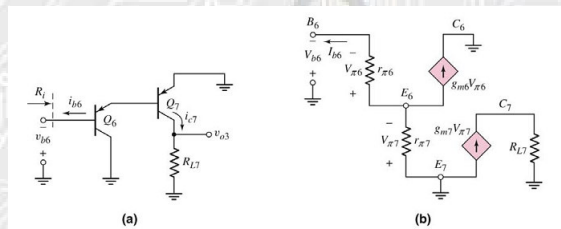


Figure 11.47: The Darlington pair's
(a) ac equivalent circuit, and
(b) small-signal equivalent circuit

9

8.2 Darlington Pair: Input Impedance (Cont)

- Writing a KVL equation around the B-E loop of Q_6 and Q_7 can obtain

$$V_{b6} = V_{\pi6} + V_{\pi7} \quad (11.120)$$

Also $V_{\pi6} = I_{b6} r_{\pi6} \quad (11.121)$

- The KCL equation at node E_6 is

$$\frac{V_{\pi7}}{r_{\pi7}} = \frac{V_{\pi6}}{r_{\pi6}} + g_{m6} V_{\pi6}$$

or $V_{\pi7} = r_{\pi7} \left[\frac{(1+\beta)}{r_{\pi6}} \right] V_{\pi6} = r_{\pi7} (1+\beta) I_{b6} \quad (11.122(b))$

where $r_{\pi6} g_{m6} = \beta$

10

8.2 Darlington Pair: Input Impedance (Cont)

- Substitute (11.122(b)) and (11.121) into (11.120) to obtain

$$V_{b6} = I_{b6} r_{\pi6} + r_{\pi7} (1+\beta) I_{b6} \quad (11.123)$$

- The input resistance is therefore

$$R_i = \frac{V_{b6}}{I_{b6}} = r_{\pi6} + r_{\pi7} (1+\beta) \quad (11.124)$$

- Assuming $I_{C7} = I_Q$, the **hybrid- π** parameters are

$$r_{\pi7} = \frac{\beta V_T}{I_{C7}} = \frac{\beta V_T}{I_Q} \quad (11.125(a))$$

$$r_{\pi6} = \frac{\beta V_T}{I_{C6}} = \frac{(1+\beta) \beta V_T}{I_Q} \quad (11.125(b)) \quad 11$$

8.2 Darlington Pair: Input Impedance (Cont)

- Combining (11.125(a)), (11.125(b)), and (11.124) yields an expression for **input resistance**, as follows:

$$R_i = \frac{(1+\beta) \beta V_T}{I_Q} + \frac{(1+\beta) \beta V_T}{I_Q} = \frac{2(1+\beta) \beta V_T}{I_Q} \quad (11.126)$$

12

8.3) Darlington Pair: Voltage Gain

- To determine **small-signal voltage gain** of the Darlington pair, from **Fig 11.47(b)** can be obtained

$$v_{o3} = i_{c7} R_{L7} = (\beta i_{b7}) R_{L7} = \beta(1 + \beta) i_{b6} R_{L7}$$

$$i_{b6} = \frac{v_{b6}}{R_i}$$

Voltage Gain: $A_v = \frac{v_{o3}}{v_{b6}} = \frac{\beta(1 + \beta) R_{L7}}{R_i}$

Thus, $A_v = \frac{\beta(1 + \beta) R_{L7}}{2(1 + \beta)\beta V_T} = \left(\frac{I_Q}{2V_T}\right) R_{L7}$ (11.130)

13

8.3) Darlington Pair: Voltage Gain (Cont)

- From **Figure 11.46**, can see that R_{L7} is the **parallel combination** of the resistance looking into collector of Q_{I1} and the resistance looking into base of Q_8 .

- Resistance looking into collector of Q_{I1} is

$$R_{cI1} = r_{o11} (1 + g_{m11} R'_E) \quad (11.131)$$

where $R'_E = r_{\pi11} \parallel R_3$

- Resistance looking into base of Q_8 is

$$R_{b8} = r_{\pi8} + (1 + \beta) R_4 \quad (11.132)$$

→ Since R_{cI1} and R_{b8} are large, then the effective resistance R_{L7} is also large.

14

8.3) Darlington Pair: Voltage Gain (Cont)

Example 11.13

Objective:

Calculate the input resistance and the small-signal voltage gain of a Darlington pair.

Consider the circuit shown in **Figure 11.46**, with parameters $I_{C7} = I_Q = 0.2 \text{ mA}$, $I_{C8} = 1 \text{ mA}$, $R_4 = 10 \text{ k}\Omega$, and $R_3 = 0.2 \text{ k}\Omega$. Assume $\beta = 100$ for all transistors, and the Early voltage for Q_{I1} is **100 V**.

15

8.3) Darlington Pair: Voltage Gain (Cont)

Example 11.13 (Cont)

Solution: The input resistance, given by Equation (11.126), is

$$R_i = \frac{2(1 + \beta)\beta V_T}{I_Q} = \frac{2(101)(100)(0.026)}{0.2\text{m}} \Rightarrow 2.63 \text{ M}\Omega$$

The small-signal voltage gain is a function of R_{L7} , which in turn is a function of R_{cI1} and R_{b8} . We can find that

$$r_{\pi11} = \beta V_T / I_Q = (100)(0.026)/(0.2\text{m}) = 13 \text{ k}\Omega$$

16

8.3) Darlington Pair: Voltage Gain (Cont)

Example 11.13 (Cont)

such that

$$R'_E = 13\text{k} \parallel 0.2\text{k} = 0.197 \text{ k}\Omega$$

Also

$$g_{m11} = I_Q / V_T = 0.2\text{m}/0.026 = 7.69 \text{ mA/V}$$

and

$$r_{o11} = V_A / I_Q = 100/0.2\text{m} = 500 \text{ k}\Omega$$

Therefore,

$$R_{cI1} = r_{o11} (1 + g_{m11} R'_E) = 1.26 \text{ M}\Omega$$

17

8.3) Darlington Pair: Voltage Gain (Cont)

Example 11.13 (Cont)

We can determine that

$$r_{\pi8} = \beta V_T / I_{C8} = (100)(0.026)/(1\text{m}) = 2.6 \text{ k}\Omega$$

Then

$$R_{b8} = r_{\pi8} + (1 + \beta) R_4 = 2.6\text{k} + (101)(10\text{k}) = 1.01 \text{ M}\Omega$$

Consequently, resistance R_{L7} is

$$R_{L7} = R_{cI1} \parallel R_{b8} = 1.26\text{M} \parallel 1.01\text{M} = 0.561 \text{ M}\Omega$$

Finally, from Equation (11.130), the small-signal voltage gain is

$$A_v = (I_Q / 2V_T) R_{L7} = 2158$$

18

8.4 Emitter Follower: Output Resistance

• From **Figure 11.46**, the output resistance of the emitter follower Q_8 is

$$R_o = R_4 \left\| \left(\frac{r_{\pi 8} + Z}{1 + \beta} \right) \right. \quad (11.133)$$

where Z is the equivalent impedance, or resistance, in the base of Q_8 .

- In this case, $Z = R_{c11} \parallel R_{c7}$, where R_{c7} is resistance looking into the collector of Q_7
- The factor $(1 + \beta)$ in the denominator makes output resistance of the emitter follower **normally small**.

19

8.4 Emitter Follower: Output Resistance (Cont)

Example 11.14

Objective:

Calculate the output resistance of the circuit in **Figure 11.46**.

Consider the same circuit and transistor parameters described in **Example 11.13**. Assume the Early voltage of Q_7 is **100 V**.

20

8.4 Emitter Follower: Output Resistance (Cont)

Example 11.14 (Cont)

Solution: From **Example 11.13**, we have that $R_{c11} = 1.26 \text{ M}\Omega$ and $r_{\pi 8} = 2.6 \text{ k}\Omega$.

We can determine that

$$R_{c7} = V_A / I_Q = 100 / 0.2\text{m} = 500 \text{ k}\Omega$$

Then,

$$Z = R_{c11} \parallel R_{c7} = 1.26\text{M} \parallel 500\text{k} = 358 \text{ k}\Omega$$

Therefore

$$R_o = R_4 \left\| \left(\frac{r_{\pi 8} + Z}{1 + \beta} \right) \right. = 10\text{k} \left\| \left(\frac{2.6\text{k} + 358\text{k}}{(101)} \right) \right. = 2.63\text{k}\Omega$$

21

8.5 Overall Gain of the Op-amp circuit

- Input stage: Diff-amp with active load $\rightarrow A_{V1} \approx 10^3$
- Gain stage: Darlington pair $\rightarrow A_{V2} \approx 10^3$
- Output stage: Emitter-follower $\rightarrow A_{V3} \approx 1$
- **Overall Gain:** $A_V = (A_{V1}) \cdot (A_{V2}) \cdot (A_{V3}) \approx 10^6$
 $\Rightarrow 10^6$ is the typical value for low-frequency, open-loop gain of the op-amp circuits

22

Larger circuits

23

8.1 Darlington Pair and Simple Emitter-Follower Output (Cont)

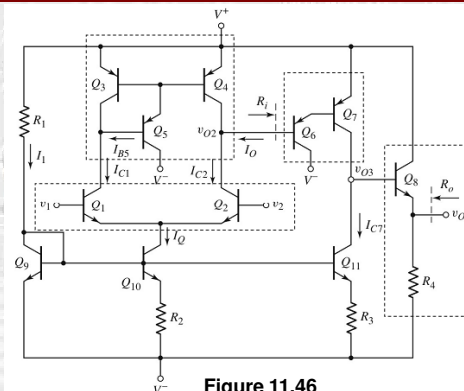


Figure 11.46

24

8.2) Darlington Pair: Input Impedance and Voltage Gain (Cont)

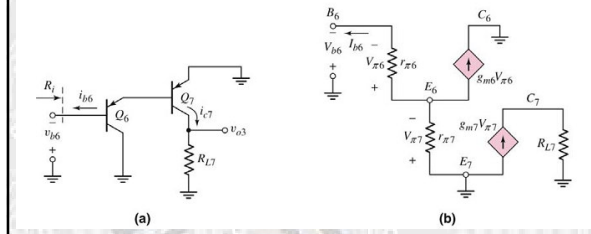


Figure 11.47: The Darlington pair's
 (a) ac equivalent circuit, and
 (b) small-signal equivalent circuit