

(9) Output Stages: Classes of Amplifiers

Reference: Neamen, Chapter 8

Learning Outcome

Able to:

- Define the various classes of power amplifiers and determine the maximum power efficiency of each class of amplifier.
- Analyze circuit configuration of:
 - ❑ Class-A operation,
 - ❑ Class-B operation,
 - ❑ Class-AB operation.

9.0) Classes of Amplifiers

- Power amplifiers in the output stage are classified according to the percent (%) of time the output transistors are conducting (turned on):
 - ❑ **Class A:** Output transistor is **biased** at a **quiescent current I_Q** and conducts for the **entire cycle** of the input signal.
 - ❑ **Class B:** Output transistor conducts for only **one-half** of each sine-wave input cycle.
 - ❑ **Class AB:** Output transistor **biased** at a **small quiescent current I_Q** , and conducts for **slightly more than half** a cycle.
 - ❑ **Class C:** Output transistors conducts for **less than half** a cycle.

9.0) Classes of Amplifiers (Cont)

Figure 8.15: Collector current versus time characteristics: (a) class-A amp, (b) class-B amp, (c) class-AB amp, and (d) class-C amp

9.1) Power Dissipation in BJT

9.1.1) Instantaneous power dissipation:

Is given by

$$P_Q = v_{CE}i_C + v_{BE}i_B \quad (8.1)$$

Generally $i_B \ll i_C$, then

$$P_Q \cong v_{CE}i_C \quad (8.2)$$

9.1.2) Average power:

Is obtained by integrating the instantaneous power dissipation over one cycle of the signal. So,

$$\overline{P_Q} = \frac{1}{T} \int_0^T v_{CE}i_C dt \quad (8.3)$$

9.1) Power Dissipation in BJT (Cont)

9.1.3) Power conversion efficiency:

Is defined as

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} \quad (8.12)$$

where $\overline{P_L}$ = average ac power delivered to load.
 $\overline{P_S}$ = average power supplied by PSU.

9.2) Class-A Operation (Ref: Sedra pp. 1231-1235)

9.2.1) Circuit diagram

Figure S1

- Emitter follower circuit, Fig S1 → low output resistance.
- Emitter follower Q_1 is biased with a constant current source I (supplied by transistor Q_2).
- Since $i_{E1} = I + i_L$
 - $I \geq$ largest negative load current
 - Else Q_1 cuts off, and class-A operation no longer maintained.

9.2) Class-A Operation (Cont)

9.2.2) Transfer Characteristics (TC)

- TC is described by:

$$v_O = v_i - v_{BE1}$$
- where v_{BE1} depends on i_{E1} and thus the load current i_L .

$$v_i = V_T \ln \left[\frac{I + \frac{v_O}{R_L}}{I_S} \right] + v_O$$

- Neglecting small changes in v_{BE1} the linear curve as shown above is obtained.

9.2) Class-A Operation (Cont)

9.2.2) Transfer Characteristics (Cont)

- Positive limit determined by the saturation of Q_1 :

$$v_{Omax} = V_{CC} - V_{CE1sat}$$
- Negative limit depends on the values of I_Q and R_L :
 - Q_1 turns off (small R_L): $v_{Omin} = -I R_L$
 - Q_2 saturating (large R_L): $v_{Omin} = -V_{CC} + V_{CE2sat}$
- Absolute lowest output voltage is when Q_2 saturating provided that:

$$I \geq \frac{-V_{CC} + V_{CE2sat}}{R_L}$$

9.2) Class-A Operation (Cont)

9.2.3) Signal Waveforms

- Assume a sine-wave input is applied to the Class A emitter follower circuit.

If bias current I is properly selected, v_O can swing from $-V_{CC}$ to $+V_{CC}$ (neglecting V_{CE1sat}).

Collector current of Q_1 waveform assuming that I is selected such that maximum negative load current is V_{CC}/R_L .

Waveform of instantaneous power dissipation in Q_1 where $p_{D1} = v_{CE1} i_{C1}$.

Maximum signal waveforms in class A output stage of Figure S1 under the condition $I = V_{CC}/R_L$.

9.2) Class-A Operation (Cont)

9.2.4) Power Dissipation

- Maximum instantaneous power dissipation in the Q_1 is $V_{CC}I$
 - $V_{CC}I =$ quiescent power dissipation in Q_1
 - Largest amount of power is dissipated when $v_O = 0$ (no-input signal).
 - Q_1 must be able to withstand a continuous power dissipation of $V_{CC}I$ since this condition (no-input signal) can easily prevail for prolonged periods of time.

9.2) Class-A Operation (Cont)

9.2.4) Power Dissipation (Cont)

- Power dissipation in Q_1 depends on R_L
 - $R_L = \infty$ (open circuit)
 - $I_{C1} = I =$ constant
 - Instantaneous power dissipation in Q_1 depends on v_O
 - Max. power dissipation occurs when $v_O = -V_{CC}$
 - $V_{CE1} = 2V_{CC} \rightarrow p_{D1} = 2V_{CC}I$
 - But condition is not prolonged
 - Average power dissipation in Q_1 is $V_{CC}I$.

9.2) Class-A Operation (Cont)
9.2.4) Power Dissipation (Cont)

- Power dissipation in Q_1 depends on R_L (Cont)
 - $R_L = 0$ (output short circuit) ~ dangerous!
 - Positive input voltage theoretically results in infinite (∞) load current.
 - Large power dissipation in Q_1 increases its temperature \rightarrow causing Q_1 to burn up.
 - Therefore, **need short circuit protection!**

13

9.2) Class-A Operation (Cont)
9.2.4) Power Dissipation (Cont)

- Power dissipation in Q_2
 - Also significant in emitter follower design.
 - Q_2 conducts constant current I .
 - $V_{CE2}(\text{max}) = 2V_{CC}$ (occurs when $v_o = V_{CC}$)
 \rightarrow Maximum instantaneous power dissipation in Q_2 is $2V_{CC}I$ and condition is not prolonged.
 - Average power dissipation in Q_2 is $V_{CC}I$

14

9.2) Class-A Operation (Cont)
9.2.5) Power Conversion Efficiency

- For the emitter follower of **Figure S1**, the output voltage is assumed a sinusoid with peak value V_p
 - The average load power will be:

$$\bar{P}_L = \frac{(V_p / \sqrt{2})^2}{R_L} = \frac{1}{2} \frac{V_p^2}{R_L}$$
 - Total average supply power is:

$$\bar{P}_S = \bar{P}_{S+} + \bar{P}_{S-} = 2V_{CC}I$$

15

9.2) Class-A Operation (Cont)
9.2.5) Power Conversion Efficiency (Cont)

- Since current in Q_2 is constant at I , average power drawn from the negative supply is $V_{CC}I$ (exclude other bias circuitry).
 - The average current in Q_1 is equal to I , thus average power drawn from the positive supply is $V_{CC}I$
- Therefore, **power conversion efficiency for Class A emitter follower:**

$$\eta = \frac{\bar{P}_L}{\bar{P}_S} = \frac{1}{4} \left(\frac{V_p}{IR_L} \right) \left(\frac{V_p}{V_{CC}} \right)$$

16

9.2) Class-A Operation (Cont)
9.2.5) Power Conversion Efficiency (Cont)

- Since $V_p \leq V_{CC}$ and $V_p \leq IR_L$, maximum efficiency is obtained when

$$V_p = V_{CC} = IR_L$$

$$\eta(\text{max}) = 1/4 \rightarrow 25\%$$
- Low $\eta(\text{max}) \rightarrow$ Class A is rarely used in high-power applications of more than 1W.
- In practice, output voltage swing is also limited to lower values to avoid transistor saturation.
- Typical efficiency is between **10% to 20%**.

17

9.2) Class-A Operation (Cont)
Example – Past question

A **class-A** emitter follower biased with a constant-current source is shown in the following **Figure**. Study the **Figure** carefully. Transistor parameters are: $\beta = 180$, $V_{BE} = 0.7$ V, and $V_{CE}(\text{sat}) = 0.2$ V. Neglecting base currents, **find**:

- The value of I_Q .
- The maximum and minimum values of i_{E1} and i_L .
- The value of R that will produce the maximum possible output signal swing.
- The conversion efficiency.

18

9.2) Class-A Operation (Cont)
Example – Past question (Cont)

19

9.2) Class-A Operation (Cont)
Example – Past question (Cont)

(i) $v_O(\max) = V^+ - V_{CE}(\text{sat}) = 10 - 0.2 = 9.8 \text{ V}$
 $I_Q = i_L(\max) = v_O(\max) / R_L = 9.8 / 1\text{k} = 9.8 \text{ mA}$

(ii) $i_{EI}(\max) = 2 I_Q = 19.6 \text{ mA}$
 $i_{EI}(\min) = 0$

$i_L(\max) = I_Q = 9.8 \text{ mA}$
 $i_L(\min) = -I_Q = -9.8 \text{ mA}$

(iii) $R = (0 - V_{BE} - (-10)) / I_Q = 9.3 / 9.8\text{m} = 949 \Omega$

20

9.2) Class-A Operation (Cont)
Example – Past question (Cont)

(iv) $\bar{P}_L = \frac{1}{2} (i_L(\max))^2 R_L = \frac{1}{2} (9.8\text{m})^2 (1\text{k})$
 $\Rightarrow \bar{P}_L = 48.02\text{mW}$
 $\bar{P}_S = I_Q(V^+ - V^-) + I_Q(0 - V^-)$
 $\Rightarrow \bar{P}_S = 9.8\text{m}(20) + 9.8\text{m}(10) = 294\text{mW}$
 $\eta = \frac{\bar{P}_L}{\bar{P}_S} = \frac{48.02\text{m}}{294\text{m}} = 16.3\%$

21

9.2) Class-A Operation (Cont)
Exercises

Exercise 1
 For the emitter follower in Fig. S1, $V_{CC} = 15\text{V}$, $V_{CE(\text{sat})} = 0.2\text{V}$, $V_{BE} = 0.7\text{V}$ and constant, and β is very high. Find the value of R that will establish a bias current sufficiently large to allow the largest possible output swing for $R_L = 1\text{k}\Omega$. Determine the resulting output signal swing and the minimum and maximum emitter currents.
 (Answer: $R = 0.97 \text{ k}\Omega$, $-14.8 \text{ V} \leq v_O \leq 14.8 \text{ V}$, $0 \leq i_{E1} \leq 29.6 \text{ mA}$)

Exercise 2
 For the emitter follower in Exercise 1, in which $I_Q = 14.8 \text{ mA}$, consider the case in which v_O is limited to the range -10 V to $+10 \text{ V}$. Let Q_1 have $v_{BE} = 0.6\text{V}$ at $i_C = 1 \text{ mA}$, and assume $\alpha \approx 1$. Find v_{in} corresponding to $v_O = -10\text{V}$, 0V , and $+10\text{V}$.
 (Answer: -9.63 V , 0.64 V , 10.68 V)

22

9.2) Class-A Operation (Cont)
Exercises (Cont)

Exercise 3 - Power Dissipation
 Consider the emitter follower in Fig. S1, with $V_{CC} = 10\text{V}$, $I_Q = 100\text{mA}$ and $R_L = 100\Omega$. Find the power dissipated in Q_1 and Q_2 under quiescent conditions ($v_O = 0$). For a sinusoidal output voltage of maximum possible amplitude (neglecting $V_{CE(\text{sat})}$), find the average power dissipation in Q_1 and Q_2 . Also find the load power.
 (Answer: 1 W , 1 W , 0.5 W , 1 W , 0.5 W)

Exercise 4 – Conversion Efficiency
 For the emitter follower of Fig. S1, let $V_{CC} = 10\text{V}$, $I_Q = 100 \text{ mA}$, and $R_L = 100\Omega$. If the output voltage is an 8-V-peak sinusoid, find the following:
 (a) Power delivered to the load
 (b) The average power drawn from the supplies
 (c) The power conversion efficiency
 Ignore the loss in Q_3 and R.
 (Answer: 0.32 W , 2 W , 16%)

23

9.3) Class-B Operation
9.3.1) Idealized Class-B Output Stage

Figure 8.18: Idealized complementary pair of electronic devices

Fig (a): $v_I = 0$, both devices off, $\Rightarrow v_O = 0$

Fig (b): $v_I > 0$, device A turns on, supply current to load.

Fig (c): $v_I < 0$, device B turns on, sink current from load.

Fig (d): Voltage transfer characteristics \rightarrow Unity voltage gain.

24

9.3) Class-B Operation (Cont)

9.3.2) Approximate Class-B Circuit

- $v_I = 0$, both Q_n & Q_p cut-off, $v_O = 0$
- Assume $V_{BE(on)} = 0.6V$
- $\rightarrow v_O$ remains 0 as long as $-0.6V \leq v_I \leq +0.6V$

Figure 8.19: Basic complementary BJT push-pull output stage.

25

9.3) Class-B Operation (Cont)

9.3.2) Approximate Class-B Circuit (Cont)

- $v_I > +0.6V$, Q_n turns on and operates as emitter follower
- I_L is positive, supplied thru Q_n
- B-E junction of Q_p is reverse-biased

Figure 8.19: Basic complementary BJT push-pull output stage.

26

9.3) Class-B Operation (Cont)

9.3.2) Approximate Class-B Circuit (Cont)

- $v_I < -0.6V$, Q_p turns on and operates as emitter follower
- Q_p sinks I_L , which is negative
- B-E junction of Q_n is reverse-biased

Figure 8.19: Basic complementary BJT push-pull output stage.

27

9.3) Class-B Operation (Cont)

9.3.2) Approximate Class-B Circuit

\rightarrow Complementary push-pull output stage:

- Q_n conducts during positive $\frac{1}{2}$ cycle.
- Q_p conducts during negative $\frac{1}{2}$ cycle.
- Q_n & Q_p do not conduct both at the same time.

Figure 8.19: Basic complementary BJT push-pull output stage.

28

9.3) Class-B Operation (Cont)

9.3.3) Transfer Characteristics

- Voltage gain of emitter follower ≈ 1 .
- Each transistor actually conducts for slightly less than half the input voltage cycle.
- Dead band: range of input voltage where v_O is zero \rightarrow Where both transistors are cut-off.

Figure 8.20: Voltage transfer characteristics of basic complementary push-pull output stage.

29

9.3) Class-B Operation (Cont)

9.3.4) Crossover Distortion

- Dead band produces a crossover distortion, Figure 8.21.
- Crossover distortion can be virtually eliminated by biasing both transistors with a small quiescent collector current when v_I is zero (class-AB output stage ~ next topic!).

Figure 8.21: Crossover distortion of basic complementary push-pull output stage.

30

9.3) Class-B Operation (Cont)

9.3.5) Idealized Power Efficiency

• **Figure 8.22** shows the effective dc load line for ideal Class B output stage (Fig 8.18), i.e. $V_{BE(on)}=0$ V.

• The Q-point is at zero collector current, or at cutoff for both transistors. The quiescent power dissipation is then zero since $p_Q = v_{CE} i_C$

Figure 8.22: Effective load line of class-B output stage.

9.3.5) Idealized Power Efficiency (Cont)

9.3.5.1) Average Power Dissipation

• **Output voltage** for the idealized class-B output stage:

$$v_o = V_p \sin \omega t \quad (8.16)$$

where **maximum** possible value of V_p is V_{CC}

• **The instantaneous power dissipation in Q_n** is

$$p_{Qn} = v_{CEn} i_{Cn} \quad (8.17)$$

where the collector current is

$$i_{Cn} = (V_p / R_L) \sin \omega t \quad \text{for } 0 \leq \omega t \leq \pi,$$

and $i_{Cn} = 0$ for $\pi \leq \omega t \leq 2\pi$

9.3.5) Idealized Power Efficiency (Cont)

9.3.5.1) Average Power Dissipation (Cont)

• From **Figure 8.22**, C-E voltage can be written as:

$$v_{CEn} = V_{CC} - V_p \sin \omega t \quad (8.19)$$

• Therefore, **the total instantaneous power dissipation in Q_n** is

$$p_{Qn} = (V_{CC} - V_p \sin \omega t)(V_p / R_L) \sin \omega t \quad \text{for } 0 \leq \omega t \leq \pi,$$

and $p_{Qn} = 0$ for $\pi \leq \omega t \leq 2\pi$

• **The average power dissipation** is therefore

$$\bar{P}_{Qn} = \frac{V_{CC} V_p}{\pi R_L} - \frac{V_p^2}{4 R_L} \quad (8.21)$$

9.3.5) Idealized Power Efficiency (Cont)

9.3.5.1) Average Power Dissipation (Cont)

• The average power dissipation in Q_p is exactly **the same as that for Q_n because of symmetry.**

• A plot of the average power dissipation in each transistor as a function of V_p is shown in **Fig 8.23**

Figure 8.23: Average power dissipation in each transistor versus peak output voltage for class-B output stage.

9.3.5) Idealized Power Efficiency (Cont)

9.3.5.1) Average Power Dissipation (Cont)

• The power dissipation first increases with increasing output voltage, reaches a maximum at $V_p = 2V_{CC}/\pi$, and finally decreases with increasing V_p .

• **The maximum average power dissipation** is given by

$$\bar{P}_{Qn}(\max) = \frac{V_{CC}^2}{\pi^2 R_L} \quad (8.22)$$

which occurs when

$$V_p \Big|_{\bar{P}_{Qn}(\max)} = \frac{2V_{CC}}{\pi} \quad (8.23)$$

9.3.5) Idealized Power Efficiency (Cont)

9.3.5.2) Power Conversion Efficiency (η)

• **The average power** delivered to the load is

$$\bar{P}_L = \frac{1}{2} \frac{V_p^2}{R_L} \quad (8.24)$$

• Since the average current supplied by each PS is $V_p / (\pi R_L)$

→ **The average power supplied** by each PS source is therefore

$$\bar{P}_{S+} = \bar{P}_{S-} = V_{CC} \left(\frac{V_p}{\pi R_L} \right) \quad (8.25)$$

9.3.5) Idealized Power Efficiency (Cont)
9.3.5.2) Power Conversion Efficiency (η) (Cont)

→ The total average power supplied by the two sources is

$$\bar{P}_s = 2V_{CC} \left(\frac{V_p}{\pi R_L} \right) \quad (8.26)$$

- The conversion efficiency (from 8.12) is then

$$\eta = \frac{\frac{1}{2} \frac{V_p^2}{R_L}}{2V_{CC} \left(\frac{V_p}{\pi R_L} \right)} = \frac{\pi}{4} \frac{V_p}{V_{CC}} \quad (8.27)$$

37

9.3.5) Idealized Power Efficiency (Cont)
9.3.5.2) Power Conversion Efficiency (η) (Cont)

- The maximum possible efficiency occurs when $V_{CC} = V_p$ is

$$\eta(\max) = \frac{\pi}{4} \Rightarrow 78.5\% \quad (8.28)$$

→ This maximum efficiency value is **substantially larger than of standard class-A amplifier.**

- From (8.24), maximum possible average power that can be delivered to the load is

$$\bar{P}_L(\max) = \frac{1}{2} \frac{V_{CC}^2}{R_L} \quad (8.29)$$

38

9.3.5) Idealized Power Efficiency (Cont)
9.3.5.2) Power Conversion Efficiency (η) (Cont)

- Practically, the conversion efficiency obtained is less than the 78.5% due to other circuit losses, and because $V_p < V_{CC}$ to avoid transistor saturation.
- Conversion efficiency at maximum transistor power dissipation (i.e. $V_p = 2 V_{CC}/\pi$) is

$$\eta = \frac{\pi}{4V_{CC}} \cdot V_p = \left(\frac{\pi}{4V_{CC}} \right) \cdot \left(\frac{2V_{CC}}{\pi} \right) = \frac{1}{2} \Rightarrow 50\%$$

39

9.3.5) Idealized Power Efficiency (Cont)
9.3.5.2) Power Conversion Efficiency (η) (Cont)

Example – Past question

An idealized class B output stage is to deliver 35 W of average power to a 25Ω load for a symmetrical input sine wave. The maximum output voltage is required to be 80% of the power supply voltage.

- Find the power supply voltage.
- With that power supply voltage, calculate the value of the power conversion efficiency η .

40

9.3.5) Idealized Power Efficiency (Cont)
9.3.5.2) Power Conversion Efficiency (η) (Cont)


Example – Past question (Cont)

$P_L^* = 35 \text{ W}, R_L = 25\Omega$
 $P_L^* = (1/2)(V_p^2/R_L) \Rightarrow 35 = (1/2)(V_p^2/25)$
 $V_p = 41.83 \text{ V} = 0.8 V_{CC}$
 $V_{CC} = V_p / 0.8 = 52.3 \text{ V}$

→ $P_S^* = (2 V_{CC})(V_p/\pi R_L) = (2 \times 52.3)(41.83/\pi(25))$
 $P_S^* = 55.7 \text{ W}$
 $\eta = P_L^* / P_S^* = 35/55.7 = 0.628 \text{ or } 62.8\%$

41

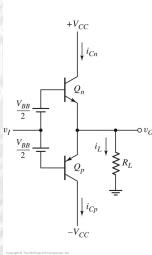9.4) Class-AB Operation
9.4.1) Circuit diagram



- Crossover distortion can be virtually eliminated by applying a small quiescent bias on each output transistor, for a zero input signal. This creates a **class-AB output stage** as shown in Figure 8.24.
- If Q_n & Q_p are matched: For $v_i = 0$, $V_{BE n} = V_{BE p} = V_{BB} / 2$, and $v_O = 0$
- Quiescent collector current $I_{CQ} = i_{Cn} = i_{Cp} = I_S \exp(V_{BB} / 2V_T)$

Figure 8.24: Bipolar class-AB output stage

42

9.4) Class-AB Operation (Cont)

9.4.2) Circuit operation

- As $v_I \uparrow$, $v_{BE_n} \uparrow$ and $v_O \uparrow$
- Q_n operates as emitter follower, supplying i_L to R_L
- Output voltage is

$$v_O = v_I + V_{BB} / 2 - v_{BE_n}$$
- Collector current of Q_n

$$i_{C_n} = i_L + i_{C_p}$$
- Since i_{C_n} must \uparrow to supply i_L , $v_{BE_n} \uparrow$. As V_{BB} constant, $v_{BE_n} \uparrow$ causes $v_{EB_p} \downarrow$, hence $i_{C_p} \downarrow$.
- As v_I goes negative, $v_{BE_p} \downarrow$ and $v_O \downarrow$
- Q_p sinks i_L from R_L
- Since $i_{C_p} \uparrow$, $v_{EB_p} \uparrow$, causes $v_{BE_n} \downarrow$, hence $i_{C_n} \downarrow$.

43

9.4) Class-AB Operation (Cont)

9.4.3) Characteristics

- **Figure 8.25** shows voltage transfer characteristics for the class-AB output stage.
- If v_{BE_n} and v_{EB_p} **do not change significantly**, then the **voltage gain is essentially unity**.
- Each Q conducts for more than $1/2$ cycle.

Figure 8.25:

- Voltage transfer curve
- Sinusoidal input signal
- Collector currents
- Output current

44

9.4) Class-AB Operation (Cont)

9.4.4) Relationship between i_{C_p} and i_{C_n}

- It is known $v_{BE_n} + v_{EB_p} = V_{BB}$

which can be written as

$$V_T \ln\left(\frac{i_{C_n}}{I_S}\right) + V_T \ln\left(\frac{i_{C_p}}{I_S}\right) = 2V_T \ln\left(\frac{I_{CQ}}{I_S}\right)$$

Combining terms, yields

$$i_{C_n} i_{C_p} = I_{CQ}^2 \quad (8.35)$$

→ The product of i_{C_n} and i_{C_p} is a constant.
Therefore, if $i_{C_n} \uparrow$ then $i_{C_p} \downarrow$, **but does not go to 0**.

45

9.4) Class-AB Operation (Cont)

9.4.4) Relationship between i_{C_p} and i_{C_n} (Cont)

Example – Past question

For the class AB output stage in **Figure 8.24**, given that $V_{CC}=15$ V and $V_{BB}=1.40$ V. $R_L=1$ k Ω . The reverse-bias saturation current for the transistors, $I_S=2 \times 10^{-15}$ A. Assume $\beta \gg 1$.

For the output voltage $v_O = -10$ V:

- Determine i_L , i_{C_n} , and i_{C_p} .
- Find the power dissipated in transistor Q_n .

46

9.4) Class-AB Operation (Cont)

9.4.4) Relationship between i_{C_p} and i_{C_n} (Cont)

Example – Past question (Cont)

$v_O = -10$ V = $i_L R_L$

→ $i_L = v_O / R_L = (-10$ V) / (1 k Ω) = **-10 mA**
Therefore, Q_p is conducting and Q_n is OFF.
 $i_L \approx i_{C_p} = I_S \exp(V_{EB_p} / V_T)$

$$V_{EB_p} = V_T \ln(i_{C_p} / I_S) = 26 \text{ m} \ln(10 \text{ m} / 2 \times 10^{-15})$$

$$V_{EB_p} = 0.7603 \text{ V}$$

$$V_{BE_n} = V_{BB} - V_{EB_p} = 1.4 - 0.7603 = 0.6397 \text{ V}$$

$$i_{C_n} = I_S \exp(V_{BE_n} / V_T) = 96.9 \text{ } \mu\text{A}$$

47

9.4) Class-AB Operation (Cont)

9.4.4) Relationship between i_{C_p} and i_{C_n} (Cont)

Example – Past question (Cont)

$$i_{C_n} = i_{C_p} + i_L$$

Actual value of $i_{C_p} = i_{C_n} - i_L = 96.9 \mu - (-10 \text{ m})$

$$i_{C_p} = 10.0969 \text{ mA}$$

$$P_{Q_n} = i_{C_n} V_{CE_n}$$

$$V_{CE_n} = +V_{CC} - v_O = +15 - (-10) = 25 \text{ V}$$

$$P_{Q_n} = (96.9 \text{ } \mu\text{A})(25 \text{ V}) = 2.42 \text{ mW}$$

48

9.4) Class-AB Operation (Cont)

Example 2 – Past question

For the class AB output stage in **Figure 8.24**, given that $V_{CC}=12\text{ V}$ and $V_{BB}=1.20\text{ V}$. $R_L=100\ \Omega$. The reverse-bias saturation current for the transistors, $I_S=4 \times 10^{-13}\text{ A}$. Assume $\beta \gg 1$.

49

9.4) Class-AB Operation (Cont)

Example 2 – Past question (Cont)

- i. For the case of the input voltage $v_I = 0$, calculate the quiescent collector currents, i_{Cn} and i_{Cp} , and the power dissipated in transistors Q_p and Q_n .
- ii. What is the maximum amplitude of the output voltage, v_O , and the corresponding maximum power that can be delivered to the load?
- iii. For the case of $v_O = -4 \sin \omega t\text{ V}$, determine i_L , i_{Cn} , i_{Cp} , and v_I .

50

9.4) Class-AB Operation (Cont)

Example 2 – Past question (Cont)

i.

$$i_{Cn} = i_{Cp} = I_S e^{\frac{V_{BB}}{2V_T}}$$

$$i_{Cn} = (4 \times 10^{-13}) \left(e^{\left[\frac{1.2}{(2)(0.026)} \right]} \right) = 4.210\text{ mA}$$

$$P_{Qn} = P_{Qp} = v_{CE} i_C$$

$$v_{CE} = 12\text{ V}$$

$$P_Q = (12)(4.210\text{ m}) = 50.52\text{ mW}$$

51

9.4) Class-AB Operation (Cont)

Example 2 – Past question (Cont)

ii.

$$v_{O(\text{max})} = 12\text{ V}$$

$$P_{L(\text{max})} = \frac{1}{2} \frac{V_p^2}{R_L} = (0.5) \left(\frac{12^2}{100} \right) = 0.72\text{ W}$$

52

9.4) Class-AB Operation (Cont)

Example 2 – Past question (Cont)

iii.

At $v_O = -4\text{ V}$ peak, the load current flows into Q_p ,

$$\text{thus } \begin{cases} i_{Cp} \cong i_L = \frac{v_O}{R_L} = \frac{-4 \sin \omega t}{100} = -40 \sin \omega t \text{ mA} \\ i_{Cn} = 0 \end{cases}$$

$$v_I = v_O - v_{EBp} + \frac{V_{BB}}{2}$$

$$v_{EBp} = V_T \ln \left[\frac{i_{Cp}}{I_S} \right] = (0.026) \ln \left[\frac{40\text{ m}}{4 \times 10^{-13}} \right] = 0.6585\text{ V}$$

$$v_I = -4 - 0.6585 + \frac{1.2}{2} = -4.0585$$

$$v_I = -4.0585 \sin \omega t\text{ V}$$

53

9.4) Class-AB Operation (Cont)

9.4.5) Comparison between class-AB and class-B

- In class-AB, quiescent collector current I_{CQ} exists even for a zero input signal. Hence:
 - The average power supplied by each source and the average power dissipated in each transistor are **larger** than class-B
 - The η will be **less** than an idealized class-B
 - The required power handling capability of Q_s in class-AB will be **slightly larger** than class-B. Since I_{CQ} is usually small compared to I_p , the increase in power dissipation is not great.

54

9.4) Class-AB Operation (Cont)

9.4.5) Comparison between class-AB and class-B (Cont)

- However, the advantage of **eliminating crossover distortion** greatly outweighs the disadvantage of reduced η and increased power dissipation.

Exercise 5
 Consider a Class AB circuit with $V_{CC} = 15\text{ V}$, $I_{CQ} = 2\text{ mA}$ and $R_L = 100\ \Omega$. Assume Q_n and Q_p are matched with $I_S = 10^{-13}\text{ A}$.

- Determine V_{BB}
- Find the values for i_{Cn} , i_{Cp} , V_{BEs} , V_{BEp} and v_{in} for $v_O = 0\text{ V}$, 1 V , 5 V , 10 V , -1 V , -5 V , -10 V .

55

9.4.6) Biasing of Class-AB

9.4.6.1) With Diode Biasing

- **Figure 8.31** shows the V_{BB} voltage established by voltage drops across diodes D_1 and D_2 .
- A constant current I_{Bias} establishes the required voltage across D_1 and D_2 (pair of diodes or diode-connected transistors)
- Since D_1 and D_2 may not be matched to Q_n and Q_p , hence I_{CQ} may not be equal to I_{Bias}

Figure 8.31: Quiescent bias established by diodes

56

9.4.6) Biasing of Class-AB (Cont)

9.4.6.1) With Diode Biasing (Cont)

- **Problem: V_{BB} is not constant**
- As $v_I \uparrow$, $v_O \uparrow$ so $i_{Cn} \uparrow$, hence $i_{Bn} \uparrow$
- $i_{Bn} \uparrow$ is supplied by I_{Bias} , the current through D_1 and $D_2 \downarrow$, hence $V_{BB} \downarrow$ slightly
- Since V_{BB} does not remain constant in this circuit, previous relationship for collector currents $i_{Cn}i_{Cp} = (I_{CQ})^2$ is not precisely valid for this situation

57

9.4.6) Biasing of Class-AB (Cont)

9.4.6.1) With Diode Biasing (Cont)

Design Example 8.9

Objective: Design the class-AB output stage in Figure 8.31 to meet specific design criteria.

Assume $I_{SD} = 3 \times 10^{-14}\text{ A}$ for D_1 and D_2 , $I_{SQ} = 10^{-13}$ for Q_n and Q_p , and $\beta_n = \beta_p = 75$. Let $R_L = 8\ \Omega$. The average power delivered to the load is to be **5 W**. The peak output voltage is to be no more than **80 percent** of V_{CC} , and the minimum value of diode current I_D is to be no less than **5 mA**.

58

9.4.6) Biasing of Class-AB (Cont)

9.4.6.1) With Diode Biasing (Cont)

Design Example 8.9 (Cont)

$$P_L^* = (1/2)(V_p^2/R_L)$$

$$V_p = \text{sqrt}[2 R_L P_L^*] = \text{sqrt}[2(8)(5)] = 8.94\text{ V}$$

The supply voltage must then be

$$V_{CC} = V_p / 0.8 = 8.94/0.8 = 11.2\text{ V}$$

At this peak output voltage, the emitter current of Q_n is approximately equal to the load current, or

$$i_{En} \approx i_L(\text{max}) = V_p(\text{max}) / R_L = 8.94/8 = 1.12\text{ A}$$

and the base current is

$$i_{Bn} = i_{En} / (1 + \beta_n) = 1.12/76 = 14.7\text{ mA}$$

59

9.4.6) Biasing of Class-AB (Cont)

9.4.6.1) With Diode Biasing (Cont)

Design Example 8.9 (Cont)

For a minimum $I_D = 5\text{ mA}$, we can choose $I_{Bias} = 20\text{ mA}$. For a zero input signal, neglecting base currents, we find that

$$V_{BB} = 2V_T \ln(I_D / I_{SD})$$

$$= 2(0.026) \ln(20 \times 10^{-3} / 3 \times 10^{-14}) = 1.416\text{ V}$$

The quiescent collector currents are then

$$I_{CQ} = I_{SQ} \exp(V_{BB} / 2 V_T)$$

$$= 10^{-13} \exp(1.416 / 2(0.026)) = 67.0\text{ mA}$$

60

9.4.6) Biasing of Class-AB (Cont)
9.4.6.1) With Diode Biasing (Cont)
Design Example 8.9 (Cont)

For $v_O = 8.94\text{ V}$ and $I_L = 1.12\text{ A}$, the base current is $i_{Bn} = 14.7\text{ mA}$, and $i_D = i_{Bias} - i_{Bn} = 5.3\text{ mA}$

The new value of V_{BB} is then

$$V_{BB} = 2V_T \ln(I_D / I_{SD}) = 2(0.026) \ln(5.3 \times 10^{-3} / 3 \times 10^{-14}) = 1.347\text{ V}$$

61

9.4.6) Biasing of Class-AB (Cont)
9.4.6.1) With Diode Biasing (Cont)
Design Example 8.9 (Cont)

The B-E voltage of Q_n is

$$v_{BE_n} = V_T \ln(i_{C_n} / I_{SQ}) = (0.026) \ln(1.12 / 10^{-13}) = 0.781\text{ V}$$

The E-B voltage of Q_p is then

$$v_{EB_p} = V_{BB} - v_{BE_n} = 1.347 - 0.781 = 0.566\text{ V}$$


and

$$i_{C_p} = I_{SQ} \exp(v_{EB_p} / V_T) = 10^{-13} \exp(0.566 / 0.026) = 0.285\text{ mA}$$

62

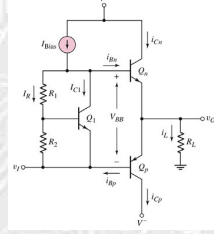9.4.6) Biasing of Class-AB (Cont)
9.4.6.2) Using the V_{BE} Multiplier

- Figure 8.32 shows voltage V_{BB} established by Q_1 , R_1 and R_2 , biased by constant-current source I_{Bias}



- Neglecting the base current in Q_1 , then $I_R = V_{BE1} / R_2$ (8.48)
- and voltage V_{BB} is $V_{BB} = I_R (R_1 + R_2) = V_{BE1} (1 + R_1 / R_2)$
- $\Rightarrow V_{BB}$ is a multiplication of V_{BE1} , circuit is **V_{BE} Multiplier**

Figure 8.32: Class-AB with V_{BE} Multiplier bias circuit

63

9.4.6) Biasing of Class-AB (Cont)
9.4.6.2) Using the V_{BE} Multiplier (Cont)

- A fraction of I_{Bias} flows through Q_1 , so that

$$V_{BE1} = V_T \ln(I_{C1} / I_S) \quad (8.50)$$

- Also, can neglect i_{Bn} and i_{Bp} because i_{Cn} and i_{Cp} are normally small. Current I_{Bias} divides between I_R and I_{C1} , satisfying both Equations (8.48) and (8.50).

$$I_{C1} = I_{Bias} - I_R$$

64

9.4.6) Biasing of Class-AB (Cont)
9.4.6.2) Using the V_{BE} Multiplier (Cont)

- Advantage of V_{BE} Multiplier:**
 - Design flexibility** as the multiplication factor is controlled by adjusting R_1 and R_2
 - V_{BB} is more constant
 - As $v_I \uparrow$, $v_O \uparrow$ so $i_{Cn} \uparrow$, hence $i_{Bn} \uparrow$
 - Now $I_{C1} \downarrow$, however the logarithmic dependence of V_{BE1} on I_{C1} means V_{BE1} and V_{BB} remains constant

65

Larger circuits

66

9.2) Class-A Operation (Ref: Sedra pp. 1231-1235)

Circuit diagram

Transfer Characteristics

Figure S1 67

9.2) Class-A Operation (Cont)

9.2.3) Signal Waveforms

Assume a **sine-wave input** is applied to the Class A emitter follower circuit.

If bias current I is properly selected, v_O can swing from $-V_{CC}$ to $+V_{CC}$ (neglecting V_{CEsat}).

Waveform of instantaneous power dissipation in Q_1 where $p_{DI} = v_{CE1}i_{C1}$

Maximum signal waveforms in class A output stage of **Figure S1** under the condition $I = V_{CC}/R_L$

9.2) Class-A Operation (Cont)

Example (Cont)

Figure 8.19: Basic Class-B circuit 69

9.3) Class-B Operation

9.3.1) Idealized Class-B Output Stage

Figure 8.18: Idealized complementary pair of electronic devices

Fig (a): $v_I = 0$, both devices off, $\rightarrow v_O = 0$

Fig (b): $v_I > 0$, device A turns on, supply current to load

Fig (c): $v_I < 0$, device B turns on, sink current from load

Fig (d): Voltage transfer characteristics \rightarrow **Unity** voltage gain 70

9.3) Class-B Operation (Cont)

9.3.2) Approximate Class-B Circuit

Figure 8.20: Voltage transfer characteristics

Figure 8.19: Basic Class-B circuit 71

9.4) Class-AB Operation

Figure 8.24: Bipolar class-AB output stage 72

Figure 8.25: (a) Voltage transfer curve (b) Sinusoidal input signal (c) Collector currents (d) Output current

9.4.6) Biasing of Class-AB

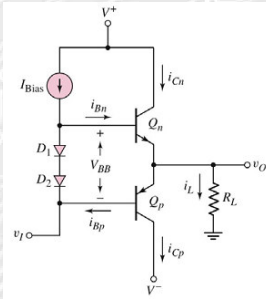


Figure 8.31: Quiescent bias established by diodes

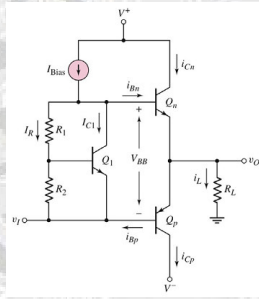


Figure 8.32: Class-AB with V_{BE} Multiplier bias circuit

73