



# **Basic Transistor Formula**

**Table 5.1: Summary of the bipolar current-voltage relationships in the active region**

For npn	For pnp
$i_C = I_S e^{v_{BE}/V_T}$	$i_C = I_S e^{v_{EB}/V_T}$
$i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{BE}/V_T}$	$i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{EB}/V_T}$
$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{BE}/V_T}$	$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{EB}/V_T}$


- $I_S$  = Saturation current (strongly dependant on device and temperature)
- $V_T$  = Thermal voltage
- $\beta$  = Common-emitter current gain
- $\alpha$  = Common-base current gain

**Table 5.1: Summary of the bipolar current-voltage relationships in the active region (Cont)**

<b>For both transistors</b>
$\alpha = \left( \frac{\beta}{1 + \beta} \right); \beta = \left( \frac{\alpha}{1 - \alpha} \right)$
$i_C = \beta i_B$
$i_C = \alpha i_E = \left( \frac{\beta}{1 + \beta} \right) i_E$
$i_E = i_B + i_C = (1 + \beta) i_B$

- $\beta$  = Common-emitter current gain
- $\alpha$  = Common-base current gain
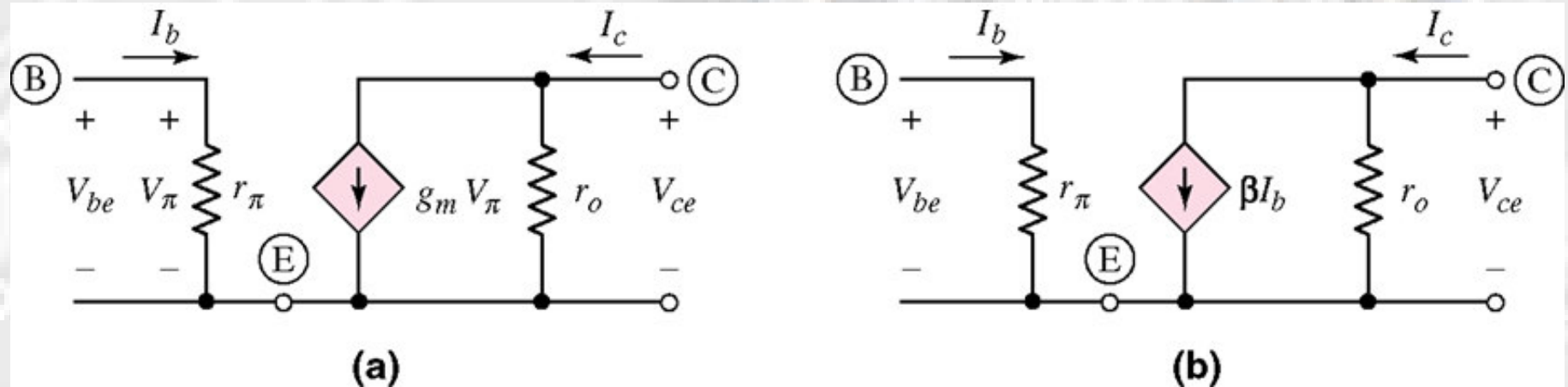
## Small-signal Hybrid- $\pi$ Equivalent Circuit of BJT



Expanded small-signal model of the BJT, including the Early effect when the circuit contains the

- (a) voltage controlled current source (transconductance)
- and (b) current controlled current source (current gain parameters)

**Note:** The small-signal model of a **pnp BJT** is the same as in **figure above** but with all ac voltage polarities and current directions reversed. All the parameter equations stated **next** still apply for the **pnp** transistor.

## Small-signal Hybrid- $\pi$ Equivalent Circuit of BJT (Cont)

<ul style="list-style-type: none"> <li>• Diffusion resistance:</li> </ul>	$r_{\pi} = \left[ \frac{\partial i_B}{\partial v_{BE}} \Big _{Q-pt} \right]^{-1} = \frac{\beta V_T}{I_{CQ}}$
<ul style="list-style-type: none"> <li>• Transconductance:</li> </ul>	$g_m = \left[ \frac{\partial i_C}{\partial v_{BE}} \Big _{Q-pt} \right] = \frac{I_{CQ}}{V_T}$
<ul style="list-style-type: none"> <li>• ac common-emitter current gain:</li> </ul>	$\beta = \left[ \frac{\partial i_C}{\partial i_B} \Big _{Q-pt} \right] = g_m r_{\pi}$
<ul style="list-style-type: none"> <li>• Small-signal transistor output resistance:</li> </ul>	$r_o = \left[ \frac{\partial i_C}{\partial v_{CE}} \Big _{Q-pt} \right]^{-1} = \frac{V_A}{I_{CQ}}$

# Current-voltage Relationships for MOSFET

Region	NMOS	PMOS
Non-saturation	$v_{DS} < v_{DS}(\text{sat})$ $i_D = K_n [2(v_{GS} - V_{TN})v_{DS} - v_{DS}^2]$	$v_{SD} < v_{SD}(\text{sat})$ $i_D = K_p [2(v_{SG} + V_{TP})v_{SD} - v_{SD}^2]$
Saturation	$v_{DS} \geq v_{DS}(\text{sat})$ $i_D = K_n [v_{GS} - V_{TN}]^2$	$v_{SD} \geq v_{SD}(\text{sat})$ $i_D = K_p [v_{SG} + V_{TP}]^2$
Transition Point	$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$	$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$
Enhancement Mode	$V_{TN} > 0V$	$V_{TP} < 0V$
Depletion Mode	$V_{TN} < 0V$	$V_{TP} > 0V$

## Current-voltage Relationships for MOSFET (Cont)

### Conduction Parameters

- NMOSFET: 
$$K_n = \frac{W\mu_n C_{ox}}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

- PMOSFET: 
$$K_p = \frac{W\mu_p C_{ox}}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

where:

$$C_{ox} = \epsilon_{ox} / t_{ox}$$

is the oxide capacitance per unit area


## Current-voltage Relationships of MOSFET (Cont)

$\mu_n$	mobility of electrons
$\mu_p$	mobility of holes
$\epsilon_{ox}$	oxide permittivity
$t_{ox}$	oxide thickness
$W$	channel Width
$L$	channel Length
$k_n' = \mu_n C_{ox}$	process conduction parameter (provided by manufacturer for a particular process)

→ The channel geometry, i.e. **width-to-length ratio ( $W/L$ )**, is a variable in the design of MOSFETs that **can be utilized to produce specific current-voltage characteristics** in MOSFET circuits.


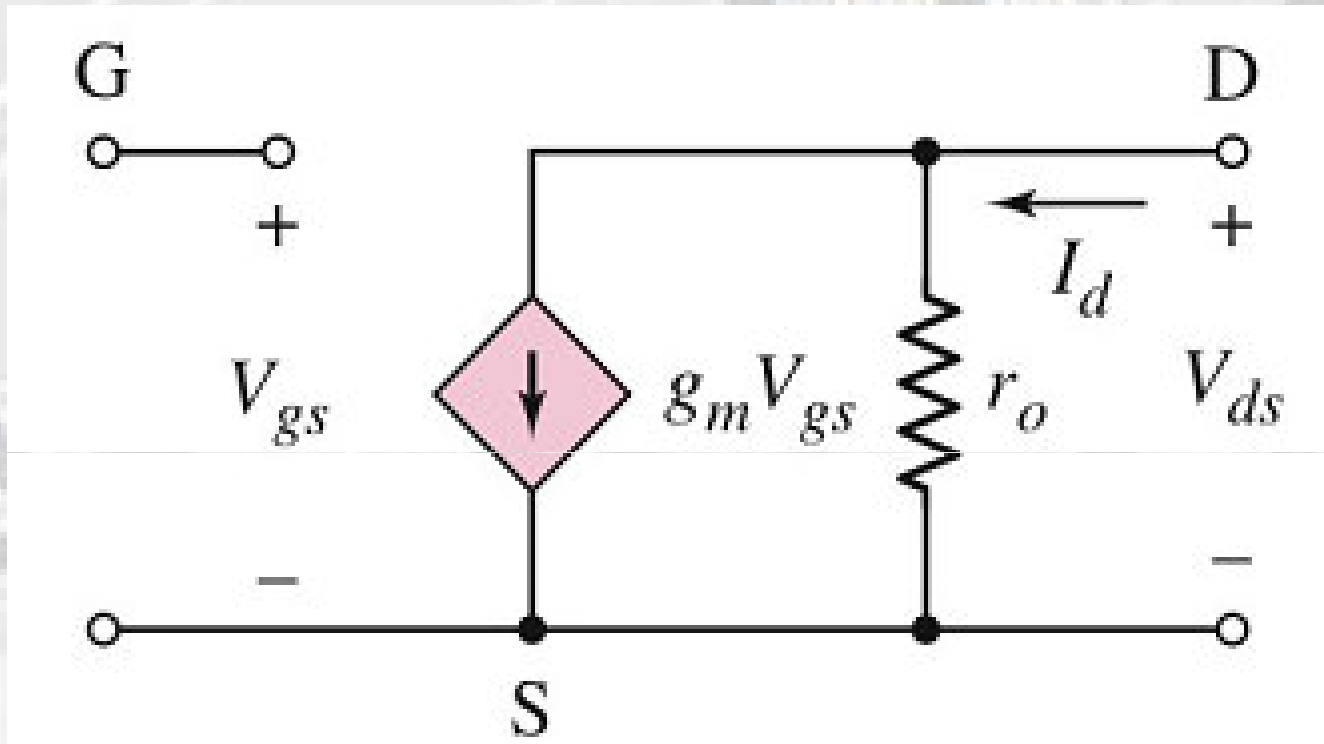
## Small-signal Hybrid- $\pi$ Equivalent Circuit of MOSFET



Expanded small-signal equivalent circuit,  
including output resistance,  
for NMOS transistor.

## Small-signal Hybrid- $\pi$ Equivalent Circuit of MOSFET (Cont)

- **Transconductance:**

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GSQ}=const} = 2K_n (V_{GSQ} - V_{TN}) = 2\sqrt{K_n I_{DQ}}$$

- **Small-signal transistor output resistance:**

$$r_o = \left[ \left. \frac{\partial i_D}{\partial v_{DS}} \right|_{v_{GS}=V_{GSQ}=const} \right]^{-1} = \left[ \lambda K_n (V_{GSQ} - V_{TN})^2 \right]^{-1} \cong \left[ \lambda I_{DQ} \right]^{-1}$$

Note: The small-signal model of a PMOS transistor is the same as in previous figure but with all ac voltage polarities and current directions reversed. All the parameter equations **stated above** still apply for the PMOS transistor.

## Finite Output Resistance

This effect is included in the drain current equation:

$$i_D = K_n \left[ (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS}) \right]$$

Output resistance,

$$r_o = \left[ \frac{\partial i_D}{\partial v_{DS}} \right]^{-1} \Big|_{v_{GS} = \text{const}} \cong \frac{1}{\lambda I_{DQ}} = \frac{V_A}{I_{DQ}}$$

where  $I_{DQ}$  = quiescent drain current.

Note:  $V_A$  is analogous to Early voltage of a BJT.