



**COLLEGE OF ENGINEERING  
PUTRAJAYA CAMPUS  
FINAL EXAMINATION**

**SEMESTER 1 2019 / 2020**

**MODEL ANSWERS**

PROGRAMME	: Bachelor of Electrical & Electronics Engineering (Honours) Bachelor of Electrical Power Engineering (Honours)
SUBJECT CODE	: EEEB273/EEEB2014
SUBJECT	: ELECTRONIC ANALYSIS AND DESIGN II
DATE	: September 2019
DURATION	: 3 hours

---


**INSTRUCTIONS TO CANDIDATES:**

1. This paper contains **FIVE** (5) questions in **EIGHT** (8) pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided. Use **pen** to write your answer.
4. Write answer to different question on a **new page**.

---

***THIS QUESTION PAPER CONSISTS OF EIGHT (8) PRINTED PAGES INCLUDING THIS COVER PAGE.***

**Question 1 [20 marks]**

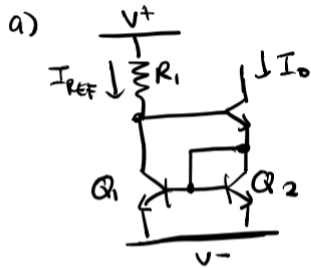

Chose Wilson CM - 2m.  
 Q2 diode connected - 1m.  
 Power Supply labelled - 1m.  
 I & Q labelled - 1m.

b)  $I_{REF} = I_{C1} + I_{B3}$  - 1m

$I_{E3} = I_{C2} + 2I_{B2} = I_{C2} (1 + \frac{2}{\beta})$  - 1m

$I_{C2} = \frac{I_{E3}}{(1 + \frac{2}{\beta})} = \frac{(1 + \beta)}{\beta(1 + \frac{2}{\beta})} I_{C3} = \frac{(1 + \beta)}{(2 + \beta)} I_{C3}$  - 1m.

$I_{REF} = \frac{(1 + \beta)}{(2 + \beta)} I_{C3} + \frac{I_{C3}}{\beta}$  - 1m

$I_O = I_{C3} = \frac{I_{REF}}{1 + \frac{2}{\beta(2 + \beta)}}$  - 1m.

c)  $\Rightarrow I_{REF} = I_O \times (1 + \frac{2}{\beta(2 + \beta)}) = 0.25m (1.0005)$   
 $= 0.25m$  - 1m.

$\Rightarrow V^+ = I_{REF} \cdot R_1 + V_{CE1} + V^-$  - 1m.

$\Rightarrow V_{CE1} = 2V_{BE}$  - 1m.

$\Rightarrow R_1 = \frac{V^+ - (2V_{BE} + V^-)}{I_{REF}}$   
 $= 34.4 k\Omega$  - 2m.

d)  $\Rightarrow \frac{dI_O}{dV_O} = \frac{1}{R_O}$   
 $dI_O = \frac{1}{R_O} \cdot dV_O$  - 1m

$\Rightarrow r_{O3} = \frac{V_A}{I_O} = \frac{100}{0.25m} = 400 k\Omega$  - 1m

$\Rightarrow R_O = \frac{\beta}{2} r_{O3} = 12 m\Omega$  - 1m

$\Rightarrow dV_O = 5 - 1 = 4V$  - 1m

$\Rightarrow dI_O = \frac{1}{12m} \times (4) = 333 nA$  - 1m.

**Question 2 [20 marks]****Q2(a) 5 marks**

$$I_{D1} = I_{D2} = 150 \mu\text{A} \quad V_{O2} = 3.5 \text{V}$$

$$R_D = \frac{V^+ - V_{O2}}{I_{D1}} \quad \text{--- 1m}$$

$$= 10 \text{ k}\Omega \quad \text{--- 1m.}$$

$$A_v = \frac{g_m R_D}{2} = \left[ \frac{2 \sqrt{K_{n1} (I_{O2})}}{2} \right] R_D \quad \text{--- 1m}$$

$$= \left[ \sqrt{100 \mu\text{A} \times 150 \mu\text{A}} \right] (10 \text{ k})$$

$$= 1.22 \text{ V/V} \quad \text{--- 1m.}$$

$$g_m = 0.245 \text{ mA/V} \quad \text{[1 mark]}$$

**Q2(b) 15 marks**

Power dissipation = 1mW = (V<sup>+</sup> - V<sup>-</sup>) (I<sub>Q</sub>) [1]

1m = (20) I<sub>Q</sub>

So I<sub>Q</sub> = 0.05mA = 50 uA [1]

Currents in diff pair ID1 = ID2 to ID6 = ½ I<sub>Q</sub> = 25 uA [1]

For V<sub>o</sub> to be 80% of power supply voltage, V<sub>o</sub> = 0.8(10) = 8 V [1]  
 -8V ≤ V<sub>o</sub> ≤ 8V

V<sub>o(max)</sub> = 8 V = V<sup>+</sup> - V<sub>SD6(sat)</sub> - V<sub>SD4(sat)</sub> [1]

Let all PMOS transistors in active load to be matched,  
 so V<sub>SD6(sat)</sub> = V<sub>SD4(sat)</sub> [1]

V<sub>o(max)</sub> = 8V = 10 - 2.V<sub>SD6(sat)</sub> [1]

V<sub>SD6(sat)</sub> = V<sub>SD4(sat)</sub> = 1 V [1]

V<sub>SD6(sat)</sub> = V<sub>SG6</sub> + V<sub>TP</sub>

1 = V<sub>SG6</sub> - 0.5

V<sub>SG6</sub> = 1.5 V = V<sub>SG4</sub> [1]

ID4 = ½ k<sub>p</sub>' (W/L)<sub>4</sub> (V<sub>SG4</sub> + V<sub>TP</sub>)<sup>2</sup> [0.5]

25u = ½ (25u) (W/L)<sub>4</sub> (1.5 - 0.5)<sup>2</sup>

(W/L)<sub>4</sub> = 2 = (W/L)<sub>3</sub> = (W/L)<sub>5</sub> = (W/L)<sub>6</sub> [1]

V<sub>o(min)</sub> = -8 V = V<sub>DS1(sat)</sub> + V<sub>IQ(min)</sub> + V<sup>-</sup> [1]

Assume for cascode,

V<sub>IQ(min)</sub> = 2 V<sub>DS(sat)</sub> = 2 V<sub>DS1(sat)</sub> [1]

V<sub>o(min)</sub> = -8 V = -10 + 3.V<sub>DS1(sat)</sub> [1]

V<sub>DS1(sat)</sub> = 0.67 V [0.5]

Thus,

ID1 = ½ k<sub>n</sub>' (W/L)<sub>1</sub> (V<sub>GS1</sub> - V<sub>TN</sub>)<sup>2</sup> [0.5]

25u = ½ (80u) (W/L)<sub>1</sub> (0.67)<sup>2</sup>

(W/L)<sub>1</sub> = 1.39 = (W/L)<sub>2</sub> [0.5]

**Question 3 [15 marks]**

**Q3(a) [5 marks]**

Q3, Q4, R4, and R5 in Gain Stage make Darlington Pair amplifier [2]

Q5, Q9, and R6 in Output Stage make voltage level translator [1]

Q6 and R7 in Output Stage make Common Collector or Emitter Follower [2]

**Q3(b) [10 marks]**

$$I_Q = 1.4 \text{ mA}$$

$$I_{C2} = I_Q / 2 = 0.7 \text{ mA} \quad [0.5]$$

$$v_{O2} = V^+ - I_{C2} R_C = 14 - (0.7\text{m})(10\text{k}) = 7 \text{ V} \quad [0.5]$$

$$I_{R4} = (v_{O2} - 2 V_{BE(\text{on})}) / (R_4) = (7 - 1.4) / (11.5\text{k}) = 0.487 \text{ mA} \quad [0.5]$$

Using  $I_{C2} = 0.7 \text{ mA}$ ,  $I_{R4} = 0.487 \text{ mA}$ :

$$A_{d1} = (g_{m2} / 2)(R_C \parallel R_{i2})$$

$$g_{m2} = I_{C2} / V_T = (0.7\text{mA}) / (26\text{mV}) = 26.923 \text{ mA/V} \quad [1]$$

$$r_{\pi4} = \beta V_T / I_{R4} = (200 \times 26\text{m}) / (0.487\text{m}) = 10.678 \text{ k}\Omega \quad [1]$$

$$r_{\pi3} \approx \beta r_{\pi4} = 200 \times 10.678\text{k} = 2135.6 \text{ k}\Omega \quad [1]$$

$$R_{i2} = r_{\pi3} + (1 + \beta) r_{\pi4} \quad [1]$$

$$= 2135.6\text{k} + (201)(10.678\text{k}) = 4281.88 \text{ k}\Omega \quad [0.5]$$

$$A_{d1} = (26.923\text{m}/2)(10\text{k} \parallel 4281.88\text{k}) = 134.3 \quad [0.5]$$

$$A_{v2} \approx (I_{R4} / 2V_T) R_5 = (0.487\text{m} / (2 \times 26\text{m}))(5\text{k}) = 46.83 \quad [1]$$


$$A_3 \approx 1 \quad (\text{Output Stage: assume gain} = 1) \quad [1]$$

$$A_d = A_{d1} A_{v2} A_3 \quad [1]$$

$$= 134.3 \times 46.83 \times 1 = 6289.27 \text{ V/V} \quad [0.5]$$

**Question 4 [25 marks]**

**Q4a [5 marks]**

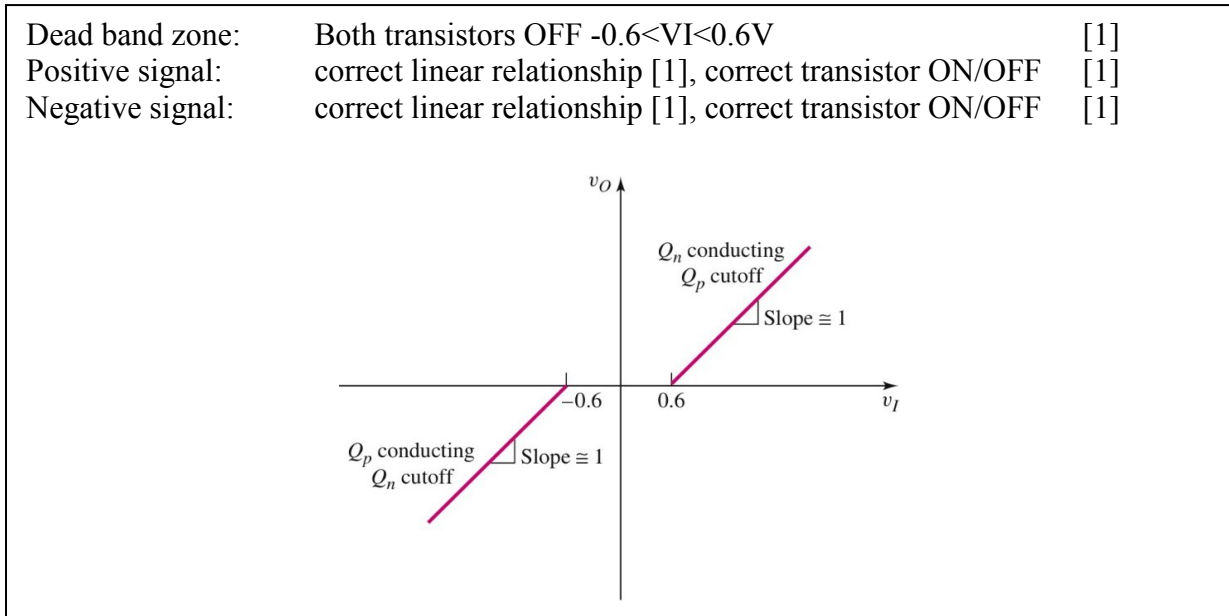

**Q4b [10 marks]**

<b><u>i) Quiescent condition</u></b>		
$V_{BB} = V_{BE_n} + V_{BE_p}$	$= 1.4 \text{ V}$	[1]
$I_{CQ} = i_{c_n} = i_{c_p} = I_S \cdot \exp((V_{BB}/2)/V_T)$		[1]
$= (5 \times 10^{-15}) \exp((1.4/2)/26m)$	$= 2.463 \text{ mA}$	[2]
<b><u>ii) <math>V_o = -3V</math></u></b>		
$I_L = V_o/R_L = -3/100$	$= -30 \text{ mA}$	[1]
I <sub>cp</sub> approx. equal to I <sub>L</sub> ,		
i.e. $I_{c_p} =  I_L $	$= 30 \text{ mA}$	[1]
$V_{BE_p} = (V_T) \ln(i_{c_p}/I_S)$		
$= (26m) \ln(30m/(5 \times 10^{-15}))$	$= 0.7649 \text{ V}$	[1]
$V_{BE_n} = V_{BB} - V_{BE_p} = 1.4 - 0.7649$	$= 0.6350 \text{ V}$	[1]
$I_{c_n} = I_S \cdot \exp((V_{BE_n})/V_T)$		
$= (5 \times 10^{-15}) \exp(0.6350V/26m)$	$= 0.2023 \text{ mA}$	[1]
Recalculate i <sub>cp</sub>		
$I_{c_p} = i_{c_n} - I_L$		
$= 0.2023 \text{ mA} - (-30mA)$	$= 30.202 \text{ mA}$	[1]

**Q4c [10 marks]**

$$\begin{aligned} \text{So } I_{set}/I_Q &= (W/L)_5/(W/L)_6 = (W/L)_5/4(W/L)_5 = 1/4 & [1] \\ \text{So } I_{set} &= I_Q/4 = 2\text{m}/4 = 0.5 \text{ mA} & [1] \end{aligned}$$

$$\begin{aligned} V_{IQ(\min)} &= V_{SD6(\text{sat})} = 1 \text{ V} & [1] \\ \text{So } V_{SD6(\text{sat})} &= V_{SG6} + V_{TP} \rightarrow 1 = V_{SG6} - 0.8 \\ V_{SG6} &= 1.8\text{V} = V_{SG5} = 1.8 \text{ V} & [1] \end{aligned}$$

From KVL,

$$\begin{aligned} R_{set} &= (V^+ - V_{SG5} - V^-) / I_{set} \\ &= (20 - 1.8) / 0.5\text{m} = 36.4 \text{ k}\Omega & [1] \end{aligned}$$

$$I_{set} = I_{D5} = \frac{1}{2} k_p' (W/L)_5 (V_{SG5} + V_{TP})^2 \quad [1]$$

$$0.5\text{m} = \frac{1}{2} (20\mu) (W/L)_5 (1.8 - 0.8)^2 = I_{D5}$$

$$(W/L)_5 = 50 \quad [0.5]$$

$$(W/L)_6 = 4(W/L)_5 = 4 \times 50 = 200 \quad [0.5]$$

$$V_{CM(\max)} = V^+ - V_{SD6(\text{sat})} - V_{SG1} \quad [1]$$

$$I_{D1} = \frac{1}{2} I_Q = \frac{1}{2} k_p' (W/L)_1 (V_{SG1} + V_{TP})^2$$

$$1\text{m} = \frac{1}{2} (20\mu) (20) (V_{SG1} - 0.8)^2$$

$$V_{SG1} = 3.0307\text{V} = 3.0307 \text{ V} \quad [1]$$

$$V_{CM(\max)} = 10 - 1 - 3.0307 = 5.9693 \text{ V} \quad [1]$$


**Question 5 [20 marks]**

**Q5(a) [6 marks]**

**Q5(a)(i) [3 marks]**

Inverting amplifier [1]

$$V_O = - (R_2 / R_1) V_I \quad [1]$$

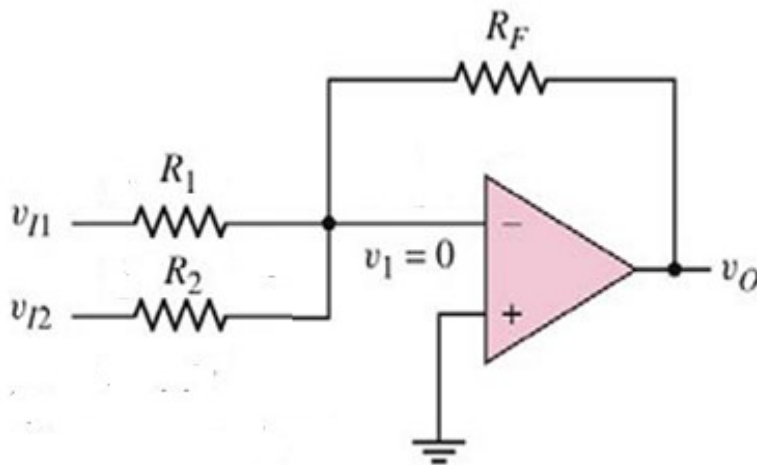

[1]

**Q5(a)(ii) [3 marks]**

Non-Inverting amplifier [1]

$$V_O = (1 + R_2 / R_1) V_I \quad [1]$$

$$V_O = (1 + 25k/25k)(1.5V) = 3V \quad [1]$$



**Q5(b) [6 marks]**

\*One method: Use **current analysis** at non-inverting input to get  $V_2$

$$\frac{V_{I1}-V_2}{40k} + \frac{V_{I2}-V_2}{20k} = \frac{V_2-0}{10k} \quad [1]$$

$$\frac{V_{I1}}{40k} + \frac{V_{I2}}{20k} = \frac{V_2}{10k} + \frac{V_2}{40k} + \frac{V_2}{20k} \quad [1]$$

$$V_{I1} + 2V_{I2} = 7V_2 \rightarrow V_2 = \frac{V_{I1}}{7} + \frac{2V_{I2}}{7} \quad [1]$$

\*May use other method (e.g. **superposition**) to get  $V_2 = \frac{V_{I1}}{7} + \frac{2V_{I2}}{7}$   
[Total marks = 3]

$$V_O = \left(1 + \frac{100k}{50k}\right) V_1 = 3 V_1 = 3 V_2 \quad \text{Virtual short!} \quad [1]$$

$$V_O = 3 \left(\frac{V_{I1}}{7} + \frac{2V_{I2}}{7}\right) = \frac{3}{7} V_{I1} + \frac{6}{7} V_{I2} \quad [1]$$

$$V_O = \frac{3}{7}(0.2) + \frac{6}{7}(0.3) = 0.3429 V \quad [1]$$

**Q5(c) [8 marks]**

$$i_1 = \frac{v_{I1}-v_{I2}}{R_1} \quad [1]$$

$$i_1 = \frac{[-0.65 + 0.05 \sin \omega t \text{ (V)}] - [-0.60 - 0.05 \sin \omega t \text{ (V)}]}{10k} \quad [0.5]$$

$$\rightarrow i_1 = -5 + 10 \sin \omega t \text{ (\mu A)} \quad [0.5]$$

$$v_{O1} = v_{I1} + i_1 R_2 \quad [1]$$

$$v_{O1} = [-0.65 + 0.05 \sin \omega t \text{ (V)}] + [-5 + 10 \sin \omega t \text{ (\mu A)}](40k) \quad [0.5]$$

$$\rightarrow v_{O1} = -0.85 + 0.45 \sin \omega t \text{ (V)} \quad [0.5]$$

$$v_{O2} = v_{I2} - i_1 R_2 \quad [1]$$

$$v_{O2} = [-0.60 - 0.05 \sin \omega t \text{ (V)}] + [-5 + 10 \sin \omega t \text{ (\mu A)}](40k) \quad [0.5]$$

$$\rightarrow v_{O2} = -0.40 - 0.45 \sin \omega t \text{ (V)} \quad [0.5]$$

$$v_O = \frac{R_4}{R_3} (v_{O2} - v_{O1}) \quad [1]$$

$$v_O = \frac{120k}{40k} ([-0.40 - 0.45 \sin \omega t \text{ (V)}] - [-0.85 + 0.45 \sin \omega t \text{ (V)}]) \quad [0.5]$$

$$\rightarrow v_O = 1.35 - 2.7 \sin \omega t \text{ (V)} \quad [0.5]$$