

Name:

Student ID Number:

Section Number: 01/02/03 A/B

Lecturer: Dr Fazrena Azlee/ Dr Jamaludin/

Dr Ahmad Wafi

Table Number:



College of Engineering
Department of Electrical and Electronics Engineering

Test 1 – MODEL ANSWERS

SEMESTER 1, ACADEMIC YEAR 2019/2020

Subject Code : **EEEEB2014/EEEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **13 July 2019**
Time Allowed : **2 hours**

Instructions to the candidates:

1. Write your Name and Student ID Number. Indicate your Section Number and Lecturer's Name. Write also your Table Number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS. Show clearly** all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.

☺ **GOOD LUCK!** ☺




Question Number	Q1(a)	Q1(b-d)	Q2(a)	Q2(b)	Q3(a)	Q3(b,c)	Total
Marks							

QUESTION 1 [35 marks]

Answers for Question 1

Question 1

(a)

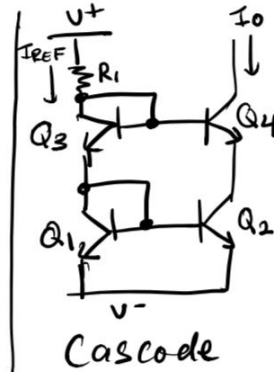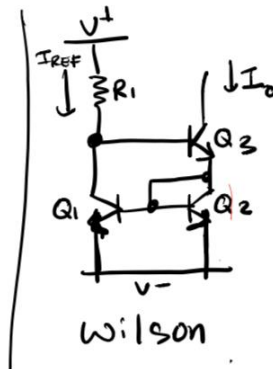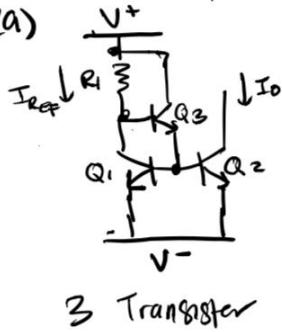

- 3 mark each for correct drawing (total 9 mark.)
- 1 mark extra for correct labelling

b)

3T

$$R_1 = \frac{V^+ - 2V_{BE} - V^-}{I_{REF}}$$

$$= \frac{20 - 2(0.7)}{1m}$$

$$= 18.6 k\Omega \text{ - 3m}$$

Wilson

$$R_1 = \frac{V^+ - 2V_{BE} - V^-}{I_{REF}}$$

$$= 18.6 k\Omega \text{ - 3m}$$

c)

3T Current Source

$$I_O = I_{REF} \times \frac{1}{1 + \frac{2}{\beta(1+\beta)}} \text{ - 1m}$$

$$= 0.992 \text{ mA}$$

- 3 m for correct equation & answer

$$R_O = r_{O2} = \frac{V_A}{I_O}$$

$$= 150 k\Omega$$

- 3 m for correct equation & answer

Wilson

$$I_O = I_{REF} \times \frac{1}{1 + \frac{2}{\beta(2+\beta)}}$$

$$= 0.992 \text{ mA}$$

- 3 m for correct equation & answer

$$R_O = \frac{\beta}{2} r_{O3} = \frac{\beta}{2} \left(\frac{V_A}{I_O} \right)$$

$$= 3.75 \text{ M}\Omega$$

- 3 m for correct equation & answer.

Answers for Question 1 (Continued)

$$d) \quad dV_o = 6 - 1 = 5V \quad -1m$$


$$\begin{aligned} & \underline{3I} \\ dI_o &= \frac{1}{R_o} \times dV_o \\ &= 33\mu A \quad -3m \end{aligned}$$

$$\begin{aligned} & \underline{wilson} \\ dI_o &= \frac{1}{R_o} \times dV_o \\ &= 1.33\mu A \quad -3m \end{aligned}$$

QUESTION 2 [30 marks]

Answers for Question 2

Q2a [5 marks]

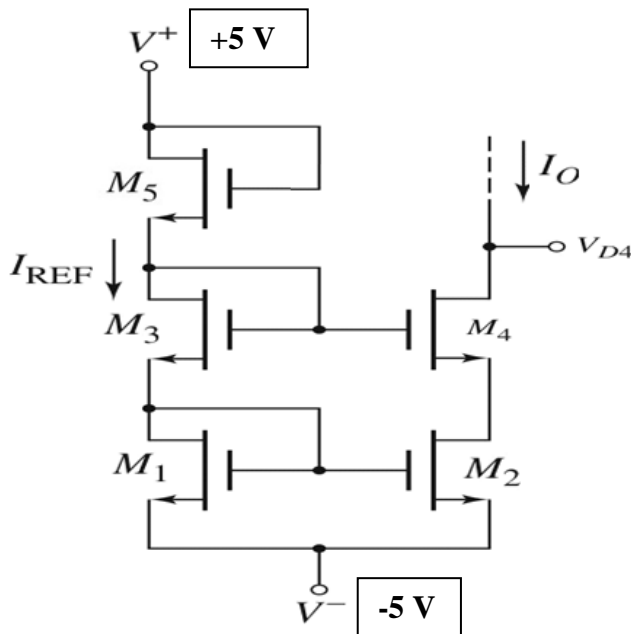

- Power supplies $+5\text{ V}$ and -5 V labelling: [1]
- Correct polarity & connection for M_1 to M_4 : [2]
- Correct polarity & connection for M_5 : [1]
- Correct labelling and arrow for I_{REF} and I_O : [1]

Answers for Question 2 (Continued)

Q2b(i) [17 marks]

$$I_{REF} = I_{D1} = I_{D3} \quad [2]$$

$$I_{REF} = \left(\frac{k'_p}{2}\right) \left(\frac{W}{L}\right)_1 (V_{SG1} + V_{TP})^2 = \left(\frac{k'_p}{2}\right) \left(\frac{W}{L}\right)_3 (V_{SG3} + V_{TP})^2 \quad [2]$$

$$V_{SG3} = 5 - V_{SG1} \quad [2]$$

$$\left(\frac{60\mu}{2}\right) (25)(V_{SG1} - 0.4)^2 = \left(\frac{60\mu}{2}\right) (5)(V_{SG3} - 0.4)^2 \quad [1]$$

$$\left(\frac{60\mu}{2}\right) (25)(V_{SG1} - 0.4)^2 = \left(\frac{60\mu}{2}\right) (5)(5 - V_{SG1} - 0.4)^2 \quad [1]$$

$$\sqrt{25/5}(V_{SG1} - 0.4) = (4.6 - V_{SG1})$$

$$2.236(V_{SG1} - 0.4) = (4.6 - V_{SG1})$$

$$3.236V_{SG1} = 5.4944 \rightarrow V_{SG1} = 1.698 \text{ V} \quad [2]$$

$$V_{SG3} = 5 - 1.698 = 3.302 \text{ V} \quad [1]$$

$$I_{REF} = I_{D1} = \left(\frac{k'_p}{2}\right) \left(\frac{W}{L}\right)_1 (V_{SG1} + V_{TP})^2 = \left(\frac{60\mu}{2}\right) (25)(1.698 - 0.4)^2 = 1.2636 \text{ mA} \quad [2]$$

$$V_{SG2} = V_{SG1} = 1.698 \text{ V} \quad [2]$$

$$I_O = I_{D2} = \left(\frac{k'_p}{2}\right) \left(\frac{W}{L}\right)_2 (V_{SG2} + V_{TP})^2 = \left(\frac{60\mu}{2}\right) (15)(1.698 - 0.4)^2 = 0.75816 \text{ mA} \quad [2]$$

Q2b(ii) [8 marks]

Maximum value of V_{D2} is when $V_{SD2} = V_{SD2}(\min) = V_{SD2}(\text{sat})$:

$$V_{D2} = V^+ - V_{SD2} \quad [1]$$

$$V_{D2}(\text{max}) = V^+ - V_{SD2}(\text{min}) = V^+ - V_{SD2}(\text{sat}) \quad [2]$$

$$V_{SD2}(\text{sat}) = V_{SG2} + V_{TP} = 1.698 - 0.4 = 1.298 \text{ V} \quad [1]$$

$$\rightarrow V_{D2}(\text{max}) = V^+ - V_{SD2}(\text{sat}) = 5 - 1.298 = 3.702 \text{ V} \quad [1]$$


Largest value of R is at $V_{D2}(\text{max})$:

$$R(\text{max}) = \frac{V_{D2}(\text{max}) - 0}{I_O} = \frac{3.702}{0.75816\text{mA}} = 4.88 \text{ k}\Omega \quad [3]$$

QUESTION 3 [35 marks]

Answers for Question 3

Q3(a) [10 marks]

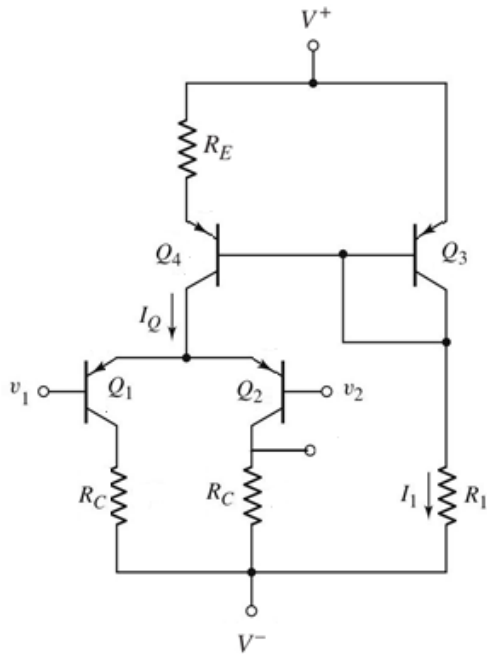

- Correct differential amplifier with R_C and inputs [2]
- Correct I_Q current source C4 to E1/E2 connection [1]
- V_+ and V_- [1]
- Correct **Widlar** current source connection [2]
- Correct I_1 (I_{ref}) side with diode connection [2]

Widlar is better than 2 transistor c.s. since it has higher output resistance (R_o) compared to 2 transistor c.s [2]

Or (choose either answer)

Widlar is used to provide a current source with lower output current [2]

Q3(b)(i)

[6 marks]

$$\begin{aligned}
 & \boxed{1} \qquad \boxed{1} \\
 i_{C1} &= I_S e^{v_{BE1}/V_T}, i_{C2} = I_S e^{v_{BE2}/V_T} \\
 I_Q &= i_{C1} + i_{C2} = I_S [e^{v_{BE1}/V_T} + e^{v_{BE2}/V_T}] \qquad \boxed{1} \\
 \frac{i_{C1}}{I_Q} &= \frac{I_S e^{v_{BE1}/V_T}}{I_S [e^{v_{BE1}/V_T} + e^{v_{BE2}/V_T}]} = \frac{I_S (e^{v_{BE1}/V_T}) / e^{v_{BE1}/V_T}}{I_S [e^{v_{BE1}/V_T} + e^{v_{BE2}/V_T}] / e^{v_{BE1}/V_T}} = \frac{1}{1 + e^{(v_{BE2}-v_{BE1})/V_T}} \qquad \boxed{1} \\
 \frac{i_{C2}}{I_Q} &= \frac{I_S e^{v_{BE2}/V_T}}{I_S [e^{v_{BE1}/V_T} + e^{v_{BE2}/V_T}]} = \frac{I_S (e^{v_{BE2}/V_T}) / e^{v_{BE2}/V_T}}{I_S [e^{v_{BE1}/V_T} + e^{v_{BE2}/V_T}] / e^{v_{BE2}/V_T}} = \frac{1}{1 + e^{-(v_{BE2}-v_{BE1})/V_T}} \qquad \boxed{1} \\
 v_{BE1} - v_{BE2} &= v_d \\
 \rightarrow i_{C1} &= \frac{I_Q}{1 + e^{(v_{BE2}-v_{BE1})/V_T}} = \frac{I_Q}{1 + e^{-v_d/V_T}} \qquad \boxed{0.5} \\
 \rightarrow i_{C2} &= \frac{I_Q}{1 + e^{-(v_{BE2}-v_{BE1})/V_T}} = \frac{I_Q}{1 + e^{+v_d/V_T}} \qquad \boxed{0.5}
 \end{aligned}$$

Q3(b)(ii)

[4 marks]

$$\begin{aligned}
 i_{C1} &= \frac{I_Q}{1 + e^{-v_d/V_T}} = \frac{I_Q}{1 + e^{-0/V_T}} = \frac{I_Q}{1 + 1} = \frac{I_Q}{2} \qquad \boxed{1} \\
 i_{C2} &= \frac{I_Q}{1 + e^{+v_d/V_T}} = \frac{I_Q}{1 + e^{0/V_T}} = \frac{I_Q}{1 + 1} = \frac{I_Q}{2} \qquad \boxed{1}
 \end{aligned}$$

When $v_d = 0$, $i_{C1} = i_{C2} = I_Q/2$ $\boxed{1}$

current I_Q splits evenly between i_{C1} and i_{C2} $\boxed{1}$

Q3(c)(i) [5 marks]

$$A_d = \frac{g_{m1}R_C}{2} \quad [1]$$

$$g_{m1} = \frac{I_{C1}}{V_T}, I_{C1} = I_{C2} = 1m \quad [1]$$

$$g_{m1} = \frac{1m}{26m} = 38.48 \text{ mA/V} \quad [1]$$

$$A_d = \frac{(38.46m)(15k)}{2} = 288.45 \text{ V/V} \quad [2]$$

Q3(c)(ii) [6 marks]

$$R_{id} = 2r_{\pi1} \quad [1]$$

$$r_{\pi1} = \frac{\beta V_T}{I_{C1}} = \frac{(100)(0.026)}{1m} = 2.6 \text{ k}\Omega \quad [0.5]$$

$$\text{So } R_{id} = 2(2.6k) = 5.2 \text{ k}\Omega \quad [0.5]$$

$$R_{icm} = (1 + \beta) \left[R_O \parallel \frac{r_{o1}}{2} \right] \quad [1]$$

$$R_o = \beta r_{o4} \quad [0.5]$$

$$r_{o4} = V_A/I_Q = 200/2m = 100k\Omega \quad [0.5]$$

$$R_o = (100)(100k\Omega) = 10M\Omega \quad [0.5]$$

$$r_{o1} = V_A/I_{c1} = 200/1m = 200k\Omega \quad [0.5]$$

$$R_{icm} = (1+100)(10M \parallel (200k/2)) = 10 \text{ M}\Omega \quad [1]$$

Q3(c)(iii) [4marks]

$$V_o = A_d V_d + A_{cm} V_{cm} \quad [1]$$

$$V_d = v_1 - v_2$$

$$= 200 \times 10^{-6} \sin \omega t \text{ V} - (-200 \times 10^{-6} \sin \omega t \text{ V}) = 400 \times 10^{-6} \sin \omega t \text{ V} \quad [1]$$

$$V_{cm} = \frac{1}{2} (v_1 + v_2) = \frac{1}{2} (200 \times 10^{-6} \sin \omega t \text{ V} + (-200 \times 10^{-6} \sin \omega t \text{ V})) = 0 \quad [1]$$

$$V_o = A_d V_d + 0$$

$$= (288.45)(400 \times 10^{-6} \sin \omega t \text{ V}) = 115.38 \times 10^{-3} \sin \omega t \text{ V} \quad [1]$$