

Name:  
Student ID Number:  
Section Number: 01/02/03 A/B  
Lecturer: Dr Fazrena Azlee/ Dr Jamaludin/  
Dr Ahmad Wafi  
Table Number:



**College of Engineering**  
Department of Electrical and Electronics Engineering

**Test 1**

**SEMESTER 1, ACADEMIC YEAR 2019/2020**

Subject Code : **EEEB2014/EEEB273**  
Course Title : **Electronics Analysis & Design II**  
Date : **13 July 2019**  
Time Allowed : **2 hours**

**Instructions to the candidates:**

1. Write your Name and Student ID Number. Indicate your Section Number and Lecturer's Name. Write also your Table Number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.** Show clearly all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

**NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.**

☺ **GOOD LUCK!** ☺

Question Number	Q1(a)	Q1(b-d)	Q2(a)	Q2(b)	Q3(a)	Q3(b,c)	Total
Marks							

## BASIC FORMULA FOR TRANSISTOR

### BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

Quadratic formula :

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

### MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

; Small signal

$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N - MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P - MOSFET}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

**This is extra page for answers. Please indicate question number clearly.**

**QUESTION 1 [35 marks]**

For all BJT current sources in this question, assume that all transistors are matched with parameters  $\beta = 50$ ,  $V_{BE(ON)} = 0.7 \text{ V}$ , and  $V_A = 150 \text{ V}$ . Other parameters are:  $V^+ = 10 \text{ V}$ ,  $V^- = -10 \text{ V}$  and  $I_{REF} = 1 \text{ mA}$

(a) Draw **nnp based Three-transistor Current Source, Wilson Current Source and Cascode Current Source**. Clearly indicate and label all components for each current sources

[10 marks]

(b) Calculate the resistor value  $R_1$  in for the **Three-transistor and Wilson current sources ONLY**

[6 marks]

(c) Calculate the **output current ( $I_o$ ) and output Resistance ( $R_o$ )** for the **current mirror given in part (b)**

[12 marks]

(d) **Find the change in output current ( $dI_o$ ) as the output voltage** for the two BJT current sources given in **part (b) changes by from 1V to 6V**.

[7 marks]

**Answers for Question 1**

**Answers for Question 1 (Continued)**

**QUESTION 2 [30 marks]**

- (a) Draw and label clearly a Cascode MOSFET current mirror using N-MOSFET devices  $M_1$  to  $M_4$  with additional transistor  $M_5$  is used to establish  $I_{REF}$ . The current mirror is powered by  $V^+ = +5\text{ V}$  and  $V^- = -5\text{ V}$  power supplies. [5 marks]
- (b) Figure 1 shows a two-transistor MOSFET current mirror with  $I_{REF}$  is established using another MOSFET  $M_3$ . The transistor parameters are:  $V_{TP} = -0.4\text{ V}$ ,  $k'_p = 60\ \mu\text{A}/\text{V}^2$ , and  $\lambda = 0$ . The transistor width-to-length ratios are  $(W/L)_1 = 25$ ,  $(W/L)_2 = 15$  and  $(W/L)_3 = 5$ .
- i) Determine  $I_O$ ,  $I_{REF}$ ,  $V_{SG1}$  and  $V_{SG3}$ . [17 marks]
- ii) Calculate the maximum value of  $V_{D2}$  and the largest value of  $R$  such that  $M_2$  remains biased in the saturation region. [8 marks]

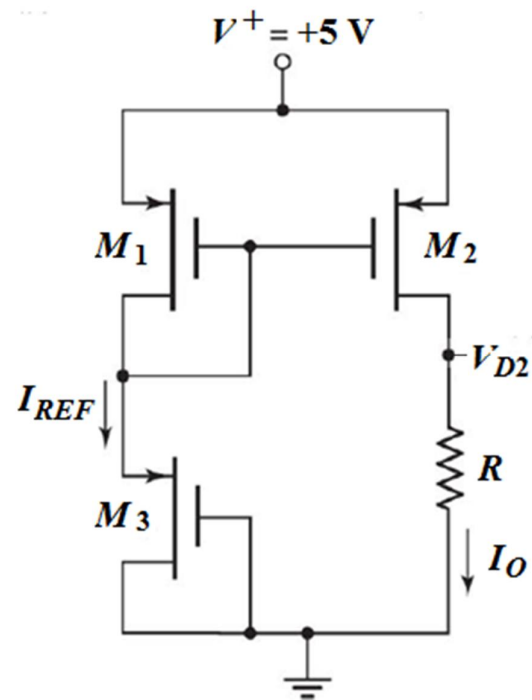
**Answers for Question 2**

Figure 1

**Answers for Question 2 (Continued)**

**QUESTION 3 [35 marks]**

(a) Draw a complete circuit diagram for a PNP differential amplifier with resistive load biased by a Widlar current source. Label the diagram clearly, showing all necessary currents, resistors, and PNP BJTs used in the circuit. Explain why the Widlar current source has an advantage over the basic two transistor current source. [10 marks]

(b) Figure 2 shows a basic BJT differential pair, biased by a constant current source  $I_Q$ . Assume that  $Q_1$  and  $Q_2$  are matched pair and operating at the same temperature.

(i) By defining  $v_d = v_{BE1} - v_{BE2}$

Show that 
$$i_{C1} = \frac{I_Q}{1 + e^{-v_d/V_T}} \quad \text{and} \quad i_{C2} = \frac{I_Q}{1 + e^{+v_d/V_T}}$$
 [6 marks]

(ii) What happen when differential-mode input voltage ( $v_d$ ) is zero? Show how the answer is obtained and explain your answer. [4 marks]

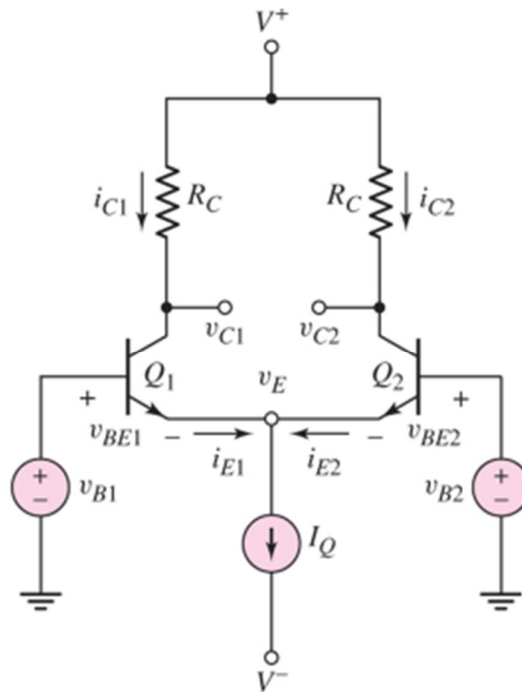


Figure 2



(c) For the differential amplifier shown in **Figure 2**, the circuit parameters are  $V^+ = 5\text{ V}$ ,  $V^- = -5\text{ V}$  and  $R_C = 15\text{ k}\Omega$ . For all transistors:  $\beta = 100$  and  $V_A = 200\text{ V}$ . The constant-current source  $I_Q$  is a **cascode** current source with output current of **2 mA**.

- (i) **Calculate** the one-sided differential-mode gain ( $A_d$ ). **[5 marks]**
- (ii) **Determine** the differential-mode input resistance ( $R_{id}$ ) and the common-mode input resistance ( $R_{icm}$ ). **[6 marks]**
- (iii) It is given for the inputs,  $v_1 = 200 \times 10^{-6} \sin \omega t\text{ V}$  and  $v_2 = -200 \times 10^{-6} \sin \omega t\text{ V}$ .  
**Calculate** the output voltage  $v_o$ . **[4 marks]**

**Answers for Question 3**

**Answers for Question 3 (Continued)**

**This is extra page for answers. Please indicate question number clearly.**