

Name:
Student ID Number:
Section Number: 01/02/03 A/B
Lecturer: Dr Fazrena Azlee/ Dr Jamaludin/
Dr Ahmad Wafi
Table Number:



College of Engineering
Department of Electrical and Electronics Engineering

Test 2 – Model Answer

SEMESTER 1, ACADEMIC YEAR 2019/2020

Subject Code : **EEEEB2014/EEEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **17 August 2019**
Time Allowed : **2 hours**

Instructions to the candidates:

1. Write your Name and Student ID Number. Indicate your Section Number and Lecturer's Name. Write also your Table Number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.** Show clearly all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!



Question Number	Q1 (abc)	Q1 (d)	Q2 (a)	Q2 (b)	Q3 (ab)	Q4 (a)	Q4 (b)	Total
Marks	20	10	8	27	20	3	12	100

QUESTION 2 [30 marks]**Answers for Question 1****Q1(a) 8 marks**

$$\text{DC balanced condition, } V_{EC4} = V_{EC3} \text{ and } V_{CE2} = V_{CE1} \quad [1]$$

$$V_{EC3} = V_{E3} - V_{C3} \quad [0.5]$$

$$V_{E3} = 5 \text{ V} \quad [1]$$

$$V_{C3} = V_{B5} = V_+ - V_{EB3} - V_{EB5} = 5 - 0.65 - 0.65 = 3.7 \text{ V} \quad [1]$$

$$\text{VEC4} = V_{EC3} = 5 - 3.7 = \underline{1.3 \text{ V}} \quad [1]$$

$$V_{CE1} = V_{C1} - V_{E1} \quad [0.5]$$

$$V_{C1} = V_{C3} = V_{B5} = 3.7 \text{ V} \quad [1]$$

$$V_{E1} = V_{B1} - V_{BE1} = 0 - 0.67 \text{ V} = -0.67 \text{ V} \quad [1]$$

$$\text{VCE2} = V_{CE1} = 3.7 - (-0.67) = \underline{4.37 \text{ V}} \quad [1]$$

Q1(b) 6 marks

$$r_{02} = V_{A_n} / I_{CQ2} = V_{A'} / (I_Q / 2) = 100 / (0.4 \text{ m} / 2) = 500 \text{ k}\Omega \quad [1]$$

$$r_{04} = V_{A_p} / I_{CQ2} = V_{A'} / (I_Q / 2) = 70 / (0.4 \text{ m} / 2) = 350 \text{ k}\Omega \quad [1]$$

$$g_{m2} = I_{CQ2} / V_T = I_Q / 2V_T = 0.4 \text{ m} / [2(26 \text{ m})] = 7.692 \text{ mA/V} \quad [2]$$

$$A_d = g_{m2} (r_{02} // r_{04}) = 7.692 \text{ m} (500 \text{ k} // 350 \text{ k}) = \underline{1584 \text{ V/V}} \quad [2]$$

Q1(c) 6 marks


$$A_d = g_{m2} (r_{02} // r_{04} // R_L) \quad [2]$$

$$0.9(1584) = 1425 = 7.692 \text{ m} (500 \text{ k} // 350 \text{ k} // R_L) \quad [2]$$

$$\underline{R_L = 1.84 \text{ M}\Omega} \quad [2]$$

Answers for Question 1 (Continued)

Q1(d) 10 marks

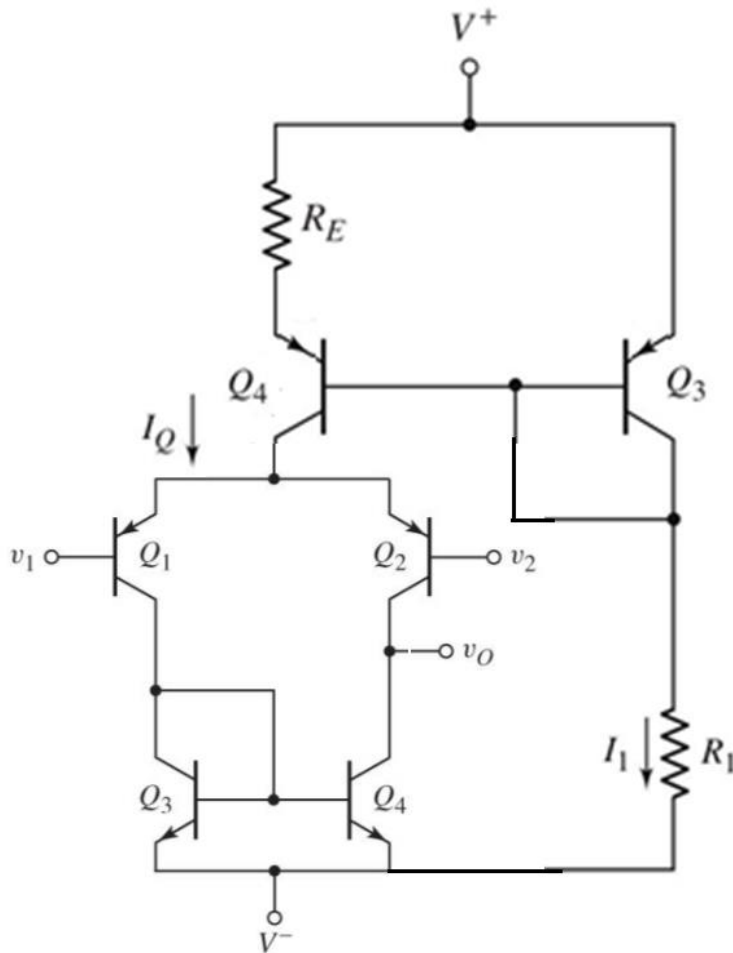

- Correct pnp differential amplifier [2]
- Correct npn 2 transistor active load [2]
- Correct pnp **Widlar** current source [2]
- Correct I_1 (I_{ref}) side with diode connection [2]
- Correct I_Q current source C4 to E1/E2 connection [1]
- V^+ and V^- [1]

Answers for Question 2 (Continued)

Q2(b) 27 marks

$$b) i) I_Q = 12.8 \text{ mA}$$

$$\Rightarrow I_D = \frac{I_Q}{2} = 6.4 \text{ mA} \quad - 1 \text{ mark}$$

$$\Rightarrow r_{o2} = \frac{1}{\lambda_n I_D} = 10.42 \text{ k}\Omega \quad - 1 \text{ mark}$$

$$r_{o4} = \frac{1}{\lambda_p I_D} = 7.81 \text{ k}\Omega \quad - 1 \text{ mark}$$

$$\Rightarrow R_o = r_{o2} \parallel r_{o4} = 4.46 \text{ k}\Omega \quad - 2 \text{ marks}$$

$$ii) g_m = 2\sqrt{k_n I_D} = 2.26 \text{ mA/V} \quad - 3 \text{ marks}$$

$$\Rightarrow A_v = g_m R_o = 10.1 \text{ V/V} \quad - 2 \text{ marks}$$

$$iii) A_d = g_m (R_o \parallel R_L) = 6.98 \text{ V/V} \quad 5 \text{ marks}$$

$$iv) CMRR = 27.7 = 20 \log \left| \frac{A_d}{A_{cm}} \right| \quad - 3 \text{ marks}$$

$$|A_{cm}| = 0.288 \text{ V/V} \quad - 2 \text{ marks}$$

$$v) v_d = v_1 - v_2 = 20 \sin \omega t \quad 2 \text{ marks}$$

$$v_{cm} = \frac{v_1 + v_2}{2} = 0.5 \sin \omega t \quad 2 \text{ marks}$$

$$v_o = A_d v_d + A_{cm} v_{cm} = 139.5 \sin \omega t$$

- 3 marks

QUESTION 3 [20 marks]

Answers for Question 3

Q3(a) 15 marks

$$I_{C7} = I_Q = 45 \mu A \quad \text{Given}$$

$$I_{C6} = \frac{\beta}{1+\beta} I_{E6} = \frac{\beta}{1+\beta} I_{B7} = \frac{\beta}{1+\beta} \frac{I_{C7}}{\beta} = \frac{I_{C7}}{1+\beta} \quad [1]$$

$$I_{C6} = \frac{I_{C7}}{1+\beta} = \frac{45 \mu}{121} = 0.3719 \mu A \quad [0.5]$$

$$r_{\pi 6} = \frac{\beta V_T}{I_{C6}} = \frac{120 \times 0.026}{0.3719 \mu} = 8.39 M\Omega \quad [1]$$

$$r_{\pi 7} = \frac{\beta V_T}{I_{C7}} = \frac{120 \times 0.026}{45 \mu} = 69.33 k\Omega \quad [1]$$

$$R_i = r_{\pi 6} + (1 + \beta)r_{\pi 7} \quad [1]$$

$$R_i = 8.39M + 121(69.33k) = 16.778 M\Omega \quad [0.5]$$

[Total for R_i = 5 marks]

$$R_i = \frac{2(1+\beta)\beta V_T}{I_Q} = \frac{2 \times 121 \times 120 \times 26m}{45 \mu} = 16.778 M\Omega \quad \text{[Optional: 2 marks]}$$

$$R_{c11} = r_{o11}[1 + g_{m11}(r_{\pi 11} || R_3)] \quad [1]$$

$$R_3 = R_2 = 2 k\Omega \quad \text{Widlar} \quad [1]$$

$$r_{o11} = V_A / I_{C7} = 120 / 45 \mu = 2.67 M\Omega \quad [0.5]$$

$$g_{m11} = I_{C7} / V_T = 45 \mu / 0.026 = 1.73 mA/V \quad [0.5]$$

$$r_{\pi 11} = \frac{\beta V_T}{I_{C7}} = \frac{120 \times 0.026}{45 \mu} = 69.33 k\Omega \quad [0.5]$$

$$R_{c11} = 2.67M[1 + (1.73m)(69.33k || 2k)] = 11.65 M\Omega \quad [0.5]$$

[Total for R_{c11} = 4 marks]

$$R_{b8} = r_{\pi 8} + (1 + \beta)R_4 \quad [1]$$

$$R_4 = 5 k\Omega \quad \text{Given}$$

$$I_{C8} = \frac{v_o - V^-}{R_4} = \frac{0 - (-10)}{5k} = 2 mA \quad [1]$$

$$r_{\pi 8} = \frac{\beta V_T}{I_{C8}} = \frac{120 \times 0.026}{2m} = 1.56 k\Omega \quad [1]$$

$$R_{b8} = 1.56k + 121(5k) = 606.56 k\Omega \quad [1]$$

[Total for R_{b8} = 4 marks]

$$R_{L7} = R_{c11} || R_{b8} \quad [1]$$

$$R_{L7} = 11.65M || 606.56k = 576.54 k\Omega \quad [1]$$

[Total for R_{L7} = 2 marks]

Q3(b) 5 marks

$$I_{C7} = (1 + \beta)I_{C6} = (1 + \beta)(\beta I_{B6}) \quad [1]$$

$$v_{O3} = I_{C7}(r_{o7} || R_{L7}) = (1 + \beta)(\beta I_{B6})(r_{o7} || R_{L7}) \quad [1]$$

$$v_{O2} = I_{B6}R_i \quad \text{Given}$$

$$r_{o7} = V_A / I_{C7} = 120 / 45 \mu = 2.67 M\Omega \quad [1]$$

$$A_2 = \frac{v_{O3}}{v_{O2}} = \frac{(1+\beta)(\beta I_{B6})(r_{o7} || R_{L7})}{I_{B6}R_i} = \frac{(1+\beta)(\beta)(r_{o7} || R_{L7})}{R_i} \quad [1]$$

$$A_2 = \frac{(1+120)(120)(2.67M || 576.54k)}{16.778M} = 410.34 \quad [1]$$

[Total for A_2 = 5 marks]

$$A_2 = (I_Q / 2V_T) R_{L7} = (45 \mu \times 576.54k) / (2 \times 26m) = 498.93 \quad \text{[Optional: 2 marks]}$$

(Ignore r_{o7})

QUESTION 4 [15 marks]

Answers for Question 4

Q4(a) 3 marks

- (a) Class A has low power conversion efficiency where its maximum efficiency is 25% [1.5]
 while Class B can reach up to 78.5% although suffering from cross-over distortion [1.5].

Q4(b) 12 marks

(b) **Class A emitter-follower circuit**

$$\begin{aligned} \text{(i)} \quad I_Q &= (V^{+CS} - V_{BE(on)} - V^-) / R && [1] \\ &= (3 - 0.6 + 5) / 2k && = \underline{3.7 \text{ mA}} && [1] \end{aligned}$$

$$\begin{aligned} \text{(ii)} \quad P_{Q1} &= I_{C1} \cdot V_{CE1} && [1] \\ &= I_Q \cdot V_{CE1} = (3.7\text{m})(5 - 0) && = \underline{18.5 \text{ mW}} && [0.5] \end{aligned}$$

$$\begin{aligned} P_{Q2} &= I_{C2} \cdot V_{CE2} && [1] \\ &= I_Q \cdot V_{CE2} = (3.7\text{m})(0 - (-5)) = \underline{18.5 \text{ mW}} && [0.5] \end{aligned}$$

$$\begin{aligned} P_{Q3} &= I_{C3} \cdot V_{CE3} && [1] \\ &= I_Q \cdot V_{BE3(on)} = (3.7\text{m})(0.6) = \underline{2.22 \text{ mW}} && [0.5] \end{aligned}$$

$$\begin{aligned} P_R &= I_R^2 R && [1] \\ &= I_Q^2 R = (3.7\text{m})^2 (2k) && = \underline{27.38 \text{ mW}} && [0.5] \end{aligned}$$

- (iii) For sine-wave output voltage (v_o) with peak value of 4 V.

$$\text{Power conversion efficiency, } \eta = P_L / P_S \times 100\% \quad [1]$$

$$P_L = (V_p)^2 / (2R_L) = 0.5 (4)^2 / 1k = \underline{8 \text{ mW}} \quad [1]$$

$$\begin{aligned} P_S &= (V^+ - V^-)I_Q + (3 - V^-)I_Q \\ &= (5 - (-5))(3.7\text{m}) + (3 - (-5))(3.7\text{m}) = \underline{66.6 \text{ mW}} \quad [1] \end{aligned}$$

$$\eta = 8\text{m} / 66.6\text{m} \times 100\% = \underline{12.01\%} \quad [1]$$

Or using power dissipation for Q1 and Q2 only:

$$\begin{aligned} P_S &= (V^+ - V^-)I_Q \\ &= (5 - (-5))(3.7\text{m}) = \underline{37 \text{ mW}} \quad [1] \end{aligned}$$

$$\eta = 8\text{m} / 37\text{m} \times 100\% = \underline{21.6\%} \quad [1]$$