

Question:

Figure 1 shows circuit diagram of a BJT current source. Study Figure 1 carefully. All transistors in the circuit are matched. The transistor parameters are: $\beta = 150$, $V_A = 100$ V, and $V_{BE}(\text{on}) = 0.7$ V.

- (a) Name the circuit for the current source. [2 marks]
- (b) Using I_{B1} as starting point, derive the relationship between I_O and I_{REF} . [5 marks]
- (c) Based on given value of β , use approximate value of I_O to estimate the output resistance, R_o , of the current source. [7 marks]
- (d) Find g_{m4} and $r_{\pi 4}$. [6 marks]

Answer:

- (a) Cascode current source [2]

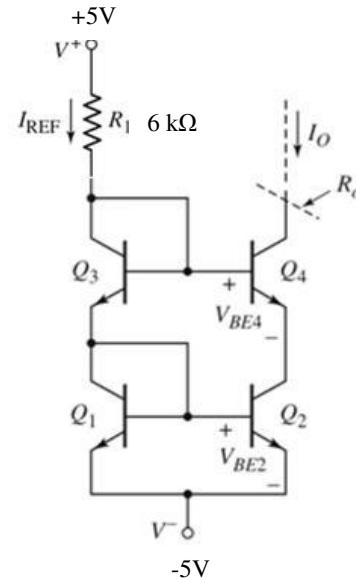


Figure 1

(b)

$$I_{C2} = \beta I_{B2} = I_{E4} = \beta I_{B1} \quad [1/2]$$

$$I_{C4} = \alpha I_{E4} = (\beta/\beta+1)(\beta I_{B1}) = I_O \quad \rightarrow I_{B1} = ((\beta+1)/\beta^2) I_O \quad [1/2]$$

$$I_{B4} = I_{E4}/(\beta+1) = (1/\beta+1)(\beta I_{B1}) \quad [1/2]$$

$$I_{C1} = \beta I_{B1} \quad [1/2]$$

$$I_{E3} = (\beta+2) I_{B1} \quad [1/2]$$

$$I_{B3} = (1/\beta+1) I_{E3} = (1/\beta+1)(\beta+2) I_{B1} \quad [1/2]$$

$$I_{C3} = \beta I_{B3} = (\beta/\beta+1)(\beta+2) I_{B1} \quad [1/2]$$

$$I_{REF} = I_{C3} + I_{B3} + I_{B4} = (\beta/\beta+1)(\beta+2) I_{B1} + (1/\beta+1)(\beta+2) I_{B1} + (1/\beta+1)(\beta I_{B1})$$

$$I_{REF} = [(\beta^2 + 2\beta + \beta + 2 + \beta)/(\beta+1)] I_{B1} \quad [1/2]$$

$$I_{REF} = [(\beta^2 + 2\beta + \beta + 2 + \beta) / (\beta + 1)] [((\beta + 1)/\beta^2) I_o] \quad [1/2]$$

$$I_o = I_{REF} / [1 + 4/\beta + 2/\beta^2] \approx I_{REF} / [1 + 4/\beta] \quad [1/2]$$

(c) $\beta = 150 \rightarrow$ Approximation: $I_o = I_{REF}$
[1]

$$I_{REF} = (V^+ - V_{BE1} - V_{BE3} - V^-) / (R_I) = (5 - 0.7 - 0.7 - (-5)) / 6k = 1.433 \text{ mA} = I_o \quad [1/2]$$

$$R_o = \beta r_{o4} = \beta V_A / I_o = (150)(100 / 1.433 \text{ mA}) = 10.465 \text{ M}\Omega \quad [1/2]$$

(d) $g_{m4} = I_o / V_T = (1.433 \text{ mA}) / (26 \text{ mV}) = 55.128 \text{ mA/V}$
[1] [1] [1]

$$r_{\pi4} = \beta V_T / I_o = (150)(26 \text{ mV} / 1.433 \text{ mA}) = 2.721 \text{ k}\Omega \quad [1/2]$$

OR

(c) $\beta = 150 \rightarrow$ Approximation: $I_o = I_{REF} / [1 + 4/\beta]$
[1]

$$I_{REF} = (V^+ - V_{BE1} - V_{BE3} - V^-) / (R_I) = (5 - 0.7 - 0.7 - (-5)) / 6k = 1.433 \text{ mA} \quad [1/2]$$

$$I_o = I_{REF} / [1 + 4/\beta] = (1.433 \text{ mA}) / [1 + 4 / 150] = 1.396 \text{ mA} \quad [1]$$

$$R_o = \beta r_{o4} = \beta V_A / I_o = (150)(100 / 1.396 \text{ mA}) = 10.744 \text{ M}\Omega \quad [1/2]$$

(d) $g_{m4} = I_o / V_T = (1.396 \text{ mA}) / (26 \text{ mV}) = 53.696 \text{ mA/V}$
[1] [1] [1]

$$r_{\pi4} = \beta V_T / I_o = (150)(26 \text{ mV} / 1.396 \text{ mA}) = 2.793 \text{ k}\Omega \quad [1]$$

Question:

Figure 1 shows circuit diagram of a BJT current source. Study Figure 1 carefully. All transistors in the circuit are matched. The transistor parameters are: $\beta = 150$, $V_A = 100$ V, and $V_{BE}(\text{on}) = 0.7$ V.

- Name the circuit for the current source. [2 marks]
- Using I_{B1} as starting point, derive the relationship between I_O and I_{REF} . [5 marks]
- Based on given value of β , use approximate value of I_O to estimate the output resistance, R_o , of the current source. [7 marks]
- Find g_{m4} and $r_{\pi 4}$. [6 marks]

Answer:

- (a) Cascode current source [2]

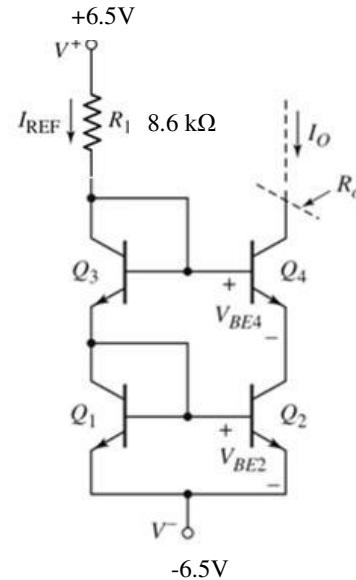


Figure 1

(b)

$$I_{C2} = \beta I_{B2} = I_{E4} = \beta I_{B1} \quad [1/2]$$

$$I_{C4} = \alpha I_{E4} = (\beta / \beta + 1)(\beta I_{B1}) = I_O \quad \rightarrow I_{B1} = ((\beta + 1) / \beta^2) I_O \quad [1/2]$$

$$I_{B4} = I_{E4} / (\beta + 1) = (1 / \beta + 1)(\beta I_{B1}) \quad [1/2]$$

$$I_{C1} = \beta I_{B1} \quad [1/2]$$

$$I_{E3} = (\beta + 2) I_{B1} \quad [1/2]$$

$$I_{B3} = (1 / \beta + 1) I_{E3} = (1 / \beta + 1)(\beta + 2) I_{B1} \quad [1/2]$$

$$I_{C3} = \beta I_{B3} = (\beta / \beta + 1)(\beta + 2) I_{B1} \quad [1/2]$$

$$I_{REF} = I_{C3} + I_{B3} + I_{B4} = (\beta / \beta + 1)(\beta + 2) I_{B1} + (1 / \beta + 1)(\beta + 2) I_{B1} + (1 / \beta + 1)(\beta I_{B1})$$

$$I_{REF} = [(\beta^2 + 2\beta + \beta + 2 + \beta) / (\beta + 1)] I_{B1} \quad [1/2]$$

$$I_{REF} = [(\beta^2 + 2\beta + \beta + 2 + \beta) / (\beta + 1)] [((\beta + 1)/\beta^2) I_O] \quad [1/2]$$

$$I_O = I_{REF} / [1 + 4/\beta + 2/\beta^2] \approx I_{REF} / [1 + 4/\beta] \quad [1/2]$$

(c) $\beta = 150 \rightarrow$ Approximation: $I_O = I_{REF}$
[1]

$$I_{REF} = (V^+ - V_{BE1} - V_{BE3} - V^-) / (R_I) = (6.5 - 0.7 - 0.7 - (-7.5)) / 8.6k = 1.349 \text{ mA} = I_O \quad [1/2]$$

$$R_O = \beta r_{o4} = \beta V_A / I_O = (150)(100/1.349\text{m}) = 11.121 \text{ M}\Omega \quad [1/2]$$

(d) $g_{m4} = I_O / V_T = (1.349\text{mA}) / (26\text{mV}) = 51.878 \text{ mA/V}$
[1] [1] [1]

$$r_{\pi4} = \beta V_T / I_O = (150)(26\text{mV} / 1.349\text{mA}) = 2.891 \text{ k}\Omega \quad [1/2]$$

OR

(c) $\beta = 150 \rightarrow$ Approximation: $I_O = I_{REF} / [1 + 4/\beta]$
[1]

$$I_{REF} = (V^+ - V_{BE1} - V_{BE3} - V^-) / (R_I) = (6.5 - 0.7 - 0.7 - (-6.5)) / 8.6k = 1.349 \text{ mA} \quad [1/2]$$

$$I_O = I_{REF} / [1 + 4/\beta] = (1.349\text{m}) / [1 + 4/150] = 1.314 \text{ mA} \quad [1]$$

$$R_O = \beta r_{o4} = \beta V_A / I_O = (150)(100/1.314\text{m}) = 11.417 \text{ M}\Omega \quad [1/2]$$

(d) $g_{m4} = I_O / V_T = (1.314\text{mA}) / (26\text{mV}) = 50.531 \text{ mA/V}$
[1] [1] [1]

$$r_{\pi4} = \beta V_T / I_O = (150)(26\text{mV} / 1.314\text{mA}) = 2.968 \text{ k}\Omega \quad [1]$$

Question:

Figure 1 shows circuit diagram of a BJT current source. Study Figure 1 carefully. All transistors in the circuit are matched. The transistor parameters are: $\beta = 150$, $V_A = 100$ V, and $V_{BE}(\text{on}) = 0.7$ V.

- (a) Name the circuit for the current source. [2 marks]
- (b) Using I_{B1} as starting point, derive the relationship between I_O and I_{REF} . [5 marks]
- (c) Based on given value of β , use approximate value of I_O to estimate the output resistance, R_o , of the current source. [7 marks]
- (d) Find g_{m4} and $r_{\pi 4}$. [6 marks]

Answer:

- (a) Cascode current source [2]

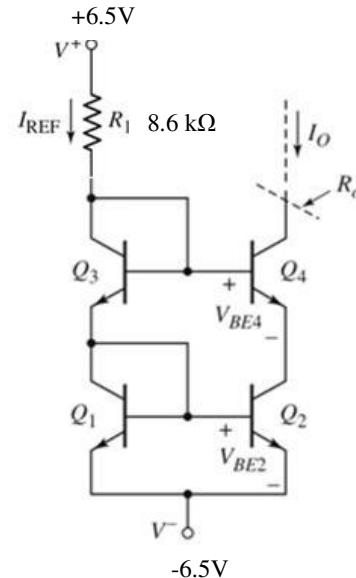


Figure 1

(b)

$$I_{C2} = \beta I_{B2} = I_{E4} = \beta I_{B1} \quad [1/2]$$

$$I_{C4} = \alpha I_{E4} = (\beta / \beta + 1)(\beta I_{B1}) = I_O \quad \rightarrow I_{B1} = ((\beta + 1) / \beta^2) I_O \quad [1/2]$$

$$I_{B4} = I_{E4} / (\beta + 1) = (1 / \beta + 1)(\beta I_{B1}) \quad [1/2]$$

$$I_{C1} = \beta I_{B1} \quad [1/2]$$

$$I_{E3} = (\beta + 2) I_{B1} \quad [1/2]$$

$$I_{B3} = (1 / \beta + 1) I_{E3} = (1 / \beta + 1)(\beta + 2) I_{B1} \quad [1/2]$$

$$I_{C3} = \beta I_{B3} = (\beta / \beta + 1)(\beta + 2) I_{B1} \quad [1/2]$$

$$I_{REF} = I_{C3} + I_{B3} + I_{B4} = (\beta / \beta + 1)(\beta + 2) I_{B1} + (1 / \beta + 1)(\beta + 2) I_{B1} + (1 / \beta + 1)(\beta I_{B1})$$

$$I_{REF} = [(\beta^2 + 2\beta + \beta + 2 + \beta) / (\beta + 1)] I_{B1} \quad [1/2]$$

$$I_{REF} = [(\beta^2 + 2\beta + \beta + 2 + \beta) / (\beta + 1)] [((\beta + 1)/\beta^2) I_o] \quad [1/2]$$

$$I_o = I_{REF} / [1 + 4/\beta + 2/\beta^2] \approx I_{REF} / [1 + 4/\beta] \quad [1/2]$$

(c) $\beta = 150 \rightarrow$ Approximation: $I_o = I_{REF}$
[1]

$$I_{REF} = (V^+ - V_{BE1} - V_{BE3} - V^-) / (R_I) = (6.5 - 0.7 - 0.7 - (-7.5)) / 8.6k = 1.349 \text{ mA} = I_o \quad [1/2]$$

$$R_o = \beta r_{o4} = \beta V_A / I_o = (150)(100/1.349\text{m}) = 11.121 \text{ M}\Omega \quad [1/2]$$

(d) $g_{m4} = I_o / V_T = (1.349\text{mA}) / (26\text{mV}) = 51.878 \text{ mA/V}$
[1] [1] [1]

$$r_{\pi4} = \beta V_T / I_o = (150)(26\text{mV} / 1.349\text{mA}) = 2.891 \text{ k}\Omega \quad [1/2]$$

OR

(c) $\beta = 150 \rightarrow$ Approximation: $I_o = I_{REF} / [1 + 4/\beta]$
[1]

$$I_{REF} = (V^+ - V_{BE1} - V_{BE3} - V^-) / (R_I) = (6.5 - 0.7 - 0.7 - (-6.5)) / 8.6k = 1.349 \text{ mA} \quad [1/2]$$

$$I_o = I_{REF} / [1 + 4/\beta] = (1.349\text{m}) / [1 + 4/150] = 1.314 \text{ mA} \quad [1]$$

$$R_o = \beta r_{o4} = \beta V_A / I_o = (150)(100/1.314\text{m}) = 11.417 \text{ M}\Omega \quad [1/2]$$

(d) $g_{m4} = I_o / V_T = (1.314\text{mA}) / (26\text{mV}) = 50.531 \text{ mA/V}$
[1] [1] [1]

$$r_{\pi4} = \beta V_T / I_o = (150)(26\text{mV} / 1.314\text{mA}) = 2.968 \text{ k}\Omega \quad [1]$$

Question:

Figure 1 shows circuit diagram of a BJT current source. Study Figure 1 carefully. All transistors in the circuit are matched. The transistor parameters are: $\beta = 150$, $V_A = 100$ V, and $V_{BE}(\text{on}) = 0.7$ V.

- (a) Name the circuit for the current source. [2 marks]
- (b) Using I_{B1} as starting point, derive the relationship between I_O and I_{REF} . [5 marks]
- (c) Based on given value of β , use approximate value of I_O to estimate the output resistance, R_o , of the current source. [7 marks]
- (d) Find g_{m4} and $r_{\pi 4}$. [6 marks]

Answer:

- (a) Cascode current source [2]

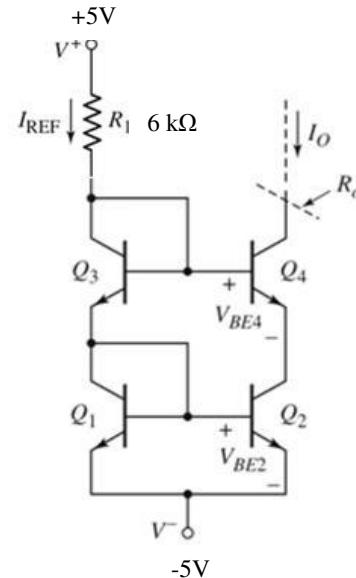


Figure 1

(b)

$$I_{C2} = \beta I_{B2} = I_{E4} = \beta I_{B1} \quad [1/2]$$

$$I_{C4} = \alpha I_{E4} = (\beta/\beta+1)(\beta I_{B1}) = I_O \quad \rightarrow I_{B1} = ((\beta+1)/\beta^2) I_O \quad [1/2]$$

$$I_{B4} = I_{E4}/(\beta+1) = (1/\beta+1)(\beta I_{B1}) \quad [1/2]$$

$$I_{C1} = \beta I_{B1} \quad [1/2]$$

$$I_{E3} = (\beta+2) I_{B1} \quad [1/2]$$

$$I_{B3} = (1/\beta+1) I_{E3} = (1/\beta+1)(\beta+2) I_{B1} \quad [1/2]$$

$$I_{C3} = \beta I_{B3} = (\beta/\beta+1)(\beta+2) I_{B1} \quad [1/2]$$

$$I_{REF} = I_{C3} + I_{B3} + I_{B4} = (\beta/\beta+1)(\beta+2) I_{B1} + (1/\beta+1)(\beta+2) I_{B1} + (1/\beta+1)(\beta I_{B1})$$

$$I_{REF} = [(\beta^2 + 2\beta + \beta + 2 + \beta)/(\beta+1)] I_{B1} \quad [1/2]$$

$$I_{REF} = [(\beta^2 + 2\beta + \beta + 2 + \beta) / (\beta + 1)] [((\beta + 1)/\beta^2) I_o] \quad [1/2]$$

$$I_o = I_{REF} / [1 + 4/\beta + 2/\beta^2] \approx I_{REF} / [1 + 4/\beta] \quad [1/2]$$

(c) $\beta = 150 \rightarrow$ Approximation: $I_o = I_{REF}$
[1]

$$I_{REF} = (V^+ - V_{BE1} - V_{BE3} - V^-) / (R_I) = (5 - 0.7 - 0.7 - (-5)) / 6k = 1.433 \text{ mA} = I_o \quad [1/2]$$

$$R_o = \beta r_{o4} = \beta V_A / I_o = (150)(100 / 1.433 \text{ mA}) = 10.465 \text{ M}\Omega \quad [1/2]$$

(d) $g_{m4} = I_o / V_T = (1.433 \text{ mA}) / (26 \text{ mV}) = 55.128 \text{ mA/V}$
[1] [1] [1]

$$r_{\pi4} = \beta V_T / I_o = (150)(26 \text{ mV} / 1.433 \text{ mA}) = 2.721 \text{ k}\Omega \quad [1/2]$$

OR

(c) $\beta = 150 \rightarrow$ Approximation: $I_o = I_{REF} / [1 + 4/\beta]$
[1]

$$I_{REF} = (V^+ - V_{BE1} - V_{BE3} - V^-) / (R_I) = (5 - 0.7 - 0.7 - (-5)) / 6k = 1.433 \text{ mA} \quad [1/2]$$

$$I_o = I_{REF} / [1 + 4/\beta] = (1.433 \text{ mA}) / [1 + 4 / 150] = 1.396 \text{ mA} \quad [1]$$

$$R_o = \beta r_{o4} = \beta V_A / I_o = (150)(100 / 1.396 \text{ mA}) = 10.744 \text{ M}\Omega \quad [1/2]$$

(d) $g_{m4} = I_o / V_T = (1.396 \text{ mA}) / (26 \text{ mV}) = 53.696 \text{ mA/V}$
[1] [1] [1]

$$r_{\pi4} = \beta V_T / I_o = (150)(26 \text{ mV} / 1.396 \text{ mA}) = 2.793 \text{ k}\Omega \quad [1]$$