

EEEB273 - Quiz 5 [Question Set 1]  
 SEMESTER 1, ACADEMIC YEAR 2010/2011  
 Date: 22 September 2010

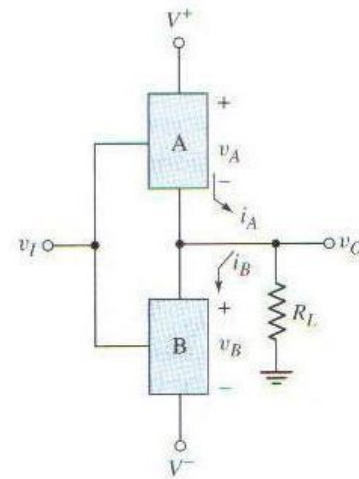
**Question:**

**Figure 1** shows an idealized class-B output stage. (The effective turn-on voltages of devices A and B are zero, and the effective “saturation” voltages of  $v_A$  and  $v_B$  are zero.) Given that  $V^+$  and  $V^-$  are **+10 V** and **-10 V**, respectively. Assume a symmetrical sine wave is produced at the output.

- (a) What is the peak output voltage at maximum power conversion efficiency?  
 [3 marks]
- (b) What is the peak output voltage when each device dissipates the maximum power?  
 [3 marks]
- (c) If the maximum allowed power dissipation in each device is **2 W** and the output voltage is at its maximum value, what is the permitted value of  $R_L$ ?  
 [4 marks]

**Answer:**

- (a)  
 At maximum power conversion efficiency  
 $V_p(\text{max}) = V^+$  [2]  
 $= 10 \text{ V}$  [1]
- (b)  
 Maximum power dissipation occurs when  
 $V_p = (2 V^+) / \pi$  [1]  
 $= (2 * 10) / \pi$  [1]  
 $= 6.366 \text{ V}$  [1]
- (c)  
 Maximum power dissipation occurs when  
 $P(\text{max}) = (V^+)^2 / (\pi^2 R_L)$  [1]  
 $R_L = (V^+)^2 / (\pi^2 P(\text{max}))$  [1]  
 $= (10)^2 / (\pi^2 * 2)$  [1]  
 $= 5.07 \Omega$  [1]

**Figure 1**

EEEB273 - Quiz 5 [Question Set 2]  
SEMESTER 1, ACADEMIC YEAR 2010/2011  
Date: 22 September 2010

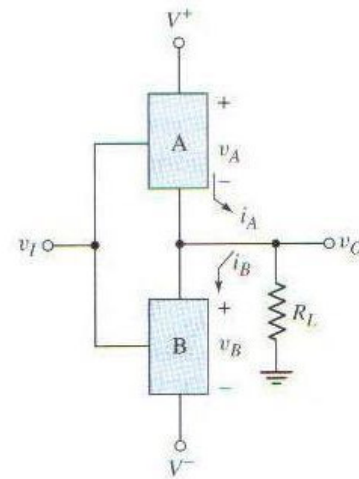
**Question:**

**Figure 1** shows an idealized class-B output stage. (The effective turn-on voltages of devices A and B are zero, and the effective “saturation” voltages of  $v_A$  and  $v_B$  are zero.) Given that  $V^+$  and  $V^-$  are  $+8\text{ V}$  and  $-8\text{ V}$ , respectively. Assume a symmetrical sine wave is produced at the output.

- (a) What is the peak output voltage at maximum power conversion efficiency?  
[3 marks]
- (b) What is the peak output voltage when each device dissipates the maximum power?  
[3 marks]
- (c) If the maximum allowed power dissipation in each device is  $3\text{ W}$  and the output voltage is at its maximum value, what is the permitted value of  $R_L$ ?  
[4 marks]

**Answer:**

- (a)  
At maximum power conversion efficiency  
 $V_p(\text{max}) = V^+$  [2]  
 $= 8\text{ V}$  [1]
- (b)  
Maximum power dissipation occurs when  
 $V_p = (2 V^+) / \pi$  [1]  
 $= (2 * 8) / \pi$  [1]  
 $= 5.093\text{ V}$  [1]
- (c)  
Maximum power dissipation occurs when  
 $P(\text{max}) = (V^+)^2 / (\pi^2 R_L)$  [1]  
 $R_L = (V^+)^2 / (\pi^2 P(\text{max}))$  [1]  
 $= (8)^2 / (\pi^2 * 3)$  [1]  
 $= 2.16\ \Omega$  [1]

**Figure 1**

EEEE273 - Quiz 5 [Question Set 1]  
 SEMESTER 1, ACADEMIC YEAR 2010/2011  
 Date: 22 September 2010

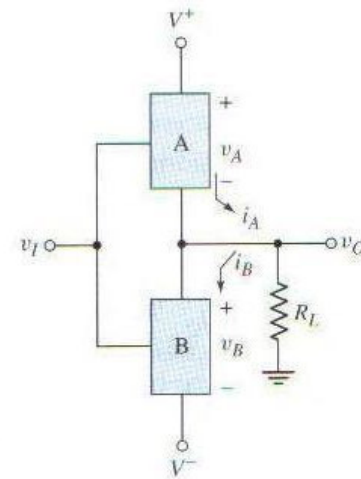
**Question:**

**Figure 1** shows an idealized class-B output stage. (The effective turn-on voltages of devices A and B are zero, and the effective “saturation” voltages of  $v_A$  and  $v_B$  are zero.) Given that  $V^+$  and  $V^-$  are **+10 V** and **-10 V**, respectively. Assume a symmetrical sine wave is produced at the output.

- (a) What is the peak output voltage at maximum power conversion efficiency?  
 [3 marks]
- (b) What is the peak output voltage when each device dissipates the maximum power?  
 [3 marks]
- (c) If the maximum allowed power dissipation in each device is **3.5 W** and the output voltage is at its maximum value, what is the permitted value of  $R_L$ ?  
 [4 marks]

**Answer:**

<b>(a)</b>		
At maximum power conversion efficiency		
$V_p$ (max)	$= V^+$	[2]
	$= 10 \text{ V}$	[1]
<b>(b)</b>		
Maximum power dissipation occurs when		
$V_p$	$= (2 V^+) / \pi$	[1]
	$= (2 * 10) / \pi$	[1]
	$= 6.366 \text{ V}$	[1]
<b>(c)</b>		
Maximum power dissipation occurs when		
$P$ (max)	$= (V^+)^2 / (\pi^2 R_L)$	[1]
$R_L$	$= (V^+)^2 / (\pi^2 P$ (max))	[1]
	$= (10)^2 / (\pi^2 * 3.5)$	[1]
	$= 2.89 \Omega$	[1]

**Figure 1**

EEEB273 - Quiz 5 [Question Set 2]  
 SEMESTER 1, ACADEMIC YEAR 2010/2011  
 Date: 22 September 2010

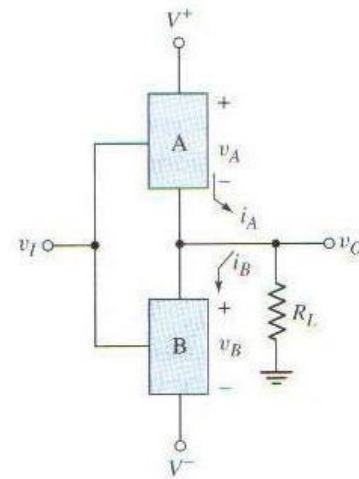
**Question:**

**Figure 1** shows an idealized class-B output stage. (The effective turn-on voltages of devices A and B are zero, and the effective “saturation” voltages of  $v_A$  and  $v_B$  are zero.) Given that  $V^+$  and  $V^-$  are  $+7.5\text{ V}$  and  $-7.5\text{ V}$ , respectively. Assume a symmetrical sine wave is produced at the output.

- (a) What is the peak output voltage at maximum power conversion efficiency?  
 [3 marks]
- (b) What is the peak output voltage when each device dissipates the maximum power?  
 [3 marks]
- (c) If the maximum allowed power dissipation in each device is **2.5 W** and the output voltage is at its maximum value, what is the permitted value of  $R_L$ ?  
 [4 marks]

**Answer:**

- (a)  
 At maximum power conversion efficiency  
 $V_p(\text{max}) = V^+$  [2]  
 $= 7.5\text{ V}$  [1]
- (b)  
 Maximum power dissipation occurs when  
 $V_p = (2 V^+) / \pi$  [1]  
 $= (2 * 7.5) / \pi$  [1]  
 $= 4.775\text{ V}$  [1]
- (c)  
 Maximum power dissipation occurs when  
 $P(\text{max}) = (V^+)^2 / (\pi^2 R_L)$  [1]  
 $R_L = (V^+)^2 / (\pi^2 P(\text{max}))$  [1]  
 $= (7.5)^2 / (\pi^2 * 2.5)$  [1]  
 $= 2.28\ \Omega$  [1]

**Figure 1**