

**Question:**

Study Figure 1 carefully. Given that  $v_{I1} = 0.6$  V and  $v_{I2} = 0.3$  V.

(a) Using superposition theorem, find  $v_2$ .

[6 marks]

(b) Find  $v_O$ .

[4 marks]

Show clearly all calculations.

**Answer:**

**(a)**

Find  $v_2$  when  $v_{I2} = 0$

$$v_2 (v_{I1}) = (40k/(20k+40k))(v_{II}) \quad [1] \\ = (40k/(20k+40k))(0.6) = 0.4 \text{ V} \quad [1]$$

Find  $v_2$  when  $v_{I1} = 0$


$$v_2 (v_{I2}) = (20k/(20k+40k))(v_{I2}) \quad [1] \\ = (20k/(20k+40k))(0.3) = 0.1 \text{ V} \quad [1]$$

$$v_2 = v_2 (v_{I1}) + v_2 (v_{I2}) \quad [1] \\ = 0.4 + 0.1 = 0.5 \text{ V} \quad [1]$$

**(b)**

Using virtual short circuit properties

$$v_O = (1+100k/50k)(v_2) \quad [2] \\ = (3)(0.5) = 1.5 \text{ V} \quad [2]$$

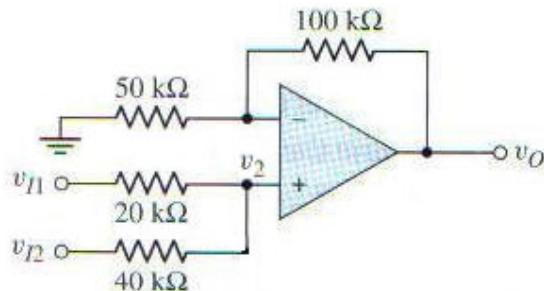

**Figure 1**

**Question:**

Study Figure 1 carefully. Given that  $v_{I1} = 0.45$  V and  $v_{I2} = 0.6$  V.

(c) Using superposition theorem, find  $v_2$ .

[6 marks]

(d) Find  $v_O$ .

[4 marks]

Show clearly all calculations.

**Answer:**

**(a)**

Find  $v_2$  when  $v_{I2} = 0$

$$v_2 (v_{I1}) = (40k/(20k+40k))(v_{I1}) \quad [1] \\ = (40k/(20k+40k))(0.45) = 0.3 \text{ V} \quad [1]$$

Find  $v_2$  when  $v_{I1} = 0$


$$v_2 (v_{I2}) = (20k/(20k+40k))(v_{I2}) \quad [1] \\ = (20k/(20k+40k))(0.6) = 0.2 \text{ V} \quad [1]$$

$$v_2 = v_2 (v_{I1}) + v_2 (v_{I2}) \quad [1] \\ = 0.3 + 0.2 = 0.5 \text{ V} \quad [1]$$

**(b)**

Using virtual short circuit properties

$$v_O = (1+100k/50k)(v_2) \quad [2] \\ = (3)(0.5) = 1.5 \text{ V} \quad [2]$$

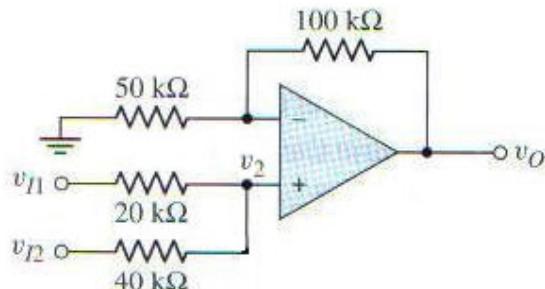

**Figure 1**

**Question:**

Study Figure 1 carefully. Given that  $v_{I1} = 0.45$  V and  $v_{I2} = 0.75$  V.

(e) Using superposition theorem, find  $v_2$ .

[6 marks]

(f) Find  $v_O$ .

[4 marks]

Show clearly all calculations.

**Answer:**

**(a)**

Find  $v_2$  when  $v_{I2} = 0$

$$v_2 (v_{I1}) = (40k/(20k+40k))(v_{I1}) \quad [1] \\ = (40k/(20k+40k))(0.45) = 0.3 \text{ V} \quad [1]$$

Find  $v_2$  when  $v_{I1} = 0$


$$v_2 (v_{I2}) = (20k/(20k+40k))(v_{I2}) \quad [1] \\ = (20k/(20k+40k))(0.75) = 0.25 \text{ V} \quad [1]$$

$$v_2 = v_2 (v_{I1}) + v_2 (v_{I2}) \quad [1] \\ = 0.3 + 0.25 = 0.55 \text{ V} \quad [1]$$

**(b)**

Using virtual short circuit properties

$$v_O = (1+100k/50k)(v_2) \quad [2] \\ = (3)(0.55) = 1.65 \text{ V} \quad [2]$$

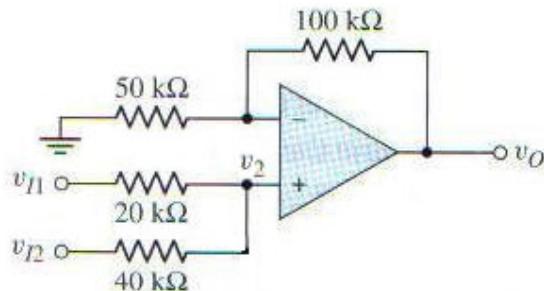

**Figure 1**

**Question:**

Study Figure 1 carefully. Given that  $v_{I1} = 0.3$  V and  $v_{I2} = 0.75$  V.

(g) Using superposition theorem, find  $v_2$ .

[6 marks]

(h) Find  $v_O$ .

[4 marks]

Show clearly all calculations.

**Answer:**

**(a)**

Find  $v_2$  when  $v_{I2} = 0$

$$v_2 (v_{I1}) = \frac{40k}{(20k+40k)}(v_{I1}) \quad [1] \\ = \frac{40k}{(20k+40k)}(0.3) = 0.2 \text{ V} \quad [1]$$

Find  $v_2$  when  $v_{I1} = 0$


$$v_2 (v_{I2}) = \frac{20k}{(20k+40k)}(v_{I2}) \quad [1] \\ = \frac{20k}{(20k+40k)}(0.75) = 0.25 \text{ V} \quad [1]$$

$$v_2 = v_2 (v_{I1}) + v_2 (v_{I2}) \quad [1] \\ = 0.2 + 0.25 = 0.45 \text{ V} \quad [1]$$

**(b)**

Using virtual short circuit properties

$$v_O = (1+100k/50k)(v_2) \quad [2] \\ = (3)(0.45) = 1.35 \text{ V} \quad [2]$$

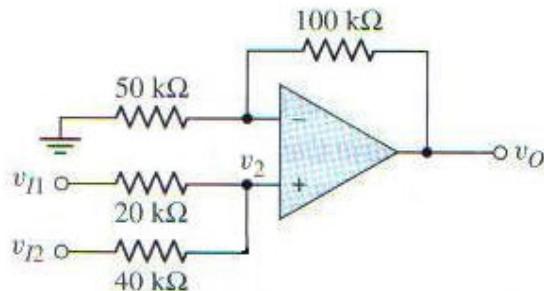

**Figure 1**