



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION
SEMESTER II 2010 / 2011**

SUBJECT CODE : **EEEB273**
SUBJECT : **ELECTRONIC ANALYSIS AND DESIGN II**
DATE : March 2011

-- MODEL ANSWERS --

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **Four** (4) questions in **Seven** (7) pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided.
4. Write answer to each question on **a new page**.
5. For all calculations, assume that $V_T = 26 \text{ mV}$.

***THIS QUESTION PAPER CONSISTS OF 7 PRINTED PAGES INCLUDING
THIS COVER PAGE.***

Question 1 [15 marks]

(a) For a BJT two-transistor current source, the transistor parameters are:

$V_{BE(on)}=0.7\text{ V}$, $\beta=120$, and $V_{AN}=100\text{ V}$. The bias voltage is $V^+=5\text{ V}$ and $V^-=-5\text{ V}$.

(i) **Design** the circuit such that $I_o = 0.50\text{ mA}$ when $V_{CE2}=0.7\text{ V}$.

(ii) What is the **change in I_o** as V_{CE2} varies between 0.7 V and 7 V ?

[8 marks]

Answers:

$$(i) I_{REF} = I_o \left[1 + \frac{2}{\beta} \right] \left[\frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{CE1}}{V_A}} \right] = 0.51\text{ mA} \quad [2]$$

$$R_1 = \frac{V^+ - V_{BE(on)} - V^-}{I_{REF}} = 18.24\text{ k}\Omega \quad [2]$$

$$(ii) \frac{\Delta I_o}{\Delta V_{CE2}} = \frac{1}{r_o} \quad [1]$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{V_A}{I_o} = 200\text{ k} \quad [2]$$

$$\Delta I_o = \frac{6.3}{200\text{ k}} = 31.5\mu\text{A} \quad [1]$$

(b) Refer to **Figure 1**. All the transistors are identical. The transistor parameters are:

$\beta=200$, $V_A=\infty$, $V_{BE(on)}=0.7$ V. Calculate V_{CE4} .

Hint: The current source equation is $I_{REF} = I_O (1 + [2/\beta(1 + \beta_3)])$.

[7 marks]

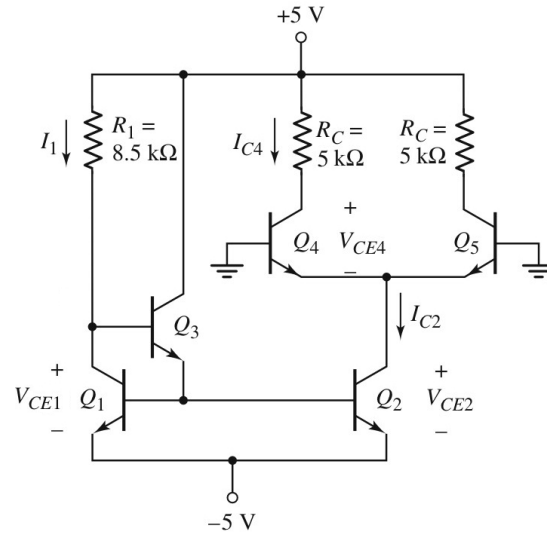


Figure 1

Answer:

$$I_1 = [V^+ - V^- - 2V_{BE(on)}] / R_1 = [5 - (-5) - 2(0.7)] / 8.5k = 1.0118 \text{ mA} \quad [2]$$

$$I_{C2} = 1.0118 \text{ mA} \quad [1]$$

$$V_{E4} = 0 - V_{BE4} = -0.7V \quad [1]$$

$$I_{C4} = \frac{1}{2} I_{C2} = 0.5059 \text{ mA} \quad [1]$$

$$V_{CE4} = V^+ - I_{C4}R_C - V_{E4} = 5 - (0.506)(5) - (-0.7) = 3.17 \text{ V} \quad [2]$$

Question 2 [15 marks]

(a) Describe how class-A, class-B, and class-AB output stages are different?

[3 marks]

Answers:

(i) Class-A, class-B, and class-AB output stages are different according to the percent (%) of time the output transistors are conducting (**turned on**), as follows:

- ❑ **Class A:** Output transistor is *biased at a quiescent current I_Q* and conducts for the *entire cycle of the input signal*. [1]
- ❑ **Class B:** Output transistor conducts for only *one-half of each sine-wave input cycle*. [1]
- ❑ **Class AB:** Output transistor *biased at a small quiescent current I_Q* , and conducts for *slightly more than half a cycle*. [1]

(b) A class-A emitter follower biased with a constant-current source is shown in **Figure 2**. Study **Figure 2** carefully. The transistor parameters are: $\beta = 200$, $V_{BE} = 0.7 \text{ V}$, and $V_{CE(\text{sat})} = 0.2 \text{ V}$. Neglecting base currents:

- (i) Find the value of I_Q . [3 marks]
- (ii) Determine the value of R that will produce the maximum possible output signal swing. [4 marks]
- (iii) Calculate the power conversion efficiency (η). [5 marks]

 


Figure 2

Answers:

(i) The value of I_Q is equivalent to the amplitude of the largest negative load

current, $i_L = v_{o(\min)}/R_L$

$$v_{o(\min)} = V^- + V_{CE(\text{sat})} = (-5) + (0.2) = -4.8\text{V} \quad [1.5]$$

$$I_Q = i_{L(\text{max})} = (4.8)/1\text{k} = 4.8\text{mA} \quad [1.5]$$

(ii) $R = (V^+ - V^- - V_{BE})/I_{\text{REF}}$ [1]

$$I_{\text{REF}} = (1 + 2/\beta) I_Q = (1 + 2/200)(4.8\text{m}) = 4.848\text{mA} \quad [2]$$

$$R = (5 - (-5) - 0.7)/(4.848\text{m}) = 1.9183\text{k}\Omega \quad [1]$$

(iii) $\eta = P_L / P_S$ [1]

$$P_L = \frac{1}{2} (V_p)^2 / R_L = (\frac{1}{2})(4.8)^2 / (1\text{k}) = 11.52\text{mW} \quad [1.5]$$

$$P_S = 2V_{CC}I_Q = 2(5)(4.8\text{m}) = 48\text{mW} \quad [1.5]$$

$$\eta = (11.52 / 48) \times 100\% = 24\% \quad [1]$$

Question 3 [25 marks]

Figure 3 shows a differential amplifier circuit with active loads and current source. The active load transistors are matched with parameters $K_p = 0.1 \text{ mA/V}^2$, $V_{TP} = -2 \text{ V}$ and $\lambda_p = 0.02 \text{ V}^{-1}$. Transistors M_1 and M_2 are driven into saturation with $V_{DS}(\text{sat}) = 1.12 \text{ V}$. Transistors M_5 , M_6 and M_7 are identical. All the NMOS transistors have the same $K_n = 0.2 \text{ mA/V}^2$, $V_{TN} = 2 \text{ V}$, and $\lambda_n = 0.015 \text{ V}^{-1}$.

 


Figure 3

- (i) Determine I_1 , I_Q , and I_{D1} when $v_1 = v_2 = 0$. [8 marks]
- (ii) Determine the **one-sided differential mode voltage gain** for this differential amplifier if $R_L = 100 \text{ k}\Omega$. [10 marks]
- (iii) It is required that the **CMRR** of this circuit to be **55dB**. What is the common mode voltage gain? [3 marks]
- (iv) Suggest ways to improve the CMRR for the circuit in **Figure 3**. [4 marks]

Answers:

(i) $I_1 = K_n(V_{GS5} - V_{TN})^2 = K_n(V_{GS7} - V_{TN})^2$ [2]

$V_{GS5} = V_{GS7}$ [1]

$V_{GS5} + V_{GS7} = 2 V_{GS5} = V^+ - V^- = 10 - (-10) = 20V$ [1.5]

$V_{GS5} = 10V = V_{GS7}$ [0.5]

$I_1 = (0.2m)(10-2)^2 = 12.8mA$ [1]

$I_Q = I_1 = 12.8mA$ [1]

$I_{D1} = \frac{1}{2}I_Q = 6.4mA$ [1]

(ii) $v_o = (g_m/2)v_d R_o$ therefore $A_d = (g_m/2)R_o$ [1.5]

$R_{o(\text{diff amp})} = r_{o2} // r_{o4} // R_L$ [1]

$r_{o2} = 1/(\lambda_n I_{D1}) = 1/(0.02)(6.4m) = 7.812k\Omega$ [1.5]

$r_{o4} = 1/(\lambda_p I_{D1}) = 1/(0.015)(6.4m) = 10.417k\Omega$ [1.5]

$R_{o(\text{diff amp})} = (7.812k) // (10.417k) // (100k) = 4.273 k\Omega$ [1.5]

$g_m = 2\sqrt{K_n I_{D1}}$ [1]

$A_d = (1/2) \times [2\sqrt{K_n I_{D1}}] \times R_{o(\text{diff amp})}$ [1]

$= [(0.2m)(6.4m)]^{1/2} (4.273k) = 4.834$ [1]

(iii) $CMRR = 20 \log [A_d/A_{cm}] = 55dB$ [1]

$A_{cm} = A_d / [\log^{-1}(55/20)] = 8.6 \times 10^{-3}$ [2]

(iv) Select two answers:

Increase the current source output resistance. [2]

Increase the diff amp output resistance by using cascode active loads. [2]

Reduce the loading effect by increasing load resistance, R_L . [2]

Question 4 [20 marks]

A simple bipolar op-amp is designed as shown in **Figure 3a**. Note that biasing for amplifiers in the circuit is provided by two-transistor current mirrors. Study the figure carefully. Neglect base currents. Assume parameters for all transistors are: $V_{BE(on)} = 0.7V$, $\beta = 100$, and $V_A = \infty$.

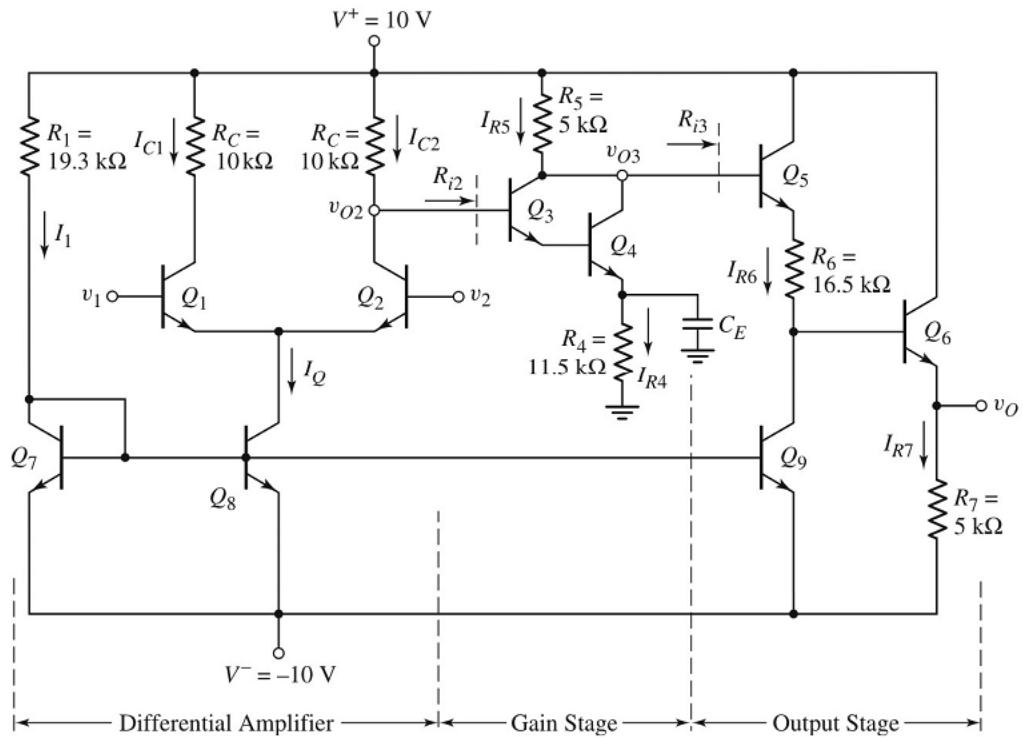


Figure 3a

- (i) Referring to **Figure 3a** find I_1 , I_Q , I_{C2} , v_{O2} , and v_{O3} . [10 marks]
- (ii) With small-signal analysis values for A_{d1} , $r_{\pi3}$, R_{i2} , and A_2 can be found using the following formula:

$$A_{d1} = \left(\frac{V_{o2}}{v_d} \right) = \frac{g_m}{2} (R_C \parallel R_{i2})$$

$$r_{\pi3} \cong \beta r_{\pi4}$$

$$R_{i2} = r_{\pi3} + (1 + \beta)r_{\pi4}$$

$$A_2 \cong \frac{I_{R4}}{2V_T} (R_5)$$

Calculate A_{d1} , A_2 , and the total overall small-signal voltage gain, A_d .

[10 marks]

Answers:

(i)

$$\begin{aligned}
 I_1 &= (V^+ - V_{BE7} - V^-) / (R_1) && [1] \\
 &= (10 - 0.7 - (-10)) / (19.3k) = 1 \text{ mA} && [1] \\
 I_Q &= I_1 / (1 + 2/\beta) = 0.9084 \text{ mA} && [2] \\
 I_{C2} &= I_Q / 2 = 0.4902 \text{ mA} && [2] \\
 v_{O2} &= V^+ - I_{C2} R_C = 10 - (0.4902m)(10k) = 5.098 \text{ V} && [2] \\
 I_{R4} &= (v_{O2} - 2 V_{BE(on)}) / (R_4) && [1/2] \\
 &= (5.098 - 1.4) / (11.5k) = 0.322 \text{ mA} && [1/2] \\
 I_{R5} &\approx I_{R4} \text{ (neglecting base currents)} = 0.322 \text{ mA} && [1/2] \\
 v_{O3} &= V^+ - I_{R5} R_5 = 10 - (0.322m)(5k) = 8.39 \text{ V} && [1]
 \end{aligned}$$

OR

$$\begin{aligned}
 I_Q &\approx I_1 \text{ [Since } \beta \gg 1] = 1 \text{ mA} && [2] \\
 I_{C2} &= I_Q / 2 = 0.5 \text{ mA} && [2] \\
 v_{O2} &= V^+ - I_{C2} R_C = 10 - (0.5m)(10k) = 5 \text{ V} && [2] \\
 I_{R4} &= (v_{O2} - 2 V_{BE(on)}) / (R_4) && [1/2] \\
 &= (5 - 1.4) / (11.5k) = 0.313 \text{ mA} && [1/2] \\
 I_{R5} &\approx I_{R4} \text{ (neglecting base currents)} = 0.313 \text{ mA} && [1/2] \\
 v_{O3} &= V^+ - I_{R5} R_5 = 10 - (0.313m)(5k) = 8.44 \text{ V} && [1]
 \end{aligned}$$

(ii)

Using $I_{C2} = 0.4902 \text{ mA}$, $I_{R4} = 0.322 \text{ mA}$:

$$\begin{aligned}
 A_{d1} &= (g_m / 2)(R_C \parallel R_{i2}) \\
 g_m &= I_{C2} / V_T = (0.4902\text{mA}) / (26\text{mV}) = 18.85 \text{ mA/V} && [1] \\
 r_{\pi4} &= \beta V_T / I_{R4} = (100 \times 26\text{m}) / (0.322\text{m}) = 8.085 \text{ k}\Omega && [1] \\
 r_{\pi3} &\approx \beta r_{\pi4} = 808.5 \text{ k}\Omega && [1] \\
 R_{i2} &= r_{\pi3} + (1 + \beta) r_{\pi4} && [1] \\
 &= 808.5k + (101)(8.085k) = 1621.1 \text{ k}\Omega && [1] \\
 A_{d1} &= (18.85\text{m}/2)(10k \parallel 1621.1k) = 93.67 && [2] \\
 A_2 &\approx (I_{R4} / 2V_T) R_5 = (0.322\text{m} / (2 \times 26\text{m}))(5k) = 30.96 && [2] \\
 A_3 &\approx 1 && [1] \\
 A_d &= A_{d1} A_2 A_3 = 93.67 \times 30.96 \times 1 = 2900 && [1]
 \end{aligned}$$

OR Using $I_{C2} = 0.5 \text{ mA}$, $I_{R4} = 0.313 \text{ mA}$:

$$\begin{aligned}
 A_{d1} &= (g_m / 2)(R_C \parallel R_{i2}) \\
 g_m &= I_{C2} / V_T = (0.5\text{mA}) / (26\text{mV}) = 19.23 \text{ mA/V} && [1] \\
 r_{\pi4} &= \beta V_T / I_{R4} = (100 \times 26\text{m}) / (0.313\text{m}) = 8.306 \text{ k}\Omega && [1] \\
 r_{\pi3} &\approx \beta r_{\pi4} = 830.6 \text{ k}\Omega && [1] \\
 R_{i2} &= r_{\pi3} + (1 + \beta) r_{\pi4} && [1] \\
 &= 830.6k + (101)(8.306k) = 1669.5 \text{ k}\Omega && [1] \\
 A_{d1} &= (19.23\text{m}/2)(10k \parallel 1669.5k) = 95.58 && [2] \\
 A_2 &\approx (I_{R4} / 2V_T) R_5 = (0.313\text{m} / (2 \times 26\text{m}))(5k) = 30 && [2] \\
 A_3 &\approx 1 && [1] \\
 A_d &= A_{d1} A_2 A_3 = 95.58 \times 30 \times 1 = 2867 && [1]
 \end{aligned}$$

Question 5 [25 marks]

- (a) The summing amplifier as in **Figure 5a** can be used as a digital-to-analog converter (DAC). The analogue output is calculated by using the equation:

$$v_o = -R_F \left[\frac{u_3}{R_3} + \frac{u_2}{R_2} + \frac{u_1}{R_1} + \frac{u_o}{R_o} \right] (V_R)$$

Suppose that we want to convert a 4-bit binary signal ($a_3a_2a_1a_0$) to its equivalent weight in decimal value. **Design** the circuit such that when switch S_3 only is closed (i.e. resistor R_3 is connected to $-5V$ supply), then $a_3 = 1$, thus an input $a_3a_2a_1a_0 = 1000$ will give $v_o = 8V$. Similarly, when all switches (i.e. $S_0, S_1, S_2,$ and S_3) are closed, the binary signal $a_3a_2a_1a_0$ combination gives $v_o = 15V$. Referring to the **Table 1**, verify your design by showing that $a_3a_2a_1a_0$ combination provides the same output as shown.

[12 marks]

Table 1

$a_3a_2a_1a_0$	1000	0100	0010	0001	0110
v_o [Volts]	8	4	2	1	6

 


Figure 5a

Answer:

When S_3 is closed:

$$v_O = -R_F[(1/R_3) + (0/R_2) + (0/R_1) + (0/R_0)](V_R) \quad [2]$$

$$v_O = -48k (1/R_3)(-5) = 8 \quad [1]$$

$$R_3 = (48k)(5)/8 = 30k\Omega \quad [1]$$

When S_2 is closed:

$$v_O = -R_F(1/R_2)(V_R) \quad [0.5]$$

$$v_O = -48k (1/R_2)(-5) = 4 \quad [0.5]$$

$$R_2 = (48k)(5)/4 = 60k\Omega \quad [1]$$

When S_1 is closed:

$$v_O = -R_F(1/R_1)(V_R) \quad [0.5]$$

$$v_O = -48k (1/R_1)(-5) = 2 \quad [0.5]$$

$$R_1 = (48k)(5)/2 = 120k\Omega \quad [1]$$

When S_0 is closed:

$$v_O = -R_F(1/R_0)(V_R) \quad [1]$$

$$v_O = -48k (1/R_0)(-5) = 1$$

$$R_0 = (48k)(5) = 240k\Omega \quad [1]$$



Verify: $0110 = 6V$ [2]

$$v_O = -R_F[(0/R_3) + (1/R_2) + (1/R_1) + (0/R_0)](V_R)$$

$$v_O = -48k[(1/60k) + (1/120k)](-5) = (240/60) + (240/120) = 6V$$

- (b) With feedback resistor of $20\text{ k}\Omega$, sketch the following circuits using **inverting op-amp** configuration.
- (i) An inverting amplifier with a closed-loop gain of **-10**. [2 marks]
 - (ii) A voltage follower. [4 marks]

Answer:

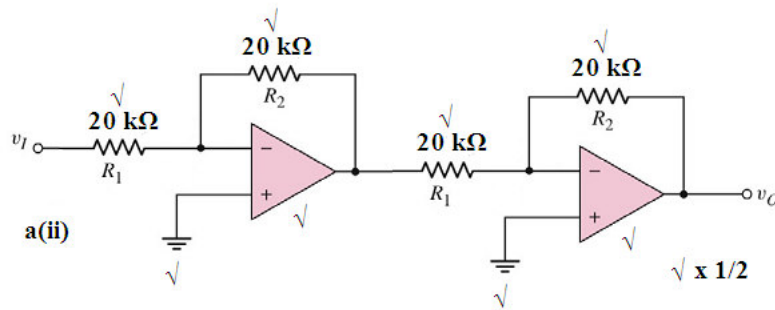 

- (c) Find the voltage gain, A_v , for the op-amp in **Figure 5b**. Assume the op-amp is ideal. [7 marks]

 


Figure 5b

Answer:

$$\begin{aligned}
 v_O &= (1 + R_2/R_1)v_2 & [2] \\
 v_2 &= [R_4/(R_3 + R_4)]v_I & [1] \\
 v_O &= (1 + R_2/R_1) [R_4/(R_3 + R_4)]v_I & [1] \\
 A_v &= v_O/v_I = (1 + R_2/R_1) [R_4/(R_3 + R_4)] & [1] \\
 &= [1 + (200\text{k}/25\text{k})][50\text{k}/(50\text{k} + 25\text{k})] = (9)(2/3) = 6 & [2]
 \end{aligned}$$