

Name:
Student ID Number:
Section:
Lecturer: Pn Azni Wati / Dr Jamaludin

**UNIVERSITI
TENAGA
NASIONAL**



College of Engineering
Department of Electronics and Communication Engineering

Midterm Test – Model Answer

SEMESTER 2, ACADEMIC YEAR 2010/2011

Subject Code : **EEEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **21 January 2011**
Time Allowed : **2 hours**

Instructions to the candidates:

1. Write your Name and Student ID number. Circle your section number.
2. Write all your answers using pen. **DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!




Question 1 [30 marks]

For a BJT cascode current source:

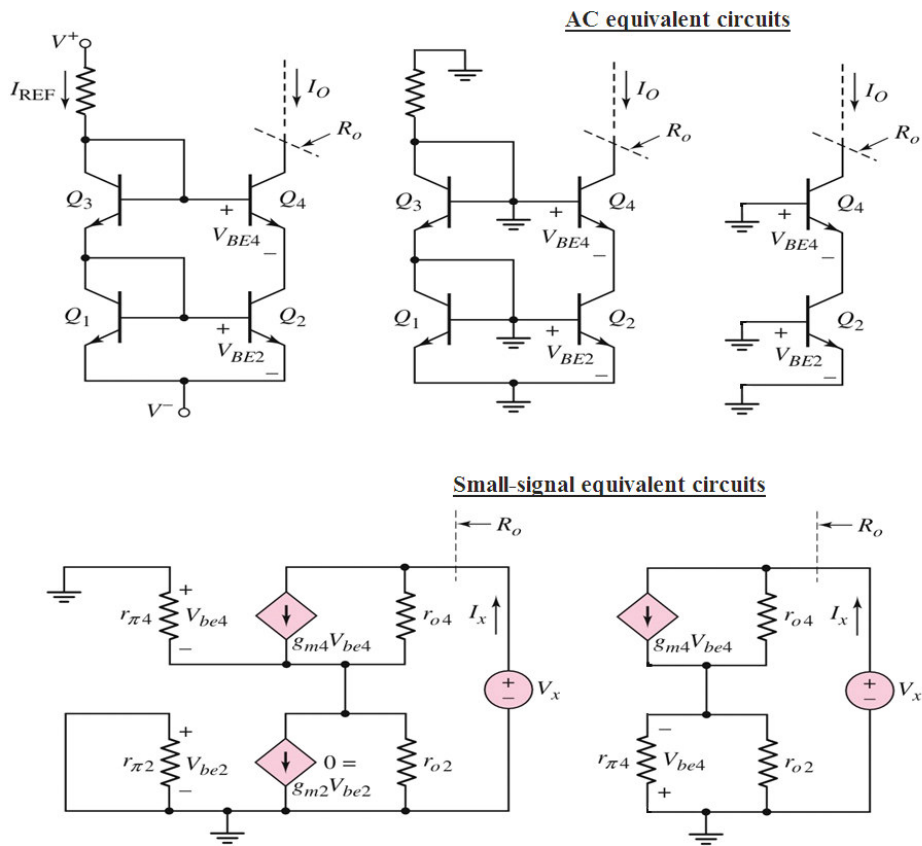- (a) Draw its circuit diagram. [5 marks]
- (b) From the circuit diagram, draw its AC equivalent circuit. [4 marks]
- (c) Draw its small-signal equivalent circuit using hybrid- π equivalent circuit for the BJT. [4 marks]
- (d) Derive a formula for its output resistance, R_O . [5 marks]
- (e) Given that $V_+ = 5\text{ V}$, $V_- = -5\text{ V}$, and for all transistors $V_{BE(on)} = 0.7\text{ V}$, $V_A = 200\text{ V}$, and $\beta = 200$:
 - (i) Design a BJT cascode current source with $I_O = 0.5\text{ mA}$ [8 marks]
 - (ii) Find the output resistance, R_O [4 marks]

Answer for Question 1

Answer (a) to (c): Give marks appropriately!



Answer for Question 1

(d)

$$V_{be4} = -I_x (r_{o2} \parallel r_{\pi4}) \quad [1/2]$$

Summing currents at output node yields

$$I_x = g_{m4} V_{be4} + \left(\frac{V_x - (-V_{be4})}{r_{o4}} \right)$$

$$I_x = -g_{m4} I_x (r_{o2} \parallel r_{\pi4}) + \left(\frac{V_x - I_x (r_{o2} \parallel r_{\pi4})}{r_{o4}} \right)$$

$$\frac{V_x}{r_{o4}} = I_x + g_{m4} I_x (r_{o2} \parallel r_{\pi4}) + \frac{I_x (r_{o2} \parallel r_{\pi4})}{r_{o4}}$$

$$V_x = I_x (r_{o4} + r_{o4} g_{m4} (r_{o2} \parallel r_{\pi4}) + (r_{o2} \parallel r_{\pi4}))$$

$$V_x = I_x (r_{o4} + r_{o4} g_{m4} (r_{\pi4}) + (r_{\pi4})) \quad [3]$$

Where $\beta = g_{m4} r_{\pi4}$ and assuming $r_{\pi4} \ll r_{o2}$

$$R_O = \frac{V_x}{I_x} = r_{o4} (1 + \beta) + r_{\pi4} \quad [1/2]$$

$$R_O \approx \beta r_{o4} \quad [1]$$

(e)

(i) $I_O \approx I_{REF} / (1 + 4/\beta)$
 $I_{REF} = I_O (1 + 4/\beta) = (0.5\text{m})(1 + 4/200) = 0.51 \text{ mA}$
[2] [1] [1]

$$R_I = (V_+ - V_- - 2V_{BE(\text{on})}) / I_{REF} = (10 - 1.4) / (0.51\text{m}) = 16.86 \text{ k}\Omega$$
[2] [1] [1]

(ii) $R_O \approx \beta r_{o4} = \beta V_A / I_O = (200 \times 200) / (0.5\text{m}) = 80000 \text{ k}\Omega = 80 \text{ M}\Omega$
[1] [1] [1] [1]

Question 2 [30 marks]

For a MOSFET current source circuit shown in **Figure 2**, the transistor parameters are $V_{TN} = 0.7 \text{ V}$, $k'_n = 60 \mu\text{A}/\text{V}^2$, and $\lambda = 0.015 \text{ V}^{-1}$. The transistor aspect ratios are $(W/L)_1 = 20$, $(W/L)_2 = 12$, and $(W/L)_3 = 3$.

- (a) Determine V_{GS1} , I_{REF} , I_O , and V_{DS2} [20 marks]
- (b) Find V_{GS3} [5 marks]
- (c) Find I_O at $V_{DS2} = 3.0 \text{ V}$ [5 marks]

Answer for Question 2

(a)

$$I_{REF} = \frac{k'_n}{2} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{TN})^2$$

$$I_{REF} = \frac{k'_n}{2} \left(\frac{W}{L} \right)_3 (V_{GS3} - V_{TN})^2$$

$$V_{GS1} + V_{GS3} = 10$$

$$I_O = \frac{k'_n}{2} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{TN})^2$$

[2] for every equation = [8]

→ $V_{GS1} = 3.1 \text{ V}$ [2]

→ $I_{REF} = 3.456 \text{ mA}$ [2]

→ $V_{GS2} = V_{GS1} = 3.1 \text{ V}$ [3]

$I_O = 2.073 \text{ mA}$ [3]

→ $V_{DS2} = V_{DS1} = V_{GS1} = 3.1 \text{ V}$ [2]

$I_O = 2.073 \text{ mA}$ at $V_{DS2} = 3.1 \text{ V}$

(b) $V_{GS3} = 10 - V_{GS1} = 6.9 \text{ V}$ [5]

(c) $I_O = 2.073 \text{ mA}$ at $V_{DS2} = 3.1 \text{ V}$ [1]

$R_O = 1/(\lambda I_O) = 32.159 \text{ k}\Omega$ [1]

At $V_{DS2} = 3.0 \text{ V}$,

$\Delta I_O = (3.0 - 3.1)/R_O = -0.003 \text{ mA}$ [2]

→ $I_O = 2.073 \text{ mA} + (-0.003 \text{ mA}) = 2.070 \text{ mA}$ [1]

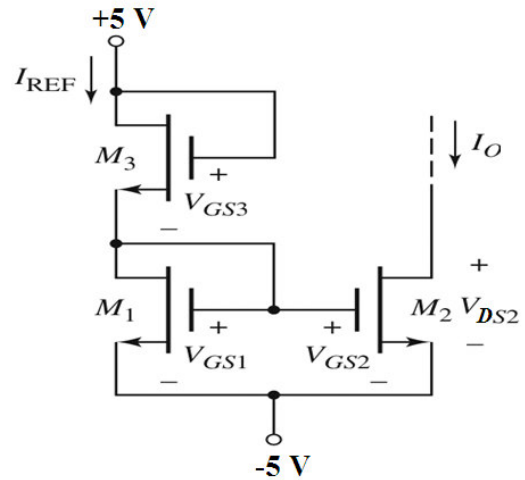


Figure 2

Question 3 [40 marks]

- (a) **Figure 3a** shows a circuit diagram for a BJT differential amplifier (**diff-amp**). Study the circuit diagram carefully. Transistor parameters are: $\beta = \infty$ (neglect base current), $V_A = \infty$, and $V_{BE(on)} = 0.7 \text{ V}$. For the circuit also, voltages measured at v_{C1} and v_{C2} are 4 V.
- (i) What are the values for v_{cm} and v_d ? Show clearly your calculations. [5 marks]
- (ii) Find I_Q [10 marks]
- (iii) Find v_{CE1} [5 marks]

Answer for Question 3a

(b)

(i)

From Figure 3a:
 $v_{B1} = v_{B2} = 0 \text{ V}$ [1]

→ $v_{cm} = (v_{B1} + v_{B2}) / 2 = 0 \text{ V}$ [2]

→ $v_d = v_{B1} - v_{B2} = 0 \text{ V}$ [2]

(ii)

Given: $v_{C1} = v_{C2} = 4 \text{ V}$
 $10 - I_{C1}R_C = v_{C1} = 4 \text{ V}$ [4]

→ $I_{C1} = 0.6 \text{ mA} = I_{C2}$ [3]

$I_Q = I_{C1} + I_{C2} = 1.2 \text{ mA}$ [3]

(iii)

Given: $v_{C1} = 4 \text{ V}$
 $v_{CE1} = v_{C1} - v_E$ [2]

$v_E = v_{B1} - V_{BE(on)} = 0 - 0.7 = -0.7 \text{ V}$ [2]

→ $v_{CE1} = v_{C1} - v_E = 4 - (-0.7) = 4.7 \text{ V}$ [1]

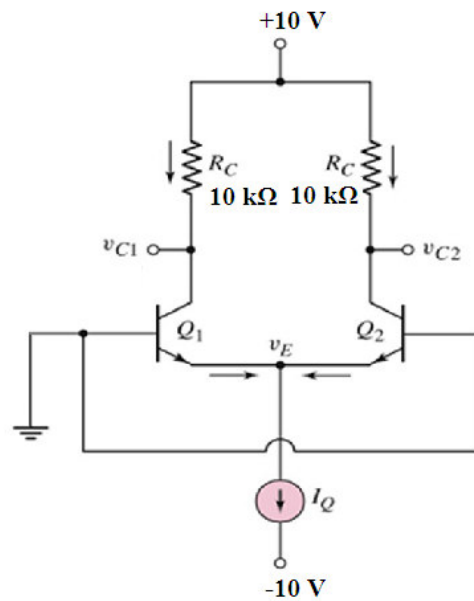


Figure 3a

- (b) The differential amplifier in **Figure 3b** has a pair of pnp transistors connected as an active load. A two-transistor current source is also incorporated to establish the bias current, $I_Q = 250\mu\text{A}$. The transistor parameters are $\beta = 150$, $V_{BE(\text{on})} = V_{EB(\text{on})} = 0.7\text{ V}$, $V_{AN} = 120\text{ V}$, and $V_{AP} = 100\text{ V}$. The output voltage can be calculated from Equation (1):

$$v_o = g_m v_d (r_{o2} \parallel r_{o4} \parallel R_L) \quad (1)$$

- (i) Draw the complete circuit incorporating the bias circuit. [5 marks]
- (ii) What is the open-circuit differential-mode voltage gain? [10 marks]
- (iii) Determine the differential-mode voltage gain if the load resistance is **100 k Ω** . [5 marks]

Answer for Question 3b


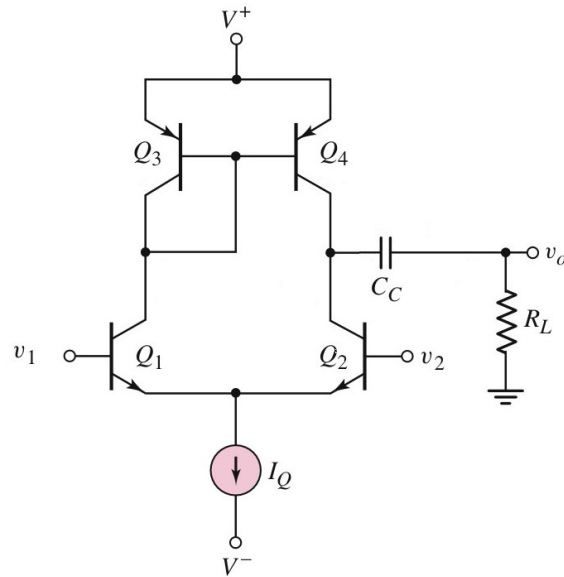


Figure 3b

(i)

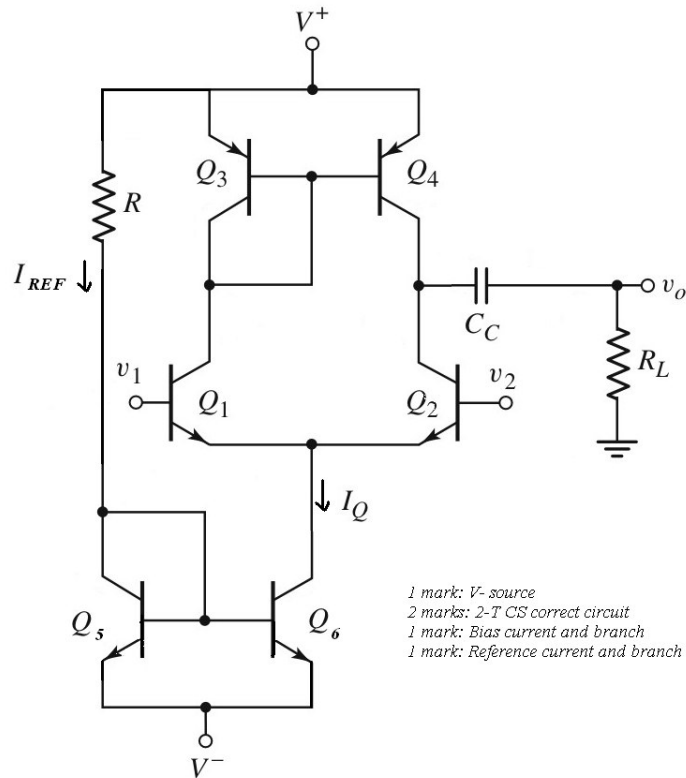

(ii)

$$v_o = g_m v_d (r_{o2} \parallel r_{o4}) \quad [1.5]$$

$$A_d = \frac{v_o}{v_d} = g_m (r_{o2} \parallel r_{o4}) \quad [1]$$

$$g_m = \frac{I_Q/2}{V_T} = \frac{250\mu/2}{0.026} = 4.808 \text{ mA/V} \quad [1.5]$$

$$r_{o2} = \frac{V_{AN}}{I_Q/2} = \frac{120}{125\mu} = 960 \text{ k}\Omega \quad [2]$$

$$r_{o4} = \frac{V_{AP}}{I_Q/2} = \frac{100}{125\mu} = 800 \text{ k}\Omega \quad [2]$$

$$r_{o2} \parallel r_{o4} = \frac{(960 \text{ k})(800 \text{ k})}{(960+800) \text{ k}} = 436.4 \text{ k}\Omega \quad [1]$$

$$A_d = (4.808 \text{ m})(436.4 \text{ k}) = 2098 \quad [1]$$

(iii)

$$v_o = g_m v_d (r_{o2} \parallel r_{o4} \parallel R_L) \quad [1]$$

$$A_d = \frac{v_o}{v_d} = g_m (r_{o2} \parallel r_{o4} \parallel R_L) \quad [1]$$

$$r_{o2} \parallel r_{o4} \parallel R_L = \frac{(436.4k)(100)k}{(436.4+100)k} = 81.36k\Omega \quad [2]$$

$$A_d = (4.808m)(81.36k) = 391.2 \quad [1]$$