

Question:

Design a two-transistor current source, **using pnp transistors**, given the following parameters:

The transistor parameters are: $\beta = 100$, V_{BE} (on) = 0.6 V, and $V_A = 100$ V.

The circuit parameters are: $V^+ = 7.5$ V and $V^- = -7.5$ V.

The output resistance of the two-transistor current source, R_O , is 120 k Ω .

Draw the final circuit for your design, showing all relevant signals including the power supply voltages.

Answer:

$$R_O = V_A / I_O$$

$$I_O = V_A / R_O = 100 / 120\text{k} = 0.833 \text{ mA}$$


[1] [0.5] [0.5]

$$I_{REF} = I_O (1 + 2/\beta) = (0.833\text{m})(1 + 2/100) = 0.850 \text{ mA}$$

[1] [1] [1]

$$R_1 = (V^+ - V_{BE} - V^-) / I_{REF} = (7.5 - 0.6 - (-7.5)) / 0.850\text{m} = 16.941 \text{ k}\Omega$$

[1] [1] [1]

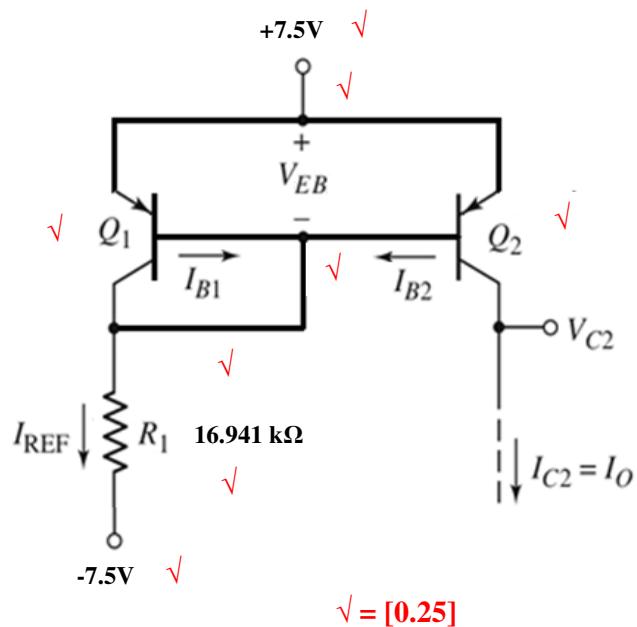

Question:

Design a two-transistor current source, **using pnp transistors**, given the following parameters:

The transistor parameters are: $\beta = 80$, V_{BE} (on) = 0.6 V, and $V_A = 180$ V.

The circuit parameters are: $V^+ = 10$ V and $V^- = -10$ V.

The output resistance of the two-transistor current source, R_O , is 98 k Ω .

Draw the final circuit for your design, showing all relevant signals including the power supply voltages.

Answer:

$$R_O = V_A / I_O$$

$$I_O = V_A / R_O = 180 / 98k = 1.837 \text{ mA}$$

[1] [0.5] [0.5]

$$I_{REF} = I_O (1 + 2/\beta) = (1.837\text{m})(1 + 2/80) = 1.883 \text{ mA}$$

[1] [1] [1]

$$R_1 = (V^+ - V_{BE} - V^-) / I_{REF} = (10 - 0.6 - (-10)) / 1.883\text{m} = 10.305 \text{ k}\Omega$$

[1] [1] [1]

