

**Question:**

Figure 1 shows circuit diagram of a BJT current source.

- (a) Name the circuit for the current source. [1 mark]
- (b) Draw the AC equivalent circuit for the current source. [2 marks]
- (c) Draw the small-signal equivalent circuit for the current source. Do not forget to connect external test signal,  $V_x$ , to the circuit. [3 marks]
- (d) Using the small-signal equivalent circuit derive the equation for output resistance,  $R_o$ , of the current source. [4 marks]

**Answer:**

- (a) BJT Cascode current source. [1]
- (b) See next page. [2]
- (c) See next page. [3]
- (d) [4]

$$V_{be4} = -I_x (r_{o2} \parallel r_{\pi4})$$

Summing currents at output node yields

$$I_x = g_{m4} V_{be4} + \left( \frac{V_x - (-V_{be4})}{r_{o4}} \right)$$

$$I_x = -g_{m4} I_x (r_{o2} \parallel r_{\pi4}) + \left( \frac{V_x - I_x (r_{o2} \parallel r_{\pi4})}{r_{o4}} \right)$$

$$\frac{V_x}{r_{o4}} = I_x + g_{m4} I_x (r_{o2} \parallel r_{\pi4}) + \frac{I_x (r_{o2} \parallel r_{\pi4})}{r_{o4}}$$

$$V_x = I_x (r_{o4} + r_{o4} g_{m4} (r_{o2} \parallel r_{\pi4}) + (r_{o2} \parallel r_{\pi4}))$$

$$V_x = I_x (r_{o4} + r_{o4} g_{m4} (r_{\pi4}) + (r_{\pi4}))$$

Where  $\beta = g_{m4} r_{\pi4}$  and assuming  $r_{\pi4} \ll r_{o2}$

$$R_o = \frac{V_x}{I_x} = r_{o4} (1 + \beta) + r_{\pi4} \approx \beta r_{o4}$$



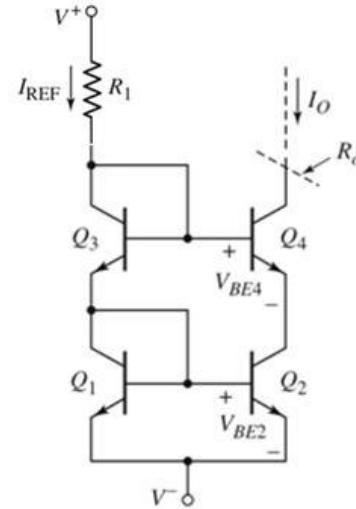


Figure 1

### AC equivalent circuits

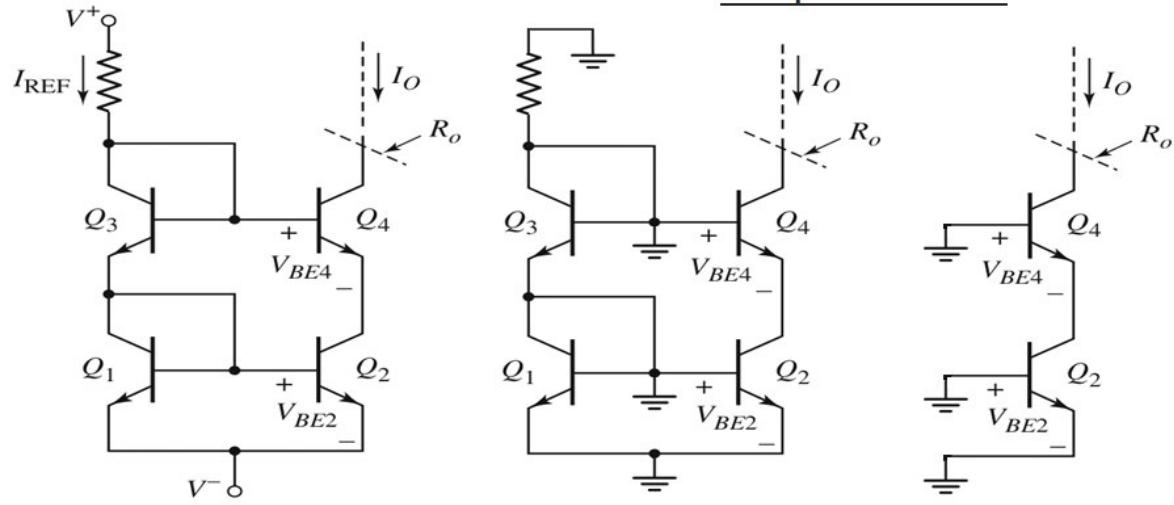

### Small-signal equivalent circuits

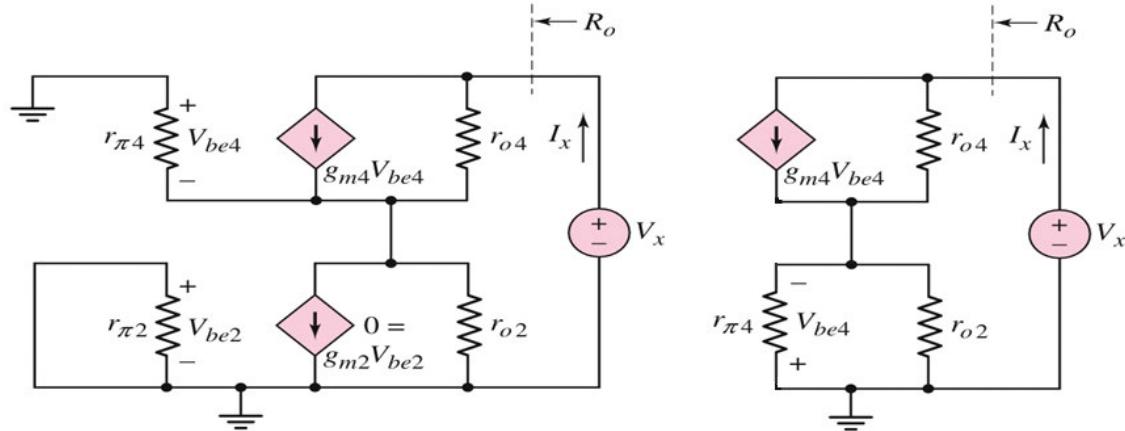

**Question:**

Figure 1 shows circuit diagram of a BJT current source.

- (e) Name the circuit for the current source. [1 mark]
- (f) Draw the AC equivalent circuit for the current source. [2 marks]
- (g) Draw the small-signal equivalent circuit for the current source. Do not forget to connect external test signal,  $V_x$ , to the circuit. [3 marks]
- (h) Using the small-signal equivalent circuit derive the equation for output resistance,  $R_O$ , of the current source. [4 marks]

**Answer:**

- (e) BJT Widlar current source. [1]
- (f) See next page. [2]
- (g) See next page. [3]
- (h) [4]

$$\text{Define } R'_E = R_E \parallel r_{\pi 2}$$

Then

$$V_{\pi 2} = -I_x R'_E$$

$$I_x = g_{m2} V_{\pi 2} + \frac{V_x - (-V_{\pi 2})}{r_{o2}}$$

$$I_x = g_{m2} (-I_x R'_E) + \frac{V_x}{r_{o2}} - \frac{I_x R'_E}{r_{o2}}$$

$$\frac{V_x}{r_{o2}} = I_x + g_{m2} (I_x R'_E) + \frac{I_x R'_E}{r_{o2}}$$

Normally  $(1/r_{o2}) \ll g_{m2}$ , producing

$$\frac{V_x}{I_x} = R_O = r_{o2} \left[ 1 + R'_E \left( g_{m2} + \frac{1}{r_{o2}} \right) \right]$$

$$R_O \approx r_{o2} (1 + g_{m2} R'_E)$$



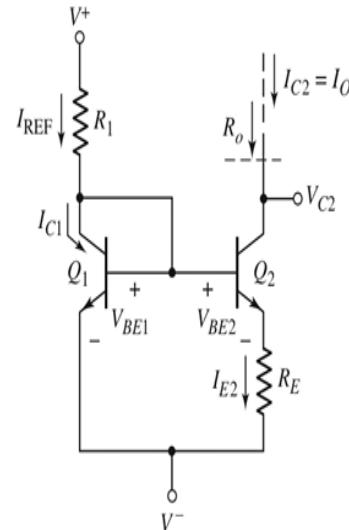


Figure 1

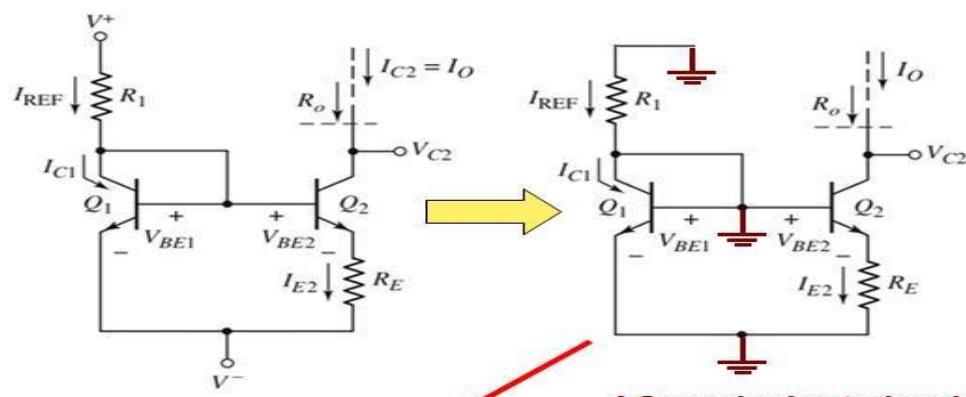

**AC equivalent circuit**

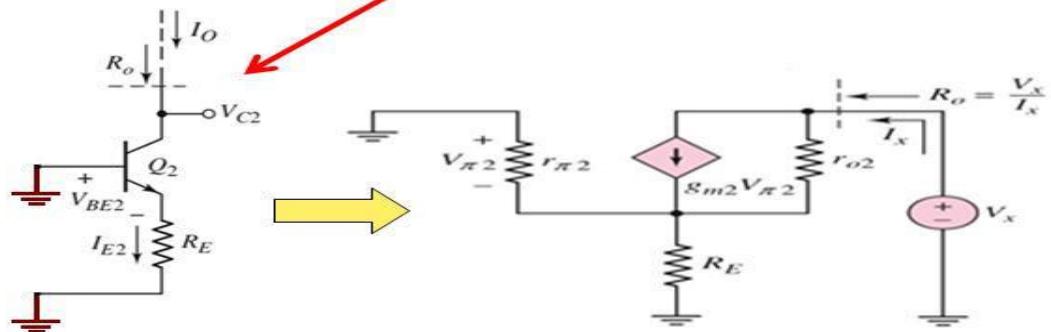

**Small-signal equivalent circuit**