

Question:

Study Figure 1 carefully. Given that $v_{I1} = 0.9 \text{ V}$ and $v_{I2} = 0.6 \text{ V}$.

(a) Using **superposition theorem**, find v_2 .

[6 marks]

(b) Find v_O .

[4 marks]

Show clearly all calculations in order to get full marks.


Answer:

(a)
 Find v_2 when $v_{I2} = 0$
 $v_2 (v_{I1}) = (40\text{k}/(20\text{k}+40\text{k}))(v_{I1})$ [1]
 $= (40\text{k}/(60\text{k}))(0.9) = 0.6 \text{ V}$ [1]

Find v_2 when $v_{I1} = 0$
 $v_2 (v_{I2}) = (20\text{k}/(20\text{k}+40\text{k}))(v_{I2})$ [1]
 $= (20\text{k}/(60\text{k}))(0.6) = 0.2 \text{ V}$ [1]

$v_2 = v_2 (v_{I1}) + v_2 (v_{I2})$ [1]
 $= 0.6 + 0.2 = 0.8 \text{ V}$ [1]

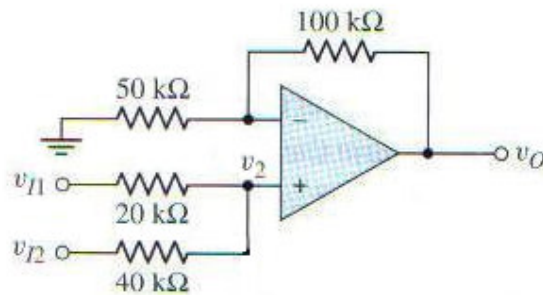(b)
 Using virtual short circuit properties
 $v_O = (1+100\text{k}/50\text{k})(v_2)$ [2]
 $= (3)(0.8) = 2.4 \text{ V}$ [2]



1

Question:

Study Figure 1 carefully. Given that $v_{I1} = 0.75 \text{ V}$ and $v_{I2} = 0.45 \text{ V}$.

(c) Using **superposition theorem**, find v_2 .

[6 marks]

(d) Find v_O .

[4 marks]

Show clearly all calculations in order to get full marks.

Answer:

(a)
 Find v_2 when $v_{I2} = 0$
 $v_2 (v_{I1}) = (40\text{k}/(20\text{k}+40\text{k}))(v_{I1})$ [1]
 $= (40\text{k}/(60\text{k}))(0.75) = 0.5 \text{ V}$ [1]

Find v_2 when $v_{I1} = 0$
 $v_2 (v_{I2}) = (20\text{k}/(20\text{k}+40\text{k}))(v_{I2})$ [1]
 $= (20\text{k}/(60\text{k}))(0.45) = 0.15 \text{ V}$ [1]

$v_2 = v_2 (v_{I1}) + v_2 (v_{I2})$ [1]
 $= 0.5 + 0.15 = 0.65 \text{ V}$ [1]

(b)
 Using virtual short circuit properties
 $v_O = (1+100\text{k}/50\text{k})(v_2)$ [2]
 $= (3)(0.65) = 1.95 \text{ V}$ [2]

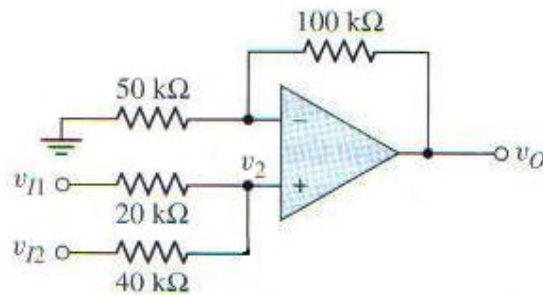


Figure 1