



**COLLEGE OF ENGINEERING  
PUTRAJAYA CAMPUS  
FINAL EXAMINATION  
SEMESTER 1 2011 / 2012**

**PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)  
Bachelor of Electrical Power Engineering (Honours)**

**SUBJECT CODE : EEEB273**

**SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II**

**DATE : August 2011**

**TIME : 9.00 am – 12.00 pm (3 hours)**

---

**MODEL ANSWERS**

---

**Question 1 [16 marks]****Answers:****Q1 (a) (i)**Starting from  $I_{E3}$ 

$$I_{REF} = (I_{C3} + I_{B3}) + I_{B4} = I_{E3} + I_{B4} \quad [0.5]$$

$$I_{REF} = I_{E3} + I_O / \beta \quad [0.5]$$

$$I_O = I_{C4} = \frac{\beta}{\beta + 1} I_{E4} = \frac{\beta}{(\beta + 1)(1 + 2/\beta)} I_{E3} \quad [1]$$

$$I_{E3} = \frac{(\beta + 1)(1 + 2/\beta)}{\beta} I_O = \frac{(\beta + 1)(\beta + 2)}{\beta^2} I_O \quad [0.5]$$

$$I_{REF} = \frac{(\beta + 1)(\beta + 2)}{\beta^2} I_O + I_O / \beta = \frac{(\beta^2 + 3\beta + 2) + \beta}{\beta^2} I_O \quad [0.5]$$

$$I_{REF} = \frac{\beta^2 + 4\beta + 2}{\beta^2} I_O = \left(1 + \frac{4}{\beta} + \frac{2}{\beta^2}\right) I_O \quad [0.5]$$

$$I_{REF} \approx \left(1 + \frac{4}{\beta}\right) I_O \quad [0.5]$$

assuming  $2/\beta^2 \approx 0$  or  $\beta^2 \gg 1$ Optional answer: Starting from  $I_{B1}$  or  $I_{B2}$ 

$$I_{B1} = I_{B2}$$

$$I_{E4} = I_{C2} = \beta I_{B2} = \beta I_{B1}$$

$$I_O = I_{C4} = \frac{\beta}{\beta + 1} I_{E4} = \frac{\beta}{\beta + 1} (\beta I_{B1}) \Rightarrow I_{B1} = \frac{\beta + 1}{\beta^2} I_O$$

$$I_{B4} = \frac{I_{E4}}{\beta + 1} = \frac{\beta I_{B1}}{\beta + 1} = \frac{\beta}{\beta + 1} I_{B1}$$

$$I_{C1} = \beta I_{B1}$$

$$I_{E3} = I_{C1} + I_{B1} + I_{B2} = I_{C1} + 2I_{B1} = (\beta + 2)I_{B1}$$

$$I_{REF} = (I_{C3} + I_{B3}) + I_{B4} = I_{E3} + I_{B4}$$

$$I_{REF} = (\beta + 2)I_{B1} + \frac{\beta}{\beta + 1} I_{B1} = \frac{(\beta + 2)(\beta + 1) + \beta}{\beta + 1} I_{B1}$$


$$I_{REF} = \left(\frac{(\beta + 2)(\beta + 1) + \beta}{(\beta + 1)}\right) \left(\frac{\beta + 1}{\beta^2} I_O\right)$$

$$I_{REF} = \frac{\beta^2 + 4\beta + 2}{\beta^2} I_O = \left(1 + \frac{4}{\beta} + \frac{2}{\beta^2}\right) I_O$$

$$I_{REF} \approx \left(1 + \frac{4}{\beta}\right) I_O$$

**Q1 (a) (ii)**

Simplified Circuit

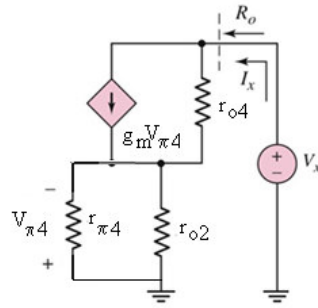

[1] for circuit

$$I_x = g_{m4}V_{\pi 4} + \left( \frac{V_x - I_x(r_{o2} \parallel r_{\pi 4})}{r_{o4}} \right) \quad [1]$$

$$I_x = -g_{m4}I_x(r_{o2} \parallel r_{\pi 4}) + \left( \frac{V_x - I_x(r_{o2} \parallel r_{\pi 4})}{r_{o4}} \right) \quad [1]$$

$$\frac{V_x}{I_x} = r_{o4}(1 + \beta) + r_{\pi 4} \cong \beta r_{o4} \quad [1]$$

**Q1 (b)**

$$I_{REF} = \frac{k'_n}{2} \left( \frac{W}{L} \right)_3 (V_{GS3} - V_{TN})^2 \quad [0.5]$$

$$I_{D1} = I_{REF} = \frac{k'_n}{2} \left( \frac{W}{L} \right)_1 (V_{GS1} - V_{TN})^2 \quad [0.5]$$

$$I_O = I_{D2} = \frac{k'_n}{2} \left( \frac{W}{L} \right)_2 (V_{GS2} - V_{TN})^2 \quad [0.5]$$

$$V_{DS2(sat)} = V_{D2} - (-3) = 1.8V \quad [1]$$

$$V_{GS2} = V_{DS2(sat)} + V_{TN} = 1.8 + 0.5 = 2.3 \quad [1]$$

$$\left( \frac{W}{L} \right)_2 = \frac{2I_O (V_{GS2} - V_{TN})^2}{k'_n} = 4.05 \quad [1]$$

$$V_{GS1} = 2.3 \quad [0.5]$$

$$\left( \frac{W}{L} \right)_1 = \frac{2I_{REF} (V_{GS1} - V_{TN})^2}{k'_n} = 12.15 \quad [1]$$

$$V_{GS3} = 3 - 2.3 - (-3) = 3.7V \quad [1]$$

$$\left( \frac{W}{L} \right)_3 = \frac{2I_{REF} (V_{GS3} - V_{TN})^2}{k'_n} = 38.4 \quad [1]$$

**Question 2 [16 marks]****Answers:****Q2 (a)**

$$V_{GS1} = \sqrt{\frac{I_{D1}}{K_{n1}}} + V_{TN} = \sqrt{\frac{60\mu}{150}} + 0.3 = 0.9324V \quad [1.5]$$

$$R_D = \frac{V^+ - V_{DS1} + V_{GS1} - v_1}{I_{D1}} = \frac{3 - 3 + 0.9324 + 1.5}{60\mu} = 40.5k\Omega \quad [1.5]$$

$$I_1 = I_Q = 2I_{D1} = 120\mu A \quad [1.5]$$

$$V_{DS3} = V_{GS3} = V_{GS4} = \sqrt{\frac{I_Q}{K_{n4}}} + V_{TN} = \sqrt{\frac{120\mu}{100}} + 0.3 = 1.3954V \quad [2]$$

$$R_1 = \frac{V^+ - V_{DS3} - V^-}{I_1} = \frac{3 - 1.3954 + 3}{120\mu} = 38.37k\Omega \quad [1.5]$$

**Q2 (b)**

$$V_{DS4}(init) = v_1(init) - V_{GS1} - V^- = -1.5 - 0.9324 + 3 = 0.5676V \quad [1.5]$$

$$V_{DS4}(fin) = v_1(fin) - V_{GS1} - V^- = 1.05 - 0.9324 + 3 = 3.1176V \quad [1.5]$$

$$\Delta V_{DS4} = V_{DS4}(fin) - V_{DS4}(init) = 3.1176 - 0.5676 = 2.5501V \quad [1]$$

**Q2 (c)**

$$R_O = 1/(\lambda_4 I_Q) = 1/((0.01)(120\mu)) = 0.8333M\Omega \quad [1.5]$$

$$\Delta I_Q / \Delta V_{DS4} = 1 / R_O \quad [1]$$

$$\Delta I_Q = \Delta V_{DS4} / R_O = 2.5501 / 0.8333M = 3.06\mu A \quad [1.5]$$

**Question 3 [16 marks]**

**Answers:**

**Q3 (a) (i)**

- In actual BJT circuits, base currents are non zero [0.5]
- For circuit to be balanced,  $I_1 = I_2$  and  $I_3 = I_4$  [0.5]
- Else the active load transistors  $Q_3$  and  $Q_4$  will not be biased in active mode [1]

**Q3 (a) (ii)**

$$I_{B5} = \frac{I_{E5}}{(1 + \beta)} = \frac{I_{B3} + I_{B4}}{(1 + \beta)} = \frac{I_{C3} + I_{C4}}{\beta(1 + \beta)} \quad [1]$$

The current  $I_{C3} + I_{C4} \cong I_O$  [1]

$$\left. \begin{aligned} I_{C1} &= I_{C3} + I_{B5} \\ I_{C1} &= I_{C4} + I_O \end{aligned} \right\} \quad [1]$$

Hence, to keep the current balanced:  $I_O = I_{B5} = \frac{I_O}{\beta(1 + \beta)}$  [1]

Given,  $I_O = 0.2$  mA, hence:  $I_O = \frac{0.2 \text{ m}}{100(1 + 100)} = 19.8$  nA [1]

**Q3 (b) (i)**

- Biasing stage:  $R_1, R_2, R_3, Q_9, Q_{10}, Q_{11}$  [1]
- Input stage: Differential amplifier with active load:  $Q_1$  to  $Q_5$  [1]
- Second gain stage: Darlington pair:  $Q_6$  and  $Q_7$  [1]
- Output stage: emitter follower output stage:  $Q_8$  and  $R_4$  [1]

**Q3 (b) (ii)**

$$R_{L7} = R_{C11} \parallel R_{B8} \quad [1]$$

$$R_{C11} = r_{o11} [1 + g_{m11} (r_{\pi11} \parallel R_3)] \quad [1]$$

$$R_{C11} = (500k) [1 + (5m)(3k \parallel 250)] = 1.08M\Omega \quad [0.5]$$

$$R_{B8} = r_{\pi8} + (1 + \beta)R_4 \quad [1]$$

$$R_{B8} = 3k + (1 + 100)(10k) = 1.01M\Omega \quad [0.5]$$

$$R_{L7} = 1.08M \parallel 1.01M = 522k\Omega \quad [1]$$

**Question 4 [16 marks]****Answers:****Q4 (a)**

$$I_{D11} = I_{D12} = I_{D13} = I_{D3} = I_{D4} = I_{REF} = 50 \mu\text{A} \quad [1.5]$$

$$I_{D1} = I_{D2} = I_{D11}/2 = 25 \mu\text{A} \quad [0.5]$$

$$I_{D5} = I_{D3} - I_{D2} = 50\mu - 25\mu = 25 \mu\text{A} = I_{D7} = I_{D9} \quad [0.5]$$

$$I_{D6} = I_{D1} - I_{D4} = 50\mu - 25\mu = 25 \mu\text{A} = I_{D8} = I_{D10} \quad [0.5]$$

**Q4 (b)**

$$A_d = g_{m1}(R_{O6} \parallel R_{O8}) \quad [1]$$

$$R_{O6} = g_{m6}r_{O6}(r_{O4} \parallel r_{O1}) \quad [0.5]$$

$$R_{O8} = g_{m8}r_{O8}r_{O10} \quad [0.5]$$

$$g_{m1} = 2\sqrt{\frac{K_{p1}I_{REF}}{2}} = 2\sqrt{\frac{k'_p}{2}\left(\frac{W}{L}\right)_1 \frac{I_{REF}}{2}} = 2\sqrt{\frac{20\mu}{2}(10)\frac{50\mu}{2}} = 0.1\text{mA/V} \quad [1]$$

$$g_{m6} = 2\sqrt{\frac{K_{n6}I_{REF}}{2}} = 2\sqrt{\frac{k'_n}{2}\left(\frac{W}{L}\right)_6 \frac{I_{REF}}{2}} = 2\sqrt{\frac{40\mu}{2}(10)\frac{50\mu}{2}} = 0.141\text{mA/V} \quad [1]$$

$$g_{m8} = 2\sqrt{\frac{K_{p8}I_{REF}}{2}} = 2\sqrt{\frac{k'_p}{2}\left(\frac{W}{L}\right)_8 \frac{I_{REF}}{2}} = 2\sqrt{\frac{20\mu}{2}(20)\frac{50\mu}{2}} = 0.141\text{mA/V} \quad [1]$$

$$r_{O6} = 1/(\lambda_n I_{REF} / 2) = 1/((0.005)(25\mu)) = 8\text{M}\Omega \quad [0.5]$$

$$r_{O4} = 1/(\lambda_n I_{REF}) = 1/((0.005)(50\mu)) = 4\text{M}\Omega \quad [0.5]$$

$$r_{O1} = r_{O8} = r_{O10} = 1/(\lambda_p I_{REF} / 2) = 1/((0.01)(25\mu)) = 4\text{M}\Omega \quad [0.5]$$

$$R_{O6} = (0.141\text{m})(8\text{M})(4\text{M} \parallel 4\text{M}) = 2256\text{M}\Omega \quad [0.5]$$

$$R_{O8} = (0.141\text{m})(4\text{M})(4\text{M}) = 2256\text{M}\Omega \quad [0.5]$$

$$A_d = (0.1\text{m})(2256\text{M} \parallel 2256\text{M}) = 112800\text{V/V} \quad [0.5]$$

**Q4 (c)**

$$A_d' = 2A_d = 2(112800) = 225600 \quad [1]$$

$$A_d' = g_{m1}'(R_{O6} \parallel R_{O8}) \quad [1]$$

$$(R_{O6} \parallel R_{O8}) = 1128M\Omega$$

$$g_{m1}' = 225600 / (1128M) = 0.2mA/V \quad [1]$$

$$g_{m1}' = 2\sqrt{\frac{k_p'}{2} \left(\frac{W}{L}\right)_1 \frac{I_{REF}}{2}} = 2\sqrt{\frac{20\mu}{2} \left(\frac{W}{L}\right)_1 \frac{50\mu}{2}} \quad [1]$$

$$0.2m = 31.62\mu\sqrt{\left(\frac{W}{L}\right)_1}$$

$$\sqrt{\left(\frac{W}{L}\right)_1} = 6.3245$$

$$\left(\frac{W}{L}\right)_1 = 40 \quad [1]$$

**Question 5 [16 marks]**

**Answers:**

**Q5 (a)**

Diagrams

[1]

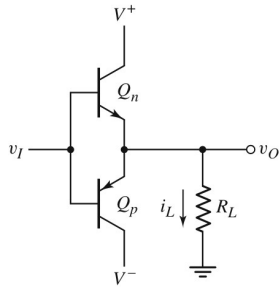


Figure (a)

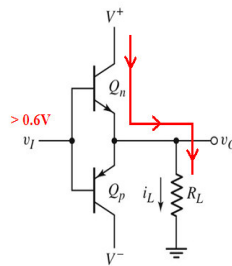


Figure (b)

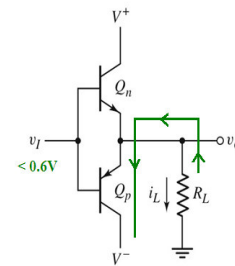


Figure (c)

- Figure (a)  $\rightarrow v_I = 0$ : both  $Q_n$  &  $Q_p$  cut-off,  $v_O = 0$ . Assume  $V_{BE(on)} = 0.6V$ :  $v_O$  remains 0 as long as  $-0.6V \leq v_I \leq +0.6V$  [1]
- Figure (b)  $\rightarrow v_I > +0.6V$ :  $Q_n$  turns on and operates as emitter follower,  $I_L$  is positive (supplied thru  $Q_n$ ), B-E junction of  $Q_p$  is reverse-biased [1]
- Figure (c)  $\rightarrow v_I < -0.6V$ :  $Q_p$  turns on and operates as emitter follower,  $Q_p$  sinks  $I_L$  (which is negative), B-E junction of  $Q_n$  is reverse-biased [1]

**Q5 (b)**

Class-AB output stage

[2]

**Q5 (c)**

$Q_{18}$  and  $Q_{19}$  establish  $2V_{BE}$  drops between base terminals of  $Q_{14}$  &  $Q_{20}$ . This  $V_{BB}$  produces quiescent collector currents in  $Q_{14}$  and  $Q_{20}$ , therefore biasing both  $Q_{14}$  and  $Q_{20}$  “on” with no signal present at the input. [2]

**Q5 (d)**

Class-AB output stage had removed crossover distortion experienced in the approximate class-B output stage. [2]



**Q5 (e)**

If we assume  $V_{BE19} = 0.6$  V, then the current in  $R_{10}$  is

$$I_{R10} = V_{BE19} / R_{10} = 0.6 / 50k = 0.012 \text{ mA} \quad [1]$$

The current in  $Q_{19}$  is

$$I_{C19} \approx I_{E19} = I_{Bias} - I_{R10} = 0.18\text{m} - 0.012\text{m} = 0.168 \text{ mA} \quad [1]$$

For that value of collector current, the B-E voltage of  $Q_{19}$  is

$$V_{BE19} = V_T \ln(I_{C19} / I_S) = (0.026) \ln(0.168\text{m} / 10^{-14}) = 0.612 \text{ V} \quad [1]$$

The base current in  $Q_{19}$  is

$$I_{B19} = I_{C19} / \beta_n = 0.168\text{m} / 200 = 0.84 \mu\text{A} \quad [0.5]$$

The current in  $Q_{18}$  is now

$$I_{C18} \approx I_{E18} = I_{R10} + I_{B19} = 0.012\text{m} + 0.84\mu = 12.84 \mu\text{A} \quad [0.5]$$

The B-E voltage of  $Q_{18}$  is therefore

$$V_{BE18} = V_T \ln(I_{C18} / I_S) = (0.026) \ln(12.84\mu / 10^{-14}) = 0.545 \text{ V} \quad [1]$$

The voltage difference  $V_{BB}$  is thus

$$V_{BB} = V_{BE18} + V_{BE19} = 0.545 + 0.612 = 1.157 \text{ V} \quad [1]$$

**Question 6 [20 marks]****Answers:****Q6 (a)**

- $A_{od}$ : Internal differential gain (open loop gain) is considered to be  $\infty$ .
- $(v_2 - v_1)$ : Differential input voltage is assumed to be 0. If  $A_{od} \rightarrow \infty$  and  $v_O$  is finite, then  $v_2 \approx v_1$ .
- $R_i$ : Effective input resistance is assumed to be  $\infty$ , so input currents  $i_1$  and  $i_2$  are essentially 0.
- $R_o$ : Effective output resistance is assumed to be 0, so output voltage is independent of any load connected to the output.
- Bandwidth  $\rightarrow \infty$ .
- $CMRR$ : Common mode rejection ratio =  $\infty$ .

$\Rightarrow$  Each answer above give [1] mark

**Q6 (b)**

$$v_{I2} = 0: \quad v_{O1}(v_{I1}) = (-R_F/R_1) v_{I1} = (-100\text{k}/100\text{k}) v_{I1} = -v_{I1}$$

[0.5]                                  [0.5]                                  [0.5]                                  [0.5]

$$v_{I1} = 0: \quad v_{O1}(v_{I2}) = (-R_F/R_2) v_{I2} = (-100\text{k}/100\text{k}) v_{I2} = -v_{I2}$$

[0.5]                                  [0.5]                                  [0.5]                                  [0.5]

$$v_{O1} = v_{O1}(v_{I1}) + v_{O1}(v_{I2}) = (-v_{I1}) + (-v_{I2}) = -(v_{I1} + v_{I2})$$

[0.5]                                  [0.5]                                  [0.5]

$$v_O = (-R_F/R_1) v_{O1} = (-100\text{k}/100\text{k}) [ -(v_{I1} + v_{I2}) ] = v_{I1} + v_{I2}$$

[0.5]                                  [0.5]                                  [0.5]

**Q6 (c)**

(i) **Difference amplifier** [1]

(ii)  $R_3 = R_4 = 100 \text{ k}\Omega$

$$A_v = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1 + R_{1POT}} \right) = \frac{100k}{100k} \left( 1 + \frac{2R_2}{R_1 + R_{1POT}} \right) = \left( 1 + \frac{2R_2}{R_1 + R_{1POT}} \right)$$

[1]

$A_v$  is maximum (i.e.  $A_v = 100$ ) when  $R_{1POT} = 0$ , i.e.

$$100 = \left( 1 + \frac{2R_2}{R_1 + 0} \right)$$

[1]

$$99 R_1 = 2 R_2 \quad \text{\{Eqn 1\}} \quad [0.5]$$

$A_v$  is minimum (i.e.  $A_v = 10$ ) when  $R_{1POT} = 100 \text{ k}\Omega$ , i.e.

$$10 = \left( 1 + \frac{2R_2}{R_1 + 100k} \right)$$

[1]

$$9(R_1 + 100k) = 2 R_2 \quad \text{\{Eqn 2\}} \quad [0.5]$$

$$\text{\{Eqn 1\}} = \text{\{Eqn 2\}}$$

$$99 R_1 = 9 R_1 + 900k \quad [1]$$

$$\rightarrow R_1 = 10 \text{ k}\Omega \quad [1]$$

$$\rightarrow R_2 = (99 R_1) / 2 = 495 \text{ k}\Omega \quad [1]$$

(iii)  $v_{I1} = 1.00 \text{ V}$ ,  $v_{I2} = 1.15 \text{ V}$ ,  $R_4 = 2 R_3$ ,  $R_{1POT} = 40 \text{ k}\Omega$

$$A_v = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1 + R_{1POT}} \right) = \frac{2R_3}{R_3} \left( 1 + \frac{2(495k)}{10k + 40k} \right) = 41.6 \quad [1.5]$$

$$v_o = A_v (v_{I2} - v_{I1}) = (41.6)(1.15 - 1.00) = 6.24V \quad [1.5]$$