



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION
SEMESTER 1 2011 / 2012**

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : August 2011

TIME : 3 hours

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **Six** (6) questions in **Ten** (10) pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided.
4. Write answer to each question on a **new page**.
5. For all calculations, assume that $V_T = 26 \text{ mV}$.

THIS QUESTION PAPER CONSISTS OF TEN (10) PRINTED PAGES INCLUDING THIS COVER PAGE.

Question 1 [16 marks]

- (a) Referring to the circuits in **Figure 1a**, the transistors in the circuit are identical.
- (i) For the circuit in **Figure 1a (i)**, show that $I_{REF} \approx (1+4/\beta) I_O$. Label the currents which you use in your equations correctly. (Hints: You may start with I_{E3} and I_{E4} relationship given in the circuit. Note that $I_{B3} \neq I_{B4}$. Assume $\beta^2 \gg 1$). [4 marks]
- (ii) For the circuit in **Figure 1a (ii)**, simplify the circuit and draw the simplified circuit. Using the simplified circuit, derive the ratio of V_x / I_x . Assume that $r_{\pi 4} \ll r_{o2}$. [4 marks]

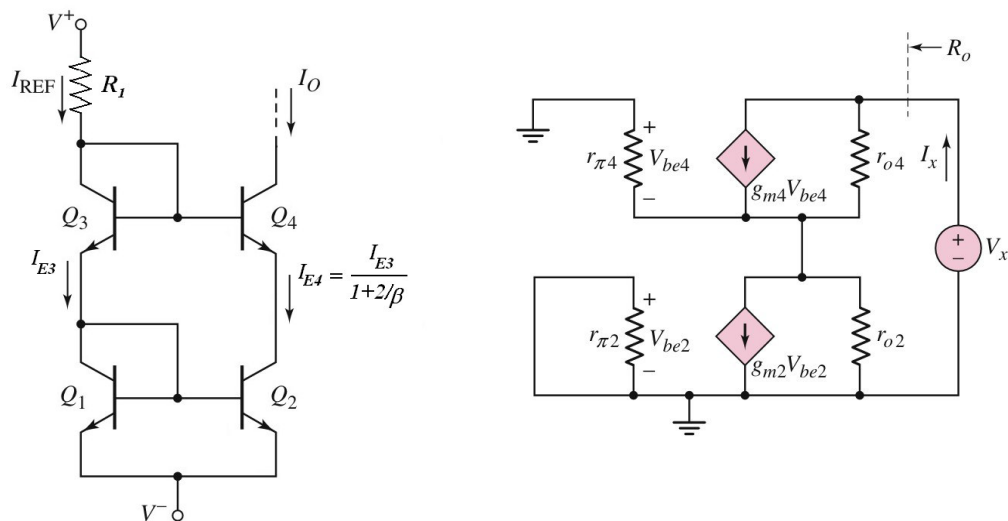


Figure 1a (i) BJT Cascode Current Source, and **(ii)** The Small Signal Equivalent Circuit.

- (b) The MOSFET current source circuit in **Figure 1b** has transistor parameters $k'_n = 80 \mu\text{A}/\text{V}^2$ and $V_{TN} = 0.5 \text{ V}$. **Design** the current source so that $I_O = 50 \mu\text{A}$ when $I_{REF} = 150 \mu\text{A}$ and V_{D2} at -1.2V . [8 marks]

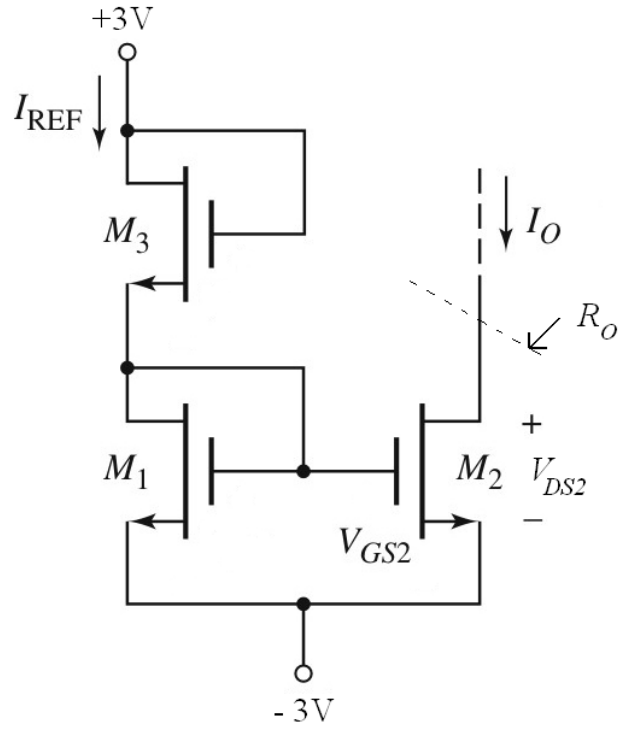


Figure 1b

Question 2 [16 marks]

Consider the circuit shown in **Figure 2**. The bias voltages are **+3 V** and **-3 V**. The transistor parameters are $K_{n1} = K_{n2} = 150 \mu\text{A}/\text{V}^2$, $K_{n3} = K_{n4} = 100 \mu\text{A}/\text{V}^2$, and $V_{TN} = 0.3 \text{ V}$ for all transistors.

 


Figure 2

- (a) Calculate R_1 and R_D for the diff-amp circuit such that $V_{DS1} = V_{DS2} = 3 \text{ V}$ and $I_{D1} = I_{D2} = 60 \mu\text{A}$ when $v_1 = v_2 = -1.5 \text{ V}$. [8 marks]
- (b) Input v_1 and v_2 are changed from $v_1 = v_2 = -1.5 \text{ V}$ to $v_1 = v_2 = +1.05 \text{ V}$. Calculate change in V_{DS4} (i.e. ΔV_{DS4}). [4 marks]
- (c) Given that $\lambda_1 = \lambda_2 = 0$ and $\lambda_3 = \lambda_4 = 0.01 \text{ V}^{-1}$. Calculate the change in I_Q (i.e. ΔI_Q) using result from **part (b)**. [4 marks]

Question 3 [16 marks]

- (a) The differential amplifier shown in **Figure 3a** has a three-transistor current mirror connected as an active load. The circuit is connected to power supply voltages of $V^+ = +5$ V and $V^- = -5$ V.

 


Figure 3a

- (i) The dc currents in the BJT differential amplifier must be balanced such that $I_{B5} = I_O$. **Explain** why this is important in a BJT circuit. [2 marks]
- (ii) **Determine** the relationship between I_O and I_Q such that the amplifier dc currents are balanced. **Calculate** the value of I_O given that $I_Q = 0.2$ mA and $\beta = 100$. [5 marks]

- (b) The circuit in **Figure 3b** shows a simple multistage BJT op-amp, **consisting of four different stages**. It is given that for all transistors, $\beta=100$.

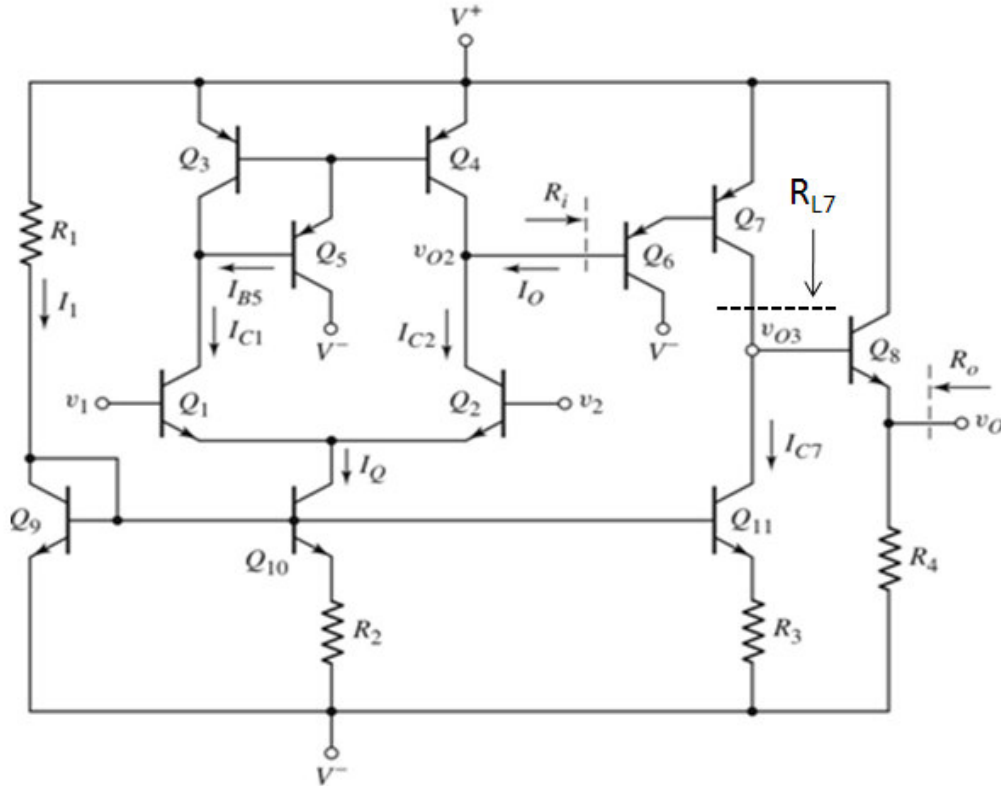


Figure 3b

- (i) **Name** the four stages in the circuit, and **indicate** which transistors and resistors belonging to each stage. [4 marks]
- (ii) Assuming that for all transistors: $r_o = 500 \text{ k}\Omega$, $g_m = 5 \text{ mA/V}$, $r_\pi = 3 \text{ k}\Omega$, $R_3 = 250 \Omega$, and $R_4 = 10 \text{ k}\Omega$. For Q_7 , the **Early voltage** V_A is assumed to be infinite. **Calculate the small signal input impedance** at the collector of Q_7 , i.e. R_{L7} as indicated in the **Figure 3b**. [5 marks]

Question 4 [16 marks]

The folded cascode CMOS op-amp in **Figure 4** is biased such that $I_{REF} = 50 \mu\text{A}$. The circuit is connected to supply voltages of $V^+ = +5 \text{ V}$ and $V^- = -5 \text{ V}$. It is given that the transistor parameters are $k'_n = 40 \mu\text{A/V}^2$, $k'_p = 20 \mu\text{A/V}^2$, $\lambda_n = 0.005 \text{ V}^{-1}$, $\lambda_p = 0.01 \text{ V}^{-1}$, and $|V_T| = 1 \text{ V}$. The transistor aspect ratios are $(W/L)_{1,2,5,6} = 10$, $(W/L)_{3,4,11,12,13} = 5$, and $(W/L)_{7,8,9,10} = 20$.

- (a) **Determine** the dc currents in each transistor in the circuit. [3 marks]
- (b) **Determine** the differential-mode voltage gain of the op-amp. [8 marks]
- (c) **Redesign** the folded cascode differential amplifier, M_1 and M_2 , such that the differential-mode voltage gain of the op-amp is **twice** of that calculated in **part (b)**. [5 marks]

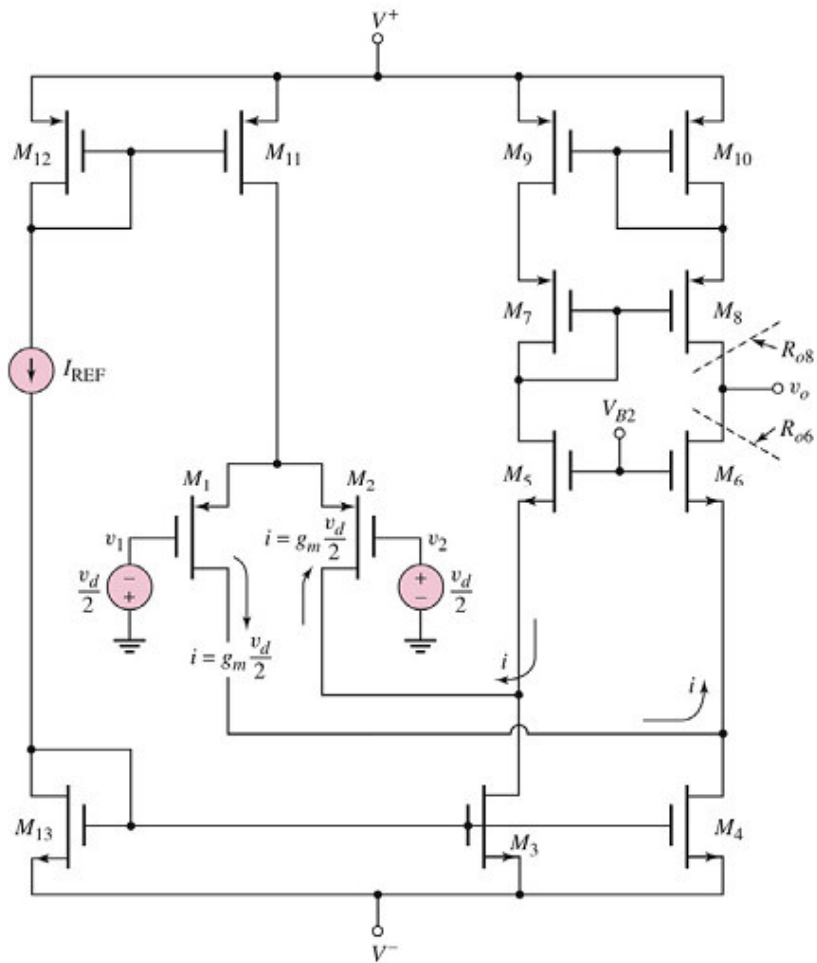


Figure 4

Question 5 [16 marks]

Figure 5 shows the output stage for 741 op-amp. Study the **Figure 5** carefully.

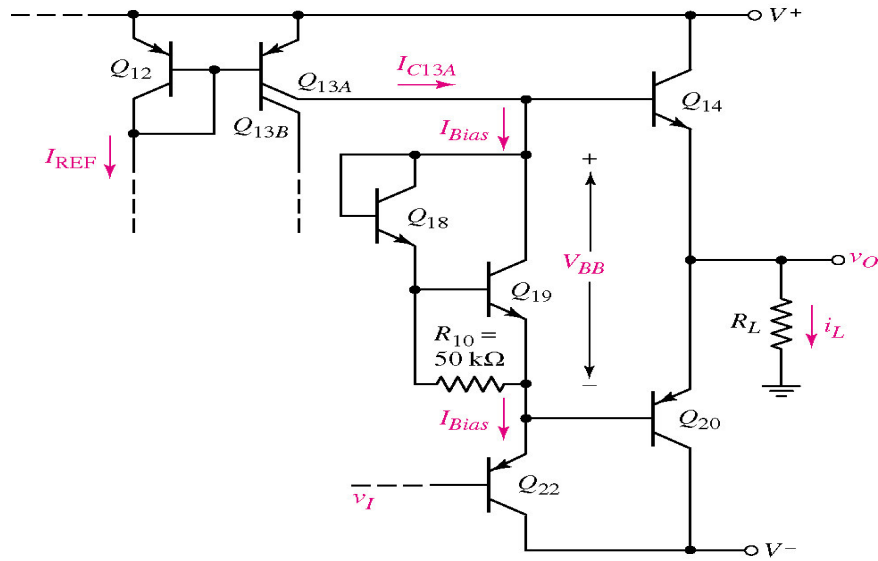


Figure 5

- (a) **Describe** the operation of an **approximate (i.e. non-ideal) class-B output stage**. Assume $V_{BEN(on)} = V_{EBP(on)} = 0.6 \text{ V}$. You may use appropriate diagrams to help your explanation. [4 marks]
- (b) **What** is the class of the output stage (which consists of transistors Q_{14} and Q_{20}) used in the **Figure 5**? [2 marks]
- (c) **Describe** how **quiescent bias current** for the output transistors Q_{14} and Q_{20} in **Figure 5** is established. [2 marks]
- (d) **What** is the advantage of the output stage given in the **Figure 5** compared to an **approximate (i.e. non-ideal) class-B output stage**? [2 marks]
- (e) For the output stage in the **Figure 5**, assume that reverse saturation currents $I_{S18} = I_{S19} = 10^{-14} \text{ A}$. Using $\beta_n = 200$, we can assume that $I_C \approx I_E$ for Q_{18} and Q_{19} . Given that $I_{Bias} = 0.18 \text{ mA}$. By initially assuming that $V_{BE19} = 0.6 \text{ V}$, **calculate** V_{BB} shown in the circuit. [6 marks]

Question 6 [20 marks]

(a) List two (2) ideal op-amp characteristics. [2 marks]

(b) For a **summing amplifier** using op-amps shown in **Figure 6b**, use appropriate ideal op-amp characteristics and **superposition theorem** to show that

$$v_O = v_{I1} + v_{I2}$$

when $R_1 = R_2 = R_F = 100 \text{ k}\Omega$. [7 marks]

 


Figure 6b

(c) **Figure 6c** shows a design for an **instrumentation amplifier** using op-amps. In the design, R_{1POT} is a **100 kΩ potentiometer** (or a variable resistor) used to provide variable resistance so that differential voltage gain (A_v) of the instrumentation amplifier can be adjustable. With analysis, it can be shown that

$$v_O = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1 + R_{1POT}} \right) (v_{I2} - v_{I1})$$

 


Figure 6c

- (i) **What** is the name of an amplifier represented by op-amp A_3 in the **Figure 6c**? [1 mark]
- (ii) With $R_3 = R_4 = 100 \text{ k}\Omega$, **design an instrumentation amplifier** using the circuit as shown in the **Figure 6c** to realize a differential voltage gain (A_v) adjustable from **10 to 100**. (Hints: A_v is smallest when R_{1POT} is at maximum value, and vice versa. You are required to determine the value of R_1 and R_2 in the circuit). [7 marks]
- (iii) With $v_{I1} = 1.00 \text{ V}$, $v_{I2} = 1.15 \text{ V}$, $R_4 = 2 R_3$, R_{1POT} is set at **40 k Ω** , and using the values of R_1 and R_2 found in step (ii) above, **calculate** A_v and v_O . [3 marks]

-END OF QUESTION PAPER-