


Name:

Student ID Number:

Section: 01/02/03/04/05 A/B

Lecturer: Dr Jamaludin/Dr Fazrena/
Ms Azni Wati

**UNIVERSITI
TENAGA
NASIONAL**

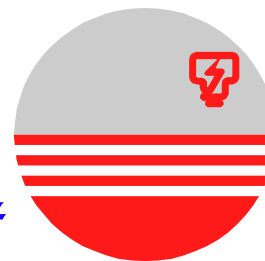

College of Engineering
Department of Electronics and Communication Engineering

Midterm Test – Model Answer

SEMESTER 1, ACADEMIC YEAR 2011/2012

Subject Code : **EEEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **17 June 2011**
Time Allowed : **2 hours**

Instructions to the candidates:

1. Write your Name and Student ID number. Circle your section number.
2. Write all your answers using pen. **DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.** Use both sides of the question paper to write your answers.
5. For all calculations, assume that $V_T = 26 \text{ mV}$.

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!



Question 1 [40 marks]

(a) List the advantage(s) of:

- (i) A basic three-transistor current source as compared to a two-transistor BJT current source. [2 marks]
- (ii) A Wilson current source as compared to a basic three-transistor BJT current source. [2 marks]
- (iii) A cascode current source as compared to a Wilson BJT current source. [2 marks]
- (iv) A Widlar current source as compared to a two-transistor BJT current source. [4 marks]

Answers for Question 1(a)

- (i) Better approximation of I_O to I_{REF} for circuit using same transistors [2]
- (ii) Higher output resistance by a factor of $\beta/2$ [2]
- (iii) Higher output resistance by a factor of 2 [2]
- (iv) Higher output resistance by a factor of $(1 + g_m R'_E)$ [2]
Using smaller resistors in the circuit [2]
Can have different values for I_O and I_{REF} where I_O is smaller than I_{REF} [2]
{Can use any two answers above}

(b) Consider a **modified three-transistor BJT current source** as in **Figure 1(b)**. Transistor parameters are $V_{BE(\text{on})} = 0.7 \text{ V}$, $V_A = \infty$, and $\beta = 80$. *Hint: Please take note of the current directions given in the Figure 1(b).*

(i) Show that

$$I_{REF} - \frac{V_{BE}}{(1+\beta)R_2} = I_O \left(1 + \frac{2}{\beta(1+\beta)} \right) \quad [10 \text{ marks}]$$

(ii) For $R_2 = 10 \text{ k}\Omega$, $V^+ = 10 \text{ V}$, and $I_O = 0.70 \text{ mA}$, find I_{REF} and R_I . [10 marks]

Answers for Question 1(b)

$$\begin{aligned} \text{(i)} \quad I_{B1} &= I_{B2} & [1] \\ I_O &= \beta I_{B2} \Rightarrow I_{B2} = I_O / \beta & [1] \\ I_{C1} &= \beta I_{B2} \Rightarrow I_{C1} = I_O & [1] \end{aligned}$$

$$\begin{aligned} I_{E3} &= 2 I_{B2} + V_{BE} / R_2 & [1] \\ I_{B3} &= I_{E3} / (1 + \beta) & [1] \\ &= (2 I_{B2}) / (1 + \beta) + (V_{BE}) / ((1 + \beta)R_2) & [1] \\ &= (2 I_O) / (\beta(1 + \beta)) + (V_{BE}) / ((1 + \beta)R_2) & [1] \end{aligned}$$

$$\begin{aligned} I_{REF} &= I_{C1} + I_{B3} & [1] \\ &= I_O + (2 I_O) / (\beta(1 + \beta)) + (V_{BE}) / ((1 + \beta)R_2) & [1] \end{aligned}$$

$$\begin{aligned} I_{REF} - (V_{BE}) / ((1 + \beta)R_2) &= I_O + (2 I_O) / (\beta(1 + \beta)) & [1] \\ &= I_O [1 + 2 / (\beta(1 + \beta))] & [1] \end{aligned}$$

$$I_{REF} - \frac{V_{BE}}{(1+\beta)R_2} = I_O \left(1 + \frac{2}{\beta(1+\beta)} \right) \quad [1]$$

$$\begin{aligned} \text{(ii)} \quad I_{REF} &= I_O (1 + 2 / (\beta(1 + \beta))) + (V_{BE}) / ((1 + \beta)R_2) & [2] \\ &= (0.70\text{m})(1 + 2 / (80 \times 81)) + (0.7) / (81 \times 10\text{k}) & [2] \\ &= 0.700216\text{m} + 0.000864\text{m} & [1] \\ &= 0.7011 \text{ mA} & [1] \end{aligned}$$

$$\begin{aligned} R_I &= (V^+ - 2V_{BE(\text{on})} - 0) / I_{REF} & [2] \\ &= (10 - 2(0.7)) / (0.7011\text{m}) & [2] \\ &= 12.27 \text{ k}\Omega & [1] \end{aligned}$$

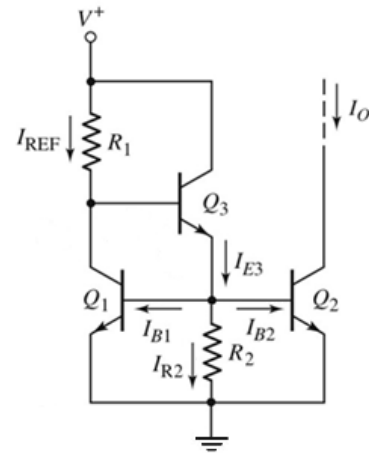


Figure 1(b)

(c) For a MOSFET current source circuit in **Figure 1(c)** the transistor parameters are $V_{TN} = 0.5 \text{ V}$, $k'_n = 80 \mu\text{A}/\text{V}^2$, and $\lambda = 0$. **Design the circuit** such that $V_{DS2}(\text{sat}) = 0.25 \text{ V}$, $I_{REF} = 50 \mu\text{A}$, and the load current is $I_O = 100 \mu\text{A}$.

[10 marks]

Answers for Question 1(c)

$$V_{DS2}(\text{sat}) = V_{GS} - V_{TN} \quad [1]$$

$$\begin{aligned} V_{GS} &= V_{DS2}(\text{sat}) + V_{TN} \\ &= 0.25 + 0.5 = 0.75 \text{ V} \end{aligned} \quad [1]$$

$$I_{REF} = (V^+ - V_{GS} - 0) / R_1 \quad [1]$$

$$\begin{aligned} R_1 &= (V^+ - V_{GS} - 0) / I_{REF} \\ &= (2 - 0.75) / (50\mu) = 25 \text{ k}\Omega \end{aligned} \quad [1]$$

$$I_{REF} = (k'_n / 2) (W/L)_1 [V_{GS} - V_{TN}]^2 \quad [1]$$

$$\begin{aligned} (W/L)_1 &= I_{REF} / \{(k'_n / 2) [V_{GS} - V_{TN}]^2\} \\ &= (50\mu) / \{(80\mu/2) [0.75 - 0.5]^2\} \\ &= 20 \end{aligned} \quad [1]$$

$$I_O = (k'_n / 2) (W/L)_2 [V_{GS} - V_{TN}]^2 \quad [1]$$

$$\begin{aligned} (W/L)_2 &= I_O / \{(k'_n / 2) [V_{GS} - V_{TN}]^2\} \\ &= (100\mu) / \{(80\mu/2) [0.75 - 0.5]^2\} \\ &= 40 \end{aligned} \quad [1]$$

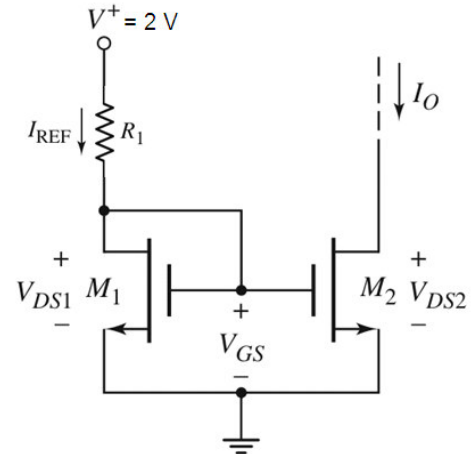


Figure 1(c)

Question 2 [30 marks]

(a) The basic differential pair is shown in **Figure 2(a)**. The circuit parameter values are: $V^+ = 10\text{ V}$, $V^- = -10\text{ V}$ and $I_Q = 1\text{ mA}$. The transistor parameters are $\beta = 100$, $V_{BE(\text{on})} = 0.7\text{ V}$ and $V_{CE(\text{sat})} = 0.2\text{ V}$. Assume that $v_{B1} = v_{B2} = 0\text{ V}$.

- (i) Design the circuit by calculating the value of the maximum possible load, R_C , before the transistors leave the active mode. [8 marks]
- (ii) Using the answer in part (i), find the maximum possible single-ended differential voltage gain (A_d). [3 marks]

Answers for Question 2(a)

(i)

$$R_C = (V^+ - v_{CE(\text{min})}) / i_{C1} \quad [1]$$

$$v_{CE(\text{min})} = v_E + V_{CE(\text{sat})} \quad [1]$$

$$v_E = v_{B1} - V_{BE(\text{on})} = 0 - 0.7 = -0.7\text{ V} \quad [1]$$

$$v_{CE(\text{min})} = v_E + V_{CE(\text{sat})} = (-0.7) + 0.2 = -0.5\text{ V} \quad [1]$$

$$i_{C1} \approx i_{E1} = I_Q / 2 = (1\text{m}) / 2 = 0.5\text{ mA} \quad [1]$$

$$R_C = (V^+ - v_{CE(\text{min})}) / i_{C1} = (10 - (-0.5)) / (0.5\text{m}) = 21\text{ k}\Omega \quad [1]$$

(ii)

$$A_d = (g_m R_C) / 2 \quad [1]$$

$$g_m = (I_{CQ}) / V_T = (i_{C1}) / V_T = (0.5\text{m}) / (26\text{m}) = 19.23\text{ mA/V} \quad [0.5]$$

$$A_d = (g_m R_C) / 2 = (19.23\text{m} \times 21\text{k}) / 2 = 201.9\text{ V/V} \quad [0.5]$$

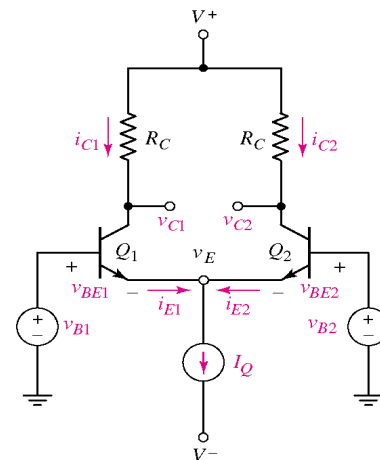



Figure 2(a)

(b) The constant current source of **Figure 2(a)** that is providing the current I_Q is implemented using the cascode current source.

- (i) Sketch the differential pair circuit to include the constant current source circuit [2 marks]
- (ii) Assume that the **Early** voltage, V_A , for all transistors in the circuit is **120 V**. What is the value of the output resistance, R_O , looking into the constant-current source? [2 marks]
- (iii) The common-mode voltage gain, A_{cm} , of the differential-amplifier in **Figure 2(a)** is given as $A_{cm} = \frac{-g_m R_C}{1 + \frac{2(1 + \beta)R_O}{r_\pi + R_B}}$. Find the value of A_{cm} for $R_B = 0$. Use the results obtained previously in part (a) and (b). [2 marks]
- (iv) It is given that the input voltages for the differential amplifier are $v_{B1} = 210 \times 10^{-6} \sin \omega t$ V and $v_{B2} = 190 \times 10^{-6} \sin \omega t$ V. Calculate the output voltage of the differential amplifier. Use values from previous calculations in part (a) and (b). [3 marks]

Answers for Question 2(b)

(i)

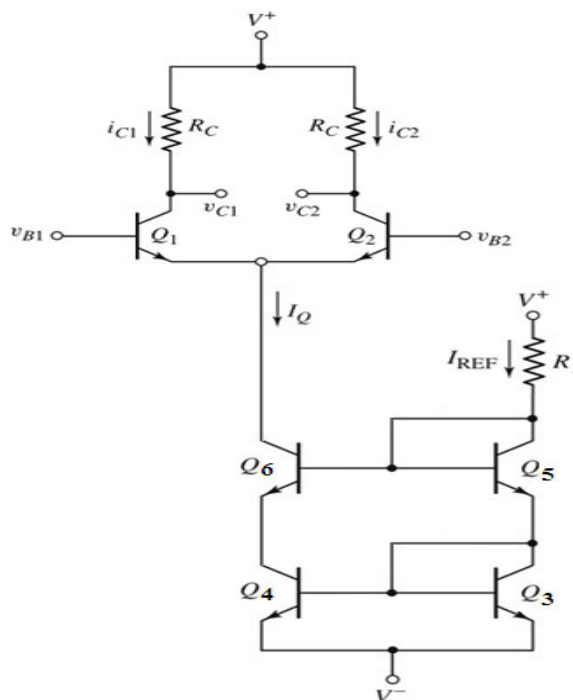

Correct sketch of cascode current source [1]

Correct connection between output of cascode to differential pair [1]

(ii)

$$\beta = 100, I_Q = 1 \text{ mA}$$

For cascode current source

$$R_O = (\beta r_{O6}) \quad [0.5]$$

$$r_{O6} = V_A / I_Q \quad [0.5]$$

$$= (120)/(1\text{m}) = 120 \text{ k}\Omega \quad [0.5]$$

$$R_O = (\beta r_{O6}) = 100 \times 120\text{k} \\ = 12 \text{ M}\Omega \quad [0.5]$$

(iii)

$$g_m = 19.23 \text{ mA/V}, R_C = 21 \text{ k}\Omega, R_B = 0, R_O = 6 \text{ M}\Omega$$

$$r_\pi = (\beta V_T) / i_{C1} \quad [0.5]$$

$$= (100 \times 26\text{m}) / (0.5\text{m})$$

$$= 5.2 \text{ k}\Omega \quad [0.5]$$

Put all values above in the given formula

$$A_{cm} = -[(19.2\text{m})(21\text{k})] / [(1 + 2(1+100)(12\text{M})] / (5.2\text{k}+0) \\ = -0.865\text{m V/V} \quad [1]$$

(iv)

$$A_d = 201.9, A_{cm} = -0.865\text{m V/V}$$

$$V_O = A_d V_d + A_{cm} V_{cm} \quad [1]$$

$$V_d = v_{B1} - v_{B2}$$

$$= 210 \times 10^{-6} \sin \omega t - 190 \times 10^{-6} \sin \omega t$$

$$= 20 \times 10^{-6} \sin \omega t \quad [0.5]$$

$$V_{cm} = (v_{B1} + v_{B2}) / 2$$

$$= 200 \times 10^{-6} \sin \omega t \quad [0.5]$$

$$V_O = (201.9)(20 \times 10^{-6} \sin \omega t) + (-0.865\text{m})(200 \times 10^{-6} \sin \omega t)$$

$$= 4.038 \times 10^{-3} \sin \omega t + (-1.73 \times 10^{-7} \sin \omega t)$$

$$= 4.038 \times 10^{-3} \sin \omega t \text{ V} \quad [1]$$

(c) It is given that the dc transfer characteristic of the differential pair is plotted in **Figure 2(c)**.

- (i) Referring to the basic differential amplifier circuit in **Figure 2(a)**, prove the following I-V relationship which is plotted in **Figure 2(c)**. [6 marks]

$$i_{C1} = \frac{I_Q}{1 + e^{-v_d/V_T}}$$

$$i_{C2} = \frac{I_Q}{1 + e^{+v_d/V_T}}$$

- (ii) What can you conclude by observing the dc transfer characteristic above? [4 marks]

Answers for Question 2(c)

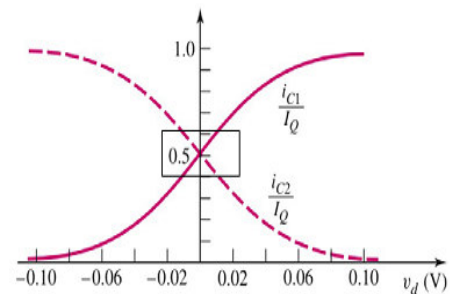


Figure 2(c)

(i)

- **Q1 and Q2 matched:**

$$i_{C1} = I_S e^{v_{BE1}/V_T} \quad \{\text{eqn 1}\} \quad [0.5]$$

and

$$i_{C2} = I_S e^{v_{BE2}/V_T} \quad \{\text{eqn 2}\} \quad [0.5]$$

- **Neglect base currents:** $I_Q = i_{C1} + i_{C2}$ {eqn 3} [1]

- **Replace eqn 1 & 2 into eqn 3:**

$$I_Q = I_S e^{v_{BE1}/V_T} + I_S e^{v_{BE2}/V_T} \quad \{\text{eqn 4}\} \quad [1]$$

- Taking ratios of collector currents to I_Q , i.e eqn1/eqn 4 and eqn2/eqn4:

$$\frac{i_{C1}}{I_Q} = \frac{I_S e^{v_{BE1}/V_T}}{I_S [e^{v_{BE1}/V_T} + e^{v_{BE2}/V_T}]} \quad \text{\{eqn 5\}} \quad \text{\[0.5]}$$

$$\frac{i_{C2}}{I_Q} = \frac{I_S e^{v_{BE2}/V_T}}{I_S [e^{v_{BE1}/V_T} + e^{v_{BE2}/V_T}]} \quad \text{\{eqn 6\}} \quad \text{\[0.5]}$$

- Defining $v_d = v_{BE1} - v_{BE2}$ \{eqn7\} \quad \text{\[1]}
- Simplifying eqn5 & 6 by dividing by e^{v_{BE1}/V_T} and e^{v_{BE2}/V_T} respectively \[0.5]
- Substituting with \{eqn7\} to get final result:

$$i_{C1} = \frac{I_Q}{1 + e^{-v_d/V_T}} \quad i_{C2} = \frac{I_Q}{1 + e^{+v_d/V_T}} \quad \text{\[0.5]}$$

(ii)

Any of the following points, 1 mark for each point:

- if $v_d = 0$, (or $v_{CM} = v_{B1} = v_{B2}$) I_Q splits evenly between Q_1 & Q_2
- if v_d is applied, a difference in collector current exist, causing difference in collector potential
- Gain is proportional to the slopes about the point $v_d = 0$.
- v_d increases beyond the maximum limit: all I_Q goes to one transistor and hence the other transistor turns off.
- To obtain a linear amplifier: excursion of v_d about zero must be small.

Question 3 [30 marks]

(a) Consider the circuit shown in **Figure 3(a)**. The circuit parameters are $\beta = 100$, $V_A = \infty$ for Q_1 and Q_2 , $V_A = 50$ V for Q_3 and Q_4 , $I_S = 10^{-14}$ A, $I_3 = 400 \mu\text{A}$, $v_{O2} = 10$ V, and $A_{cm} = -0.113$. Determine:

- (i) The differential-mode input resistance. [7 marks]
- (ii) The *CMRR*. [3 marks]
- (iii) Draw the ac equivalent circuit of the **differential amplifier part**. Label all the components clearly. [5 marks]

Answers for Question 3(a)

(i)

$$R_{id} = 2(r_{\pi} + R_B) \quad [1]$$

$$R_B = 10 \text{ k}\Omega \quad [1]$$

$$r_{\pi} = (\beta V_T) / I_{CQ} \quad [1]$$

$$= (\beta V_T) / (I_Q / 2) \quad [1]$$

$$= (2\beta V_T) / I_Q \quad [1]$$

$$= (2\beta V_T) / I_3 \quad [1]$$

$$= (2 \times 100 \times 26 \text{ m}) / (400 \mu) = 13 \text{ k}\Omega \quad [1]$$

$$R_{id} = 2(13 \text{ k} + 10 \text{ k}) \quad [1]$$

$$= 46 \text{ k}\Omega \quad [1]$$

(ii)

$$CMRR = |A_d / A_{cm}|$$

$$A_d = (\beta R_c) / (2(r_{\pi} + R_B))$$

$$R_c = (V^+ - v_{O2}) / I_{C2} \quad [0.5]$$

$$= (V^+ - v_{O2}) / (I_3 / 2) \quad [0.5]$$

$$= (15 - 10) / (400 \mu / 2)$$

$$A_d = (\beta R_c) / (2(r_{\pi} + R_B)) \quad [0.5]$$

$$= (100 \times 25 \text{ k}) / (2(13 \text{ k} + 10 \text{ k})) \quad [0.5]$$

$$= 54.34$$

$$CMRR = |A_d / A_{cm}| \quad [0.5]$$

$$= |54.34 / (-0.113)| \quad [0.5]$$

$$= 480.88$$


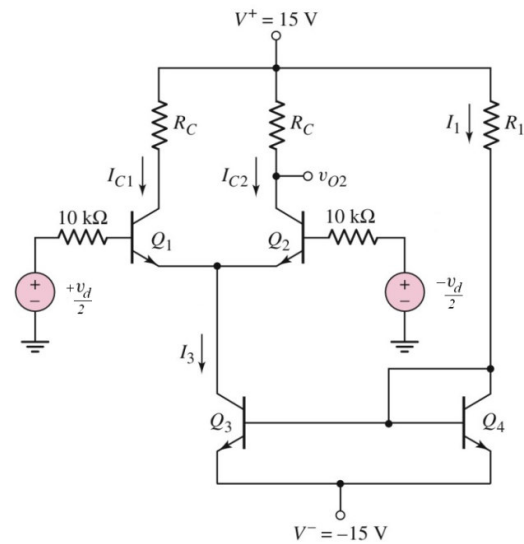


Figure 3(a)

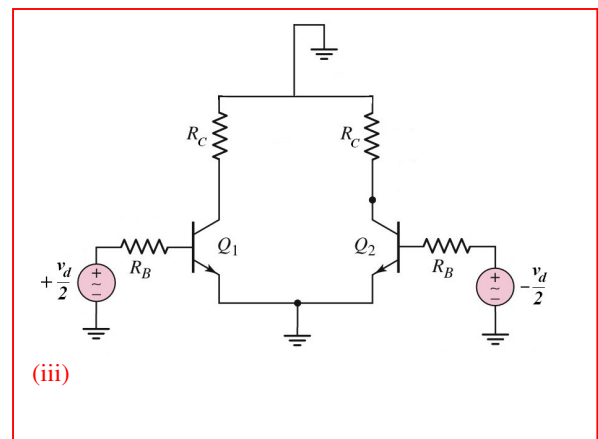

(iii)

Grounds [2], R_C [1], R_B [1], Q [1]

(b) The circuit parameters for the diff-amp shown in **Figure 3(b)** are $V^+ = 3.3 \text{ V}$, $V^- = -3.3 \text{ V}$, and $I_Q = 0.4 \text{ mA}$. The transistor parameters are $\beta = 120$, $V_A = 120 \text{ V}$ for Q_1 and Q_2 , $V_A = 80 \text{ V}$ for Q_3 and Q_4 , and $V_A = \infty$ for Q_5 .

- (i) Determine the output resistance of the diff-amp. [7 marks]
- (ii) Determine the open-circuit differential-mode voltage gain. [5 marks]
- (iii) What is the effect of R_L on the differential-mode voltage gain of the diff-amp? Provide support for your answer. [3 marks]

Answers for Question 3(b)

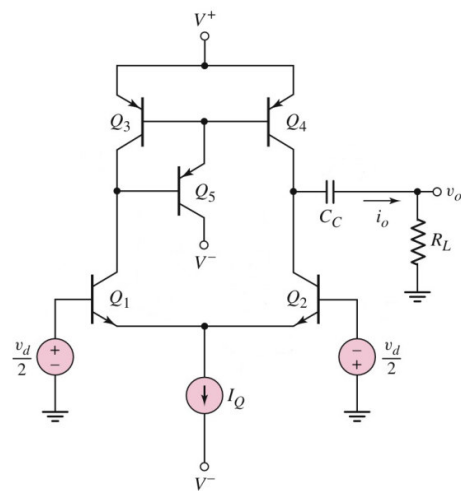


Figure 3(b)

- (i)

$I_{CQ} = I_Q / 2 = (0.4\text{m})/2$	$= 0.2 \text{ mA}$	[1]
$r_{O2} = V_{A2}/I_{CQ} = 120/(0.2\text{m})$	$= 600 \text{ k}\Omega$	[2]
$r_{O4} = V_{A4}/I_{CQ} = 80/(0.2\text{m})$	$= 400 \text{ k}\Omega$	[2]
$R_O = r_{O2} \parallel r_{O4} = 600\text{k} \parallel 400\text{k}$	$= 240\text{k}\Omega$	[2]
- (ii)

$g_m = I_{CQ}/V_T = (0.2\text{m})/(26\text{m})$	$= 7.692 \text{ mA/V}$	[2]
$A_v = g_m(r_{O2} \parallel r_{O4}) = (7.692\text{m})(600\text{k} \parallel 400\text{k})$	$= 1846$	[3]
- (iii) **New $R_O = r_{O2} \parallel r_{O4} \parallel R_L$: $A_v = g_m R_O$ will become smaller. Therefore large value for R_L is required so as not to change the differential-mode voltage gain so much.** [3]