

Question:

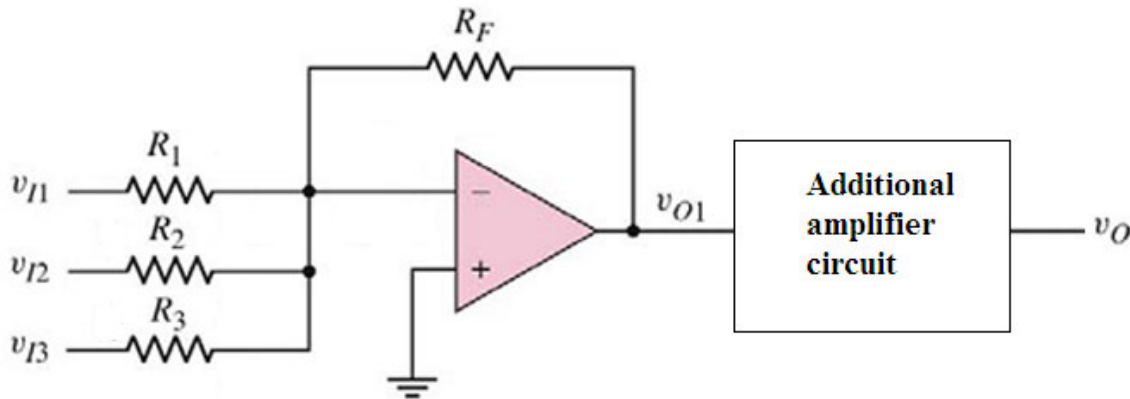


Figure 1

Refer to Figure 1.

- (a) By using the **smallest resistance** in the circuit is **10 kΩ**, **design an ideal inverting summing amplifier** to produce an output voltage of

$$v_{O1} = -2.5(2.4v_{I1} + 0.24v_{I2} + 1.2v_{I3}) \quad \text{--Equation 1--}$$

[8 marks]

Hint: Use the general equation for the ideal inverting summing amplifier.

- (b) **Design an additional amplifier circuit** (using ideal inverting operational amplifier) to be connected to the output of the ideal inverting summing amplifier so that the equation for the output voltage of the **new summing amplifier** can be modified to

$$v_O = +2.5(2.4v_{I1} + 0.24v_{I2} + 1.2v_{I3}) \quad \text{--Equation 2--}$$

[2 marks]

Hint: Note that **negative sign** in **Equation 1** is inverted in order to produce **Equation 2**.

Show clearly all calculations in order to get full marks.

Answer:

(a)

$$\begin{aligned}v_{O1} &= -2.5(2.4v_{I1} + 0.24v_{I2} + 1.2v_{I3}) \\v_{O1} &= (-6v_{I1}) + (-0.6v_{I2}) + (-3v_{I3}) && [1/2] \\&= -(R_F/R_1)v_{I1} + -(R_F/R_2)v_{I2} + -(R_F/R_3)v_{I3} && [1/2]\end{aligned}$$

$$-6v_{I1} = -(R_F/R_1) \quad \rightarrow \quad R_F = 6R_1 \quad [1]$$

$$-0.6v_{I2} = -(R_F/R_2) \quad \rightarrow \quad R_F = 0.6R_2 \quad [1]$$

$$-3v_{I3} = -(R_F/R_3) \quad \rightarrow \quad R_F = 3R_3 \quad [1]$$

Therefore, the smallest resistor is R_1 . So, set $R_1 = 10 \text{ k}\Omega$ [1]

$$R_F = 6R_1 = 60 \text{ k}\Omega \quad [1]$$

$$R_2 = R_F/0.6 = 60\text{k}/0.6 = 100 \text{ k}\Omega \quad [1]$$

$$R_3 = R_F/3 = 60\text{k}/3 = 20 \text{ k}\Omega \quad [1]$$

(b)

To invert the negative sign in Equation 1 to a positive sign, then the voltage gain of the additional amplifier circuit is -1. [1/2]

For the additional amplifier circuit using the inverting operational amplifier, let its feedback resistor as R_5 and its input resistor as R_4 .

$$\text{Then } -1 = -(R_5/R_4) \quad \rightarrow \quad R_5 = R_4 \quad [1/2]$$

$$\text{Let } R_4 = 10 \text{ k}\Omega, \quad \text{then } R_5 = 10 \text{ k}\Omega. \quad [1]$$

Question:

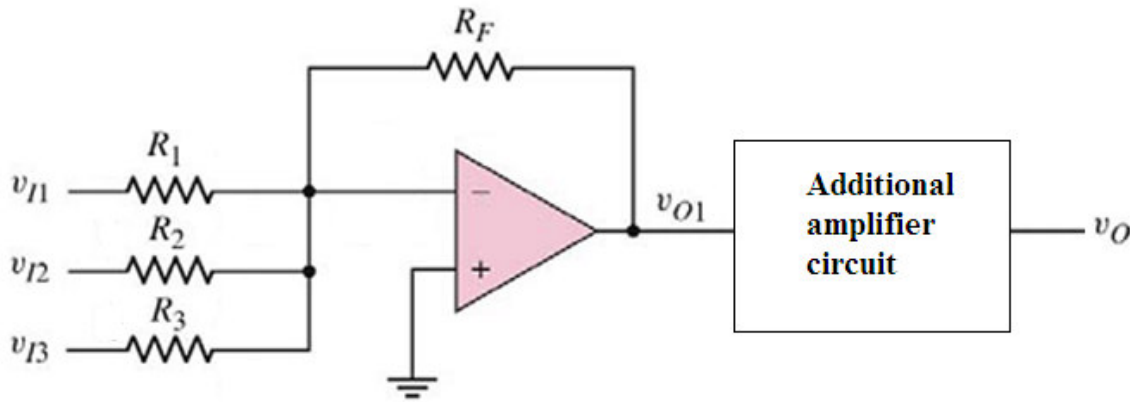


Figure 1

Refer to Figure 1.

- (a) By using the **smallest resistance** in the circuit is **15 kΩ**, **design an ideal inverting summing amplifier** to produce an output voltage of

$$v_{O1} = -2.5(0.24v_{I1} + 1.2v_{I2} + 2.4v_{I3}) \quad \text{--Equation 1--}$$

[8 marks]

Hint: Use the general equation for the ideal inverting summing amplifier.

- (b) **Design an additional amplifier circuit** (using ideal inverting operational amplifier) to be connected to the output of the ideal inverting summing amplifier so that the equation for the output voltage of the **new summing amplifier** can be modified to

$$v_O = +2.5(0.24v_{I1} + 1.2v_{I2} + 2.4v_{I3}) \quad \text{--Equation 2--}$$

[2 marks]

Hint: Note that **negative sign** in **Equation 1** is inverted in order to produce **Equation 2**.

Show clearly all calculations in order to get full marks.

Answer:

(a)

$$\begin{aligned}v_{O1} &= -2.5(0.24v_{I1} + 1.2v_{I2} + 2.4v_{I3}) \\v_{O1} &= (-0.6v_{I1}) + (-3v_{I2}) + (-6v_{I3}) && [1/2] \\&= -(R_F/R_1)v_{I1} + -(R_F/R_2)v_{I2} + -(R_F/R_3)v_{I3} && [1/2]\end{aligned}$$

$$-0.6v_{I1} = -(R_F/R_1) \quad \rightarrow \quad R_F = 0.6R_1 \quad [1]$$

$$-3v_{I2} = -(R_F/R_2) \quad \rightarrow \quad R_F = 3R_2 \quad [1]$$

$$-6v_{I3} = -(R_F/R_3) \quad \rightarrow \quad R_F = 6R_3 \quad [1]$$

Therefore, the smallest resistor is R_3 . So, set $R_3 = 15 \text{ k}\Omega$ [1]

$$R_F = 6R_3 = 90 \text{ k}\Omega \quad [1]$$

$$R_1 = R_F/0.6 = 90\text{k}/0.6 = 150 \text{ k}\Omega \quad [1]$$

$$R_2 = R_F/3 = 90\text{k}/3 = 30 \text{ k}\Omega \quad [1]$$

(b)

To invert the negative sign in Equation 1 to a positive sign, then the voltage gain of the additional amplifier circuit is -1. [1/2]

For the additional amplifier circuit using the inverting operational amplifier, let its feedback resistor as R_5 and its input resistor as R_4 .

$$\text{Then } -1 = -(R_5/R_4) \quad \rightarrow \quad R_5 = R_4 \quad [1/2]$$

$$\text{Let } R_4 = 15 \text{ k}\Omega, \text{ then } R_5 = 15 \text{ k}\Omega. \quad [1]$$

Question:

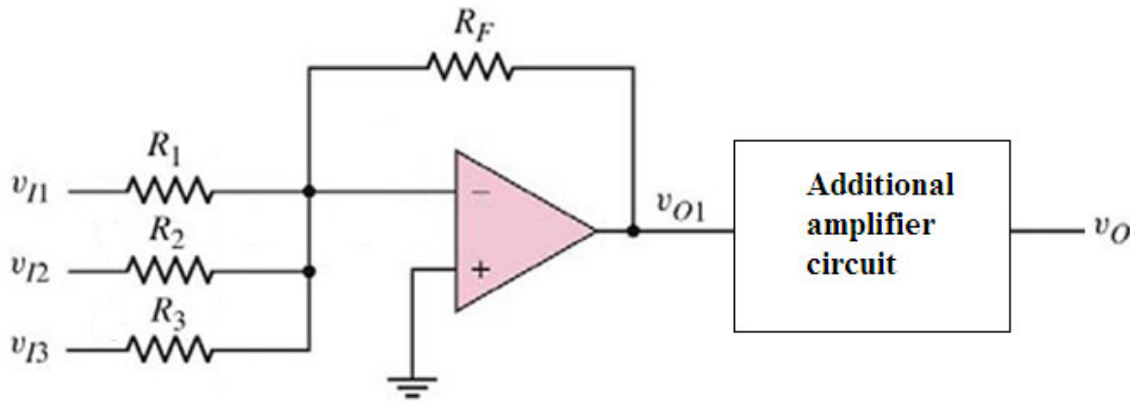


Figure 1

Refer to Figure 1.

- (a) By using the **smallest resistance** in the circuit is **12 kΩ**, **design an ideal inverting summing amplifier** to produce an output voltage of

$$v_{O1} = -2.5(1.2v_{I1} + 0.24v_{I2} + 2.4v_{I3}) \quad \text{--Equation 1--}$$

[8 marks]

Hint: Use the general equation for the ideal inverting summing amplifier.

- (b) **Design an additional amplifier circuit** (using ideal inverting operational amplifier) to be connected to the output of the ideal inverting summing amplifier so that the equation for the output voltage of the **new summing amplifier** can be modified to

$$v_O = +2.5(1.2v_{I1} + 0.24v_{I2} + 2.4v_{I3}) \quad \text{--Equation 2--}$$

[2 marks]

Hint: Note that **negative sign** in **Equation 1** is inverted in order to produce **Equation 2**.

Show clearly all calculations in order to get full marks.

Answer:

(a)

$$\begin{aligned}v_{O1} &= -2.5(1.2v_{I1} + 0.24v_{I2} + 2.4v_{I3}) \\v_{O1} &= (-3v_{I1}) + (-0.6v_{I2}) + (-6v_{I3}) && [1/2] \\&= -(R_F/R_1)v_{I1} + -(R_F/R_2)v_{I2} + -(R_F/R_3)v_{I3} && [1/2]\end{aligned}$$

$$-3v_{I1} = -(R_F/R_1) \quad \rightarrow \quad R_F = 3R_1 \quad [1]$$

$$-0.6v_{I2} = -(R_F/R_2) \quad \rightarrow \quad R_F = 0.6R_2 \quad [1]$$

$$-6v_{I3} = -(R_F/R_3) \quad \rightarrow \quad R_F = 6R_3 \quad [1]$$

Therefore, the smallest resistor is R_3 . So, set $R_3 = 12 \text{ k}\Omega$ [1]

$$R_F = 6R_3 = 72 \text{ k}\Omega \quad [1]$$

$$R_1 = R_F/3 = 72\text{k}/3 = 24 \text{ k}\Omega \quad [1]$$

$$R_2 = R_F/0.6 = 72\text{k}/0.6 = 120 \text{ k}\Omega \quad [1]$$

(b)

To invert the negative sign in Equation 1 to a positive sign, then the voltage gain of the additional amplifier circuit is -1. [1/2]

For the additional amplifier circuit using the inverting operational amplifier, let its feedback resistor as R_5 and its input resistor as R_4 .

$$\text{Then } -1 = -(R_5/R_4) \quad \rightarrow \quad R_5 = R_4 \quad [1/2]$$

$$\text{Let } R_4 = 12 \text{ k}\Omega, \text{ then } R_5 = 12 \text{ k}\Omega. \quad [1]$$

Question:

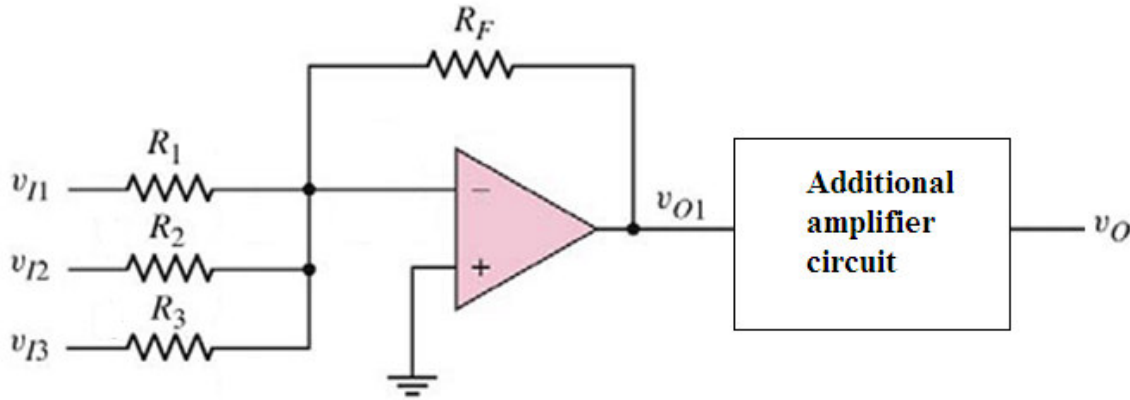


Figure 1

Refer to Figure 1.

- (a) By using the **smallest resistance** in the circuit is **18 kΩ**, **design an ideal inverting summing amplifier** to produce an output voltage of

$$v_{O1} = -2.5(0.24v_{I1} + 1.2v_{I2} + 2.4v_{I3}) \quad \text{--Equation 1--}$$

[8 marks]

Hint: Use the general equation for the ideal inverting summing amplifier.

- (b) **Design an additional amplifier circuit** (using ideal inverting operational amplifier) to be connected to the output of the ideal inverting summing amplifier so that the equation for the output voltage of the **new summing amplifier** can be modified to

$$v_O = +2.5(0.24v_{I1} + 1.2v_{I2} + 2.4v_{I3}) \quad \text{--Equation 2--}$$

[2 marks]

Hint: Note that **negative sign** in **Equation 1** is inverted in order to produce **Equation 2**.

Show clearly all calculations in order to get full marks.

Answer:

(a)

$$\begin{aligned}v_{O1} &= -2.5(0.24v_{I1} + 1.2v_{I2} + 2.4v_{I3}) \\v_{O1} &= (-0.6v_{I1}) + (-3v_{I2}) + (-6v_{I3}) & [1/2] \\ &= -(R_F/R_1)v_{I1} + -(R_F/R_2)v_{I2} + -(R_F/R_1)v_{I3} & [1/2]\end{aligned}$$

$$-0.6v_{I1} = -(R_F/R_1) \quad \rightarrow \quad R_F = 0.6R_1 \quad [1]$$

$$-3v_{I2} = -(R_F/R_2) \quad \rightarrow \quad R_F = 3R_2 \quad [1]$$

$$-6v_{I3} = -(R_F/R_3) \quad \rightarrow \quad R_F = 6R_3 \quad [1]$$

Therefore, the smallest resistor is R_3 . So, set $R_3 = 18 \text{ k}\Omega$ [1]

$$R_F = 6R_3 = 108 \text{ k}\Omega \quad [1]$$

$$R_1 = R_F/0.6 = 108\text{k}/0.6 = 180 \text{ k}\Omega \quad [1]$$

$$R_2 = R_F/3 = 108\text{k}/3 = 36 \text{ k}\Omega \quad [1]$$

(b)

To invert the negative sign in Equation 1 to a positive sign, then the voltage gain of the additional amplifier circuit is -1. [1/2]

For the additional amplifier circuit using the inverting operational amplifier, let its feedback resistor as R_5 and its input resistor as R_4 .

$$\text{Then } -1 = -(R_5/R_4) \quad \rightarrow \quad R_5 = R_4 \quad [1/2]$$

$$\text{Let } R_4 = 18 \text{ k}\Omega, \text{ then } R_5 = 18 \text{ k}\Omega. \quad [1]$$