

Name: **MODEL ANSWERS**

Student ID Number:

Section: 01A/01B/02A/02B

Lecturer: Dr Jamaludin/Dr Azni Wati



College of Engineering
Department of Electronics and Communication Engineering

Midterm Test
SEMESTER 2, ACADEMIC YEAR 2011/2012

Subject Code : **EEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **14 November 2011**
Time Allowed : **2 hours (8 – 10 PM)**

Instructions to the candidates:

1. Write your Name and Student ID number. Circle your section number.
2. Write all your answers using pen. **DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.

☺ **GOOD LUCK!** ☺

Question No.									
Marks									

Question 1 [40 marks]

(a) For all **BJT current sources** given in **Table 1**, all transistors are matched and have same parameters. The transistor parameters are: $\beta = 50$, $V_{BE(on)} = 0.6 \text{ V}$, and $V_A = 120 \text{ V}$. The circuit parameters are: $V^+ = 10 \text{ V}$, $V^- = -10 \text{ V}$, and $R_1 = 18 \text{ k}\Omega$.

(i) **Calculate** reference current (I_{REF}), output current (I_O), and output resistance (R_O) for every BJT current source given in the **Table 1** and fill in the **Table 1** with your answers. **Show all calculations** in the area provided after the **Table 1** and **do not forget** to put proper **Units** for I_{REF} , I_O , and R_O in the **Table 1**.

Table 1

BJT current source	Reference current, I_{REF}	Output current, I_O	Output resistance, R_O
Three-transistor current source	1.044 mA	1.044 mA	114.98 kΩ
Wilson current source	1.044 mA	1.044 mA	2.847 MΩ
Cascode current source	1.044 mA	0.967 mA	6.204 MΩ

[0.5 mark each]

[4.5 marks]

(ii) Based on the value of R_O , **which current source** has the most stable I_O ?

[2 marks]

Cascode [2]

Show all your calculations for I_{REF} , I_O , and R_O for every BJT current source given in the **Table 1** in the following space:

[13.5 marks]

Three-transistor current source	Wilson current source	Cascode current source
$I_{REF} = (V^+ - 2V_{BE} - V^-) / R_1 = (10 - 2 \times 0.6 - (-10)) / (18\text{k}) = 1.044 \text{ mA}$ -- same for all CS		
$I_O = I_{REF} / (1 + 2/(\beta(1+\beta)))$ = $(1.044\text{m}) / (1 + 2/(50 \times 51))$ = 1.044 mA	$I_O = I_{REF} / (1 + 2/(\beta(2+\beta)))$ = $(1.044\text{m}) / (1 + 2/(50 \times 52))$ = 1.044 mA	$I_O = I_{REF} / (1 + 4/\beta)$ = $(1.044\text{m}) / (1 + 4/(50))$ = 0.967 mA
$r_{O2} = V_A / I_O$ = $120 / (1.044\text{m})$ = 114.98 k Ω	$r_{O3} = V_A / I_O$ = $120 / (1.044\text{m})$ = 114.98 k Ω	$r_{O4} = V_A / I_O$ = $120 / (1.278\text{m})$ = 124.08 k Ω
$R_O = r_{O2}$ = 114.98 k Ω	$R_O = (\beta r_{O3}) / 2$ = $(50 \times 114.98\text{k}) / 2$ = 2.847 M Ω	$R_O = \beta r_{O4}$ = $50 \times 117.391\text{k}$ = 6.204 M Ω

[1.5 mark each]

- (b) Consider the MOSFET current source circuit shown in Figure 1 for the following questions. The circuit parameters are $V^+ = 10\text{ V}$, $V^- = -10\text{ V}$, $I_O = 0.25\text{ mA}$, and the transistor parameters are: $V_{TN} = 1.5\text{ V}$, $V_{DS2}(\text{sat}) = 2.5\text{ V}$, $k'_{n1} = k'_{n2} = 40\text{ }\mu\text{A/V}^2$, $k'_{n3} = 20\text{ }\mu\text{A/V}^2$ and $\lambda = 0$.

(i) Determine the voltages V_{GS1} and V_{GS3} , and the current I_{REF} .

[8 marks]

$$V_{DS2}(\text{sat}) = V_{GS2} - V_{TN}$$

$$V_{GS2} = V_{DS2}(\text{sat}) + V_{TN} = 2.5 + 1.5 = 4\text{ V}$$

$$V_{GS1} = V_{GS2} = 4\text{ V} \quad [2]$$

$$V_{GS3} = V^+ - V_{GS1} - V^- = 10 - 4 + 10 = 16\text{ V} \quad [2]$$

Since $k'_{n1} = k'_{n2}$ and $V_{GS1} = V_{GS2}$

Assume $(W/L)_1 = (W/L)_2$

Then $I_{REF} = I_O = 0.25\text{ mA} \quad [4]$

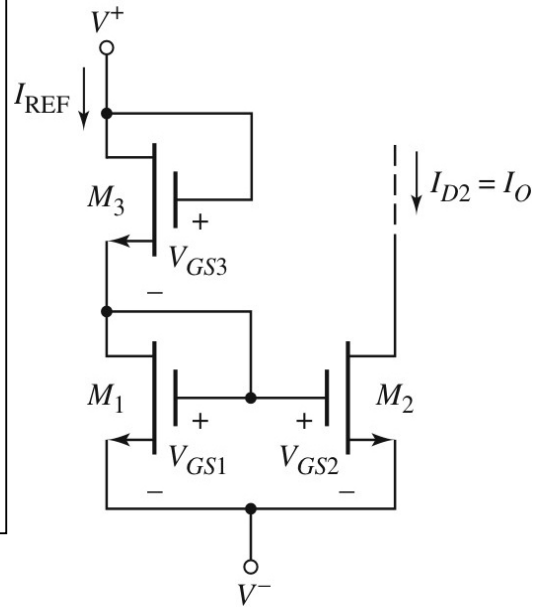


Figure 1

(ii) Calculate the width-to-length ratio of M_3 , i.e. $(W/L)_3$.

[4 marks]

$$I_{REF} = (k'_{n3}/2)(W/L)_3[V_{GS3} - V_{TN}]^2$$

$$(W/L)_3 = I_{REF} / \{(k'_{n3}/2)[V_{GS3} - V_{TN}]^2\} = 0.25\text{m} / \{(20\mu/2)(16-1.5)^2\} = 0.1189 \quad [3]$$

$$= 0.1189 \quad [1]$$

- (iii) If $\lambda = 0.01 \text{ V}^{-1}$, what is the change in output current (I_O) as the output voltage at V_{D2} has changed by 9 V ?

[4 marks]

$$R_O = r_{O2} = 1/(\lambda I_O) = 1/(0.01 \times 0.25 \text{ mA}) = 400 \text{ k}\Omega \quad [2]$$

$$R_O = \Delta V_{D2} / \Delta I_O$$

$$\Delta I_O = \Delta V_{D2} / R_O = 9 / 400 \text{ k} = 0.0225 \text{ mA} = 22.5 \text{ }\mu\text{A} \quad [2]$$

- (iv) **Suggest** a suitable **circuit** to stabilize the output current against variations in the output voltage of the MOSFET current source.

[4 marks]

Use other MOSFET current source circuits with higher R_O , such as cascode CS and modified Wilson CS.

Answer in drawing of cascode CS and modified Wilson CS also can be accepted.

[4] for any answer above.

Question 2 [30 marks]

The BJT differential amplifier as shown in Figure 2 has these following parameters: $V^+ = 10\text{ V}$, $V^- = -10\text{ V}$, $R_1 = 30\text{ k}\Omega$, $\beta = 100$, $V_{CE1} = V_{CE2} = 6\text{ V}$, $A_{cm} = 0.5$, and $V_T = 26\text{ mV}$. The Early voltages are $V_A = 100\text{ V}$ for Q_1 and Q_2 , and $V_A = 80\text{ V}$ for Q_3 and Q_4 . Use $V_{BE(\text{on})} = 0.6\text{ V}$.

(a) Determine the currents I_1 and I_{C2} of the transistors for $v_1 = v_2 = 0\text{ V}$.

[8 marks]

$$I_1 = (V^+ - V_{BE(\text{on})} - V^-) / R_1 = (10 - 0.6 - (-10)) / (30\text{k}) = 0.647\text{ mA} \quad [4]$$

$$I_{C2} = I_{C4} / 2 = [I_1 / (1 + 2/\beta)] / 2 = [0.647\text{m} / (1 + 2/100)] / 2 = 0.3171\text{ mA} \quad [4]$$

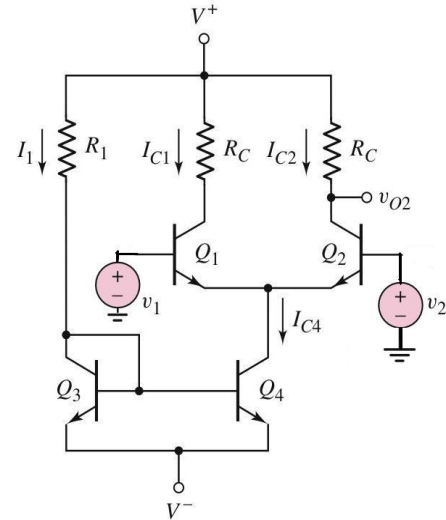


Figure 2

(b) Determine the values of R_C , r_{o4} , r_{o2} .

[9 marks]

$$\begin{aligned} R_C &= (V^+ - V_{C2}) / I_{C2} = (10 - 5.4) / 0.3171\text{m} = 13.876\text{ k}\Omega \quad [3] \\ V_{C2} &= (V_{CE2} + V_{E2}) = 6 + (-0.6) = 5.4\text{ V} \\ V_{E2} &= (V_{B2} - V_{BE2}) = (v_2 - V_{BE2}) = 0 - 0.6 = -0.6\text{ V} \end{aligned}$$

$$r_{o4} = V_{A4} / I_{C4} = 80 / 0.647\text{m} = 123.64\text{ k}\Omega \quad [3]$$

$$r_{o2} = V_{A2} / I_{C2} = 100 / 0.3171\text{m} = 315.36\text{ k}\Omega \quad [3]$$

(c) **Determine** the differential mode voltage gain (A_d) and **CMRR** for a **two-sided output**. [8 marks]

$$A_d = g_{m2} R_C = (12.196 \text{ m})(13.876 \text{ k}) = 169.23 \quad [3]$$

$$g_{m2} = I_{C2} / V_T = 0.3171 \text{ mA} / 26 \text{ mV} = 12.196 \text{ mA/V} \quad [2]$$

$$CMRR = |A_d / A_{cm}| = 176.89 / 0.5 = 353.78 \quad [3]$$

(d) **What is the impact** of including an emitter resistor R_E for Q_1 and Q_2 on the differential mode voltage gain (A_d)? **Write down** the equation of the differential mode voltage gain when emitter resistor R_E for Q_1 and Q_2 are included in the circuit. [5 marks]

$$A_d \quad \text{is reduced.} \quad [2]$$

$$\text{Original: } A_d = (\beta R_C) / 2[r_\pi]$$


$$\text{With } R_E: A_d = (\beta R_C) / 2[r_\pi + (1 + \beta) R_E] \quad [3]$$

Question 3 [30 marks]

With aid of circuit diagram, **design a MOSFET differential amplifier with cascode current source** to establish the desired bias current $I_Q = 0.58 \text{ mA}$. The supply voltages for the overall circuit are $V^+ = 10 \text{ V}$ and $V^- = -10 \text{ V}$. The transistor parameters for the MOSFET differential amplifier pair are $k'_n = 80 \mu\text{A}/\text{V}^2$ and for the current source pair are $k'_n = 40 \mu\text{A}/\text{V}^2$. For all transistors assume $\lambda = 0.02 \text{ V}^{-1}$ and $V_{TN} = 1 \text{ V}$. Consider a **one-sided output** with $V_{DS2}(\text{sat}) = 0.8 \text{ V}$ and a differential-mode voltage gain of $A_d = 10$.

(a) **Draw the designed circuit. Label the circuit clearly.**

[7 marks]

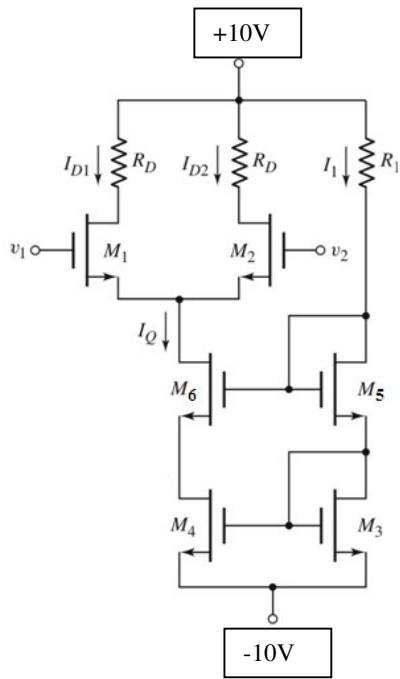

Diff-amp pair	[1]
RD pair	[1]
NMOS for diff-amp and CS	[1]
IQ	[1]
Output	[1]
Cascode CS	[1]
Supplies	[1]

(b) **Determine the (W/L) ratio for transistors in the differential amplifier pair.**

[8 marks]

$$\begin{aligned}
 (W/L)_{1,2} &= (2I_{D1})/[k'_n(V_{GS1}-V_{TN})^2] && [2] \\
 &= (I_Q)/[k'_n(V_{DS2}(\text{sat}))^2] && [3] \\
 &= (0.58\text{m})/[(80\mu)(0.8)^2] && [2] \\
 &= 11.33 && [1]
 \end{aligned}$$

(c) Determine the drain resistance (R_D) in the differential amplifier.

[6 marks]

$$A_d = (g_{m2} R_D)/2$$

$$R_D = (2 A_d) / g_{m2} \quad [2]$$

$$g_{m2} = 2[\sqrt{(K_n I_D)}] = (I_Q)/(V_{DS2}(\text{sat})) = 0.725 \text{ mA/V} \quad [2]$$

$$R_D = (2 A_d) / g_{m2} = (2 \times 10) / (0.725 \text{ mA}) = 27.58 \text{ k}\Omega \quad [2]$$

(d) Draw the output voltage of the differential amplifier when a differential-mode input voltage of $v_d = 0.2 \sin \omega t$ V is applied.


[4 marks]

$$v_O = A_d v_d = (10)(0.2 \sin \omega t) \text{ V or } 2 \sin \omega t \text{ V} \quad [1]$$

Amplitude [1]

Shape [1]

Axis [1]

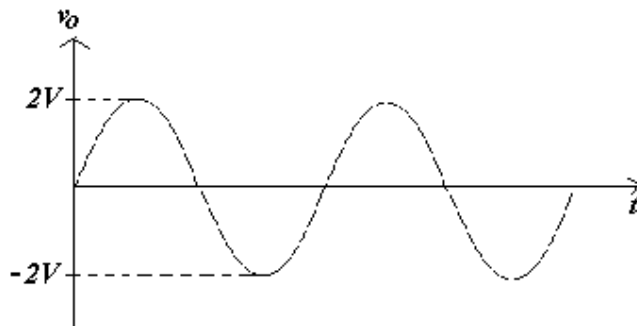

- (e) With reference to your designed circuit in **part (a)** above, and using a **P-MOSFET cascode** current source as an **active load** to replace the drain resistances (R_D) in the differential amplifier, as shown in **Figure 3**, calculate the differential-mode voltage gain (A_d) of the new circuit for a **one-sided output**. For all **P-MOSFET** transistors M_{11} to M_{14} , assume $\lambda = 0.02 \text{ V}^{-1}$ and $V_{TP} = -1 \text{ V}$. R_O in the **Figure 3** can be calculated using $R_O \approx g_m r_{o12} r_{o14}$

[5 marks]

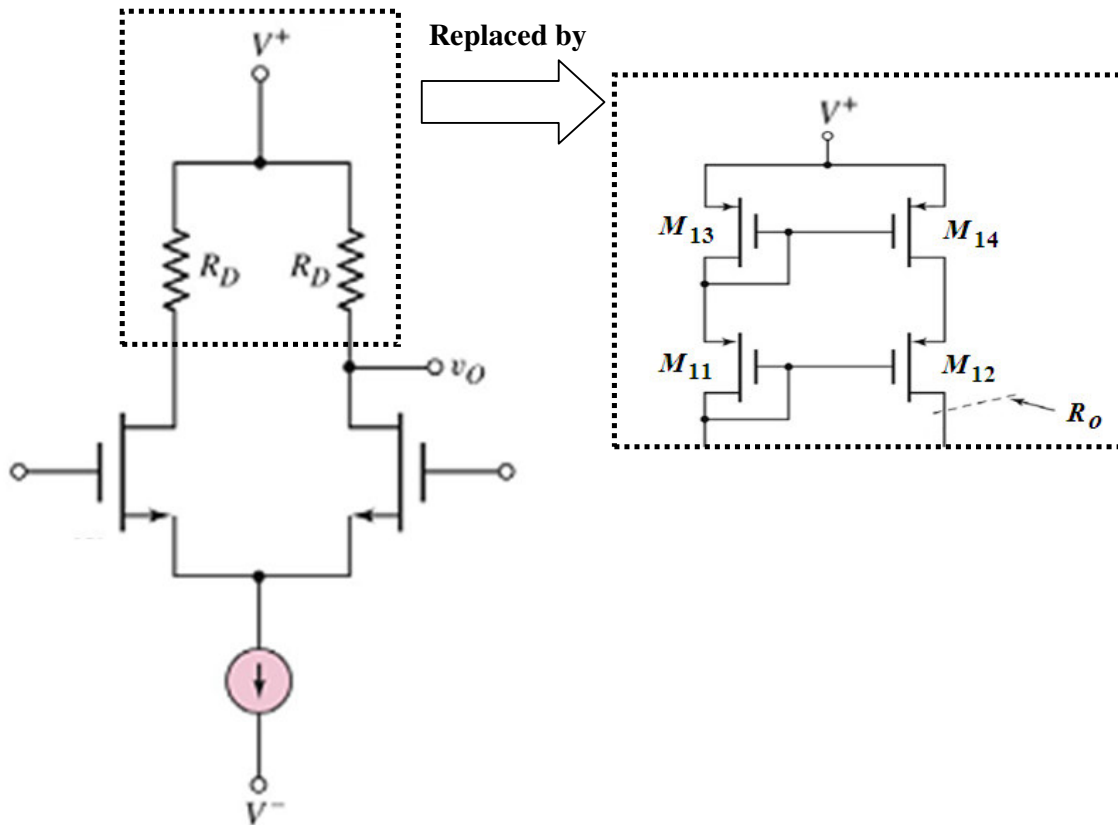


Figure 3

$$r_{o2} = 1/(\lambda_{D2}) = 1/[(0.02)(0.29\text{m})] = 172.4 \text{ k}\Omega \quad [1]$$

$$r_{o12} = r_{o14} = r_{o2} = 172.4\text{k} \quad [1]$$

$$g_m = 2[\sqrt{(K_n I_D)}] = (I_Q)/[V_{DS2}(\text{sat})] = 0.725 \text{ mA/V}$$

$$R_o = (0.725\text{m})(172.4\text{k})(172.4\text{k}) = 21.548 \text{ M}\Omega \quad [1]$$

$$R_{\text{out}} = r_{o2} \parallel R_o \approx r_{o2} = 172.4 \text{ k}\Omega \quad [1]$$

$$A_d = g_m R_{\text{out}} = (0.725\text{m})(172.4\text{k}\Omega) = 124.99 \quad [1]$$

-End of Questions-