

EEEE273 - Quiz 3 [Question Set 1]
 SEMESTER 2, ACADEMIC YEAR 2011/2012
 Date: 2 November 2011

Question:

Refer to **Figure 1**. Assume $\beta = 200$ and $V_{BE(on)} = 0.7 \text{ V}$ for all BJTs in the circuit. For $R_1 = 12.8 \text{ k}\Omega$ and $R_C = 12 \text{ k}\Omega$, find the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output**. [10 marks]

Answer:

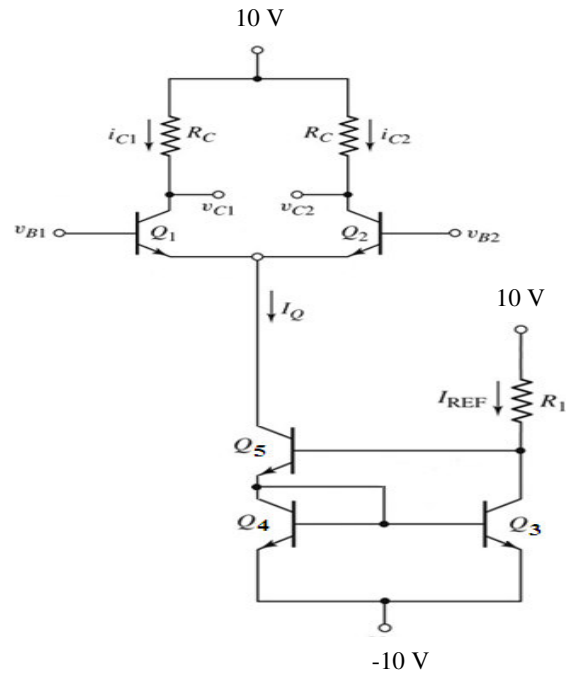


Figure 1

$$I_{REF} = (V^+ - V_{BE5} - V_{BE3} - V^-) / (R_1) \approx I_Q \quad (\beta = 200) \quad [2 \text{ marks}]$$

$$= (10 - 0.7 - 0.7 - (-10)) / (12.8\text{k}) = 1.453 \text{ mA} \quad [2 \text{ marks}]$$

$$A_d = (g_m R_C) / 2 \quad [2 \text{ marks}]$$

$$g_m = I_Q / (2V_T) = (1.453\text{m}) / (2 \times 26\text{m}) = 27.944 \text{ mA/V} \quad [2 \text{ marks}]$$

$$A_d = (27.944\text{m})(12\text{k}) / (2) = 167.7 \quad [2 \text{ marks}]$$

EEEE273 - Quiz 3 [Question Set 2]
 SEMESTER 2, ACADEMIC YEAR 2011/2012
 Date: 2 November 2011

Question:

Refer to **Figure 1**. Assume $\beta = 200$ and $V_{BE(on)} = 0.7$ V for all BJTs in the circuit. For $R_1 = 12$ k Ω and $R_C = 10$ k Ω , find the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output**. [10 marks]

Answer:

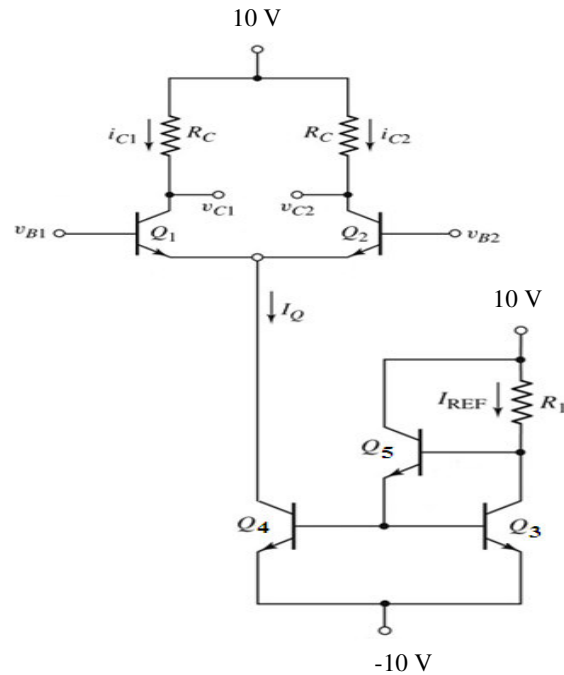


Figure 1

$$I_{REF} = (V^+ - V_{BE5} - V_{BE3} - V^-) / (R_1) \approx I_Q \quad (\beta = 200) \quad [2 \text{ marks}]$$

$$= (10 - 0.7 - 0.7 - (-10)) / (12k) = 1.55 \text{ mA} \quad [2 \text{ marks}]$$

$$A_d = (g_m R_C) / 2 \quad [2 \text{ marks}]$$

$$g_m = I_Q / (2V_T) = (1.55m) / (2 \times 26m) = 29.807 \text{ mA/V} \quad [2 \text{ marks}]$$

$$A_d = (29.807m)(10k) / (2) = 149.0 \quad [2 \text{ marks}]$$

EEEE273 - Quiz 3 [Question Set 3]
 SEMESTER 2, ACADEMIC YEAR 2011/2012
 Date: 2 November 2011

Question:

Refer to **Figure 1**. Assume $\beta = 200$ and $V_{BE(on)} = 0.7$ V for all BJTs in the circuit. For $R_1 = 10$ k Ω and $R_C = 14$ k Ω , find the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output**. [10 marks]

Answer:

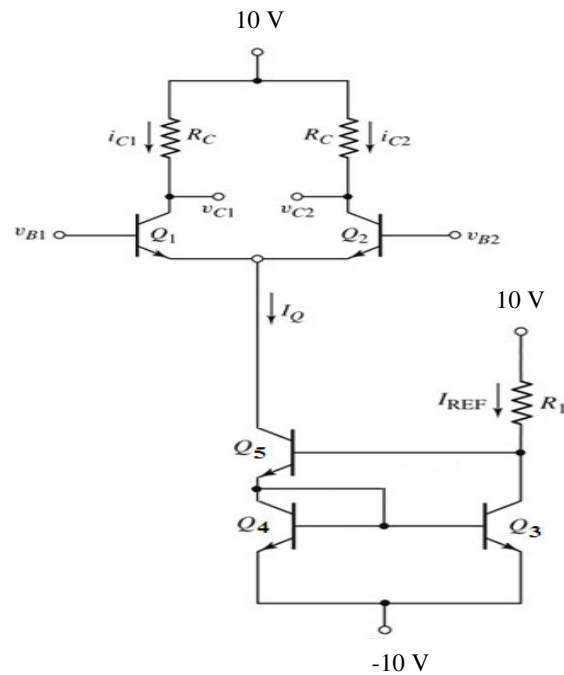


Figure 1

$$I_{REF} = (V^+ - V_{BE5} - V_{BE3} - V^-) / (R_1) \approx I_Q \quad (\beta = 200) \quad [2 \text{ marks}]$$

$$= (10 - 0.7 - 0.7 - (-10)) / (10k) = 1.86 \text{ mA} \quad [2 \text{ marks}]$$

$$A_d = (g_m R_C) / 2 \quad [2 \text{ marks}]$$

$$g_m = I_Q / (2V_T) = (1.86m) / (2 \times 26m) = 35.769 \text{ mA/V} \quad [2 \text{ marks}]$$

$$A_d = (35.769m)(14k) / (2) = 250.4 \quad [2 \text{ marks}]$$

EEEE273 - Quiz 3 [Question Set 4]
 SEMESTER 2, ACADEMIC YEAR 2011/2012
 Date: 2 November 2011

Question:

Refer to **Figure 1**. Assume $\beta = 200$ and $V_{BE(on)} = 0.7 \text{ V}$ for all BJTs in the circuit. For $R_1 = 10 \text{ k}\Omega$ and $R_C = 12 \text{ k}\Omega$, find the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output**. [10 marks]

Answer:

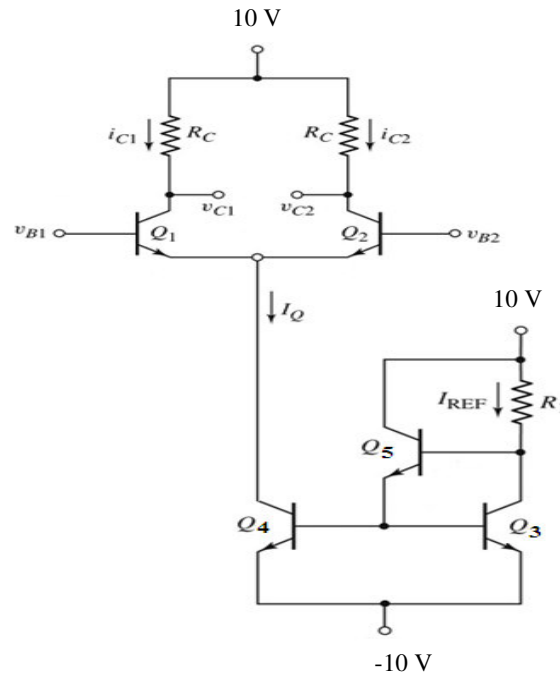


Figure 1

$$I_{REF} = (V^+ - V_{BE5} - V_{BE3} - V^-) / (R_1) \approx I_Q \quad (\beta = 200) \quad [2 \text{ marks}]$$

$$= (10 - 0.7 - 0.7 - (-10)) / (10\text{k}) = 1.86 \text{ mA} \quad [2 \text{ marks}]$$

$$A_d = (g_m R_C) / 2 \quad [2 \text{ marks}]$$

$$g_m = I_Q / (2V_T) = (1.86\text{m}) / (2 \times 26\text{m}) = 35.769 \text{ mA/V} \quad [2 \text{ marks}]$$

$$A_d = (35.769\text{m})(12\text{k}) / (2) = 214.6 \quad [2 \text{ marks}]$$