

Question:

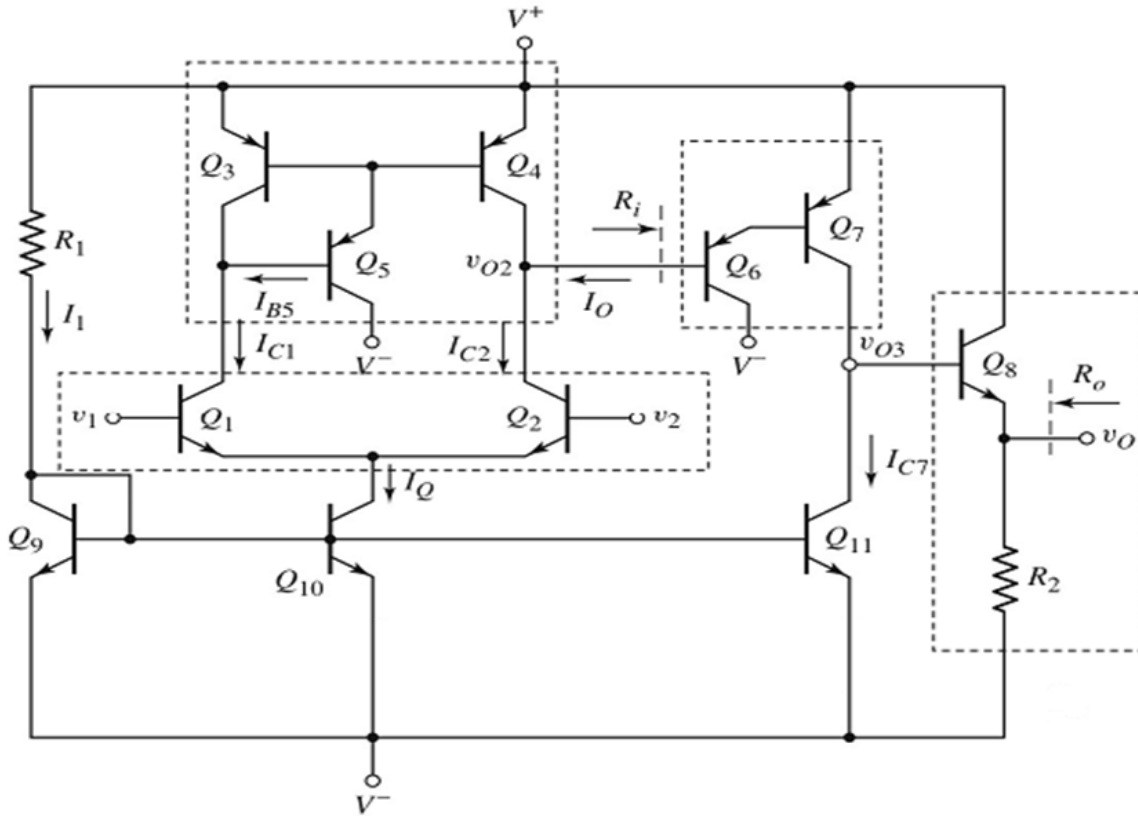


Figure 1

Consider the circuit shown in **Figure 1**, with parameters $I_{C7} = I_Q = 0.2 \text{ mA}$, $I_{C8} = 1 \text{ mA}$, and $R_2 = 12 \text{ k}\Omega$. Study the figure carefully. Note that biasing for amplifiers in the circuit is provided by *two-transistor current mirrors*. Assume that $\beta = 120$ for all transistors, and the **Early voltage** for Q_{11} is **100 V**.

- (i) Calculate the input resistance (R_i) of the **Darlington pair**. [5 marks]
- (ii) Calculate the output resistance (R_o) of the **Emitter follower**. [5 marks]

Answer:

$$R_i = [2 (1+\beta) \beta V_T] / I_Q \quad [3]$$

$$\rightarrow R_i = [2 (1+120)(120)(0.026)] / (0.2\text{m}) = 3.7752 \text{ M}\Omega \quad [2]$$

$$R_o = R_2 \parallel \{[r_{\pi 8} + (R_{c11} \parallel R_{c7})]/(1+\beta)\} \quad [1]$$

$$R_{c11} = r_{o11} = V_{A11} / I_{c11} = V_{A11} / I_Q = 100/0.2\text{m} = 500 \text{ k}\Omega \quad [1]$$

$$R_{c7} = r_{o7} = V_{A7} / I_{c7} = V_{A7} / I_Q = 100/0.2\text{m} = 500 \text{ k}\Omega \quad [1]$$

$$r_{\pi 8} = \beta V_T / I_{C8} = (120)(0.026)/(1\text{m}) = 3.12 \text{ k}\Omega \quad [1]$$

$$\rightarrow R_o = (12\text{k}) \parallel \{[3.12\text{k} + (500\text{k} \parallel 500\text{k})]/(1+120)\} = (12\text{k}) \parallel (2.09\text{k}) = 1.78 \text{ k}\Omega \quad [1]$$

Question:

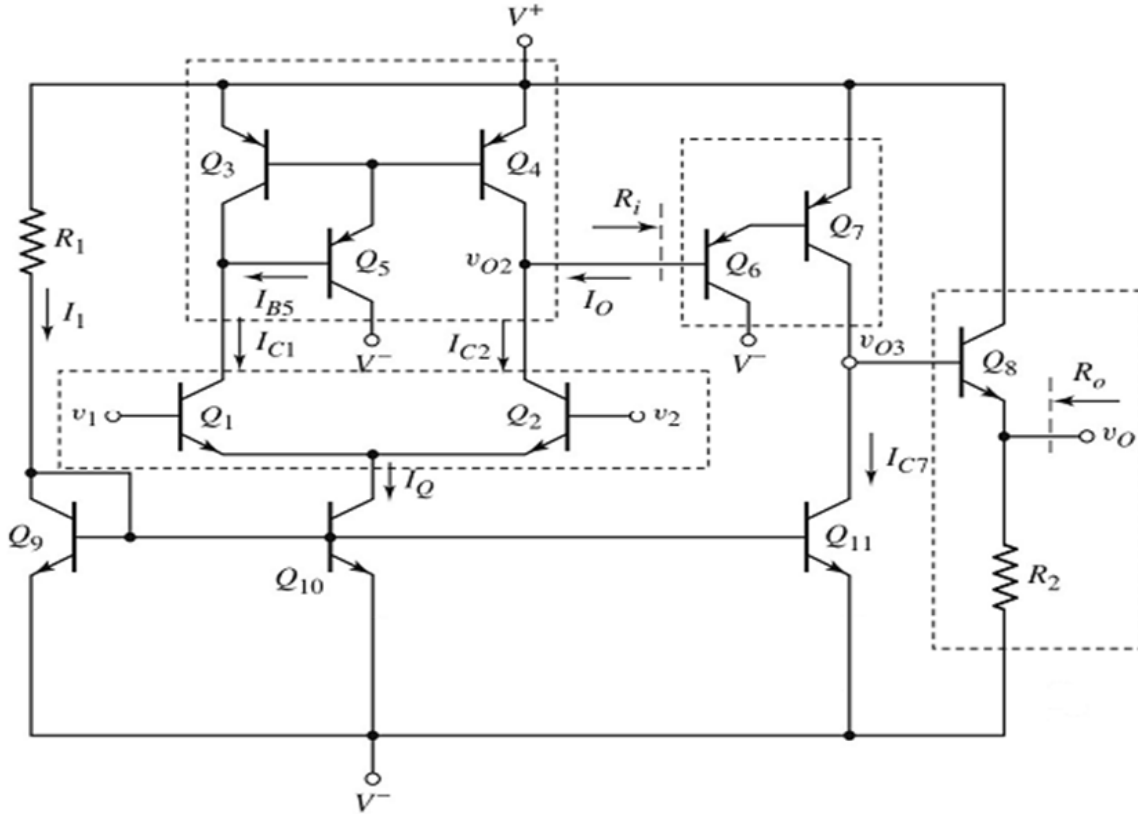


Figure 1

Consider the circuit shown in **Figure 1**, with parameters $I_{C7} = I_Q = 0.2 \text{ mA}$, $I_{C8} = 1.2 \text{ mA}$, and $R_2 = 10 \text{ k}\Omega$. Study the figure carefully. Note that biasing for amplifiers in the circuit is provided by **two-transistor current mirrors**. Assume that $\beta = 120$ for all transistors, and the **Early voltage** for Q_{11} is 100 V .

- (i) Calculate the input resistance (R_i) of the **Darlington pair**. [5 marks]
- (ii) Calculate the output resistance (R_O) of the **Emitter follower**. [5 marks]

Answer:

$$R_i = [2 (1+\beta) \beta V_T] / I_Q \quad [3]$$

$$\rightarrow R_i = [2 (1+120)(120)(0.026)] / (0.2\text{m}) = 3.7752 \text{ M}\Omega \quad [2]$$

$$R_O = R_2 \parallel \{[r_{\pi 8} + (R_{c11} \parallel R_{c7})]/(1+\beta)\} \quad [1]$$

$$R_{c11} = r_{o11} = V_{A11} / I_{c11} = V_{A11} / I_Q = 100/0.2\text{m} = 500 \text{ k}\Omega \quad [1]$$

$$R_{c7} = r_{o7} = V_{A7} / I_{c7} = V_{A7} / I_Q = 100/0.2\text{m} = 500 \text{ k}\Omega \quad [1]$$

$$r_{\pi 8} = \beta V_T / I_{C8} = (120)(0.026)/(1.2\text{m}) = 2.6 \text{ k}\Omega \quad [1]$$

$$\rightarrow R_O = (10\text{k}) \parallel \{[2.6\text{k} + (500\text{k} \parallel 500\text{k})]/(1+120)\} = (10\text{k}) \parallel (2.08\text{k}) = 1.72 \text{ k}\Omega \quad [1]$$

Question:

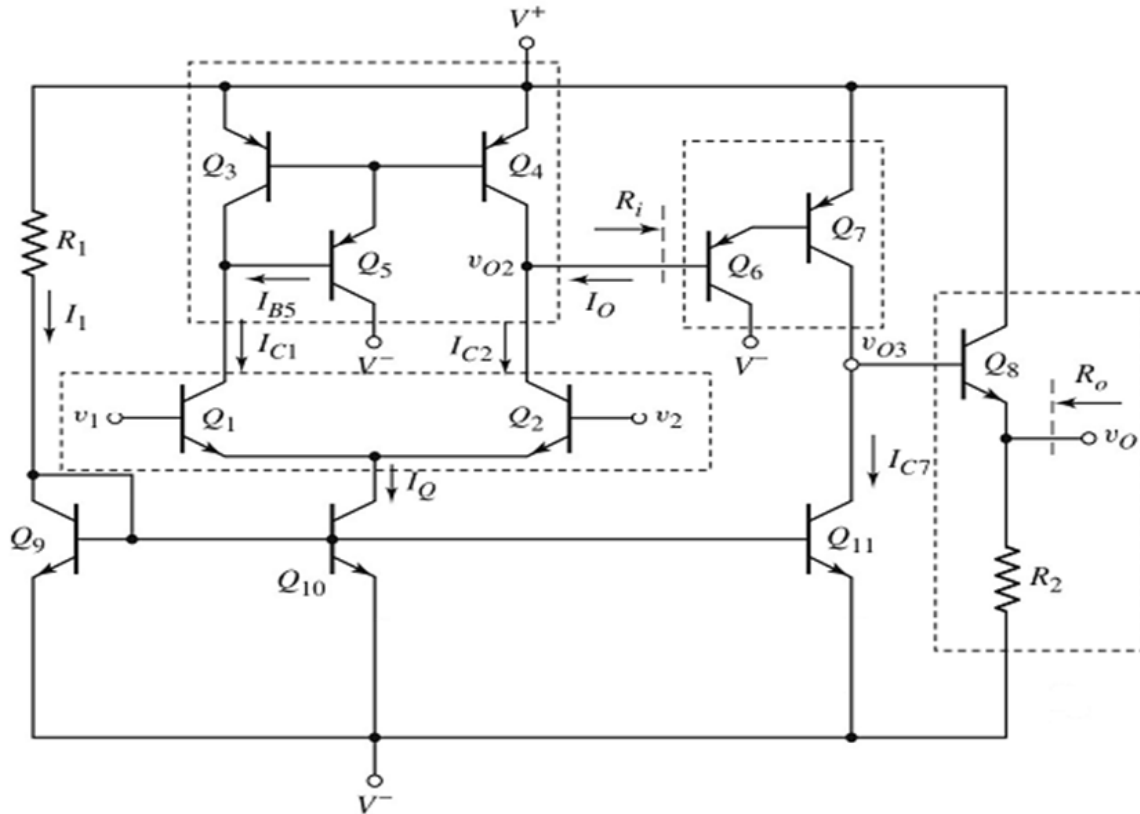


Figure 1

Consider the circuit shown in **Figure 1**, with parameters $I_{C7} = I_Q = 0.2 \text{ mA}$, $I_{C8} = 1.2 \text{ mA}$, and $R_2 = 12 \text{ k}\Omega$. Study the figure carefully. Note that biasing for amplifiers in the circuit is provided by **two-transistor current mirrors**. Assume that $\beta = 100$ for all transistors, and the **Early voltage** for Q_{11} is 100 V .

- (i) Calculate the input resistance (R_i) of the **Darlington pair**. [5 marks]
- (ii) Calculate the output resistance (R_O) of the **Emitter follower**. [5 marks]

Answer:

$$R_i = [2 (1+\beta) \beta V_T] / I_Q \quad [3]$$

$$\rightarrow R_i = [2 (1+100)(100)(0.026)] / (0.2\text{m}) = 2.626 \text{ M}\Omega \quad [2]$$

$$R_O = R_2 \parallel \{[r_{\pi 8} + (R_{c11} \parallel R_{c7})]/(1+\beta)\} \quad [1]$$

$$R_{c11} = r_{o11} = V_{A11} / I_{c11} = V_{A11} / I_Q = 100/0.2\text{m} = 500 \text{ k}\Omega \quad [1]$$

$$R_{c7} = r_{o7} = V_{A7} / I_{c7} = V_{A7} / I_Q = 100/0.2\text{m} = 500 \text{ k}\Omega \quad [1]$$

$$r_{\pi 8} = \beta V_T / I_{C8} = (100)(0.026)/(1.2\text{m}) = 2.16 \text{ k}\Omega \quad [1]$$

$$\rightarrow R_O = (12\text{k}) \parallel \{[2.16\text{k} + (500\text{k} \parallel 500\text{k})]/(1+100)\} = (12\text{k}) \parallel (2.49\text{k}) = 2.06 \text{ k}\Omega \quad [1]$$

Question:

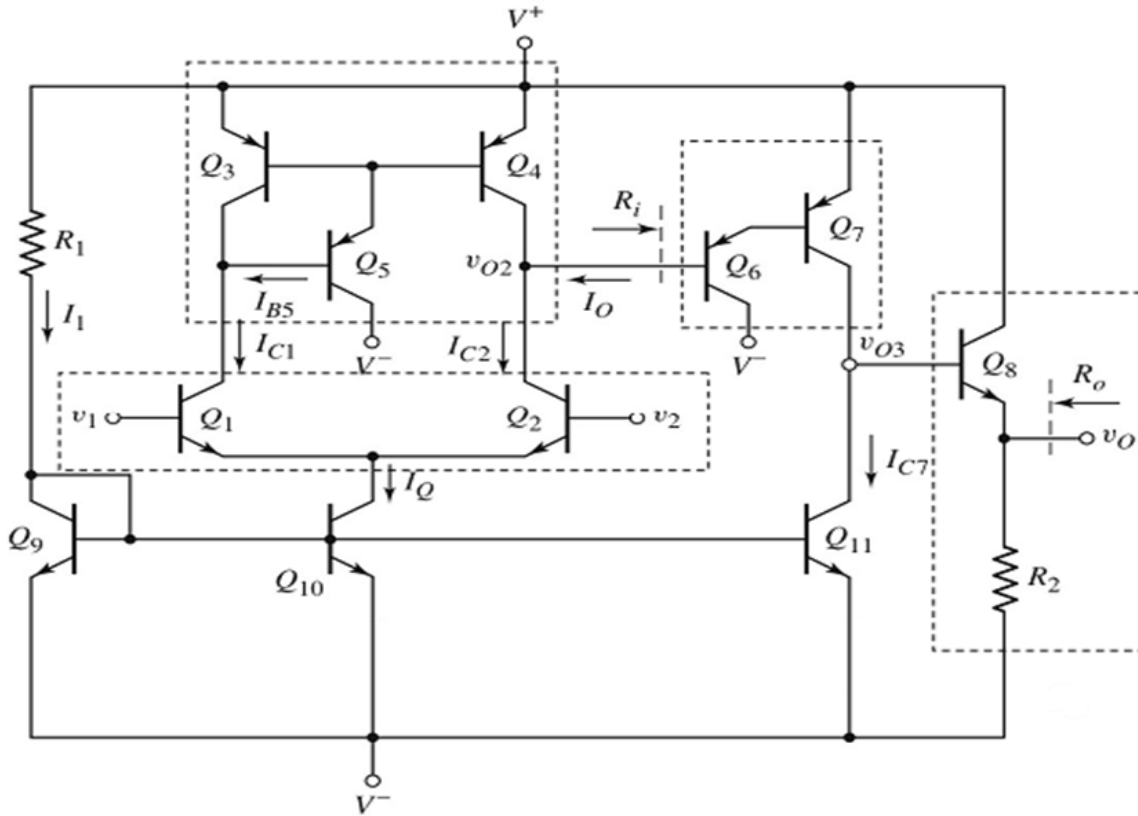


Figure 1

Consider the circuit shown in **Figure 1**, with parameters $I_{C7} = I_Q = 0.2 \text{ mA}$, $I_{C8} = 1 \text{ mA}$, and $R_2 = 14 \text{ k}\Omega$. Study the figure carefully. Note that biasing for amplifiers in the circuit is provided by two-transistor current mirrors. Assume that $\beta = 120$ for all transistors, and the Early voltage for Q_{11} is 100 V .

- (i) Calculate the input resistance (R_i) of the Darlington pair. [5 marks]
- (ii) Calculate the output resistance (R_O) of the Emitter follower. [5 marks]

Answer:

$$R_i = [2 (1+\beta) \beta V_T] / I_Q \quad [3]$$

$$\rightarrow R_i = [2 (1+120)(120)(0.026)] / (0.2\text{m}) = 3.7752 \text{ M}\Omega \quad [2]$$

$$R_O = R_2 \parallel \{[r_{\pi 8} + (R_{c11} \parallel R_{c7})]/(1+\beta)\} \quad [1]$$

$$R_{c11} = r_{o11} = V_{A11} / I_{c11} = V_{A11} / I_Q = 100/0.2\text{m} = 500 \text{ k}\Omega \quad [1]$$

$$R_{c7} = r_{o7} = V_{A7} / I_{c7} = V_{A7} / I_Q = 100/0.2\text{m} = 500 \text{ k}\Omega \quad [1]$$

$$r_{\pi 8} = \beta V_T / I_{C8} = (120)(0.026)/(1\text{m}) = 3.12 \text{ k}\Omega \quad [1]$$

$$\rightarrow R_O = (14\text{k}) \parallel \{[3.12\text{k} + (500\text{k} \parallel 500\text{k})]/(1+120)\} = (14\text{k}) \parallel (2.09\text{k}) = 1.81 \text{ k}\Omega \quad [1]$$