



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION**

SEMESTER 3 2011 / 2012

MODEL ANSWERS

PROGRAMME	: Bachelor of Electrical & Electronics Engineering (Honours) Bachelor of Electrical Power Engineering (Honours)
SUBJECT CODE	: EEEB273
SUBJECT	: ELECTRONIC ANALYSIS AND DESIGN II
DATE	: May 2012
TIME	: 3 hours


INSTRUCTIONS TO CANDIDATES:

1. This question paper contains **SIX (6)** questions in **THIRTEEN (13)** pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided.
4. Write answer to each question on **a new page**.
5. For all calculations, assume that $V_T = 26 \text{ mV}$.
6. Use at least **4 significant numbers** in all calculations.

**THIS QUESTION PAPER CONSISTS OF THIRTEEN (13) PRINTED PAGES
INCLUDING THIS COVER PAGE AND APPENDIX.**

Question 1(a)

(i)

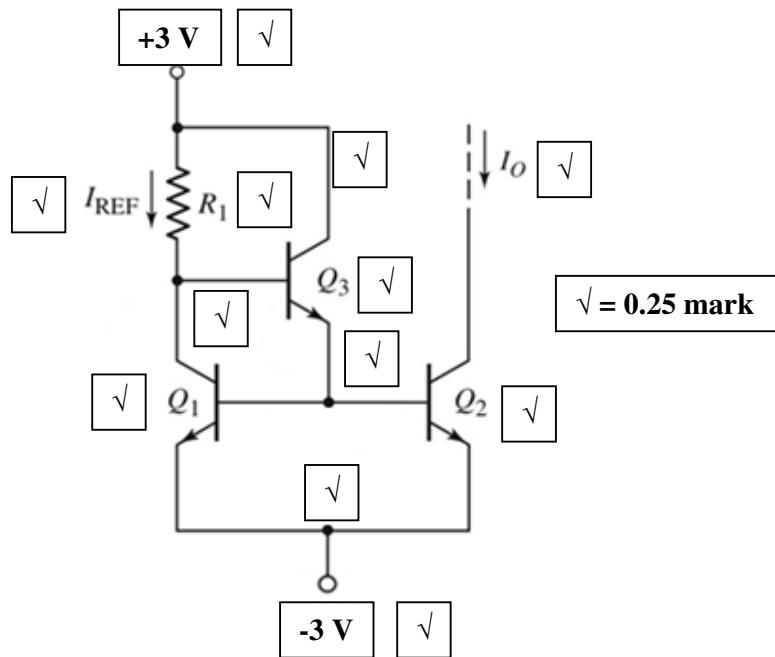

(ii)

$$I_{REF} = I_O [1 + 2/\beta(1 + \beta)] \quad [1]$$

$$= (0.25\text{m})[1 + 2/(50 \times 51)] = 0.250196 \text{ mA} \quad [1]$$

$$R_1 = (V^+ - V_{BE3} - V_{BE1} - V^-) / I_{REF} \quad [1]$$

$$= (3 - 0.7 - 0.7 - (-3)) / (0.250196\text{m}) = 18.385 \text{ k}\Omega \quad [1]$$

(iii)

I_O of a BJT three-transistor current source is closer to its I_{REF} at lower value of β compared to the two-transistor current source, thus it has more stable I_O . This is due to a better approximation of the relationship between I_O and I_{REF} due to addition of transistor Q₃ in the circuit. [2]

Question 1(b)

(i)

$$V_{DS2} (\text{sat}) = V_{GS2} - V_{TN} \quad [0.5]$$

$$0.4 = V_{GS2} - 0.4 \quad \rightarrow \quad V_{GS2} = 0.8 \text{ V} \quad [0.5]$$

$$V_{GS1} = V_{GS2} = 0.8 \text{ V} \quad [0.5]$$

$$(W/L)_1 = I_{REF} / [(k'n/2) (V_{GS1} - V_{TN})^2] \quad [0.5]$$

$$= (100\mu) / [(100\mu/2)(0.8 - 0.4)^2] = 12.5 \quad [0.5]$$

$$(W/L)_2 = I_O / [(k'n/2) (V_{GS2} - V_{TN})^2] \quad [0.5]$$

$$= (60\mu) / [(100\mu/2)(0.8 - 0.4)^2] = 7.5 \quad [0.5]$$

$$V_{GS3} = V^+ - V_{GS1} - V^+ = 2.5 - 0.8 - (-2.5) = 4.2 \text{ V} \quad [0.5]$$

$$(W/L)_3 = I_{REF} / [(k'n/2) (V_{GS3} - V_{TN})^2] \quad [0.5]$$

$$= (100\mu) / [(100\mu/2)(4.2 - 0.4)^2] = 0.138 \quad [0.5]$$

(ii)

$$R_O = r_{O2} = 1 / (\lambda I_O) \quad [0.5]$$

$$= 1 / (0.01 \times 60\mu) = 1.6667 \text{ M}\Omega \quad [0.5]$$

$$R_O = \Delta V_{D2} / \Delta I_O \quad [0.5]$$

$$\Delta I_O = \Delta V_{D2} / R_O = 3 / (1.6667 \text{ M}) = 1.8 \mu\text{A} \quad [0.5]$$

Question 2(a)

(i)

$$\begin{aligned}
 A_d &= v_o / v_d = (g_{m2} R_C) / 2 & [2] \\
 A_d &= v_o / v_d = 7.5 / 0.05 = 150 & [0.5] \\
 g_{m2} &= I_{CQ2} / V_T = I_Q / (2V_T) = (1\text{m}) / (2 \times 26\text{m}) = 19.231 \text{ mA/V} & [0.5] \\
 A_d &= (g_{m2} R_C) / 2 = (19.231\text{m} \times R_C) / 2 = 150 & [0.5] \\
 R_C &= 300 / 19.231\text{m} = 15.599 \text{ k}\Omega & [0.5]
 \end{aligned}$$

(ii)


$$\begin{aligned}
 R_{id} &= 2 r_\pi = (2 \beta V_T) / I_{CQ} & [0.5, 0.5] \\
 &= (4 \beta V_T) / I_Q = (4 \times 100 \times 0.026) / (1\text{m}) = 10.4 \text{ k}\Omega & [0.5, 0.5]
 \end{aligned}$$

(iii)

$$\begin{aligned}
 CMRR &= |A_d / A_{cm}| = |150 / -0.2| = 750 & [0.5, 0.5] \\
 CMRR_{dB} &= 20 \log_{10} (750) = 57.5 & [0.5, 0.5]
 \end{aligned}$$

Question 2(b)

(i)

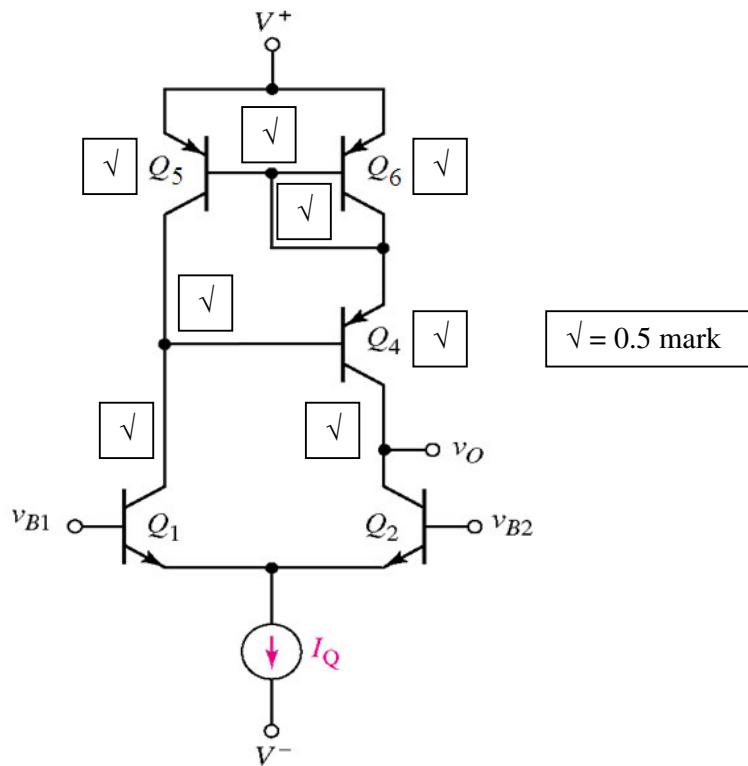

(ii)

$$\begin{aligned}
 R_{OAL} &\approx (\beta r_{o4}) / 2 & [1] \\
 &= (\beta V_{A4}) / (2 I_{C4}) = (\beta V_{AP}) / (I_Q) & [0.5] \\
 &= (150 \times 100) / (0.18\text{m}) = 83.333 \text{ M}\Omega & [0.5]
 \end{aligned}$$

(iii)

$$\begin{aligned}
 v_O &= v_{C2} = g_{m2} v_d (r_{o2} \parallel R_{OAL}) \\
 A_d &= v_O / v_d = g_{m2} (r_{o2} \parallel R_{OAL}) & [0.5]
 \end{aligned}$$

$$\begin{aligned}
 g_{m2} &= I_{CQ2} / V_T = I_Q / 2V_T \\
 &= (0.18\text{m})/(2 \times 26\text{m}) = 3.461 \text{ mA/V} & [0.5]
 \end{aligned}$$

$$\begin{aligned}
 r_{o2} &= V_{A2} / I_{C2} = (V_{AN}) / (I_Q / 2) \\
 &= (120) / (0.18\text{m} / 2) = 1.333 \text{ M}\Omega & [0.5]
 \end{aligned}$$

$$r_{o2} \parallel R_{OAL} = 1.333\text{M} \parallel 83.333\text{M} = 1.312 \text{ M}\Omega \approx r_{o2}$$

$$\begin{aligned}
 A_d &= (3.461\text{m})(1.312\text{M}) \\
 &= 4540.832 & [0.5]
 \end{aligned}$$

Question 3(a)

(i)		
R_O	$= (r_{o2} \parallel r_{o4})$	[0.5]
I_{D2}	$= I_{D4} = I_Q / 2 = (0.4\text{m})/2 = 0.2 \text{ mA}$	[0.5, 0.5]
r_{o2}	$= 1 / (\lambda_p I_{D2}) = 1 / (0.01 \times 0.2\text{m}) = 500 \text{ k}\Omega$	[0.5]
r_{o4}	$= 1 / (\lambda_n I_{D4}) = 1 / (0.02 \times 0.2\text{m}) = 250 \text{ k}\Omega$	[0.5]
R_O	$= (500\text{k} \parallel 250\text{k}) = 166.67 \text{ k}\Omega$	[0.5]

(ii)

A_d	$= g_{m2}(r_{o2} \parallel r_{o4}) = g_{m2}(R_O)$	[1]
g_{m2}	$= 2 \text{ SQRT}[K_p I_{D2}] = 2 \text{ SQRT}[(60\mu)(0.2\text{m})] = 0.219 \text{ mA/V}$	[1]
A_d	$= (0.219\text{m})(166.67\text{k}) = 36.515 \text{ V/V}$	[1]

(iii)

$$v_O = A_d v_d = [36.515 \text{ V/V}] \times [(20 \sin \omega t) \mu\text{V}] = (0.730 \sin \omega t) \text{ mV} \quad [1]$$

Question 3(b)

(i)

$$\begin{aligned} I_{CQ2} &= I_Q / 2 &= 0.5\text{m} / 2 &= 0.25 \text{ mA} \\ v_{o2} &= V^+ - I_{CQ2} R &= 5 - (0.25\text{m})x(12\text{k}) &= 2 \text{ V} \end{aligned} \quad [1]$$

$$v_{o3} = V^+ - I_{CQ3} R_C = 5 - (0.5\text{m})x(4\text{k}) = 3 \text{ V} \quad [1]$$

$$\begin{aligned} v_O &= v_{o3} - V_{BE4} &= 3 - 0.7 &= 2.3 \text{ V} \\ \text{or } v_O &\approx V + I_{CQ4} R_{E2} &= -5 + (3\text{m})x(2.43\text{k}) &= 2.29 \text{ V} \end{aligned} \quad [1]$$

(ii)

$$\begin{aligned} A_v &= v_O/v_d = (v_{o2}/v_d)(v_{o3}/v_{o2})(v_O/v_{o3}) = A_d A_{v2} A_{v3} \\ A_d &= (g_m/2)(R \parallel R_{in3}) \end{aligned}$$

$$g_{m2} = I_{CQ2}/V_T = I_Q/(2V_T) = (0.5\text{m})/(2 \times 26\text{m}) = 9.615 \text{ mA/V} \quad [0.5]$$

$$r_{\pi3} = \beta V_T / I_{CQ3} = (100 \times 26\text{m}) / (0.5\text{m}) = 5.2 \text{ k}\Omega \quad [0.5]$$

$$R_{in3} = r_{\pi3} + (1 + \beta) R_{E1} = 5.2\text{k} + (1+100)(2.6\text{k}) = 267.8 \text{ k}\Omega \quad [1]$$

$$A_d = (g_{m2}/2)(R \parallel R_{in3}) = (9.615\text{m}/2)(12\text{k} \parallel 267.8\text{k}) = 55.218 \text{ V/V} \quad [1, 0.5]$$

$$A_{v2} = v_{o3}/v_{o2} = -1.47 \text{ V/V} \quad [0.5]$$

$$A_{v3} \approx 1 \quad [0.5]$$

$$A_v = A_d A_{v2} A_{v3} = 55.218 \times (-1.47) \times 1 = -81.17 \text{ V/V} \quad [1, 0.5]$$

Question 4(a)

$$\begin{aligned}
 I_{REF} &= (V^+ - V_{EB12} - V_{BE11} - V^-) / R_5 & [1] \\
 &= (12 - 0.6 - 0.6 - (-12)) / (40k) = 0.57 \text{ mA} & [1] \\
 I_{C17} &= I_{C13B} = 0.70 I_{REF} & [1] \\
 &= (0.70)(0.57\text{m}) = 0.399 \text{ mA} & [0.5] \\
 I_{C16} &\approx I_{E16} \quad (\text{With } \beta = 200) & [1] \\
 &= I_{B17} + (I_{E17} R_8 + V_{BE17})/R_9 & [1] \\
 &= I_{C17}/\beta + (I_{C17} R_8 + V_{BE17})/R_9 & [1] \\
 &= (0.399\text{m}/200) + [(0.399\text{m})(100) + 0.6]/(50k) & [1] \\
 &= 14.793 \mu\text{A} & [0.5]
 \end{aligned}$$

Question 4(b)

(i)

$$\begin{aligned}
 I_{D3} &= (k'_p/2)(W/L)_3(V_{SG3} + V_{TP})^2 & [0.5] \\
 150\mu &= (40\mu/2)(50)(V_{SG3} - 0.4)^2 \\
 V_{SG3} &= 0.7873 \text{ V} & [0.5] \\
 R_{D1} &= V_{SG3} / I_{D1} = V_{SG3} / (I_Q/2) & [0.5] \\
 &= 0.7873 / (200\mu/2) = 7.87 \text{ k}\Omega & [0.5]
 \end{aligned}$$

$$\begin{aligned}
 I_{D4} &= (k'_n/2)(W/L)_4(V_{GS4} - V_{TN})^2 & [0.5] \\
 200\mu &= (100\mu/2)(40)(V_{GS4} - 0.4)^2
 \end{aligned}$$

$$\begin{aligned}
 V_{GS4} &= 0.7162 \text{ V} & [0.5] \\
 V_{G4} &= V_O + V_{GS4} = 0 + 0.7162 = 0.7162 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 R_{D2} &= (V_{G4} - (V)) / I_{D3} & [0.5] \\
 &= (0.7162 - (-3))/(150\mu) = 24.8 \text{ k}\Omega & [0.5]
 \end{aligned}$$

$$\begin{aligned}
 R_S &= (V_O - (V)) / I_{D4} & [1] \\
 &= (0 - (-3))/(200\mu) = 15 \text{ k}\Omega & [1]
 \end{aligned}$$

(ii)

$$\begin{aligned}
 A_{d1} &= (g_{m1}/2)(R_{D1}) & [0.5] \\
 g_{m1} &= 2 \text{ SQRT}[(k'_n/2)(W/L)_1(I_Q/2)] & [0.5] \\
 &= 2 \text{ SQRT}[(100\mu/2)(20)(200\mu/2)] = 0.6325 \text{ mA/V} & [0.5] \\
 A_{d1} &= (0.6325\text{m} / 2)(7.87\text{k}) = 2.49 & [0.5]
 \end{aligned}$$

Question 5

- (a) Cross-over distortion is a condition where the output voltage v_O of an actual class-B output stage circuit is zero [1] when its input voltage is in a certain voltage range. In this condition, both transistors in the circuit are cut-off because the input voltage is within V_{EBP} to V_{BEN} [1], thus producing $v_O = \text{zero}$ and causing distortion at the output of the actual class-B output stage [1].
- (b) Its advantage over class-A is less power dissipation and increased power conversion efficiency [1], while its advantage over class-B is no cross-over distortion [1].
- (c) Calculation of i_L , i_{Cp} , and i_{Cn} :

$$v_O = -4 \text{ V} = i_L R_L \quad [1]$$

$$\Rightarrow i_L = v_O / R_L = (-4 \text{ V}) / (1 \text{ k}\Omega) = -4 \text{ mA} \quad [1]$$

Therefore, Q_p is conducting and Q_n is OFF.

$$\text{Approximate value } i_L \approx i_{Cp} = I_S \exp(V_{EBP}/V_T) = 4 \text{ mA} \quad [0.5]$$

$$V_{EBP} = V_T \ln(i_{Cp} / I_S) = (26 \text{ m}) \ln(4 \text{ m} / 2 \times 10^{-15})$$

$$V_{EBP} = 0.7364 \text{ V} \quad [0.5]$$

$$V_{BEN} = V_{BB} - V_{EBP} = 1.4 - 0.7364 = 0.6636 \text{ V} \quad [0.5]$$

$$\Rightarrow i_{Cn} = I_S \exp(V_{BEN}/V_T) = (2 \times 10^{-15}) \exp(0.6636/0.026) = 0.2429 \text{ mA} \quad [1]$$

$$i_{Cn} = i_{Cp} + i_L \quad [1]$$

$$\text{Actual value of } i_{Cp} = i_{Cn} - i_L = 0.2429 \text{ m} - (-4 \text{ m}) \quad [0.5]$$

$$\Rightarrow i_{Cp} = 4.2429 \text{ mA} \quad [1]$$

- (d) Calculation of power dissipation:

$$P_{Qn} = i_{Cn} V_{CEn} \quad [1]$$

$$V_{CEn} = +V_{CC} - v_O = +6 - (-4) = 10 \text{ V} \quad [0.5]$$

$$\Rightarrow P_{Qn} = (0.2429 \text{ mA})(10 \text{ V}) = 2.429 \text{ mW} \quad [0.5]$$

$$P_{Qp} = i_{Cp} V_{ECp} \quad [1]$$

$$V_{ECp} = v_O - (-V_{CC}) = -4 - (-6) = 2 \text{ V} \quad [0.5]$$

$$\Rightarrow P_{Qp} = (4.2429 \text{ mA})(2 \text{ V}) = 8.4858 \text{ mW} \quad [0.5]$$

Question 6

(a) Any 4 applications from the following list. Give 1 mark for each answer. [4]

1. Current-to-voltage converter
2. Voltage-to-current converter
3. Difference Amplifier
4. Instrumentation Amplifier
5. Integrator
6. Differentiator

(b) Answer for finding v_o/v_I :

$$R_1 = 20 \text{ k}\Omega, R_2 = 100 \text{ k}\Omega, R_3 = 80 \text{ k}\Omega, \text{ and } R_4 = 40 \text{ k}\Omega$$

$$v_o/v_I = (v_o/v_{o1}) \times (v_{o1}/v_I) \quad [2]$$

$$v_o/v_{o1} = - (R_4/R_3) \quad [1]$$

$$v_{o1}/v_I = - (R_2/R_1) \quad [1]$$

$$v_o/v_I = [- (R_4/R_3)] \times [- (R_2/R_1)] = (R_4 R_2) / (R_3 R_1) \quad [1]$$

$$= (40 \text{ k} \times 100 \text{ k}) / (80 \text{ k} \times 20 \text{ k}) = 2.5 \quad [1]$$

(c) Answer for finding A_d , A_{cm} , and calculate the CMRR in dB:

$$R_1 = R_3 = 10 \text{ k}\Omega, R_2 = 100 \text{ k}\Omega, \text{ and } R_4 = 110 \text{ k}\Omega$$

$$v_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3} \right) v_{I2} - \left(\frac{R_2}{R_1} \right) v_{I1}$$

$$v_o = \left(1 + \frac{100 \text{ k}}{10 \text{ k}}\right) \left(\frac{110 \text{ k} / 10 \text{ k}}{1 + 110 \text{ k} / 10 \text{ k}} \right) v_{I2} - \left(\frac{100 \text{ k}}{10 \text{ k}} \right) v_{I1}$$

$$v_o = (1+10) \left(\frac{11}{12} \right) v_{I2} - 10 v_{I1} \quad [2]$$

$$v_o = 10.083 v_{I2} - 10 v_{I1} = 10.083(v_{cm} + \frac{v_d}{2}) - 10(v_{cm} - \frac{v_d}{2})$$

$$v_o = 10.0415 v_d + 0.083 v_{cm}$$

$$A_d = 10.0415, \quad A_{cm} = 0.083$$

[2, 2]

$$CMRR = 20 \log_{10}[10.0415/0.083] = 41.65 \text{ dB}$$

[2]