



**COLLEGE OF ENGINEERING  
PUTRAJAYA CAMPUS  
FINAL EXAMINATION  
SEMESTER 3 2011 / 2012**

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)  
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : May 2012

TIME : 3 hours

---

**INSTRUCTIONS TO CANDIDATES:**

1. This question paper contains **SIX (6)** questions in **THIRTEEN (13)** pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided.
4. Write answer to each question on **a new page**.
5. For all calculations, assume that  $V_T = 26 \text{ mV}$ .
6. Use at least **4 significant numbers** in all calculations.

---

***THIS QUESTION PAPER CONSISTS OF THIRTEEN (13) PRINTED PAGES  
INCLUDING THIS COVER PAGE AND APPENDIX.***

**Question 1 [16 marks]**

(a) A basic **three-transistor current source** consists of matched **nnp transistors  $Q_1$ ,  $Q_2$ , and  $Q_3$** , has output current ( $I_O$ ) and reference current ( $I_{REF}$ ). A resistor  $R_1$  is used to establish  $I_{REF}$ . The circuit parameters are  $V^+ = 3\text{ V}$  and  $V^- = -3\text{ V}$ , and the transistor parameters are  $V_{BE(\text{on})} = 0.7\text{ V}$ ,  $\beta = 50$ , and  $V_A = \infty$ .

(i) Let the second transistor,  $Q_2$ , be the output transistor. **Draw and label** the circuit and its components **clearly**.

[3 marks]

(ii) If the output current is **0.25 mA**, what are the values of  $I_{REF}$  and  $R_1$ ?

[4 marks]

(iii) **Discuss the advantage** of a BJT three-transistor current source over **two-transistor current source**.

[2 marks]


(b) For a MOSFET current source shown in **Figure 1**, the transistor parameters are  $k'_n = 100 \mu\text{A}/\text{V}^2$ ,  $V_{TN} = 0.4 \text{ V}$  and  $\lambda = 0.01 \text{ V}^{-1}$ . Given that  $V^+ = 2.5 \text{ V}$ ,  $V^- = -2.5 \text{ V}$ ,  $I_{REF} = 100 \mu\text{A}$ ,  $I_O = 60 \mu\text{A}$ , and  $V_{DS2}(\text{sat}) = 0.4 \text{ V}$ , find:

(i) The width-to-length (**W/L**) ratio for all transistors in the circuit.

[5 marks]

(ii) How much the output current ( $I_O$ ) would change if the output voltage at  $V_{D2}$  changes by  $3\text{V}$ ?

[2 marks]

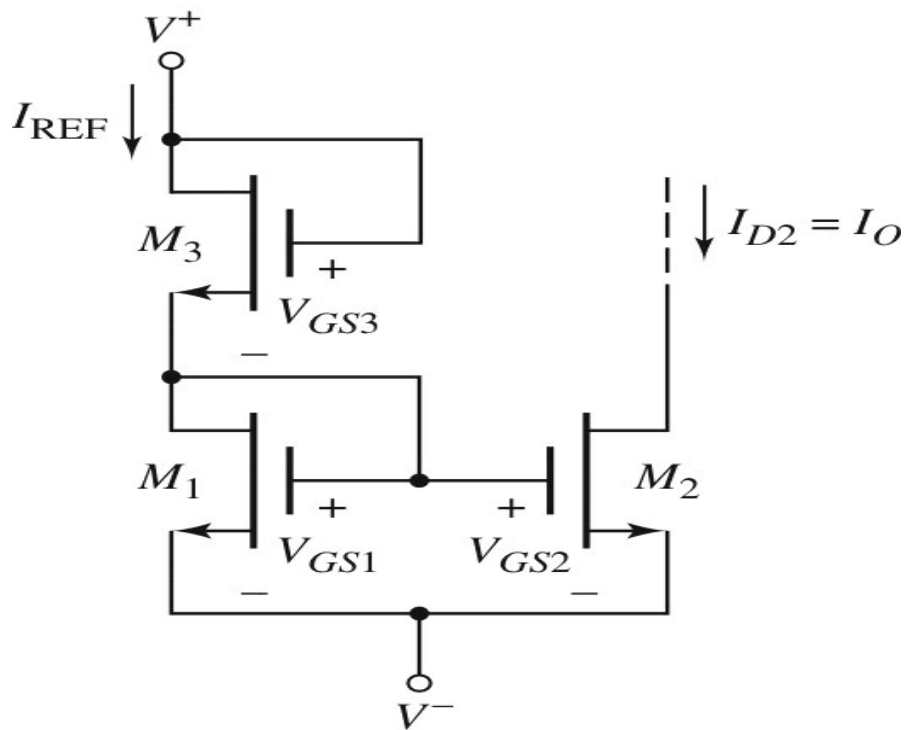

**Figure 1**

**Question 2 [16 marks]**

(a) Consider the BJT differential amplifier in **Figure 2a**. Study **Figure 2a** carefully. The circuit and transistor parameters are  $I_Q = 1 \text{ mA}$ ,  $\beta = 100$ , and Early voltage  $V_A = \infty$ .

(i) **Design** the circuit such that **one-sided** differential-mode **output** voltage at  $v_{C2} = 7.5 \text{ V}$  when a differential-mode input voltage of  $v_d = 0.05 \text{ V}$  is applied.


[4 marks]

(ii) **Determine** the differential-mode input resistance ( $R_{id}$ ).

[2 marks]

(iii) **Determine** the  $CMRR_{dB}$  when the common-mode voltage gain ( $A_{cm}$ ) is  $-0.2 \text{ V/V}$ .

[2 marks]

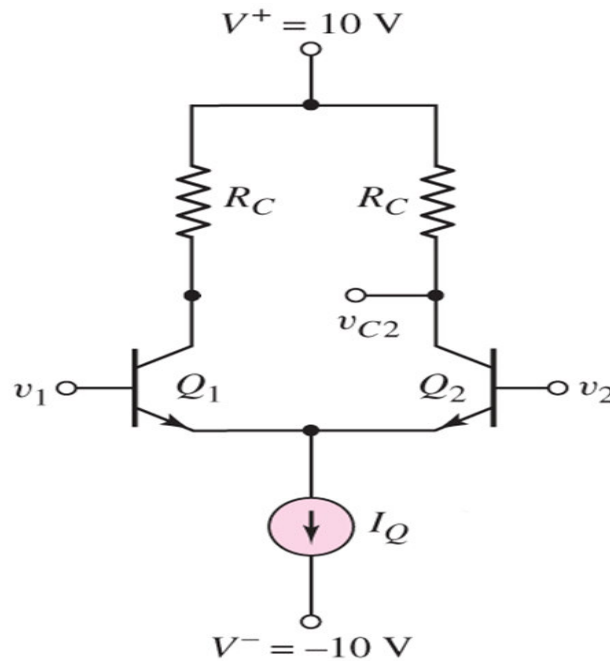**Figure 2a**

(b) The BJT differential amplifier shown in **Figure 2b** is biased by a **0.18 mA** constant current source (i.e.  $I_Q = 0.18 \text{ mA}$ ). It is to be redesigned to use an active load in order to increase its differential-mode voltage gain ( $A_d$ ). The active load to be used is a **BJT Wilson current source** using **pnp transistors** to replace the collector resistors ( $R_C$ ) in the differential amplifier, as graphically shown in **Figure 2b**.

The transistor parameters are  $\beta = 150$ ,  $V_{BE(\text{on})} = V_{EB(\text{on})} = 0.7 \text{ V}$ ,  $V_{AN} = 120 \text{ V}$ , and  $V_{AP} = 100 \text{ V}$ . The one-sided output voltage taken at  $v_{C2}$  can be calculated using:

$$v_O = v_{C2} = g_{m2} v_d (r_{O2} \parallel R_{OAL})$$

where  $R_{OAL}$  is the output resistance of the **BJT Wilson current source**.

(i) **Draw the new circuit** incorporating the **active load's full circuit diagram**. Label the circuit correctly and clearly with appropriate symbols and numbering for transistors used in circuit. Leave  $I_Q$  symbol as it is in the **Figure 2b**.


[4 marks]

(ii) **Find** the output resistance of the **BJT Wilson current source** ( $R_{OAL}$ ).

[2 marks]

(iii) **Determine** the differential-mode voltage gain ( $A_d$ ) of **the new circuit**.

[2 marks]

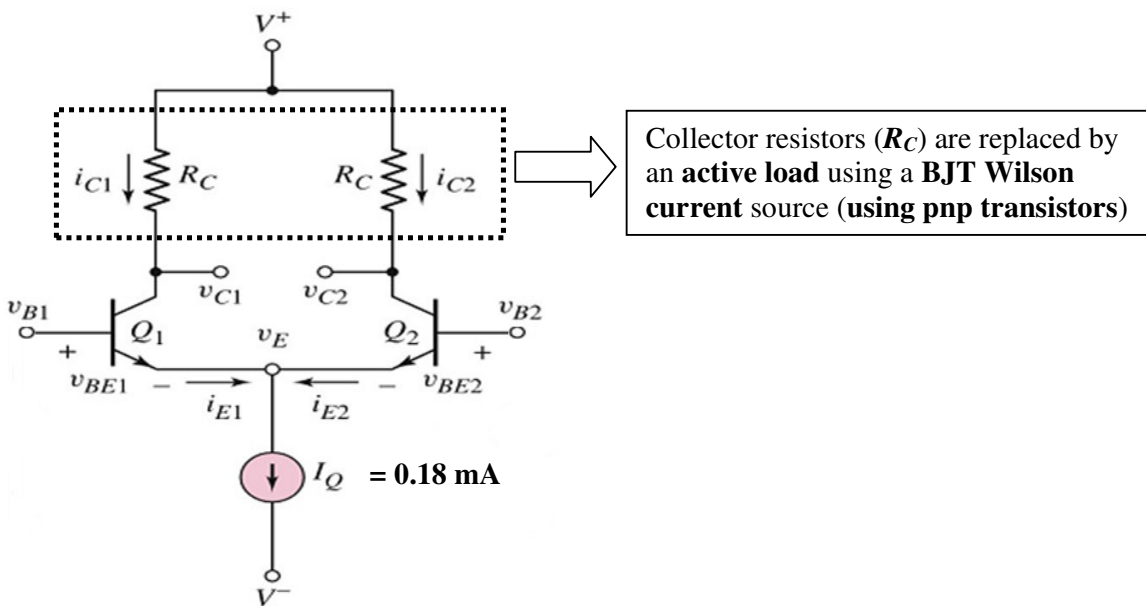


**Figure 2b**

**Question 3 [16 marks]**

(a) Consider the MOSFET differential amplifier with an active load as shown in **Figure 3a**. The transistors parameters are  $V_{TN} = 1 \text{ V}$ ,  $V_{TP} = -1 \text{ V}$ ,  $K_n = 90 \mu\text{A}/\text{V}^2$ ,  $K_p = 60 \mu\text{A}/\text{V}^2$ ,  $I_Q = 0.4 \text{ mA}$ ,  $\lambda_n = 0.02 \text{ V}^{-1}$  and  $\lambda_p = 0.01 \text{ V}^{-1}$ . Assume that the differential amplifier transistors  $M_1$  and  $M_2$  are identical and active load transistors  $M_3$  and  $M_4$  are identical. Determine:

- (i) The **output resistance** of the amplifier. [3 marks]
- (ii) The **differential-mode** voltage gain. [3 marks]
- (iii) The **output voltage**,  $v_o$ , if the differential input voltage applied is  $v_d = (20 \sin \omega t) \mu\text{V}$ . [1 mark]

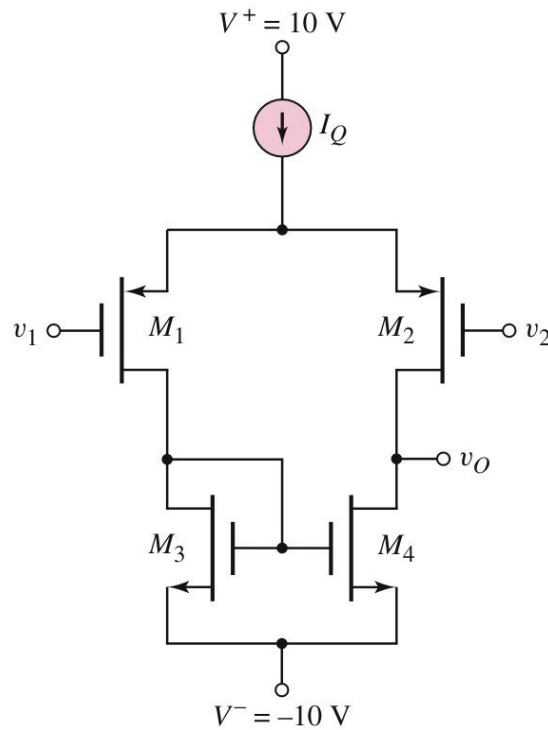

**Figure 3a**


(b) Consider the multistage bipolar circuit in **Figure 3b**, in which base currents are negligible. The transistors and circuits parameters are:  $V_{BE(\text{on})} = 0.7 \text{ V}$ ,  $\beta = 100$  and  $V_A = \infty$ ,  $R = 12 \text{ k}\Omega$ ,  $R_C = 4 \text{ k}\Omega$ ,  $R_{E1} = 2.6 \text{ k}\Omega$ ,  $R_{E2} = 2.43 \text{ k}\Omega$ ,  $I_Q = 0.5 \text{ mA}$ ,  $I_{CQ3} = 0.5 \text{ mA}$  and  $I_{CQ4} = 3 \text{ mA}$ . Determine:

(i) The **output voltage**  $v_{O2}$ ,  $v_{O3}$ , and  $v_O$  when  $v_1 = v_2 = 0 \text{ V}$ .

[3 marks]

(ii) The **overall voltage gain** ( $v_O/v_d$ ) if the voltage gain of the second stage (i.e.  $v_{O3}/v_{O2}$ ) = **-1.47 V/V**.

[6 marks]

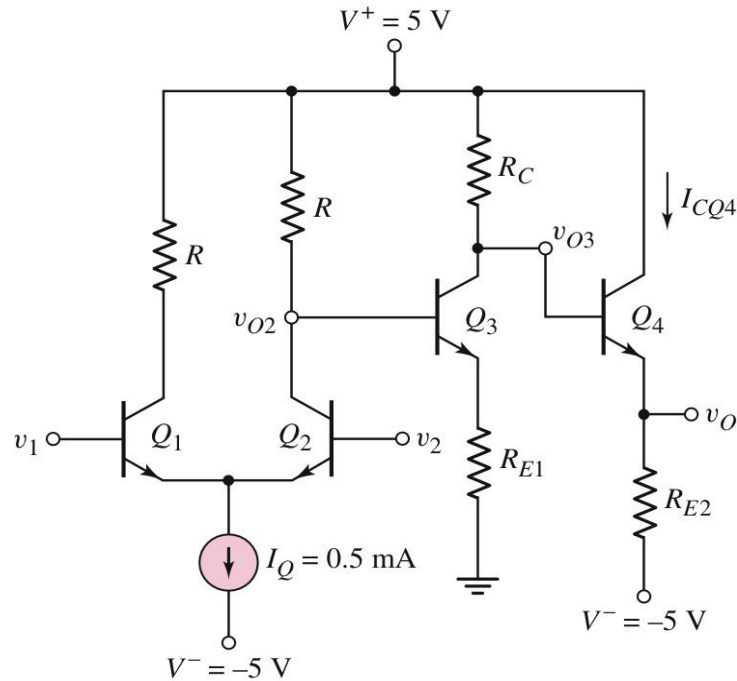


**Figure 3b**

**Question 4 [16 marks]**

(a) **Figure 4a** shows reference circuit and gain stage of **741 op-amp**. Transistors  $Q_{12}$  and  $Q_{13}$  form a current mirror, and  $Q_{13B}$  has a scale factor **0.70** times that of  $Q_{12}$ . Power supply voltages are  $V^+ = +12\text{ V}$  and  $V^- = -12\text{ V}$ . Assume  $V_{BE} = V_{EB} = 0.6\text{ V}$  and  $\beta = 200$  for npn transistors. Calculate  $I_{REF}$  and  $I_{C16}$ .

[8 marks]

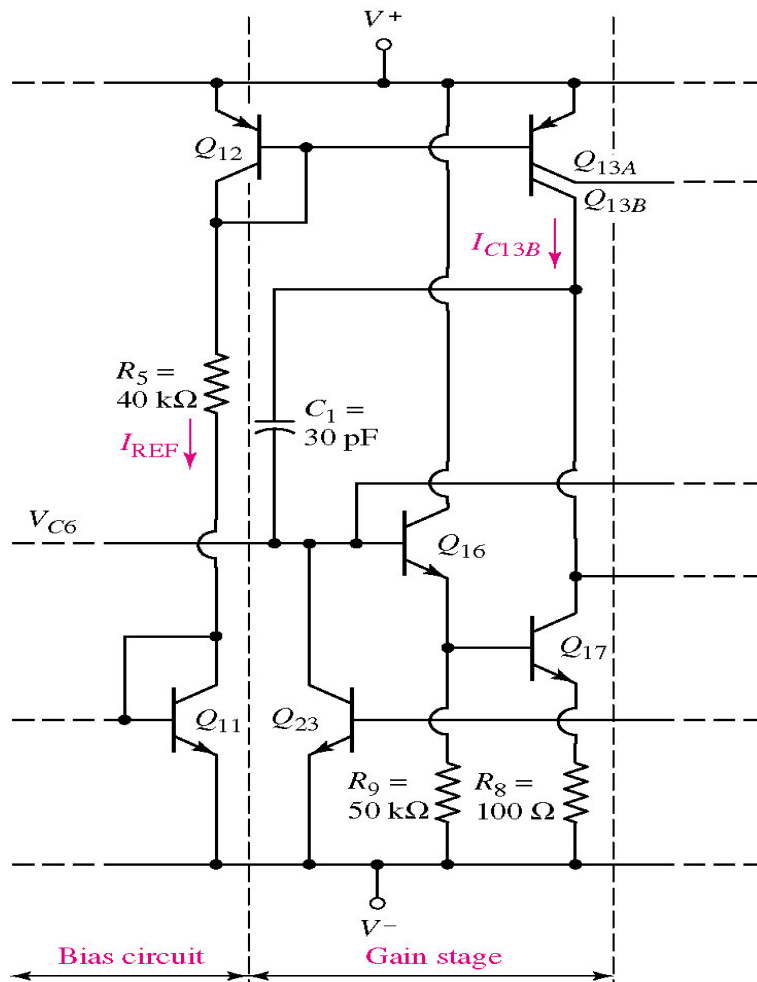

**Figure 4a**




(b) A MOSFET op-amp circuit as shown in **Figure 4b** is biased with  $I_Q = 200 \mu\text{A}$ . The transistor parameters are  $k'_n = 100 \mu\text{A}/\text{V}^2$ ,  $k'_p = 40 \mu\text{A}/\text{V}^2$ ,  $V_{TN} = 0.4 \text{ V}$ ,  $V_{TP} = -0.4 \text{ V}$ , and  $\lambda_n = \lambda_p = 0$ . The transistor aspect ratios are  $(W/L)_1 = (W/L)_2 = 20$ ,  $(W/L)_3 = 50$ , and  $(W/L)_4 = 40$ .

(i) **Design** the circuit (i.e. find the values of  $R_{D1}$ ,  $R_{D2}$ , and  $R_S$ ) such that  $I_{D3} = 150 \mu\text{A}$ ,  $I_{D4} = 200 \mu\text{A}$ , and  $v_o = 0$  for  $v_1 = v_2 = 0$ .

[6 marks]

(ii) **Find** the differential voltage gain ( $A_d$ ) of the differential amplifier in the circuit.

[2 marks]

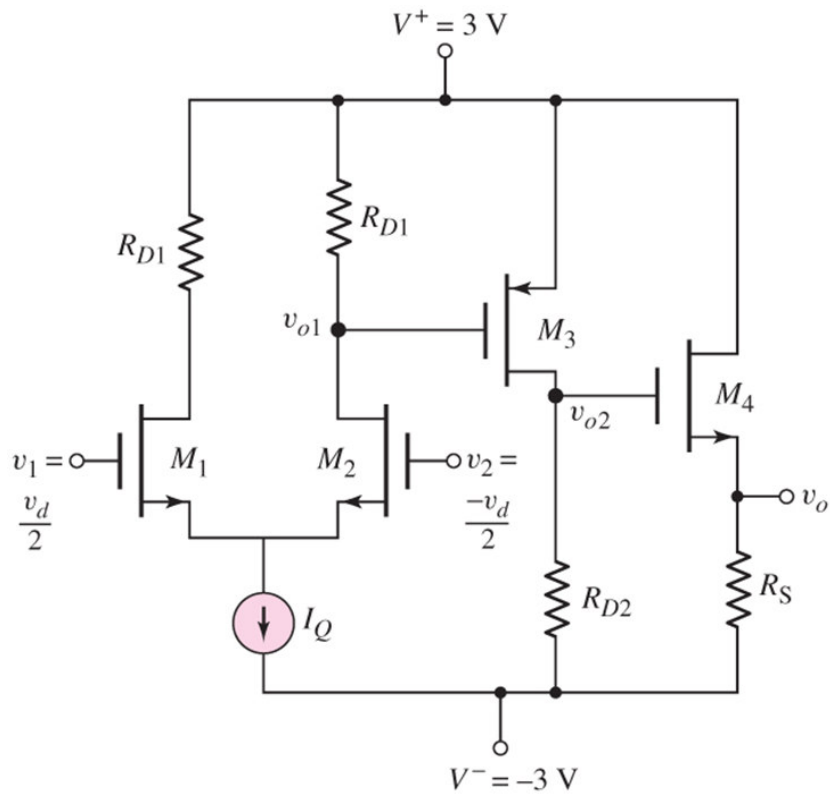


**Figure 4b**

**Question 5 [16 marks]**

**Study** the output stage circuit shown in **Figure 5** carefully. Let  $R_L = 1 \text{ k}\Omega$ ,  $V_{BB} = 1.40 \text{ V}$  and the reverse saturation current for the transistors,  $I_S = 2 \times 10^{-15} \text{ A}$ . Assume  $\beta \gg 1$ .

- (a) **Explain** the “cross-over distortion” phenomenon in **class-B output stage**. [3 marks]
  
- (b) What is the **advantage** of the output stage shown in **Figure 5** compared to the **class-A** and **class-B** output stages? [2 marks]
  
- (c) Referring to **Figure 5**, for the case of the output voltage  $v_O = -4 \text{ V}$ , **determine**  $i_L$ ,  $i_{Cp}$ , and  $i_{Cn}$ . [7 marks]
  
- (d) Referring to **Figure 5**, for the case of the output voltage  $v_O = -4 \text{ V}$ , **calculate** the power dissipated in transistor  $Q_n$  and  $Q_p$ . [4 marks]

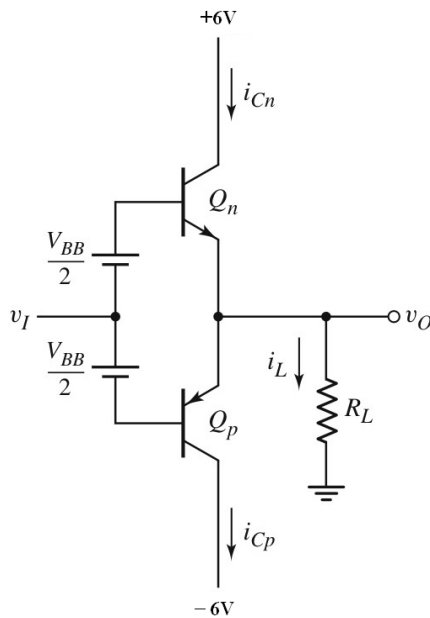

**Figure 5**


**Question 6 [20 marks]**

(a) States four (4) applications of an ideal operational amplifier.


[4 marks]

(b) Consider the two inverting op-amp circuit connected in cascade as shown in **Figure 6a**. Let  $R_1 = 20 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ ,  $R_3 = 80 \text{ k}\Omega$ , and  $R_4 = 40 \text{ k}\Omega$ . Find  $v_O/v_I$  for the circuit.

[6 marks]

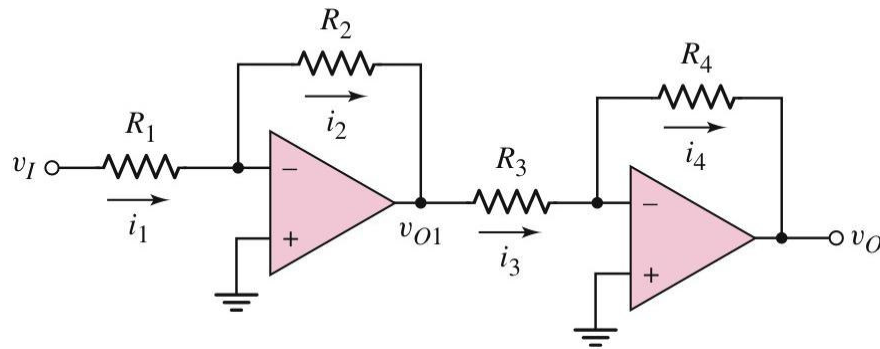

**Figure 6a**

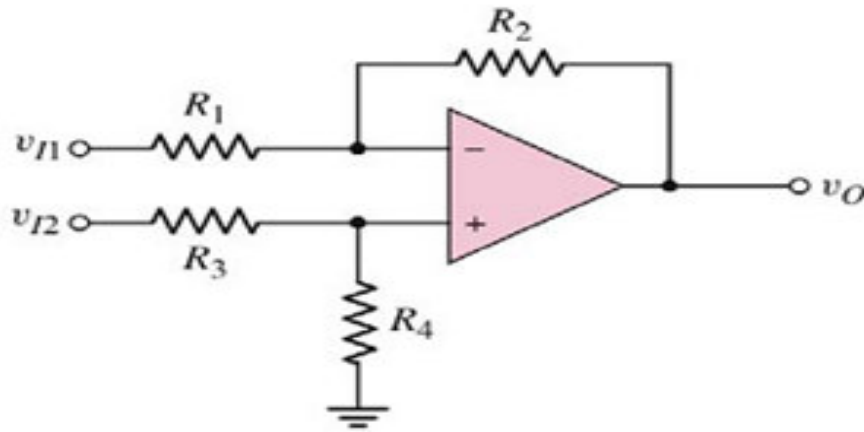

**Figure 6b**

(c) A general output equation for a difference amplifier shown in **Figure 6b** is

$$v_O = A_d v_d + A_{cm} v_{cm}$$

For the difference amplifier in **Figure 6b**, the circuit parameters are  $R_1 = R_3 = 10 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ , and  $R_4 = 110 \text{ k}\Omega$  and the output voltage equation is as follows:

$$v_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_{I2} - \left(\frac{R_2}{R_1}\right) v_{I1}$$

where

$$v_{I1} = v_{cm} - \frac{v_d}{2}$$

and

$$v_{I2} = v_{cm} + \frac{v_d}{2}$$

Find  $A_d$ ,  $A_{cm}$ , and then calculate the **CMRR in dB**.

[10 marks]

**-END OF QUESTION PAPER-**

## APPENDIX

BASIC FORMULABJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$