


Name:

Student ID Number:

Section: 01A / 01B / 02A / 02B

Lecturer: Dr Jamaludin / Dr Azni Wati

**UNIVERSITI
TENAGA
NASIONAL**

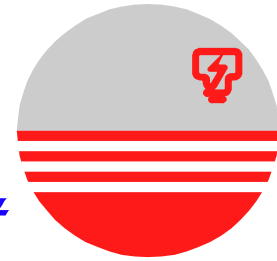

College of Engineering
Department of Electronics and Communication Engineering

Midterm Test – Model Answer

SEMESTER 3, ACADEMIC YEAR 2011/2012

Subject Code : **EEEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **10 March 2012**
Time Allowed : **2 hours**

Instructions to the candidates:

1. Write your Name and Student ID number. Circle your section number.
2. Write all your answers using pen. **DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**
5. For BJT, use $V_T = 26 \text{ mV}$ where appropriate.

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!



Question 1 [30 marks]

The circuit in **Figure 1** is a BJT current source with $R_1 = 8.6 \text{ k}\Omega$. The transistor parameters are: $V_{BE1} = 0.65 \text{ V}$, $V_A = 100 \text{ V}$ and $\beta = 80$. The quiescent load current, I_O , is $12.5 \mu\text{A}$. Answer the following questions:

- (a) Calculate R_E . [7 marks]
- (b) Find V_{BE2} . [5 marks]
- (c) Draw the small-signal equivalent circuit for the current source. [5 marks]
- (d) Determine the output resistance, R_O , of the current source. [8 marks]
- (e) Find the new load current if V_{C2} changes by 4 V . [5 marks]

Answers for Question 1

(a)

$$I_{REF} = \frac{V^+ - V_{BE(on)} - V^-}{R_1} = \frac{5 - 0.65 + 5}{8.6k} = 1.0872 \text{ mA}$$

[1, 1, 1]

$$I_O R_E = V_T \ln \left[\frac{I_{REF}}{I_O} \right]$$

[1]

$$R_E = \frac{V_T}{I_O} \ln \left[\frac{I_{REF}}{I_O} \right] = \frac{(0.026)}{(12.5\mu)} \ln \left[\frac{1.0872 \times 10^{-3}}{12.5 \times 10^{-6}} \right] = 9.2885 \text{ k}\Omega$$

[1, 1, 1]

(b)

$$I_E = \frac{(1 + \beta)}{\beta} I_C = \frac{(1 + 80)}{80} \times 12.5 \mu = 12.6562 \mu\text{A}$$

[1, 1, 0.5]

$$V_{BE2} = V_{BE1} - I_E R_E$$

[1]

$$V_{BE2} = 0.65 - (12.6562 \mu)(9.2885 \text{ k}) = 0.5324 \text{ V}$$

[1, 0.5]

(c)

✓✓ - Correct connections

✓ = 0.5 mark


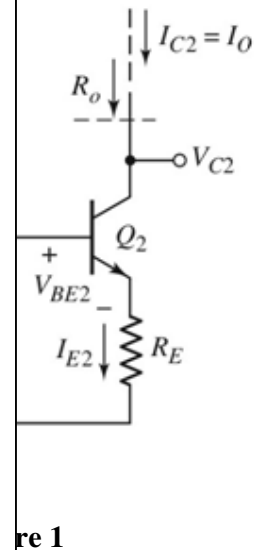


Figure 1

Answers for Question 1 (Cont.)

(d)

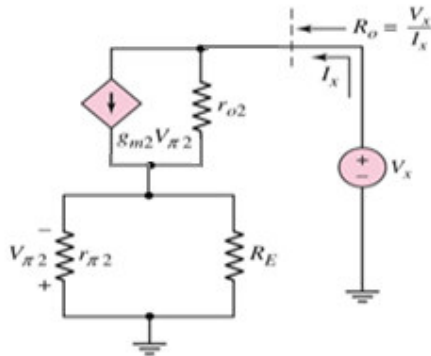

$$R'_E = R_E \parallel r_{\pi 2} \quad [0.5]$$

$$V_{\pi 2} = -I_x R'_E \quad [0.5]$$

$$V_x = r_{o2}(I_x - g_{m2}V_{\pi 2}) - V_{\pi 2}$$

$$V_x = I_x r_{o2} - I_x g_{m2} V_{\pi 2} - V_{\pi 2} \quad [0.5]$$

$$V_x = r_{o2} I_x + g_{m2} r_{o2} R'_E I_x + R'_E I_x \quad [0.5]$$

$$\frac{V_x}{I_x} = r_{o2} + g_{m2} r_{o2} R'_E + R'_E \cong r_{o2}(1 + g_{m2} R'_E) \quad [1]$$

$$R_O = r_{o2}(1 + g_{m2} R'_E)$$

$$r_{\pi 2} = \frac{\beta V_T}{I_O} = \frac{(80)(0.026)}{12.5\mu} = 166.4k\Omega \quad [1]$$

$$R'_E = (9.2885k) \parallel 166.4k = 8.797k\Omega \quad [1]$$

$$r_{o2} = \frac{V_A}{I_{C2}} = \frac{V_A}{I_O} = \frac{100}{12.5\mu} = 8M\Omega \quad [1]$$

$$g_{m2} = \frac{I_O}{V_T} = \frac{12.5\mu}{0.026} = 4.8077 \times 10^{-4} \quad [1]$$

$$R_O = (8M)[1 + (4.8077 \times 10^{-4})(8.797k)] = 41.83M\Omega \quad [1]$$

(e)

$$\frac{\Delta I_C}{\Delta V_{C2}} = \frac{1}{R_O} \quad [2]$$

$$\Delta I_O = \frac{\Delta V_{C2}}{R_O} = \frac{4}{41.83M} = 0.09563\mu A \quad [1, 0.5]$$

$$I_{O(\text{new})} = 12.5\mu A + 0.09563\mu A = 12.59563\mu A \quad [1, 0.5]$$

Question 2 [30 marks]

Refer to **Figure 2**. The circuit parameters are: $V^+ = 5\text{ V}$, $V^- = -5\text{ V}$, and $I_{REF} = 20\text{ }\mu\text{A}$. Let $K_n = 80\text{ }\mu\text{A/V}^2$, $V_{TN} = 1\text{ V}$, and $\lambda = 0.002\text{ V}^{-1}$ for **all transistors**.

- (a) **Find** the bias current, I_O . [2 marks]
- (b) **Determine** the gate-to-source voltage, V_{GS} , for each transistor. [5 marks]
- (c) **Calculate** the lowest possible value of V_{D4} . [5 marks]
- (d) **Draw** the ac equivalent circuit of the current source. [5 marks]
- (e) **Determine** the output resistance R_O looking into the drain of M_4 . [13 marks]

Answers for Question 2

(a) Assume all transistors are identical because parameters given are for **all transistors**.

$$I_O = I_{REF} = 20\text{ }\mu\text{A} \quad [2]$$

(b) $I_{REF} = K_n (V_{GS3} - V_{TN})^2 = K_n (V_{GS1} - V_{TN})^2$

$$I_O = I_{REF} = K_n (V_{GS2} - V_{TN})^2 = K_n (V_{GS4} - V_{TN})^2$$

Since $V_{GS1} = V_{GS2}$ and $V_{GS1} = V_{GS3}$,

$$\text{then } V_{GS1} = V_{GS2} = V_{GS3} = V_{GS4} = \sqrt{\frac{I_{REF}}{K_n}} + V_{TN} = \sqrt{\frac{20\mu\text{A}}{80\mu\text{A}}} + 1 = 1.5\text{V} \quad [5]$$

(c) $V_{D4}(\text{min}) = V^+ + V_{GS1} + V_{GS3} - V_{GS4} + V_{DS4}(\text{sat}) \quad [2]$

$$V_{D4}(\text{min}) = V^+ + V_{GS1} + V_{GS3} - V_{GS4} + (V_{GS4} - V_{TN}) \quad [1]$$

$$V_{D4}(\text{min}) = V^+ + 2V_{GS} - V_{TN} \quad [1]$$


$$= (-5) + 2(1.5) - 1 = -3\text{ V} \quad [1]$$

V^+

Figure 2

Answers for Question 2 (Cont.)


(d)

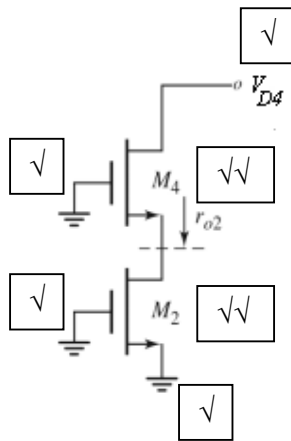

√√ - Correct connections

√ = 0.5 mark

(e)

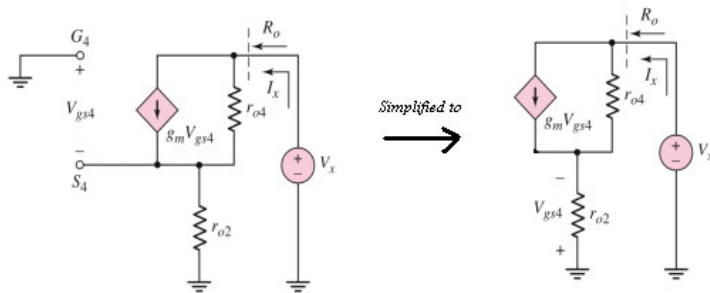

[1] for drawing

$$V_{gs4} = -I_x r_{o2}$$

[1]

$$V_x = (I_x - g_{m4} V_{gs4}) r_{o4} - V_{gs4}$$

[1]

$$V_x = I_x r_{o4} - g_{m4} V_{gs4} r_{o4} - V_{gs4}$$

[1]

$$V_x = I_x r_{o4} + g_{m4} I_x r_{o2} r_{o4} + I_x r_{o2}$$

[1]

$$R_O = \frac{V_x}{I_x} = r_{o4} + r_{o2}(1 + g_{m4} r_{o4}) \approx g_{m4} r_{o4} r_{o2}$$

[1, 1, 1]

$$r_{o4} = r_{o2} = 1/(\lambda I_D) = 1/(0.002 \times 20\mu) = 25 \text{ M}\Omega$$

[1, 1, 0.5]

$$g_{m4} = 2\sqrt{K_n I_D} = 2\sqrt{(80\mu)(20\mu)} = 80\mu\text{A/V}^2$$

[1, 0.5]

$$R_O = (80\mu)(25\text{M})(25\text{M}) = 50000 \text{ M}\Omega$$

[0.5, 0.5]

Question 3 [40 marks]

- (a) **Figure 3a** shows a circuit diagram for a BJT differential amplifier (**diff-amp**). Study the circuit diagram carefully. Transistor parameters are: $\beta = \infty$ (neglect base current), $V_A = \infty$, and $V_{BE(on)} = 0.7 \text{ V}$. For the circuit also, voltages measured at v_{C1} and v_{C2} are **+3.5 V**.
- (i) **What** are the values for v_{cm} and v_d ? Show clearly your calculations. [5 marks]
- (ii) Find I_Q . [5 marks]
- (iii) Find v_{CE1} . [5 marks]
- (iv) **Determine** the differential mode voltage gain (A_d) for a one-sided output taken at v_{C2} . [5 marks]

Answers for Question 3a

<p>(i)</p> <p>$v_{B1} = v_{B2} = 0.3 \text{ V}$ [1, 1]</p> <p>$v_{cm} = (v_{B1} + v_{B2}) / 2 = (0.3 + 0.3) / 2 = 0.3 \text{ V}$ [1, 0.5]</p> <p>$v_d = (v_{B1} - v_{B2}) = (0.3 - 0.3) = 0 \text{ V}$ [1, 0.5]</p> <p>(ii)</p> <p>$I_{RC} = [(+10) - v_{C1}] / R_C = [(+10) - v_{C2}] / R_C$ [1]</p> <p>$= [(+10) - 3.5] / (10\text{k}) = 0.65 \text{ mA}$ [0.5, 0.5]</p> <p>$I_Q = 2 I_{RC} = 2 (0.65\text{m}) = 1.3 \text{ mA}$ [2, 1]</p> <p>(iii)</p> <p>$v_{CE1} = v_{C1} - v_{E1}$ [1.5]</p> <p>$= v_{C1} - (v_{B1} - v_{BE1})$ [1.5]</p> <p>$= 3.5 - (0.3 - 0.7) = 3.9 \text{ V}$ [2]</p> <p>(iv)</p> <p>$A_d = (g_{m2} R_C) / 2 = (I_Q R_C) / (4 V_T)$ [2]</p> <p>$g_{m2} = I_{C2} / V_T = I_Q / 2 V_T$ [1]</p> <p>$= (1.3\text{m}) / (2 \times 26\text{m}) = 0.025 \text{ A/V}$ [1]</p> <p>$A_d = (0.025 \times 10\text{k}) / 2 = 125$ [1]</p>	<p>Figure 3a</p>
---	------------------

- (b) The BJT differential amplifier shown in **Figure 3b** is biased by a **0.20 mA** constant current source (i.e. $I_Q = 0.20 \text{ mA}$). It is to be redesigned to use an active load in order to increase its differential-mode voltage gain (A_d). The active load to be used is a **BJT cascode current source** using **pnp transistors** to replace the collector resistors (R_C) in the differential amplifier, as graphically shown in **Figure 3b**.

The transistor parameters are $\beta = 150$, $V_{BE(\text{on})} = V_{EB(\text{on})} = 0.7 \text{ V}$, $V_{AN} = 120 \text{ V}$, and $V_{AP} = 100 \text{ V}$. The one-sided output voltage taken at v_{C2} can be calculated using **Equation (1)**:

$$v_O = v_{C2} = g_{m2} v_d (r_{O2} \parallel R_{OAL}) \quad (1)$$

where R_{OAL} is the output resistance of the **BJT cascode current source**.

- (i) **Draw the new circuit** incorporating the **active load's full circuit diagram**. Label the circuit correctly and clearly with appropriate symbols and numbering for transistors used in circuit. Leave I_Q symbol as it is in **Figure 3b**. [10 marks]
- (ii) **Find** the output resistance of the **BJT cascode current source** (R_{OAL}). [5 marks]
- (iii) **Determine** the differential-mode voltage gain (A_d) of **the new circuit**. [5 marks]


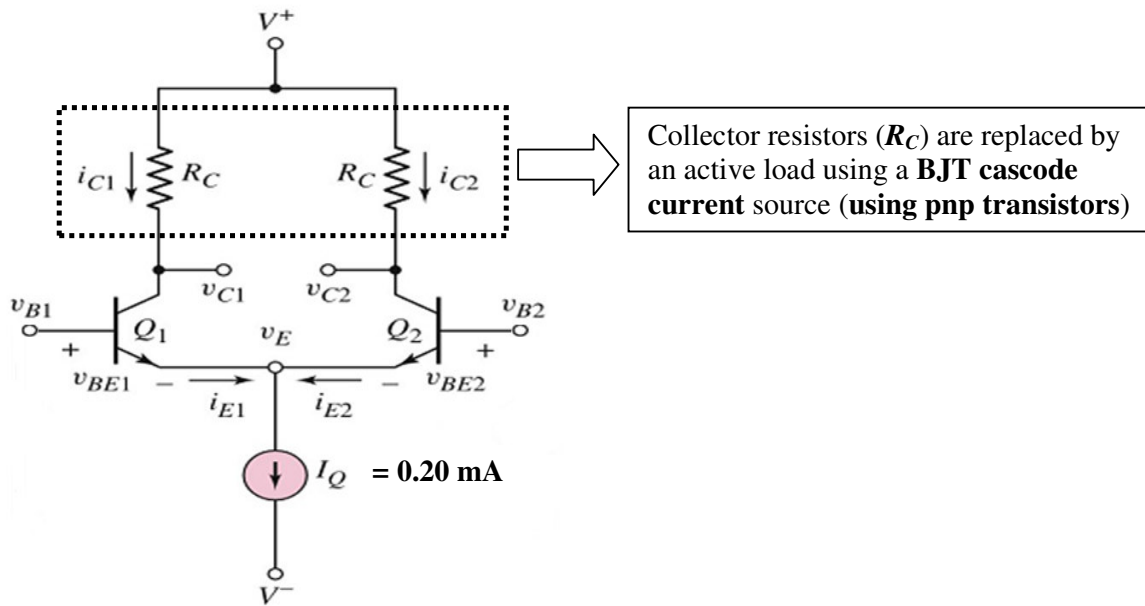


Figure 3b

Answers for Question 3b

Answers for Question 3b (Cont.)

(i)

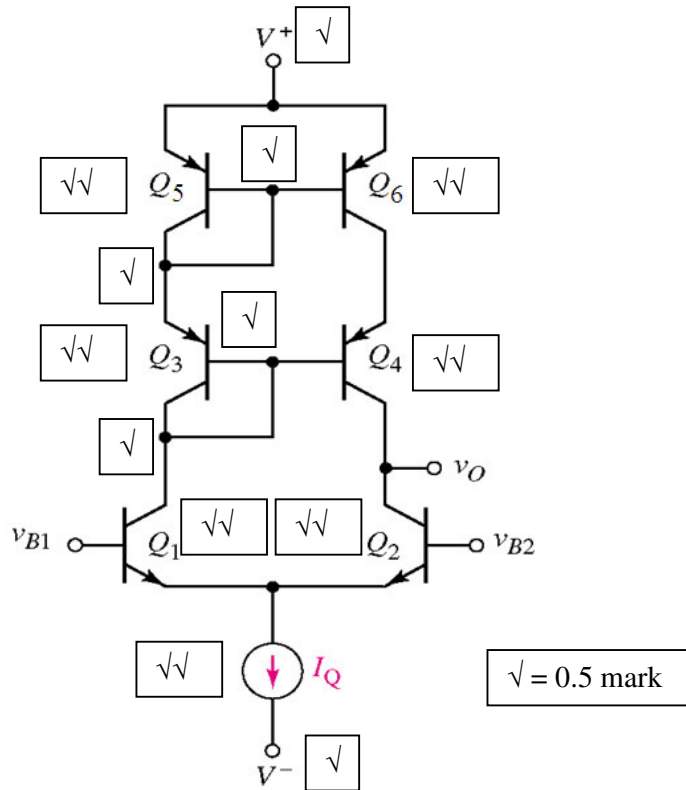

(ii)

$$\begin{aligned}
 R_{OAL} &\approx \beta r_{O4} && [2] \\
 &= \beta (V_{A4} / I_{C4}) = (\beta V_{AP}) / (I_Q / 2) && [2] \\
 &= (150 \times 100) / (0.20\text{m} / 2) = 150 \text{ M}\Omega && [1]
 \end{aligned}$$

(iii)

$$\begin{aligned}
 v_O &= v_{C2} = g_{m2} v_d (r_{O2} \parallel R_{OAL}) \\
 A_d &= v_O / v_d = g_{m2} (r_{O2} \parallel R_{OAL}) && [1]
 \end{aligned}$$

$$\begin{aligned}
 g_{m2} &= I_{CQ2} / V_T = I_Q / 2V_T && [1] \\
 &= (0.20\text{m}) / (2 \times 26\text{m}) = 3.846 \text{ mA/V} && [0.5]
 \end{aligned}$$

$$\begin{aligned}
 r_{O2} &= V_{A2} / I_{C2} = (V_{AN}) / (I_Q / 2) && [1] \\
 &= (120) / (0.20\text{m} / 2) = 1.2 \text{ M}\Omega && [0.5]
 \end{aligned}$$

$$r_{O2} \parallel R_{OAL} = 1.2\text{M} \parallel 150\text{M} = 1.19 \text{ M}\Omega \approx r_{O2}$$

$$\begin{aligned}
 A_d &= (3.846\text{m})(1.2\text{M} \parallel 150\text{M}) \\
 &= 4578.57 && [1]
 \end{aligned}$$

Appendix: BASIC FORMULA

BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2K_n (V_{GSQ} - V_{TN}) = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$