

EEEE273 - Quiz 3 [Question Set 1]
 SEMESTER 3, ACADEMIC YEAR 2011/2012
 Date: 14 March 2012

Question:

Refer to **Figure 1**. Transistors are matched with $K_n = 0.1 \text{ mA/V}^2$, $\lambda = 0$ and $V_{TN} = 1 \text{ V}$. Given that $R_D = 16 \text{ k}\Omega$ and $I_Q = 0.6 \text{ mA}$. Find the **one-sided output voltage** (V_o) taken at V_{D2} of the differential amplifier when $v_1 = 0.10 \text{ V}$ and $v_2 = 0.15 \text{ V}$. [10 marks]

Hints: You need to find A_d and v_d first.

Answer:

I_{D2}	$= I_Q/2 = (0.6\text{m})/2 = 0.3 \text{ mA}$	[1, 1]
g_{m2}	$= 2 \text{ SQRT}(K_n I_{D2})$	[1]
	$= 2 \text{ SQRT}(0.1\text{m} \times 0.3\text{m}) = 0.3464 \text{ mA/V}$	[1]
A_d	$= (g_{m2} R_D)/2$	[2]
	$= (0.3464\text{m} \times 16\text{k})/2 = 2.77 \text{ V/V}$	[1]
A_d	$= V_o / v_d = V_o / (v_1 - v_2)$	[1]
V_o	$= A_d (v_1 - v_2)$	[1]
	$= (2.77)(0.10 - 0.15) = -0.1385 \text{ V}$	[1]

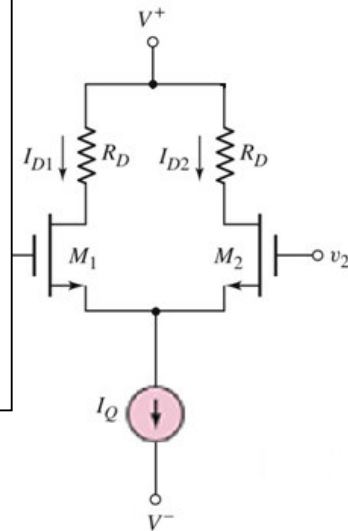


Figure 1

Question:

Refer to **Figure 1**. Transistors are matched with $K_n = 0.1 \text{ mA/V}^2$, $\lambda = 0$ and $V_{TN} = 1 \text{ V}$. Given that $R_D = 18 \text{ k}\Omega$ and $I_Q = 0.62 \text{ mA}$. Find the **one-sided output voltage** (V_o) taken at V_{D2} of the differential amplifier when $v_1 = 0.15 \text{ V}$ and $v_2 = 0.10 \text{ V}$. [10 marks]

Hints: You need to find A_d and v_d first.

Answer:

I_{D2}	$= I_Q/2 = (0.62\text{m})/2 = 0.31 \text{ mA}$	[1, 1]
g_{m2}	$= 2 \text{ SQRT}(K_n I_{D2})$	[1]
	$= 2 \text{ SQRT}(0.1\text{m} \times 0.31\text{m}) = 0.3521 \text{ mA/V}$	[1]
A_d	$= (g_{m2} R_D)/2$	[2]
	$= (0.3521\text{m} \times 18\text{k})/2 = 3.169 \text{ V/V}$	[1]
A_d	$= V_o/v_d = V_o/(v_1 - v_2)$	[1]
V_o	$= A_d (v_1 - v_2)$	[1]
	$= (3.169)(0.15 - 0.10) = 0.1584 \text{ V}$	[1]

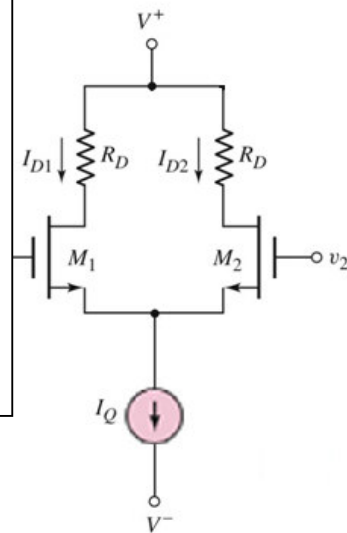


Figure 1

Question:

Refer to **Figure 1**. Transistors are matched with $K_n = 0.1 \text{ mA/V}^2$, $\lambda = 0$ and $V_{TN} = 1 \text{ V}$. Given that $R_D = 16 \text{ k}\Omega$ and $I_Q = 0.62 \text{ mA}$. Find the **one-sided output voltage** (V_o) taken at V_{D2} of the differential amplifier when $v_1 = 0.15 \text{ V}$ and $v_2 = 0.10 \text{ V}$. [10 marks]

Hints: You need to find A_d and v_d first.

Answer:

I_{D2}	$= I_Q/2 = (0.62\text{m})/2 = 0.31 \text{ mA}$	[1, 1]
g_{m2}	$= 2 \text{ SQRT}(K_n I_{D2})$	[1]
	$= 2 \text{ SQRT}(0.1\text{m} \times 0.31\text{m}) = 0.3521 \text{ mA/V}$	[1]
A_d	$= (g_{m2} R_D)/2$	[2]
	$= (0.3521\text{m} \times 16\text{k})/2 = 2.816 \text{ V/V}$	[1]
A_d	$= V_o / v_d = V_o / (v_1 - v_2)$	[1]
V_o	$= A_d (v_1 - v_2)$	[1]
	$= (2.816)(0.15 - 0.10) = 0.1408 \text{ V}$	[1]

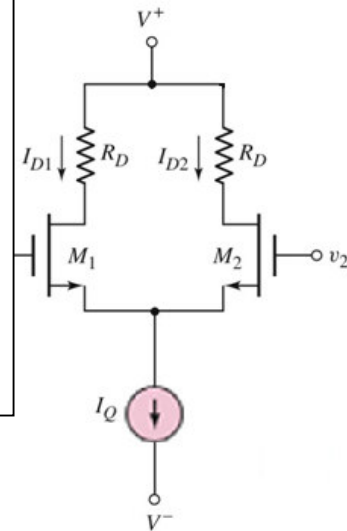


Figure 1

Question:

Refer to **Figure 1**. Transistors are matched with $K_n = 0.1 \text{ mA/V}^2$, $\lambda = 0$ and $V_{TN} = 1 \text{ V}$. Given that $R_D = 18 \text{ k}\Omega$ and $I_Q = 0.6 \text{ mA}$. Find the **one-sided output voltage** (V_o) taken at V_{D2} of the differential amplifier when $v_1 = 0.10 \text{ V}$ and $v_2 = 0.13 \text{ V}$. [10 marks]

Hints: You need to find A_d and v_d first.

Answer:

I_{D2}	$= I_Q/2 = (0.6\text{m})/2 = 0.3 \text{ mA}$	[1, 1]
g_{m2}	$= 2 \text{ SQRT}(K_n I_{D2})$	[1]
	$= 2 \text{ SQRT}(0.1\text{m} \times 0.3\text{m}) = 0.3464 \text{ mA/V}$	[1]
A_d	$= (g_{m2} R_D)/2$	[2]
	$= (0.3464\text{m} \times 18\text{k})/2 = 3.117 \text{ V/V}$	[1]
A_d	$= V_o / v_d = V_o / (v_1 - v_2)$	[1]
V_o	$= A_d (v_1 - v_2)$	[1]
	$= (3.117)(0.10 - 0.13) = -0.0935 \text{ V}$	[1]

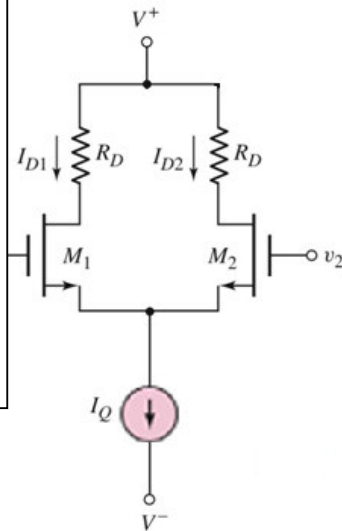


Figure 1