

EEEE273 - Quiz 4 [Question Set 1]  
 SEMESTER 3, ACADEMIC YEAR 2011/2012  
 Date: 28 March 2012


**Question:**

Referring to **Figure 1**, let  $R_L = 1 \text{ k}\Omega$ ,  $V_{BB} = 1.40 \text{ V}$ ,  $V_{CC} = 6 \text{ V}$  and the reverse saturation current for the transistors,  $I_S = 2 \times 10^{-15} \text{ A}$ . Assume  $\beta \gg 1$ .

For the case of the output voltage  $v_O = -3 \text{ V}$ , determine  $i_L$ ,  $i_{Cp}$ , and  $i_{Cn}$ . [10 marks]

**Answer:**

$v_O = i_L R_L = -3\text{V}$	[1]
$i_L = v_O / R_L$	[1]
$= (-3\text{V}) / (1\text{k}\Omega) = -3 \text{ mA}$	[1]
Therefore, $Q_p$ is conducting and $Q_n$ is OFF.	
$i_L \approx i_{Cp} = I_S \exp(V_{EBP} / V_T)$	[1]
$V_{EBP} = V_T \ln(i_{Cp} / I_S)$	[0.5]
$= 26\text{m} \ln(3\text{m} / 2 \times 10^{-15})$	[0.5]
$= 0.7289 \text{ V}$	[0.5]
$V_{BEN} = V_{BB} - V_{EBP}$	[1]
$= 1.4 - 0.7289 = 0.6711 \text{ V}$	[0.5]
$i_{Cn} = I_S \exp(V_{BEN} / V_T)$	[1]
$= 2 \times 10^{-15} \exp(0.6711 / 26\text{m})$	[0.5]
$= 324.22 \mu\text{A}$	[0.5]
$i_{Cn} = i_{Cp} + i_L$	[1]
Actual value of $i_{Cp} = i_{Cn} - i_L$	[1]
$i_{Cp} = 324.22\mu - (-3\text{m})$	[1]
$= 3.324 \text{ mA}$	[1]

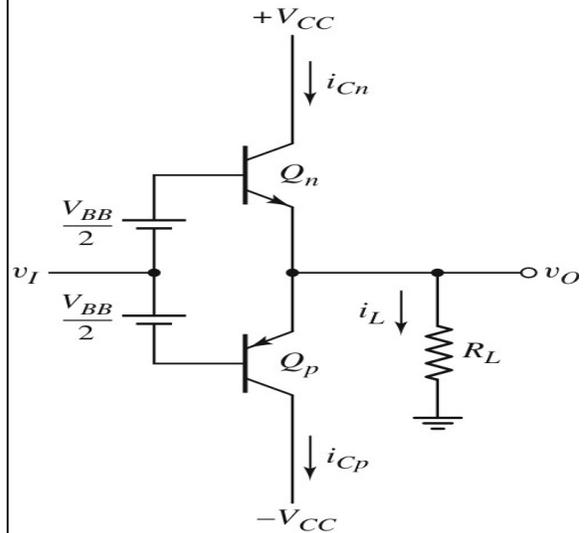

**Figure 1**

EEEE273 - Quiz 4 [Question Set 2]  
 SEMESTER 3, ACADEMIC YEAR 2011/2012  
 Date: 28 March 2012


**Question:**

Referring to **Figure 1**, let  $R_L = 1.2 \text{ k}\Omega$ ,  $V_{BB} = 1.50 \text{ V}$ ,  $V_{CC} = 6 \text{ V}$  and the reverse saturation current for the transistors,  $I_S = 2 \times 10^{-15} \text{ A}$ . Assume  $\beta \gg 1$ .

For the case of the output voltage  $v_O = -3 \text{ V}$ , determine  $i_L$ ,  $i_{Cp}$ , and  $i_{Cn}$ . [10 marks]

**Answer:**

$v_O = i_L R_L = -3\text{V}$	[1]
$i_L = v_O / R_L$	[1]
$= (-3\text{V}) / (1.2\text{k}\Omega) = -2.5 \text{ mA}$	[1]
Therefore, $Q_p$ is conducting and $Q_n$ is OFF.	
$i_L \approx i_{Cp} = I_S \exp(V_{EBP} / V_T)$	[1]
$V_{EBP} = V_T \ln(i_{Cp} / I_S)$	[0.5]
$= 26\text{m} \ln(2.5\text{m} / 2 \times 10^{-15})$	[0.5]
$= 0.7242 \text{ V}$	[0.5]
$V_{BEN} = V_{BB} - V_{EBP}$	[1]
$= 1.5 - 0.7242 = 0.7758 \text{ V}$	[0.5]
$i_{Cn} = I_S \exp(V_{BEN} / V_T)$	[1]
$= 2 \times 10^{-15} \exp(0.7758 / 26\text{m})$	[0.5]
$= 18.184 \text{ mA}$	[0.5]
$i_{Cn} = i_{Cp} + i_L$	[1]
Actual value of $i_{Cp} = i_{Cn} - i_L$	[1]
$i_{Cp} = 18.184\text{m} - (-2.5\text{m})$	[1]
$= 20.684 \text{ mA}$	[1]

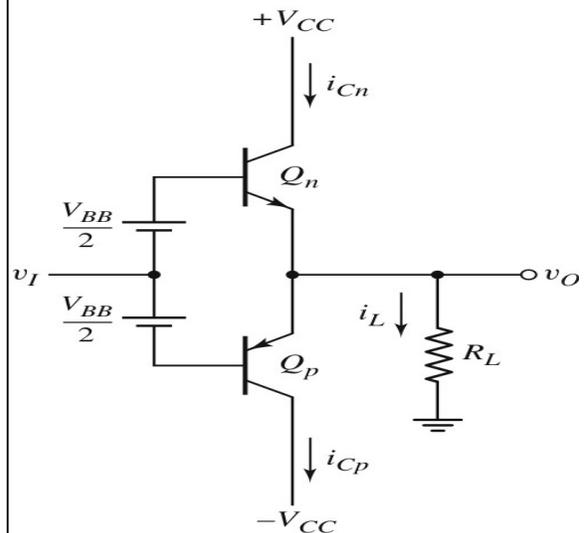

**Figure 1**

EEEB273 - Quiz 4 [Question Set 3]  
 SEMESTER 3, ACADEMIC YEAR 2011/2012  
 Date: 28 March 2012


**Question:**

Referring to **Figure 1**, let  $R_L = 1 \text{ k}\Omega$ ,  $V_{BB} = 1.50 \text{ V}$ ,  $V_{CC} = 8 \text{ V}$  and the reverse saturation current for the transistors,  $I_S = 2 \times 10^{-15} \text{ A}$ . Assume  $\beta \gg 1$ .

For the case of the output voltage  $v_O = -4 \text{ V}$ , determine  $i_L$ ,  $i_{Cp}$ , and  $i_{Cn}$ . [10 marks]

**Answer:**

$v_O = i_L R_L = -4\text{V}$	[1]
$i_L = v_O / R_L$	[1]
$= (-4\text{V}) / (1\text{k}\Omega) = -4 \text{ mA}$	[1]
Therefore, $Q_p$ is conducting and $Q_n$ is OFF.	
$i_L \approx i_{Cp} = I_S \exp(V_{EBP} / V_T)$	[1]
$V_{EBP} = V_T \ln(i_{Cp} / I_S)$	[0.5]
$= 26\text{m} \ln(4\text{m} / 2 \times 10^{-15})$	
$= 0.7364 \text{ V}$	[0.5]
$V_{BEN} = V_{BB} - V_{EBP}$	[1]
$= 1.5 - 0.7364 = 0.7636 \text{ V}$	[0.5]
$i_{Cn} = I_S \exp(V_{BEN} / V_T)$	[1]
$= 2 \times 10^{-15} \exp(0.7636 / 26\text{m})$	
$= 11.374 \text{ mA}$	[0.5]
$i_{Cn} = i_{Cp} + i_L$	
Actual value of $i_{Cp} = i_{Cn} - i_L$	[1]
$i_{Cp} = 11.374\text{m} - (-4\text{m})$	
$= 15.374 \text{ mA}$	[1]

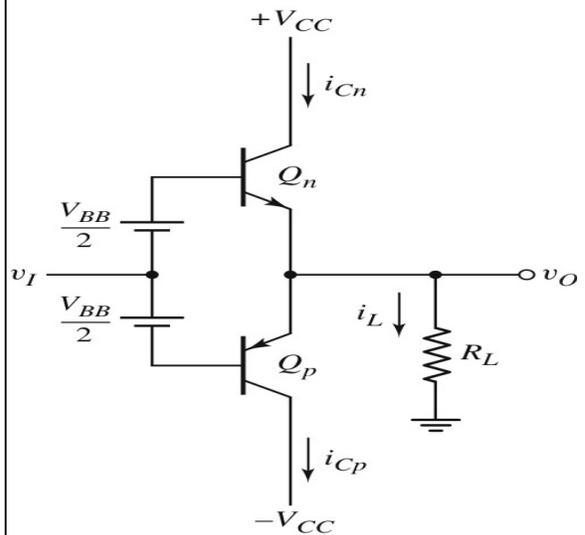

**Figure 1**

EEEE273 - Quiz 4 [Question Set 4]  
 SEMESTER 3, ACADEMIC YEAR 2011/2012  
 Date: 28 March 2012


**Question:**

Referring to **Figure 1**, let  $R_L = 1.8 \text{ k}\Omega$ ,  $V_{BB} = 1.40 \text{ V}$ ,  $V_{CC} = 8 \text{ V}$  and the reverse saturation current for the transistors,  $I_S = 2 \times 10^{-15} \text{ A}$ . Assume  $\beta \gg 1$ .

For the case of the output voltage  $v_O = -4.8 \text{ V}$ , determine  $i_L$ ,  $i_{Cp}$ , and  $i_{Cn}$ . [10 marks]

**Answer:**

$v_O = i_L R_L = -4.8\text{V}$	[1]
$i_L = v_O / R_L$	[1]
$= (-4.8\text{V}) / (1.8\text{k}\Omega) = -2.667 \text{ mA}$	[1]
Therefore, $Q_p$ is conducting and $Q_n$ is OFF.	
$i_L \approx i_{Cp} = I_S \exp(V_{EBP} / V_T)$	[1]
$V_{EBP} = V_T \ln(i_{Cp} / I_S)$	[0.5]
$= 26\text{m} \ln(2.667\text{m} / 2 \times 10^{-15})$	
$= 0.7259 \text{ V}$	[0.5]
$V_{BEN} = V_{BB} - V_{EBP}$	[1]
$= 1.4 - 0.7259 = 0.6741 \text{ V}$	[0.5]
$i_{Cn} = I_S \exp(V_{BEN} / V_T)$	[1]
$= 2 \times 10^{-15} \exp(0.6741 / 26\text{m})$	
$= 363.87 \mu\text{A}$	[0.5]
$i_{Cn} = i_{Cp} + i_L$	
Actual value of $i_{Cp} = i_{Cn} - i_L$	[1]
$i_{Cp} = 363.87\mu - (-2.667\text{m})$	
$= 3.030 \text{ mA}$	[1]

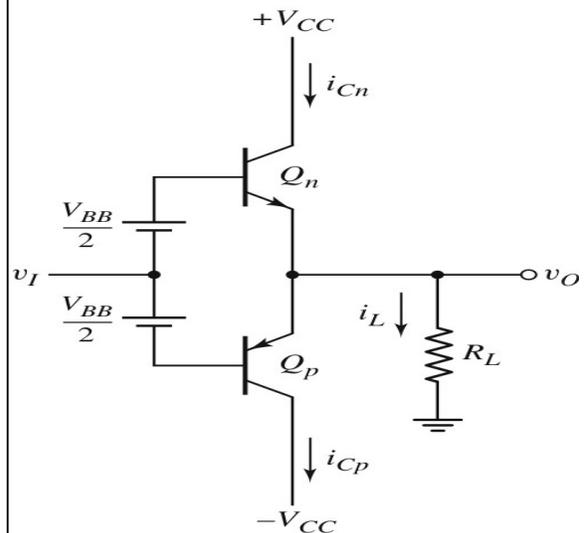

**Figure 1**