

FINAL EXAM, SEMESTER 1 2012/2013

Answer: Question 1

(a)

$$I_o R_E = V_T \ln\left(\frac{I_{REF}}{I_o}\right) \quad \boxed{0.5}$$

$$I_{REF} = I_o e^{\frac{I_o R_E}{V_T}} = (20\mu)(e^{(20\mu)(4.2k)/0.026}) = 0.506 \text{ mA} \quad \boxed{2}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{REF}}{I_{S1}}\right) = 0.026 \ln\left(\frac{0.506\text{m}}{4 \times 10^{-15}}\right) = 0.6646 \text{ V} \quad \boxed{1.5}$$

$$I_{REF} R_1 = V^+ - V_{BE1} \quad \boxed{0.5}$$

$$R_1 = \frac{V^+ - V_{BE1}}{I_{REF}} = \frac{10 - 0.6646}{0.506\text{m}} = 18.45 \text{ k}\Omega \quad \boxed{1.5}$$

$$V_{BE2} = V_{BE1} - I_o R_E = 0.6646 - (20\mu)(4.2k) = 0.5806 \text{ V} \quad \boxed{2}$$

(b)

At $I_o = I_{REF}$:

$$V_{GS2} = V_{GS1} = V_{DS1} \Rightarrow V_{DS1} = V_{DS2} \quad \boxed{0.5}$$

$$V_{GS3} = V_{DS3} = V_{GS1} \\ \Rightarrow V_{DS4} = V_{DS3} = V_{DS2} \quad \boxed{1}$$

$$V_{D4} = V^- + V_{DS2} + V_{DS4} = -5 + 1.8 + 1.8 = -1.4 \text{ V} \quad \boxed{1.5}$$

$$dV_{D4} = 2.5 - (-1.4) = 3.9 \text{ V} \quad \boxed{1}$$

$$r_{O4} = r_{O2} = \frac{1}{\lambda I_o} = \frac{1}{(0.025)(200\mu)} = 200 \text{ k}\Omega \quad \boxed{1}$$

$$dI_o = \frac{dV_{D4}}{R_o} = \frac{(dV_{D4})}{(g_m r_{O4} r_{O2})} = \frac{(3.9)}{(300\mu)(200k)(200k)} = 0.325 \mu\text{A} \quad \boxed{1.5}$$

$$I_{O(new)} = I_o + dI_o = (200 + 0.325)\mu\text{A} = 200.325 \mu\text{A} \quad \boxed{1.5}$$

Answer: Question 2

(a)

- i) Calculate the one-sided small-signal differential voltage gain (A_d) of the differential amplifier. [1.5 marks]

$$A_d = \frac{g_m R_C}{2} \quad \boxed{0.5}$$

$$g_m = \frac{I_C}{V_T} = \frac{I_Q}{2V_T} = \frac{2\text{m}}{2(26\text{m})} = 38.46 \text{ mA/V} \quad \boxed{0.5}$$

$$A_d = \frac{(38.46\text{m})(5\text{k})}{2} = 96.15 \quad \boxed{0.5}$$

- ii) The constant current source of Figure 1 that is providing the current I_Q is implemented using the basic two transistor current source. Find the value of A_{cm} , the common-mode voltage gain of the differential-amplifier, with equation given below. Assume $R_B = 0$. [2 marks]

$$R_o(2\text{TCS}) = r_o = \frac{V_A}{I_Q} = \frac{100}{2\text{m}} = 50 \text{ k}\Omega \quad \boxed{1}$$

$$r_\pi = \frac{\beta V_T}{I_C} = \frac{100(26\text{m})}{1\text{m}} = 2.6 \text{ k}\Omega \quad \boxed{0.5}$$

$$A_{cm} = -49.5 \times 10^{-3} \quad \boxed{0.5}$$

- iii) The input voltages for the differential amplifier are $v_{B1} = 210 \times 10^{-6} \sin \omega t$ V and $v_{B2} = 190 \times 10^{-6} \sin \omega t$ V. Calculate the output voltage of the differential amplifier, taking into account the effect of the non-ideal current source. Use values from previous calculations. What is the output voltage if an ideal current source is used instead? Justify your answer. [4 marks]

$$V_o = A_d V_d + A_{cm} V_{cm} \quad \boxed{1}$$

$$V_d = v_{B1} - v_{B2} = (210 \times 10^{-6} - 190 \times 10^{-6}) \sin \omega t \text{ V} = 20 \times 10^{-6} \sin \omega t \text{ V} \quad \boxed{0.5}$$

$$V_{cm} = (v_{B1} + v_{B2}) / 2 = [(210 \times 10^{-6} + 190 \times 10^{-6}) \sin \omega t \text{ V}] / 2 = 200 \times 10^{-6} \sin \omega t \text{ V} \quad \boxed{0.5}$$

$$V_o = [(96.15)(20 \times 10^{-6}) + (-49.5 \times 10^{-3})(200 \times 10^{-6})] \sin \omega t \text{ V} = 1.914 \times 10^{-3} \sin \omega t \text{ V} \quad \boxed{0.5}$$

For Ideal current source, its R_o is infinite, hence A_{cm} is zero [0.5 mark]

Thus, $V_o = A_d V_d$ [0.5 mark]

$$V_o = (96.15)(20 \times 10^{-6}) \sin \omega t \text{ V} = 1.923 \times 10^{-3} \sin \omega t \text{ V} \quad \boxed{0.5 \text{ mark}}$$

iv) Calculate the value of V_{cm} (max) of this differential amplifier. [4.5 marks]

$$\begin{aligned}
 &V_{cm}(\max) = V_B \text{ when } Q1, Q2 \text{ almost entering saturation mode,} \\
 \text{i.e. } &V_{CE} = V_{CE}(\text{sat}) = 0.3V \quad [0.5 \text{ mark}] \\
 &V_{CE} = V_C - V_E \quad [0.5 \text{ mark}] \\
 &V_C = V^+ - I_{C3}R_C = 15 - (1\text{m})(5\text{k}) = 10V \quad [1 \text{ mark}] \\
 &V_E = V_B - V_{BE}(\text{on}) = V_B - 0.7V \quad [1 \text{ mark}] \\
 &V_{CE}(\text{sat}) = 0.3V = 10 - (V_{cm}(\max) - 0.7) \quad [1 \text{ mark}] \\
 &V_{cm}(\max) = 10.7 - 0.3 = 10.4V \quad [0.5 \text{ mark}]
 \end{aligned}$$

Answer: Question 2

(b)

- Determine the relationship between I_O and I_Q such that the amplifier dc currents are balanced. [3 marks]
- Calculate the value of I_O given that $I_Q = 0.2 \text{ mA}$ and $\beta = 100$. [1 mark]

$$I_{B5} = \frac{I_{E5}}{(1 + \beta)} = \frac{I_{B3} + I_{B4}}{(1 + \beta)} = \frac{I_{C3} + I_{C4}}{\beta(1 + \beta)} \quad [1 \text{ mark}]$$

$$\text{The current } I_{C3} + I_{C4} \cong I_Q \quad [0.5 \text{ mark}]$$

$$\left. \begin{aligned}
 I_{C1} &= I_{C3} + I_{B5} \\
 I_{C1} &= I_{C4} + I_O
 \end{aligned} \right\} \quad [0.5 \text{ mark}]$$

$$\text{Hence, to keep the current balanced: } I_O = I_{B5} = \frac{I_Q}{\beta(1 + \beta)} \quad [1 \text{ mark}]$$

Given, $I_Q = 0.2 \text{ mA}$, hence:

$$I_O = \frac{0.2 \text{ m}}{100(1 + 100)} = 19.8 \text{ nA} \quad [1 \text{ mark}]$$

Answer: Question 3

(a) $V_{GS5} = V_{GS7}$ {Identical transistors} [0.5]
 $V_{GS5} + V_{GS7} = 2 V_{GS5} = V^+ - V^- = 10 - (-10) = 20 \text{ V}$ [0.5]
 $V_{GS5} = 10 \text{ V} = V_{GS7}$ [0.5]
 $I_1 = K_n (V_{GS5} - V_{TN})^2 = K_n (V_{GS7} - V_{TN})^2$ [1]
 $I_1 = (0.2 \text{ m})(10 - 2)^2 = 12.8 \text{ mA}$ [0.5]
 $I_Q = I_1 = 12.8 \text{ mA}$ [1]
 $I_{D1} = \frac{1}{2} I_Q = 6.4 \text{ mA}$ [1]

(b) $v_o = (g_m)v_d(r_{o2} \parallel r_{o4} \parallel R_L)$ therefore $A_d = (g_m)(r_{o2} \parallel r_{o4} \parallel R_L)$ [1.5]

$g_m = 2\sqrt{(K_n I_{D1})} = 2\sqrt{[(0.2 \text{ m})(6.4 \text{ m})]} = 2.26 \text{ mA/V}$ [1]

$r_{o2} = 1/(\lambda_n I_{D1}) = 1/(0.02)(6.4 \text{ m}) = 7.812 \text{ k}\Omega$ [1]

$r_{o4} = 1/(\lambda_p I_{D1}) = 1/(0.015)(6.4 \text{ m}) = 10.417 \text{ k}\Omega$ [1]

$(r_{o2} \parallel r_{o4} \parallel R_L) = (7.812 \text{ k}) \parallel (10.417 \text{ k}) \parallel (100 \text{ k}) = 4.273 \text{ k}\Omega$ [0.5]

$A_d = (2.26 \text{ mA/V}) \times (4.273 \text{ k}\Omega) = 9.668$ [1]

(c) $CMRR = 20 \log [A_d / A_{cm}] = 60 \text{ dB}$ [1, 0.5]
 $A_{cm} = A_d / [10^{60/20}] = 9.668 \times 10^{-3}$ [1, 0.5]

(d) Select two answers:

Increase the current source output resistance. [1]

Increase the diff amp output resistance by using cascode active loads. [1]

Reduce the loading effect by increasing load resistance, R_L . [1]

Answer: Question 4

(a) Q3 and Q4 are lateral pnp devices which provide additional protection against voltage breakdown. This is because the breakdown voltage of a lateral pnp B-E junctions is a lot higher than the reverse biased npn B-E junction.

2

(b)

$$I_{C10} = I_S e^{\frac{V_{BE10}}{V_T}}$$

0.5

$$V_{BE10} = V_T \ln\left(\frac{I_{C10}}{I_S}\right) = 0.026 \ln\left(\frac{10\mu}{1 \times 10^{-14}}\right) = 0.5388 \text{ V}$$

1.5

$$I_{C10} R_4 = V_{BE11} - V_{BE10}$$

0.5

$$R_4 = \frac{V_{BE11} - V_{BE10}}{I_{C10}} = \frac{0.6 - 0.5388}{10\mu} = 6.12 \text{ k}\Omega$$

1.5

(c)

$$r_{\pi 6} = \frac{\beta V_T}{I_{C6}} = \frac{200(0.026)}{5\mu} = 1.04 \text{ M}\Omega$$

2

(d)

$$R_O = r_{O4} \parallel R_{act1}$$

1

$$r_{O4} = \frac{V_A}{I_{C4}} = \frac{50}{5\mu} = 10 \text{ M}\Omega$$

1.5

$$R_{act1} = r_{O6} [1 + g_{m6} (R_2 \parallel r_{\pi 6})]$$

1

$$r_{O6} = r_{O4} = \frac{V_A}{I_{C6}} = \frac{50}{5\mu} = 10 \text{ M}\Omega$$

1

$$r_{\pi 6} = 1.040 \text{ M}\Omega$$

0.5

$$g_{m6} = \frac{I_{C6}}{V_T} = \frac{5\mu}{0.026} = 0.1923 \text{ mA/V}^2$$

1

$$R_{act1} = 10 \text{ M} [1 + (0.1923 \text{ m})(1 \text{ k})] = 10.92 \text{ M}\Omega$$

1

$$R_O = 10 \text{ M} \parallel 10.92 \text{ M} = 5.220 \text{ M}\Omega$$

1

Answer: Question 5

- a) State the main disadvantage of both Class A and Class B output stages. Comment on the power conversion efficiency of both output stages. [2 marks]

Disadvantage of class A is that the power conversion efficiency is low, [0.5 mark]
the maximum attainable efficiency is only 25% [0.5 mark]

The disadvantage of Class B is that it suffers from cross-over distortion [0.5 mark]
although the efficiency can be up to 78.5% [0.5 mark]

b) .

- i) Find the minimum required I_Q and the value of R. [4 marks]

$$I_{Qmin} = |\text{most negative } I_L| = |v_{omin}/R_L| \quad [1 \text{ mark}]$$
$$= |-8V/1k\Omega| = 8 \text{ mA} \quad [1 \text{ mark}]$$

$$R = (V_+ - V_{BE3(on)} - V_-) / I_Q \quad [1 \text{ mark}]$$
$$= (10 - 0.7 - (-10))/8m = 2.41 \text{ k}\Omega \quad [1 \text{ mark}]$$

- ii) For $v_o = 0$, find the power dissipated in the transistor Q_1 , and the power dissipated in the current source (Q_2 , Q_3 , and R). [5 marks]

$$P_{Q1} = (I_{C1})(V_{CE1}) \quad [1 \text{ mark}]$$
$$= (I_Q)(V_{C1} - V_{E1}) = (8m)(10 - 0) = 80 \text{ mW} \quad [1 \text{ mark}]$$

$$P_{Q2} = (I_{C2})(V_{CE2})$$
$$= (I_Q)(V_{C2} - V_{E2}) = (8m)(0 - (-10)) = 80 \text{ mW} \quad [1 \text{ mark}]$$

$$P_{Q3} = (I_{C3})(V_{CE3})$$
$$= (I_Q)(V_{BE(on)}) = (8m)(0.7) = 5.6 \text{ mW} \quad [1 \text{ mark}]$$

$$P_{Resistor} = (I)^2(R) \quad [0.5 \text{ mark}]$$
$$= (8m)^2(2.41k) = 0.154 \text{ mW} \quad [0.5 \text{ mark}]$$

- iii) Determine the conversion efficiency for a symmetric sine-wave output voltage with peak value of 8V. [5 marks]

$$\text{Power conversion efficiency} = P_L/P_S \times 100\% \quad [1 \text{ mark}]$$

$$P_L = 0.5(V_p)^2/R_L \quad [1 \text{ mark}]$$
$$= 0.5(8)^2/(1k) = 32 \text{ mW} \quad [0.5 \text{ mark}]$$

$$P_S = (V^+ - V^-)(2I_Q) \quad [1 \text{ mark}]$$
$$= (20)(2 \times 8m) = 320 \text{ mW} \quad [0.5 \text{ mark}]$$

$$\text{Efficiency} = 32m/320m \times 100\% = 10\% \quad [1 \text{ mark}]$$

Answer: Question 6

(a)

$$\begin{aligned} v_O &= (1+R_2/R_1)v_2 & [1] \\ v_2 &= [R_4/(R_3+R_4)]v_1 & [1] \\ v_O &= (1+R_2/R_1) [R_4/(R_3+R_4)]v_1 & [1] \\ A_v &= v_O/v_1 = (1+R_2/R_1) [R_4/(R_3+R_4)] & [1] \\ &= [1+(200k/25k)][50k/(50k+25k)] = (9)(2/3) = 6 & [1] \end{aligned}$$

(b)

$$\begin{aligned} v_O &= (-R_4/R_3)v_{O1} & [1] \\ v_{O1} &= (-R_2/R_1)v_1 & [1] \\ v_O &= (-R_4/R_3)(-R_2/R_1)v_1 & [1] \\ &= [(-60k/150k)(-100k/20k)(0.12)] = 0.24 \text{ V} & [1] \end{aligned}$$

(c)

(i) Difference amplifier [1]

(ii) $R_3 = R_4 = 100 \text{ k}\Omega$

$$A_v = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1 + R_{1POT}} \right) = \frac{100k}{100k} \left(1 + \frac{2R_2}{R_1 + R_{1POT}} \right) = \left(1 + \frac{2R_2}{R_1 + R_{1POT}} \right) \quad [1]$$

A_v is maximum (i.e. $A_v = 100$) when $R_{1POT} = 0$, i.e.

$$100 = \left(1 + \frac{2R_2}{R_1 + 0} \right) \quad [1]$$

$$99 R_1 = 2 R_2 \quad \{\text{Eqn 1}\} \quad [0.5]$$

A_v is minimum (i.e. $A_v = 10$) when $R_{1POT} = 100 \text{ k}\Omega$, i.e.

$$10 = \left(1 + \frac{2R_2}{R_1 + 100k} \right) \quad [1]$$

$$9(R_1 + 100k) = 2 R_2 \quad \{\text{Eqn 2}\} \quad [0.5]$$

{Eqn 1} = {Eqn 2}

$$99 R_1 = 9 R_1 + 900k \quad [1]$$

$$\rightarrow R_1 = 10 \text{ k}\Omega \quad [1]$$

$$\rightarrow R_2 = (99 R_1) / 2 = 495 \text{ k}\Omega \quad [1]$$

(iii) $v_{I1} = 1.00 \text{ V}$, $v_{I2} = 1.15 \text{ V}$, $R_4 = 2 R_3$, $R_{1POT} = 40 \text{ k}\Omega$,
 $R_1 = 10 \text{ k}\Omega$, $R_2 = 496 \text{ k}\Omega$,

$$A_v = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1 + R_{1POT}} \right) = \frac{2R_3}{R_3} \left(1 + \frac{2(495k)}{10k + 40k} \right) = 41.6 \quad [1.5]$$

$$v_O = A_v(v_{I2} - v_{I1}) = (41.6)(1.15 - 1.00) = 6.24 \text{ V} \quad [1.5]$$