



**COLLEGE OF ENGINEERING  
PUTRAJAYA CAMPUS  
FINAL EXAMINATION  
SEMESTER 1 2012 / 2013**

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)  
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : September 2012

TIME : 3 hours

---

**INSTRUCTIONS TO CANDIDATES:**

1. This question paper contains **SIX (6)** questions in **ELEVEN (11)** pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided.
4. Write answer to each question on **a new page**.
5. For all calculations, assume that  $V_T = 26 \text{ mV}$ .
6. Use at least **4 significant numbers** in all calculations.


---

***THIS QUESTION PAPER CONSISTS OF ELEVEN (11) PRINTED PAGES INCLUDING THIS COVER PAGE AND APPENDIX.***

**Question 1 [16 marks]**

- (a) Consider the **Widlar current source** as in **Figure 1a**. Let  $I_O = 20 \mu\text{A}$  and  $R_E = 4.2\text{k}\Omega$ . Neglect base currents and assume  $I_{S1} = 4 \times 10^{-15} \text{ A}$ . Determine  $I_{REF}$ ,  $V_{BE1}$ ,  $V_{BE2}$ , and  $R_1$ .


[8 marks]

 

**Figure 1a**

- (b) Refer to **Figure 1b**. Consider the **cascode current source** with parameters  $V^+ = 5 \text{ V}$ ,  $V^- = -5 \text{ V}$ , and  $I_{REF} = 200 \mu\text{A}$  at  $V_{GS1} = 1.8 \text{ V}$ . All transistors are matched and operating in saturation region with parameters  $g_m = 0.3 \text{ mA/V}^2$  and  $\lambda = 0.025\text{V}^{-1}$ . Determine  $I_o$  at  $V_{D4} = +2.5 \text{ V}$ .


[8 marks]

 

**Figure 1b**

**Question 2 [16 marks]**

- (a) The basic differential pair is shown in **Figure 2a**. It is given that  $V^+ = 15\text{ V}$ ,  $V^- = -15\text{ V}$ ,  $R_C = 5\text{ k}\Omega$ ,  $I_Q = 2\text{ mA}$ , and transistor parameters are  $\beta = 100$ ,  $V_A = 100\text{ V}$ ,  $V_{BE(\text{on})} = 0.7\text{ V}$ ,  $V_{CE(\text{sat})} = 0.3\text{ V}$ .

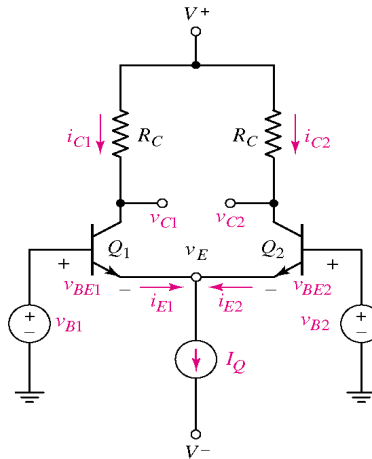


**Figure 2a**

- (i) **Calculate** the **one-sided** small-signal differential voltage gain ( $A_d$ ) of the differential amplifier. [2 marks]
- (ii) The constant current source of **Figure 2a** that is providing the current  $I_Q$  is implemented using the **basic two transistor current source**. **Find** the value of  $A_{cm}$ , the **common-mode voltage gain** of the differential-amplifier, using **equation given below**. Assume  $R_B = 0$ . [2 marks]

$$A_{cm} = \frac{-g_m R_C}{1 + \frac{2(1 + \beta)R_O}{r_\pi + R_B}}$$

- (iii) The input voltages for the differential amplifier are  $v_{B1} = 210 \times 10^{-6} \sin \omega t\text{ V}$  and  $v_{B2} = 190 \times 10^{-6} \sin \omega t\text{ V}$ . **Calculate the output voltage** of the differential amplifier **applying superposition theorem**, taking into account the effect of the non-ideal current source. **Use values from previous calculations**. **What** is the output voltage if an ideal current source is used instead? **Justify** your answer. [4 marks]
- (iv) **Calculate** the value of  $V_{cm(\text{max})}$  of this differential amplifier. [4 marks]

- (b) The differential amplifier shown in **Figure 2b** has a **three-transistor current mirror** connected as an **active load**. The circuit is connected to power supply voltages of  $V^+ = +5\text{ V}$  and  $V^- = -5\text{ V}$ .

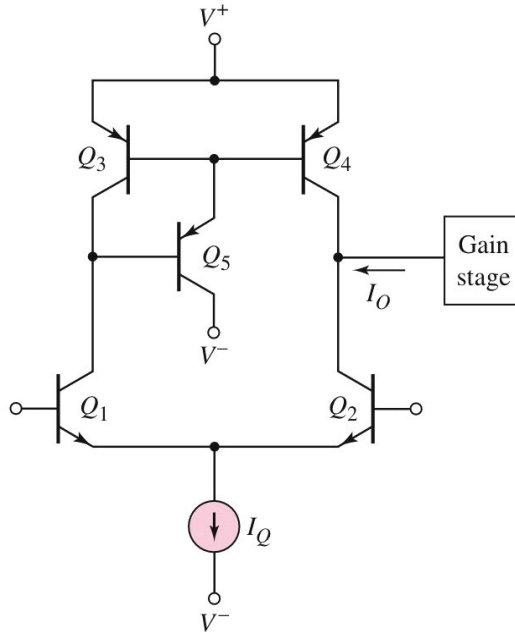


**Figure 2b**

- (i) **Determine** the relationship between  $I_O$  and  $I_Q$  such that the amplifier **dc currents are balanced**. [3 marks]
- (ii) **Calculate** the value of  $I_O$  given that  $I_Q = 0.2\text{ mA}$  and  $\beta = 100$ . [1 mark]

**Question 3 [16 marks]**

**Figure 3** shows a differential amplifier circuit with active loads and biased by a current source using MOSFET. Transistors  $M_1$  and  $M_2$  are driven into saturation with  $V_{DS}(\text{sat}) = 1.12 \text{ V}$ . The active load transistors ( $M_3$  and  $M_4$ ) are matched with parameters  $K_p = 0.1 \text{ mA/V}^2$ ,  $V_{TP} = -2 \text{ V}$ , and  $\lambda_p = 0.02 \text{ V}^{-1}$ . Transistors  $M_5$ ,  $M_6$  and  $M_7$  are **identical**. All the NMOS transistors have the same  $K_n = 0.2 \text{ mA/V}^2$ ,  $V_{TN} = 2 \text{ V}$ , and  $\lambda_n = 0.015 \text{ V}^{-1}$ .

 


**Figure 3**

- (a) Determine  $I_1$ ,  $I_Q$ , and  $I_{D1}$  when  $v_1 = v_2 = 0$ . [5 marks]
  
- (b) Determine the **one-sided differential mode voltage gain** ( $A_d$ ) for the differential amplifier if  $R_L = 100 \text{ k}\Omega$ . [6 marks]
  
- (c) It is required that the **CMRR** of the circuit to be **60 dB**. What is the **common mode voltage gain** ( $A_{cm}$ )? [3 marks]
  
- (d) **Suggest 2 ways** to improve the **CMRR** for the circuit in the **Figure 3**. [2 marks]

**Question 4 [16 marks]**

Consider the **input stage and bias circuit** of the **741 operational amplifier** in **Figure 4a**, with  $V^+ = 5\text{ V}$  and  $V^- = -5\text{ V}$ ,  $V_A = 50\text{ V}$ ,  $V_{BE6} = V_{BE7} = 0.6\text{ V}$ ,  $\beta = 200$  and  $I_{C9} = 10\text{ }\mu\text{A}$ . The reverse saturation current  $I_S = 10^{-14}\text{ A}$  for each transistor and the current flow through resistor  $R_5$  is **0.4 mA**. Ignore the base currents for dc calculations and assume the **dc currents in the input stage are exactly balanced**.

- (a) What is the **purpose** of  $Q_3$  and  $Q_4$  in the circuit? [2 marks]
- (b) **Determine** the resistance  $R_4$ . [4 marks]
- (c) **Calculate** the value of  $r_{\pi 6}$ . [2 marks]

 


**Figure 4a**

(d) **Figure 4b** shows the **ac equivalent circuit** of the input stage of the **741 op-amp** shown in the **Figure 4a**. **Determine** the effective output resistance,  $R_O$ , looking at  $v_{o1}$ . **Neglect** the effective resistances in the emitters of  $Q_4$  and  $Q_2$ .

(Hint: The output resistance ( $R_O$ ) of a **Widlar current source** can be calculated using the following formula:  $R_O = r_o [1 + g_m (r_\pi \parallel R_E)]$  ).


[8 marks]

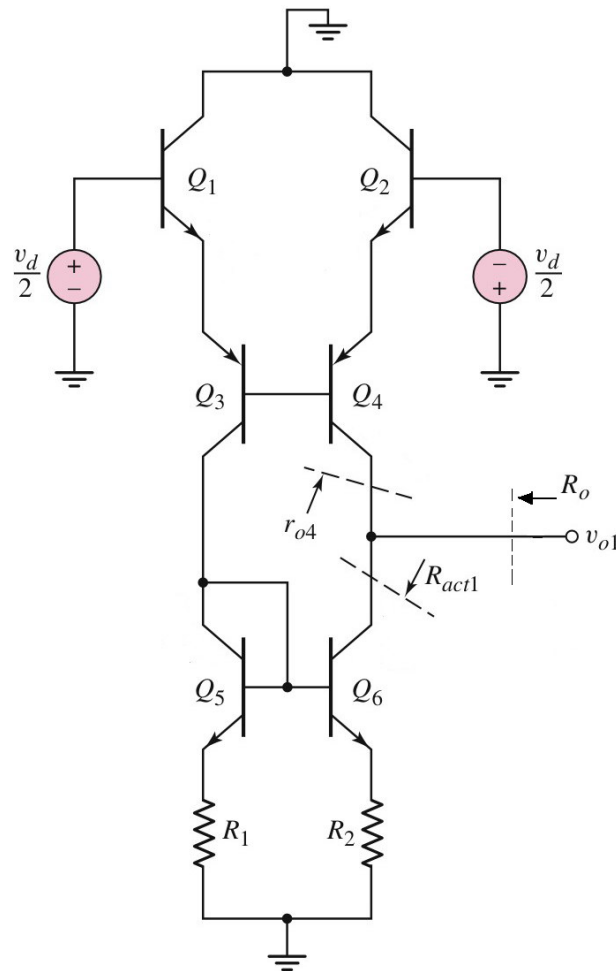

**Figure 4b**

**Question 5 [16 marks]**

- (a) **State** the main disadvantage of both **Class A** and **Class B** output stages. **Comment** on the **power conversion efficiency** of both output stages. [2 marks]
- (b) The circuit parameters for the **emitter follower** circuit in **Figure 5** is  $V^+ = 10\text{ V}$ ,  $V^- = -10\text{ V}$ , and  $R_L = 1\text{ k}\Omega$ . The transistor parameters are  $V_{BE(\text{on})} = 0.7\text{ V}$ ,  $V_{CE(\text{sat})} = 0.2\text{ V}$ , and  $V_A = \infty$ . **Neglect** base currents. The **output voltage** is varying from **-8 V** to **+8 V**.

 


**Figure 5**

- (i) **Find** the required  $I_Q$  and the value of  $R$ . [4 marks]
- (ii) For  $v_O = 0\text{ V}$ , **find** the power dissipated in the transistor  $Q_1$ , and the power dissipated in the current source ( $Q_2$ ,  $Q_3$ , and  $R$ ). [5 marks]
- (iii) **Determine** the conversion efficiency for a symmetric sine-wave output voltage with peak value of **8 V**. [5 marks]




**Question 6 [20 marks]**

- (a) Find the voltage gain,  $A_v = v_o/v_I$ , for the circuit in **Figure 6a**. Assume that the op-amp is ideal. [5 marks]

 

**Figure 6a**

- (b) Consider the two inverting op-amp circuit connected in cascade as shown in **Figure 6b**. Let  $R_1 = 20 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ ,  $R_3 = 150 \text{ k}\Omega$ , and  $R_4 = 60 \text{ k}\Omega$ . Find  $v_o$  when  $v_I = 0.12 \text{ V}$ . [4 marks]

 

**Figure 6b**

- (c) **Figure 6c**, in next page, shows a design for an **instrumentation amplifier** using op-amps. In the design,  $R_{1POT}$  is a **100 kΩ potentiometer** (or a variable resistor) used to provide **variable resistance** so that differential voltage gain ( $A_v$ ) of the instrumentation amplifier can be adjustable. With analysis, it can be shown that

$$v_o = \frac{R_4}{R_3} \left( 1 + \frac{2R_2}{R_1 + R_{1POT}} \right) (v_{I2} - v_{I1})$$

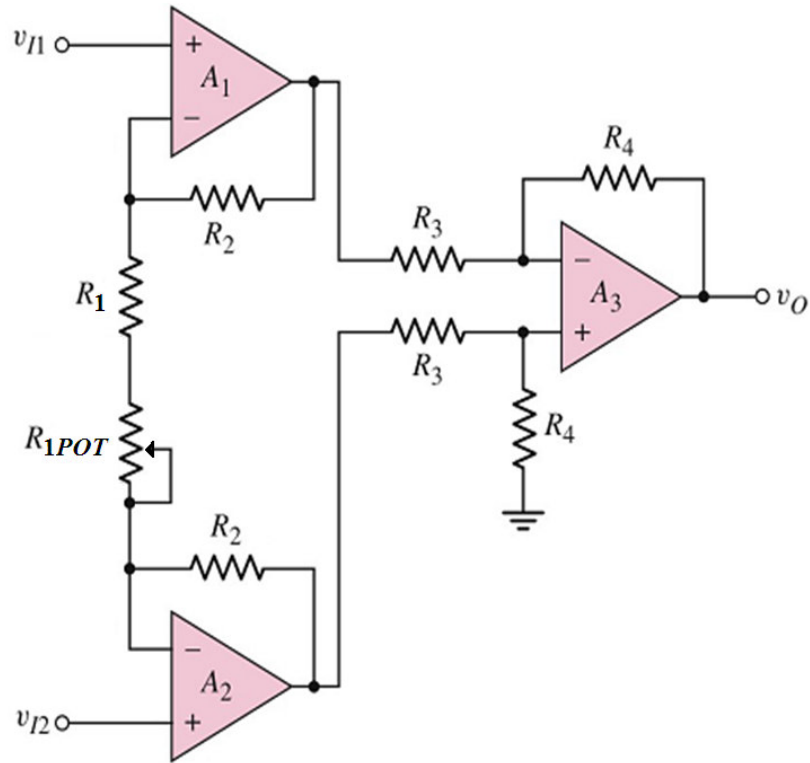


Figure 6c

- (i) **What** is the name of an amplifier represented by op-amp  $A_3$ ,  $R_3$ , and  $R_4$  in the **Figure 6c**? [1 mark]
- (ii) With  $R_3 = R_4 = 100 \text{ k}\Omega$ , **design an instrumentation amplifier** using the circuit as shown in the **Figure 6c** to realize a differential voltage gain ( $A_v$ ) adjustable from **10 to 100**. (Hints:  $A_v$  is smallest when  $R_{1POT}$  is at maximum value. You are required to determine the value of  $R_1$  and  $R_2$  in the circuit). [7 marks]
- (iii) With  $v_{I1} = 1.00 \text{ V}$ ,  $v_{I2} = 1.15 \text{ V}$ ,  $R_4 = 2 R_3$ ,  $R_{1POT}$  is set at **40 k $\Omega$** , and using the values of  $R_1$  and  $R_2$  found in **step (ii)** above, **calculate**  $A_v$  and  $v_O$ . [3 marks]

**-END OF QUESTION PAPER-**

## APPENDIX

BASIC FORMULABJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

; Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$