

Question:

Refer to **Figure 1**. Assume $\beta = 200$ and $V_{BE(on)} = 0.7$ V for all BJTs in the circuit. For $R_1 = 12$ k Ω and $R_C = 12$ k Ω , find the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output**. [10 marks]

Answer:

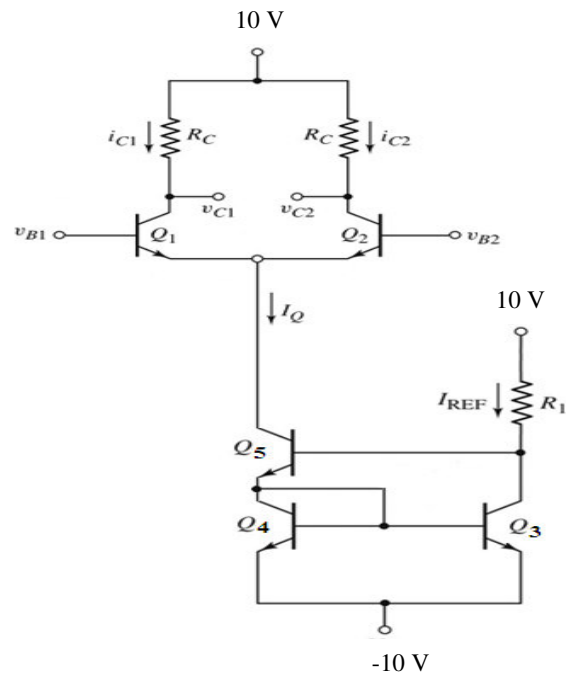


Figure 1

$$I_{REF} = (V^+ - V_{BE5} - V_{BE3} - V^-) / (R_1) \approx I_Q \quad (\beta = 200) \quad [2 \text{ marks}]$$

$$= (10 - 0.7 - 0.7 - (-10)) / (12k) = 1.55 \text{ mA} \quad [2 \text{ marks}]$$

$$A_d = (g_m R_C) / 2 = (I_Q R_C) / (4V_T) \quad [2 \text{ marks}]$$

$$g_m = I_Q / (2V_T) = (1.55m) / (2 \times 26m) = 29.8077 \text{ mA/V} \quad [2 \text{ marks}]$$

$$A_d = (29.8077m)(12k) / (2) = 178.846 \text{ V/V} \quad [2 \text{ marks}]$$

EEEE273 - Quiz 2 [Question Set 2]
 SEMESTER 1, ACADEMIC YEAR 2012/2013
 Date: 10 July 2012

Question:

Refer to **Figure 1**. Assume $\beta = 200$ and $V_{BE(on)} = 0.7 \text{ V}$ for all BJTs in the circuit. For $R_1 = 12 \text{ k}\Omega$ and $R_C = 10.8 \text{ k}\Omega$, find the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output**. [10 marks]

Answer:

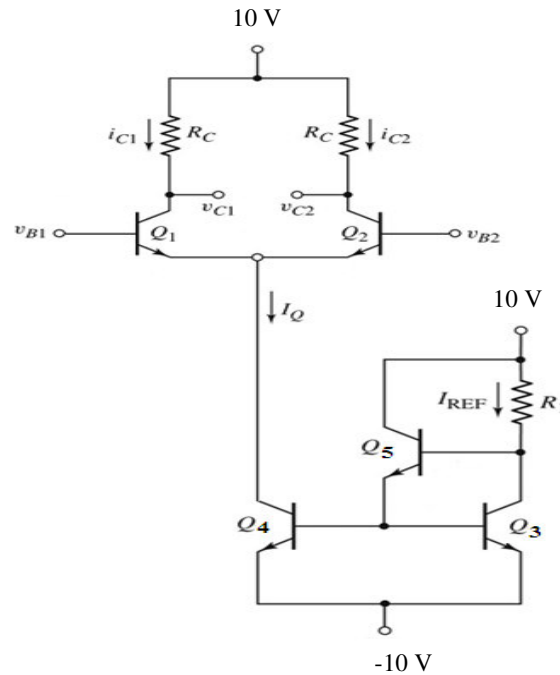


Figure 1

$$I_{REF} = (V^+ - V_{BE5} - V_{BE3} - V^-) / (R_1) \approx I_Q \quad (\beta = 200) \quad [2 \text{ marks}]$$

$$= (10 - 0.7 - 0.7 - (-10)) / (12\text{k}) = 1.55 \text{ mA} \quad [2 \text{ marks}]$$

$$A_d = (g_m R_C) / 2 = (I_Q R_C) / (4V_T) \quad [2 \text{ marks}]$$

$$g_m = I_Q / (2V_T) = (1.55\text{m}) / (2 \times 26\text{m}) = 29.8077 \text{ mA/V} \quad [2 \text{ marks}]$$

$$A_d = (29.8077\text{m})(10.8\text{k}) / (2) = 160.96 \text{ V/V} \quad [2 \text{ marks}]$$

Question:

Refer to **Figure 1**. Assume $\beta = 200$ and $V_{BE(on)} = 0.7$ V for all BJTs in the circuit. For $R_1 = 10.8$ k Ω and $R_C = 14$ k Ω , find the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output**. [10 marks]

Answer:

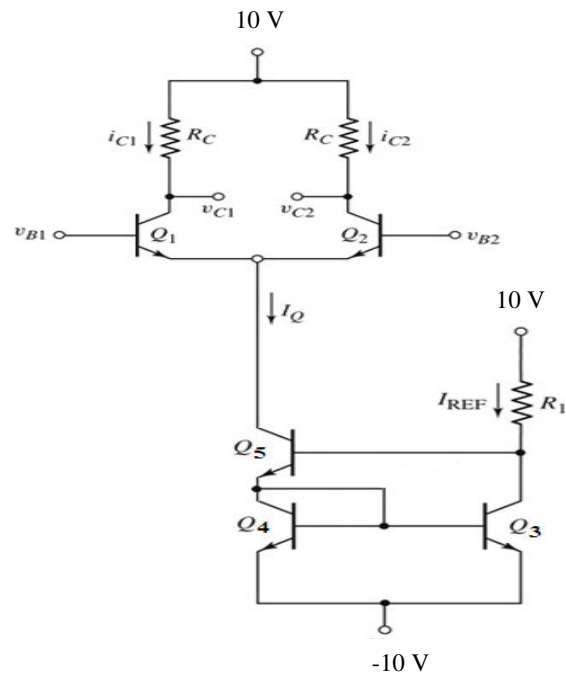


Figure 1

$$I_{REF} = (V^+ - V_{BE5} - V_{BE3} - V^-) / (R_1) \approx I_Q \quad (\beta = 200) \quad [2 \text{ marks}]$$

$$= (10 - 0.7 - 0.7 - (-10)) / (10.8k) = 1.722 \text{ mA} \quad [2 \text{ marks}]$$

$$A_d = (g_m R_C) / 2 = (I_Q R_C) / (4V_T) \quad [2 \text{ marks}]$$

$$g_m = I_Q / (2V_T) = (1.722m) / (2 \times 26m) = 33.1154 \text{ mA/V} \quad [2 \text{ marks}]$$

$$A_d = (33.1154m)(14k) / (2) = 231.808 \text{ V/V} \quad [2 \text{ marks}]$$

EEEE273 - Quiz 2 [Question Set 4]
 SEMESTER 1, ACADEMIC YEAR 2012/2013
 Date: 10 July 2012

Question:

Refer to **Figure 1**. Assume $\beta = 200$ and $V_{BE(on)} = 0.7 \text{ V}$ for all BJTs in the circuit. For $R_1 = 10 \text{ k}\Omega$ and $R_C = 12.8 \text{ k}\Omega$, find the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output**. [10 marks]

Answer:

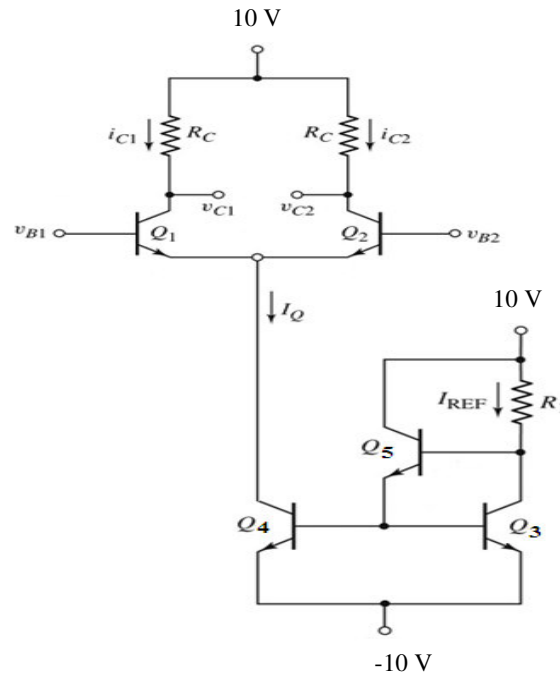


Figure 1

$$I_{REF} = (V^+ - V_{BE5} - V_{BE3} - V^-) / (R_1) \approx I_Q \quad (\beta = 200) \quad [2 \text{ marks}]$$

$$= (10 - 0.7 - 0.7 - (-10)) / (10\text{k}) = 1.86 \text{ mA} \quad [2 \text{ marks}]$$

$$A_d = (g_m R_C) / 2 = (I_Q R_C) / (4V_T) \quad [2 \text{ marks}]$$

$$g_m = I_Q / (2V_T) = (1.86\text{m}) / (2 \times 26\text{m}) = 35.7692 \text{ mA/V} \quad [2 \text{ marks}]$$

$$A_d = (35.7692\text{m})(12.8\text{k}) / (2) = 228.923 \text{ V/V} \quad [2 \text{ marks}]$$