

EEEB273 - Quiz 3 [Question Set 1]  
 SEMESTER 1, ACADEMIC YEAR 2012/2013  
 Date: 14 August 2012

**Question:**

**Figure 1** shows the **ac equivalent circuit** of the input stage of the **741 op-amp**. For all transistors  $V_A = 50 \text{ V}$ ,  $\beta = 200$ , and **neglect** the base currents. Given that  $I_{C2} = 5.5 \mu\text{A}$ , and  $R_1 = R_2 = 1 \text{ k}\Omega$ . **Determine** the effective output resistance,  $R_O$ , looking at  $v_{o1}$ . **Neglect** the effective resistances in the emitters of  $Q_4$  and  $Q_2$ .

[10 marks]

**Answer:**

$$R_O = r_{O4} \parallel R_{act1} \quad [2]$$

$$I_{C4} = I_{C2} = 5.5 \mu\text{A} \quad [0.5]$$

$$r_{O4} = \frac{V_A}{I_{C4}} = \frac{50}{5.5 \mu} = 9.09 \text{M}\Omega \quad [1]$$

$$R_{act1} = r_{O6} [1 + g_{m6} (R_2 \parallel r_{\pi 6})] \quad [1]$$

$$I_{C6} = I_{C2} = 5.5 \mu\text{A} \quad [0.5]$$

$$r_{O6} = \frac{V_A}{I_{C6}} = \frac{50}{5.5 \mu} = 9.09 \text{M}\Omega \quad [1]$$


$$g_{m6} = \frac{I_{C6}}{V_T} = \frac{5.5 \mu}{0.026} = 0.2115 \text{mA/V}^2 \quad [1]$$

$$r_{\pi 6} = \frac{\beta V_T}{I_{C6}} = \frac{200(0.026)}{5.5 \mu} = 0.945 \text{M}\Omega \quad [1]$$

$$R_{act1} = (9.09 \text{M}) [1 + (0.2115 \text{m})(1 \text{k} \parallel 0.945 \text{M})] \quad [0.5]$$

$$R_{act1} = 11.01 \text{M}\Omega \quad [0.5]$$

$$R_O = 9.09 \text{M} \parallel 11.01 \text{M}\Omega = 4.979 \text{M}\Omega \quad [1]$$

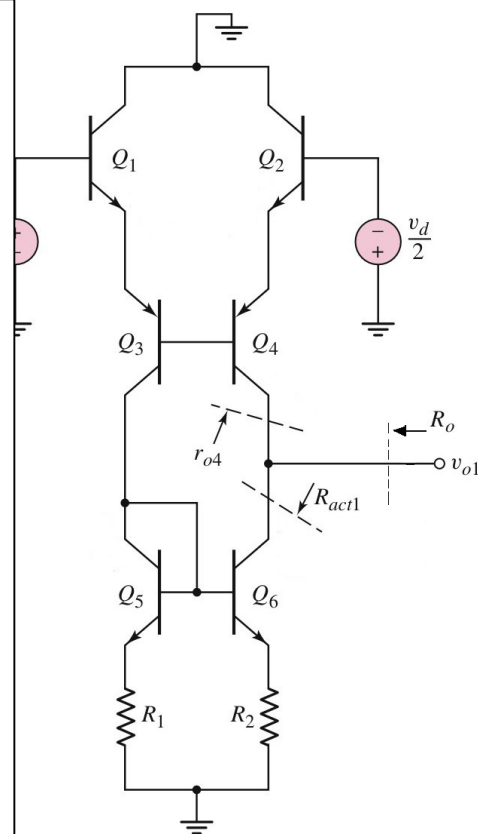

**Figure 1**

EEEB273 - Quiz 3 [Question Set 2]  
 SEMESTER 1, ACADEMIC YEAR 2012/2013  
 Date: 14 August 2012

**Question:**

**Figure 1** shows the **ac equivalent circuit** of the input stage of the **741 op-amp**. For all transistors  $V_A = 50 \text{ V}$ ,  $\beta = 200$ , and **neglect** the base currents. Given that  $I_{C2} = 5.3 \mu\text{A}$ , and  $R_1 = R_2 = 1 \text{ k}\Omega$ . **Determine** the effective output resistance,  $R_O$ , looking at  $v_{o1}$ . **Neglect** the effective resistances in the emitters of  $Q_4$  and  $Q_2$ .

[10 marks]

**Answer:**

$$R_O = r_{O4} \parallel R_{act1} \quad [2]$$

$$I_{C4} = I_{C2} = 5.3 \mu\text{A} \quad [0.5]$$

$$r_{O4} = \frac{V_A}{I_{C4}} = \frac{50}{5.3 \mu} = 9.43 \text{ M}\Omega \quad [1]$$

$$R_{act1} = r_{O6} [1 + g_{m6} (R_2 \parallel r_{\pi 6})] \quad [1]$$

$$I_{C6} = I_{C2} = 5.3 \mu\text{A} \quad [0.5]$$

$$r_{O6} = \frac{V_A}{I_{C6}} = \frac{50}{5.3 \mu} = 9.43 \text{ M}\Omega \quad [1]$$


$$g_{m6} = \frac{I_{C6}}{V_T} = \frac{5.3 \mu}{0.026} = 0.2038 \text{ mA/V}^2 \quad [1]$$

$$r_{\pi 6} = \frac{\beta V_T}{I_{C6}} = \frac{200(0.026)}{5.3 \mu} = 0.981 \text{ M}\Omega \quad [1]$$

$$R_{act1} = (9.43 \text{ M}) [1 + (0.2038 \text{ m})(1 \text{ k} \parallel 0.981 \text{ M})] \quad [0.5]$$

$$R_{act1} = 11.35 \text{ M}\Omega \quad [0.5]$$

$$R_O = 9.43 \text{ M} \parallel 11.35 \text{ M}\Omega = 5.151 \text{ M}\Omega \quad [1]$$

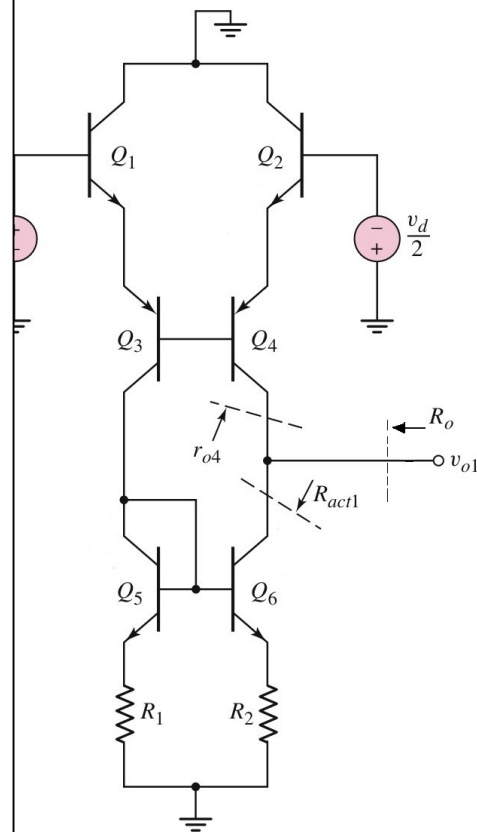

**Figure 1**

EEEB273 - Quiz 3 [Question Set 3]  
 SEMESTER 1, ACADEMIC YEAR 2012/2013  
 Date: 14 August 2012

**Question:**

**Figure 1** shows the **ac equivalent circuit** of the input stage of the **741 op-amp**. For all transistors  $V_A = 50 \text{ V}$ ,  $\beta = 200$ , and **neglect** the base currents. Given that  $I_{C2} = 5.7 \mu\text{A}$ , and  $R_1 = R_2 = 1.2 \text{ k}\Omega$ . **Determine** the effective output resistance,  $R_O$ , looking at  $v_{o1}$ . **Neglect** the effective resistances in the emitters of  $Q_4$  and  $Q_2$ .

[10 marks]

**Answer:**

$$R_O = r_{O4} \parallel R_{act1} \quad [2]$$

$$I_{C4} = I_{C2} = 5.7 \mu\text{A} \quad [0.5]$$

$$r_{O4} = \frac{V_A}{I_{C4}} = \frac{50}{5.7 \mu} = 8.77 \text{ M}\Omega \quad [1]$$

$$R_{act1} = r_{o6} [1 + g_{m6} (R_2 \parallel r_{\pi6})] \quad [1]$$

$$I_{C6} = I_{C2} = 5.7 \mu\text{A} \quad [0.5]$$

$$r_{O6} = \frac{V_A}{I_{C6}} = \frac{50}{5.7 \mu} = 8.77 \text{ M}\Omega \quad [1]$$


$$g_{m6} = \frac{I_{C6}}{V_T} = \frac{5.7 \mu}{0.026} = 0.2192 \text{ mA/V}^2 \quad [1]$$

$$r_{\pi6} = \frac{\beta V_T}{I_{C6}} = \frac{200(0.026)}{5.7 \mu} = 0.9122 \text{ M}\Omega \quad [1]$$

$$R_{act1} = (8.77 \text{ M}) [1 + (0.2192 \text{ m})(1.2 \text{ k} \parallel 0.9122 \text{ M})] \quad [0.5]$$

$$R_{act1} = 11.076 \text{ M}\Omega \quad [0.5]$$

$$R_O = 8.77 \text{ M} \parallel 11.076 \text{ M}\Omega = 4.894 \text{ M}\Omega \quad [1]$$

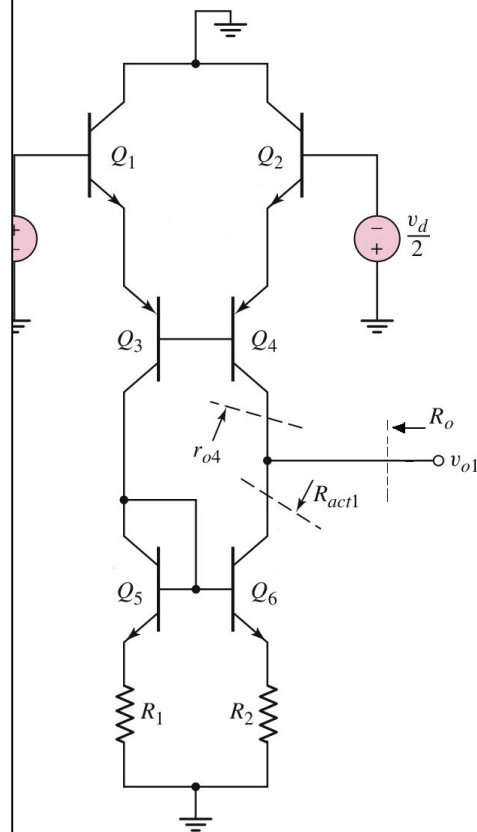

**Figure 1**

**Question:**

**Figure 1** shows the **ac equivalent circuit** of the input stage of the **741 op-amp**. For all transistors  $V_A = 50 \text{ V}$ ,  $\beta = 200$ , and **neglect** the base currents. Given that  $I_{C2} = 5.3 \mu\text{A}$ , and  $R_1 = R_2 = 1.2 \text{ k}\Omega$ . **Determine** the effective output resistance,  $R_O$ , looking at  $v_{o1}$ . **Neglect** the effective resistances in the emitters of  $Q_4$  and  $Q_2$ .

[10 marks]

**Answer:**

$$R_O = r_{O4} \parallel R_{act1} \quad [2]$$

$$I_{C4} = I_{C2} = 5.3 \mu\text{A} \quad [0.5]$$

$$r_{O4} = \frac{V_A}{I_{C4}} = \frac{50}{5.3 \mu} = 9.43 \text{ M}\Omega \quad [1]$$

$$R_{act1} = r_{O6} [1 + g_{m6} (R_2 \parallel r_{\pi6})] \quad [1]$$

$$I_{C6} = I_{C2} = 5.3 \mu\text{A} \quad [0.5]$$

$$r_{O6} = \frac{V_A}{I_{C6}} = \frac{50}{5.3 \mu} = 9.43 \text{ M}\Omega \quad [1]$$


$$g_{m6} = \frac{I_{C6}}{V_T} = \frac{5.3 \mu}{0.026} = 0.2038 \text{ mA/V}^2 \quad [1]$$

$$r_{\pi6} = \frac{\beta V_T}{I_{C6}} = \frac{200(0.026)}{5.3 \mu} = 0.981 \text{ M}\Omega \quad [1]$$

$$R_{act1} = (9.43 \text{ M}) [1 + (0.2038 \text{ m})(1.2 \text{ k} \parallel 0.981 \text{ M})] \quad [0.5]$$

$$R_{act1} = 11.736 \text{ M}\Omega \quad [0.5]$$

$$R_O = 9.43 \text{ M} \parallel 11.736 \text{ M}\Omega = 5.228 \text{ M}\Omega \quad [1]$$

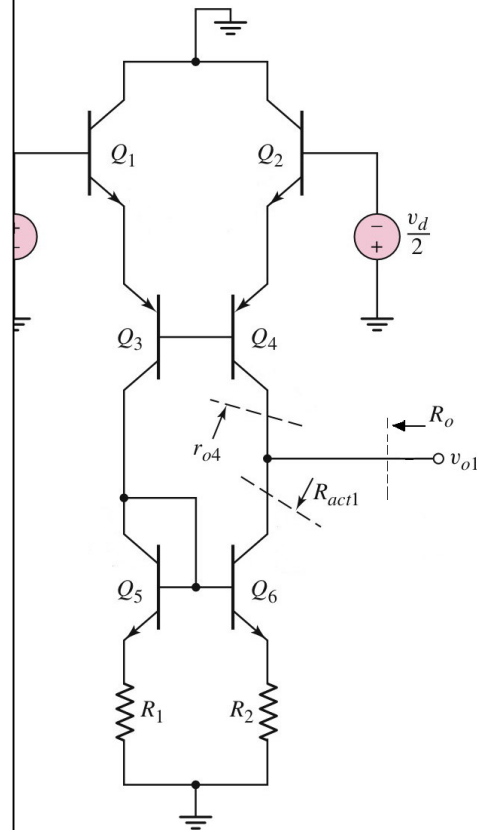

**Figure 1**