

EEEE273 - Quiz 4 [Question Set 1]
 SEMESTER 1, ACADEMIC YEAR 2012/2013
 Date: 28 August 2012

Question:

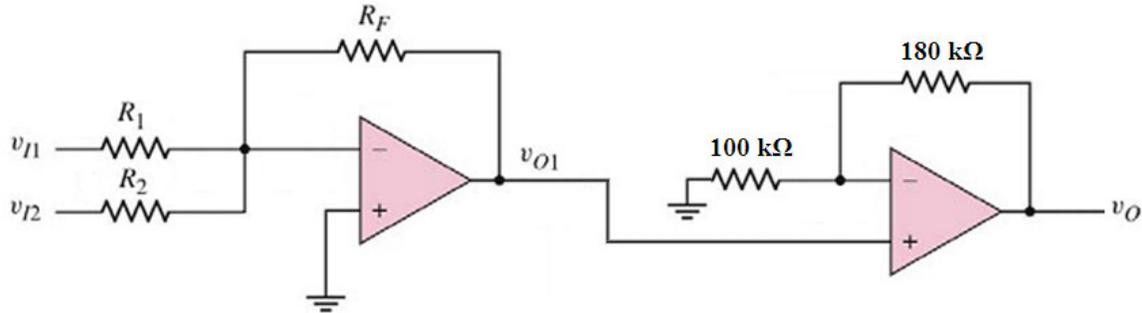


Figure 1

Refer to **Figure 1**. Using ideal properties of the op-amps:

- (a) Determine v_{O1} when $R_1 = 12 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, $R_F = 24 \text{ k}\Omega$, $v_{I1} = 15 \text{ mV}$, and $v_{I2} = -20 \text{ mV}$. [6 marks]
- (b) Find v_O . [4 marks]

Show clearly all calculations in order to get full marks.

Answers:

(a)

Superposition theorem:

$$v_{I2} = 0, \quad v_{O1}(v_{I1}) = -(R_F / R_1)(v_{I1}) = -(24\text{k}/12\text{k})(15\text{m}) = -30 \text{ mV} \quad [2]$$

$$v_{I1} = 0, \quad v_{O1}(v_{I2}) = -(R_F / R_2)(v_{I2}) = -(24\text{k}/20\text{k})(-20\text{m}) = 24 \text{ mV} \quad [2]$$

$$v_{O1} = v_{O1}(v_{I1}) + v_{O1}(v_{I2}) = (-30\text{m}) + (24\text{m}) = -6 \text{ mV} \quad [2]$$

(b)

$$v_O = (1 + 180\text{k}/100\text{k})(v_{O1}) \quad [2]$$

$$= (1 + 180\text{k}/100\text{k})(-6\text{m}) = -16.8 \text{ mV} \quad [2]$$

EEEE273 - Quiz 4 [Question Set 2]
 SEMESTER 1, ACADEMIC YEAR 2012/2013
 Date: 28 August 2012

Question:

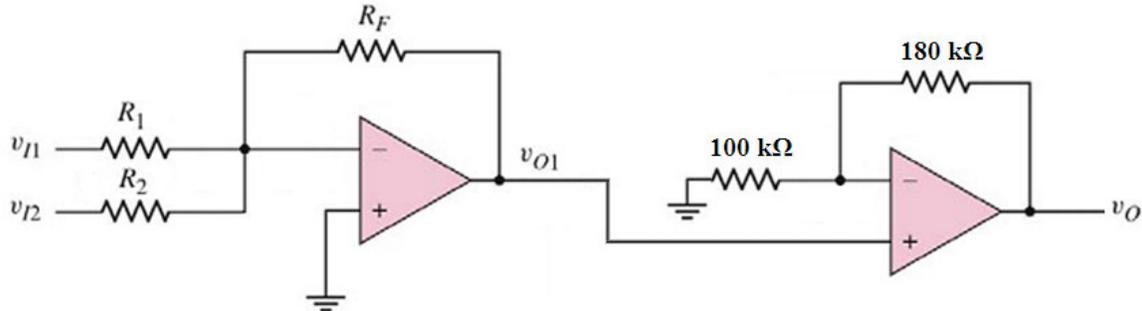


Figure 1

Refer to **Figure 1**. Using ideal properties of the op-amps:

- (c) Determine v_{O1} when $R_1 = 12 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, $R_F = 24 \text{ k}\Omega$, $v_{I1} = -15 \text{ mV}$, and $v_{I2} = 20 \text{ mV}$. [6 marks]
- (d) Find v_O . [4 marks]

Show clearly all calculations in order to get full marks.

Answers:

(a)

Superposition theorem:

$$v_{I2} = 0, \quad v_{O1}(v_{I1}) = -(R_F / R_1)(v_{I1}) = -(24\text{k}/12\text{k})(-15\text{m}) = 30 \text{ mV} \quad [2]$$

$$v_{I1} = 0, \quad v_{O1}(v_{I2}) = -(R_F / R_2)(v_{I2}) = -(24\text{k}/20\text{k})(20\text{m}) = -24 \text{ mV} \quad [2]$$

$$v_{O1} = v_{O1}(v_{I1}) + v_{O1}(v_{I2}) = (30\text{m}) + (-24\text{m}) = 6 \text{ mV} \quad [2]$$

(b)

$$v_O = (1 + 180\text{k}/100\text{k})(v_{O1}) \quad [2]$$

$$= (1 + 180\text{k}/100\text{k})(6\text{m}) = 16.8 \text{ mV} \quad [2]$$

EEEE273 - Quiz 4 [Question Set 3]
 SEMESTER 1, ACADEMIC YEAR 2012/2013
 Date: 28 August 2012

Question:

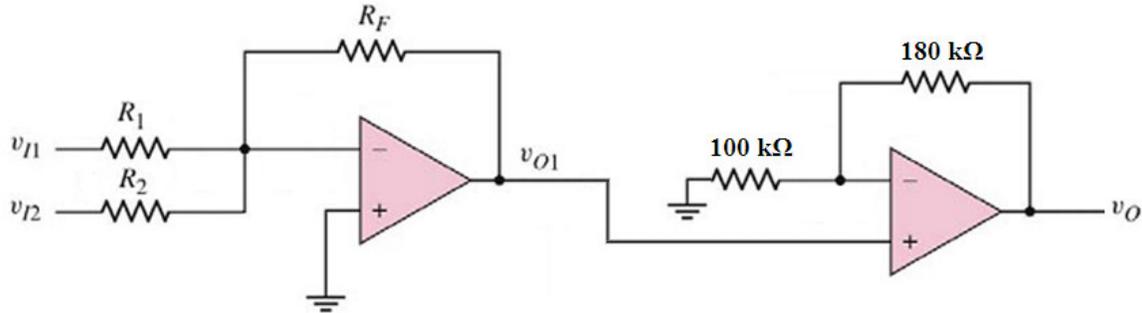


Figure 1

Refer to **Figure 1**. Using ideal properties of the op-amps:

- (e) Determine v_{O1} when $R_1 = 24 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, $R_F = 24 \text{ k}\Omega$, $v_{I1} = -15 \text{ mV}$, and $v_{I2} = 20 \text{ mV}$. [6 marks]
- (f) Find v_O . [4 marks]

Show clearly all calculations in order to get full marks.

Answers:

(a)

Superposition theorem:

$$v_{I2} = 0, \quad v_{O1}(v_{I1}) = -(R_F / R_1)(v_{I1}) = -(24\text{k}/24\text{k})(-15\text{m}) = 15 \text{ mV} \quad [2]$$

$$v_{I1} = 0, \quad v_{O1}(v_{I2}) = -(R_F / R_2)(v_{I2}) = -(24\text{k}/20\text{k})(20\text{m}) = -24 \text{ mV} \quad [2]$$

$$v_{O1} = v_{O1}(v_{I1}) + v_{O1}(v_{I2}) = (15\text{m}) + (-24\text{m}) = -9 \text{ mV} \quad [2]$$

(b)

$$v_O = (1 + 180\text{k}/100\text{k})(v_{O1}) \quad [2]$$

$$= (1 + 180\text{k}/100\text{k})(-9\text{m}) = -25.2 \text{ mV} \quad [2]$$

EEEE273 - Quiz 4 [Question Set 4]
 SEMESTER 1, ACADEMIC YEAR 2012/2013
 Date: 28 August 2012

Question:

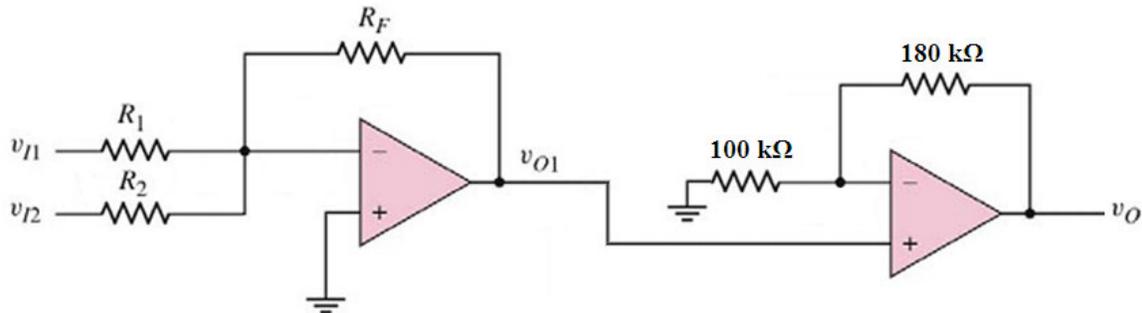


Figure 1

Refer to **Figure 1**. Using ideal properties of the op-amps:

- (g) Determine v_{O1} when $R_1 = 24 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, $R_F = 24 \text{ k}\Omega$, $v_{I1} = 15 \text{ mV}$, and $v_{I2} = -20 \text{ mV}$. [6 marks]
- (h) Find v_O . [4 marks]

Show clearly all calculations in order to get full marks.

Answers:

(a)

Superposition theorem:

$$v_{I2} = 0, \quad v_{O1}(v_{I1}) = -(R_F / R_1)(v_{I1}) = -(24\text{k}/24\text{k})(15\text{m}) = -15 \text{ mV} \quad [2]$$

$$v_{I1} = 0, \quad v_{O1}(v_{I2}) = -(R_F / R_2)(v_{I2}) = -(24\text{k}/20\text{k})(-20\text{m}) = 24 \text{ mV} \quad [2]$$

$$v_{O1} = v_{O1}(v_{I1}) + v_{O1}(v_{I2}) = (-15\text{m}) + (24\text{m}) = 9 \text{ mV} \quad [2]$$

(b)

$$v_O = (1 + 180\text{k}/100\text{k})(v_{O1}) \quad [2]$$

$$= (1 + 180\text{k}/100\text{k})(9\text{m}) = 25.2 \text{ mV} \quad [2]$$