



**COLLEGE OF ENGINEERING  
PUTRAJAYA CAMPUS  
FINAL EXAMINATION  
SEMESTER 2 2012 / 2013**

PROGRAMME : **Bachelor of Electrical & Electronics Engineering (Honours)**  
**Bachelor of Electrical Power Engineering (Honours)**

SUBJECT CODE : **EEEB273**

SUBJECT : **ELECTRONIC ANALYSIS AND DESIGN II**

DATE : **January 2013**

TIME : **3 hours (0900 – 1200)**

---

**INSTRUCTIONS TO CANDIDATES:**

1. This paper contains **Five (5)** questions in **Ten (10)** pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided.
4. Write answer to different question on a **new page**.
5. For all calculations, assume that  $V_T = 26 \text{ mV}$ .
6. Use at least **4 significant numbers** in all calculations.


**MODEL ANSWERS**

---

***THIS QUESTION PAPER CONSISTS OF TEN (10) PRINTED PAGES INCLUDING THIS COVER PAGE.***

**Answer for Q1(a)**

(i)

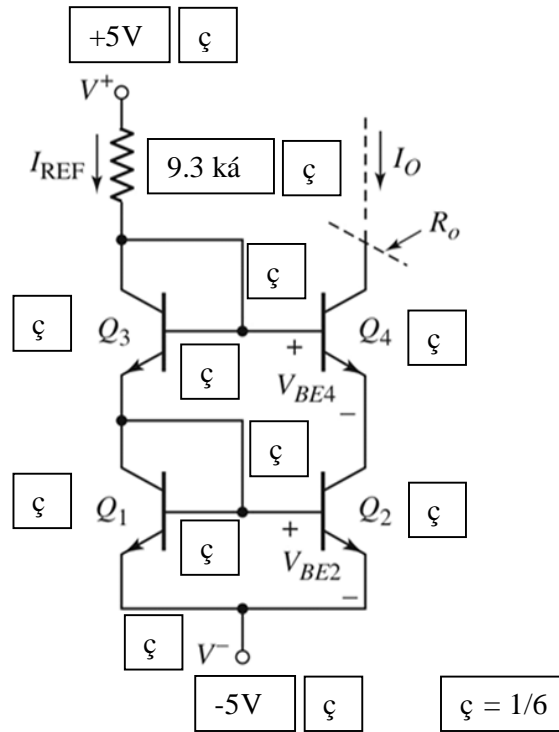

(ii)

$$I_{E4} = \frac{I_{E3}}{1 + 2/\beta} \text{ ; From 2T CS} \quad \boxed{1}$$

$$I_O = I_{C4} = \frac{\beta}{1 + \beta} I_{E4} \rightarrow I_{E4} = \frac{1 + \beta}{\beta} I_O \quad \boxed{0.5}$$

$$I_{E3} = (1 + 2/\beta) I_{E4} = (1 + 2/\beta) \frac{1 + \beta}{\beta} I_O = \frac{2 + \beta}{\beta} \frac{1 + \beta}{\beta} I_O \quad \boxed{0.5}$$

$$I_{B4} = \frac{I_{E4}}{1 + \beta} = \frac{1}{1 + \beta} \frac{1 + \beta}{\beta} I_O = \frac{I_O}{\beta} \quad \boxed{0.5}$$

$$I_{C3} + I_{B3} = I_{E3} = \frac{2 + \beta}{\beta} \frac{1 + \beta}{\beta} I_O = \frac{\beta^2 + 3\beta + 2}{\beta^2} I_O \quad \boxed{0.5}$$

$$I_{REF} = I_{C3} + I_{B3} + I_{B4} = \frac{\beta^2 + 3\beta + 2}{\beta^2} I_O + \frac{I_O}{\beta} \quad \boxed{0.5}$$

$$I_{REF} = \frac{\beta^2 + 4\beta + 2}{\beta^2} I_O = (1 + 4/\beta + 2/\beta^2) I_O \quad \boxed{0.5}$$

$$I_O = \frac{I_{REF}}{1 + 4/\beta + 2/\beta^2} \cong \frac{I_{REF}}{1 + 4/\beta} \text{ when } \beta^2 \gg 2 \quad \boxed{1}$$

**Answer for Q1(b)**


(i)

$$V_{GS1} = V_{DS1}(sat) + V_{TN} = 1.5 + 0.8 = 2.3 \text{ V}$$

$$I_{REF} = I_O$$

$$R_1 = \frac{V^+ - V_{GS1} - V^-}{I_{REF}} = \frac{15 - 2.3 - (-15)}{1\text{m}} = 27.7 \text{ k}\Omega$$

1

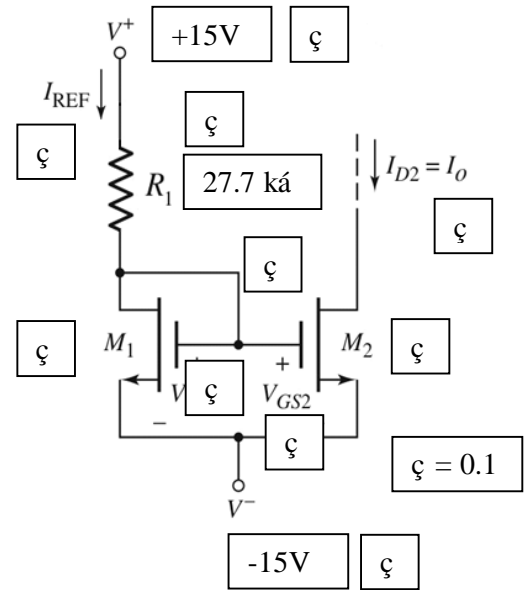

(ii)

$$I_{D1} = I_{D2} = I_O = 1 \text{ mA}$$

0.5

$$I_{D2} = \frac{k'_n}{2} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_T)^2$$

0.5

$$\left(\frac{W}{L}\right)_2 = \frac{I_{D2}}{\frac{k'_n}{2} (V_{GS2} - V_T)^2} = \frac{1 \times 10^{-3}}{\frac{50 \times 10^{-6}}{2} (2.3 - 1.5)^2} = 62.5$$

0.5

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 62.5$$

0.5

(iii)

$$R_o = dV_o / dI_o = 1 / (\lambda I_o) = 1 / (0 \times I_o) = \infty$$

1

$$dI_o = dV_o / \infty = 0$$

1

(iv)

Since MOSFETs can be configured to act like a resistor. The reference current in MOSFET current mirrors can be established using additional transistors.

2

**Question 2 [20 marks]****Answer for Q2(a)**

(i)

$$CMRR_{dB} = 20 \log(A_d/A_{cm}) = 55 \text{ dB}$$

1

$$562.34 = A_d/A_{cm} = A_d / 0.2$$

$$A_d = 112.46$$

1

$$A_d = (g_{m1} R_D) / 2$$

0.5

$$112.46 = (g_{m1} \times 18k) / 2$$

1

$$g_{m1} = (2 \times 112.46) / (18k) = 12.496 \text{ mA/V}$$

$$g_{m1} = 2 \text{ SQRT}(K_{n1} \times I_{D1})$$

0.5

$$I_{D1} = (g_{m1} / 2)^2 / K_{n1} = (12.496 \text{ mA} / 2)^2 / (125 \mu) = 0.3123 \text{ A}$$

1

$$I_Q = 2 I_{D1} = 2 \times 0.3123 = 0.6246 \text{ A}$$

1

(ii)

- To achieve larger  $A_d$  and maintaining  $A_{cm}$ , active load such as cascode may be used to replace  $R_D$ . 1.5
- To maintain  $A_d$ ,  $A_{cm}$  may be decreased if the current source design is used using an improved implementation, e.g. cascode, to increase its output resistance ( $R_O$ ). 1.5

**Answer for Q2(b)**

(i)

$$I_{B5} = \frac{I_{E5}}{(1 + \beta)} = \frac{I_{B3} + I_{B4}}{(1 + \beta)} = \frac{I_{C3} + I_{C4}}{\beta(1 + \beta)} \quad [3]$$

The current  $I_{C3} + I_{C4} \cong I_Q$  [2]

$$\left. \begin{aligned} I_{C1} &= I_{C3} + I_{B5} \\ I_{C2} &= I_{C4} + I_O \end{aligned} \right\} \quad [2]$$

Hence, to keep the current balanced:

$$I_O = I_{B5} = \frac{I_Q}{\beta(1 + \beta)} \quad [2]$$

(ii)

Given,  $I_Q = 0.2$  mA, hence:

$$I_O = \frac{I_Q}{\beta(1 + \beta)} = \frac{0.2\text{m}}{120(1 + 120)} = 13.774 \text{ nA} \quad [2]$$

**Question 3 [25 marks]**

**Answer for Q3(a)**

(i)

$$\begin{aligned}
 I_1 &= (V^+ - V_{BE7} - V^-) / (R_1) && [0.5] \\
 &= (10 - 0.7 - (-10)) / (19.3k) = 1 \text{ mA} && [0.5] \\
 I_Q &= I_1 / (1 + 2/\beta) = 0.9836 \text{ mA} && [1] \\
 I_{C2} &= I_Q / 2 = 0.4918 \text{ mA} && [1] \\
 v_{O2} &= V^+ - I_{C2} R_C = 10 - (0.4918m)(10k) = 5.082 \text{ V} && [1] \\
 I_{R4} &= (v_{O2} - 2 V_{BE(on)}) / (R_4) \\
 &= (5.082 - 1.4) / (11.5k) = 0.320 \text{ mA} \\
 I_{R5} &\approx I_{R4} \text{ (neglecting base currents)} = 0.320 \text{ mA} && [0.5] \\
 v_{O3} &= V^+ - I_{R5} R_5 = 10 - (0.320m)(5k) = 8.399 \text{ V} && [0.5]
 \end{aligned}$$

(ii)

Using  $I_{C2} = 0.4918 \text{ mA}$ ,  $I_{R4} = 0.320 \text{ mA}$ :

$$\begin{aligned}
 A_{d1} &= (g_m / 2)(R_C \parallel R_{i2}) && [1] \\
 g_m &= I_{C2} / V_T = (0.4918\text{mA}) / (26\text{mV}) = \mathbf{18.9153 \text{ mA/V}} && [1] \\
 r_{\pi4} &= \beta V_T / I_{R4} = (120 \times 26\text{m}) / (0.320\text{m}) = 9.750 \text{ k}\Omega && [1] \\
 r_{\pi3} &\approx \beta r_{\pi4} = 120 \times 9.750\text{k} = 1170 \text{ k}\Omega && [1] \\
 R_{i2} &= r_{\pi3} + (1 + \beta) r_{\pi4} \\
 &= 1170\text{k} + (121)(9.750\text{k}) = 2349.75 \text{ k}\Omega && [1] \\
 A_{d1} &= (\mathbf{18.9153\text{m}/2})(10\text{k} \parallel 2349.75\text{k}) = \mathbf{94.176} && [1] \\
 A_2 &\approx (I_{R4} / 2 V_T) R_5 = (0.320\text{m} / (2 \times 26\text{m}))(5\text{k}) = 30.76 && [2] \\
 A_3 &\approx 1 && [1] \\
 A_d &= A_{d1} A_2 A_3 = \mathbf{94.176} \times 30.76 \times 1 = \mathbf{2896.85} && [1]
 \end{aligned}$$

OR

(i)

$$\begin{aligned}
 I_1 &= (V^+ - V_{BE7} - V^-) / (R_1) && [0.5] \\
 &= (10 - 0.7 - (-10)) / (19.3k) = 1 \text{ mA} && [0.5] \\
 I_Q &\approx I_1 \text{ [Since } \beta \gg 1] = 1 \text{ mA} && [1] \\
 I_{C2} &= I_Q / 2 = 0.5 \text{ mA} && [1] \\
 v_{O2} &= V^+ - I_{C2} R_C = 10 - (0.5\text{m})(10\text{k}) = 5 \text{ V} && [1] \\
 I_{R4} &= (v_{O2} - 2 V_{BE(on)}) / (R_4) \\
 &= (5 - 1.4) / (11.5k) = 0.313 \text{ mA} \\
 I_{R5} &\approx I_{R4} \text{ (neglecting base currents)} = 0.313 \text{ mA} && [0.5] \\
 v_{O3} &= V^+ - I_{R5} R_5 = 10 - (0.313\text{m})(5\text{k}) = 8.44 \text{ V} && [0.5]
 \end{aligned}$$

(ii)

Using  $I_{C2} = 0.5 \text{ mA}$ ,  $I_{R4} = 0.313 \text{ mA}$ :

$$\begin{aligned}
 A_{d1} &= (g_m / 2)(R_C \parallel R_{i2}) && [1] \\
 g_m &= I_{C2} / V_T = (0.5\text{mA}) / (26\text{mV}) = 19.23 \text{ mA/V} && [1] \\
 r_{\pi4} &= \beta V_T / I_{R4} = (120 \times 26\text{m}) / (0.313\text{m}) = 9.968 \text{ k}\Omega && [1] \\
 r_{\pi3} &\approx \beta r_{\pi4} = 120 \times 9.968\text{k} = 1196.16 \text{ k}\Omega && [1] \\
 R_{i2} &= r_{\pi3} + (1 + \beta) r_{\pi4} \\
 &= 1196.16\text{k} + (121)(9.968\text{k}) = 2402.29 \text{ k}\Omega && [1] \\
 A_{d1} &= (19.23\text{m}/2)(10\text{k} \parallel 2402.29\text{k}) = 95.75 && [1] \\
 A_2 &\approx (I_{R4} / 2 V_T) R_5 = (0.313\text{m} / (2 \times 26\text{m}))(5\text{k}) = 30.09 && [2] \\
 A_3 &\approx 1 && [1] \\
 A_d &= A_{d1} A_2 A_3 = 95.75 \times 30.09 \times 1 = 2872.54 && [1]
 \end{aligned}$$

**Answer for Q3(b)**

(i)

$$I_Q = I_{D6} = I_{D5}$$

1

$$I_{D5} = K_p (V_{SG5} + V_{TP})^2 = (100 \text{ A/V}^2) \times (1.5 - 0.5)^2 = 100 \text{ A}$$

1

$$\Rightarrow I_Q = I_{D5} = 100 \text{ A} = 0.1 \text{ mA}$$

1

(ii)

$$A_v = A_d A_{v2}$$

0.5

$$A_d = g_m (r_{o2} \parallel r_{o4})$$

0.5

$$g_m = \sqrt{2K_p I_Q} = \sqrt{2(100)(100)} = 141.42 \text{ A/V}$$

1

$$r_{o2} = \frac{1}{\lambda_p I_{D2}} = \frac{1}{0.02 \times 50} = 1 \text{ M}$$

0.5

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{0.01 \times 50} = 2 \text{ M}$$

0.5

$$A_d = (141.42)(1 \text{ M} \parallel 2 \text{ M}) = 94.286$$

0.5

$$A_{v2} = g_{m7} (r_{o7} \parallel r_{o8})$$

0.5

$$g_{m7} = 2\sqrt{K_{n7} I_{D7}} = 2\sqrt{(125)(100)} = 223.6 \text{ A/V}$$

1

$$r_{o7} = \frac{1}{\lambda_n I_{D7}} = \frac{1}{0.01 \times 100} = 1 \text{ M}$$

0.5

$$r_{o8} = \frac{1}{\lambda_p I_{D8}} = \frac{1}{0.02 \times 100} = 0.5 \text{ M}$$

0.5

$$A_{v2} = (223.6)(1 \text{ M} \parallel 0.5 \text{ M}) = 74.53$$

0.5

$$A_v = A_d A_{v2} = 94.286 \times 74.53 = 7027.45$$

0.5

**Question 4 [15 marks]**

**Answer for Q4**

- (a) Cross-over distortion is a condition where the output voltage  $v_O$  of an actual class-B output stage circuit is zero when its input voltage is in a certain voltage range [1].  
 In this condition, both transistors in the circuit are cut-off because the input voltage is within  $V_{EBP}$  to  $V_{BEN}$  [1],  
 thus producing  $v_O = \text{zero}$  and causing distortion at the output of the actual class-B output stage [1].
- (b) Its advantage over class-A is less power dissipation and increased power conversion efficiency [1],  
 while its advantage over class-B is no cross-over distortion [1].

(c) Calculation of  $i_L$ ,  $i_{Cp}$ , and  $i_{Cn}$ :

$$v_O = -3.5 \text{ V} = i_L R_L \quad [0.5]$$

$$\rightarrow i_L = v_O / R_L = (-3.5 \text{ V}) / (1 \text{ k}\Omega) = -3.5 \text{ mA} \quad [1]$$

Therefore,  $Q_p$  is conducting and  $Q_n$  is OFF.

$$\text{Approximate value } |i_L| \hat{=} i_{Cp} = I_S \exp(V_{EBP} / V_T) = 3.5 \text{ mA} \quad [0.5]$$

$$V_{EBP} = V_T \ln(i_{Cp} / I_S) = (26 \text{ mV}) \ln(3.5 \text{ mA} / 2 \times 10^{-15}) = 0.7329 \text{ V} \quad [0.5]$$

$$V_{BEN} = V_{BB} - V_{EBP} = 1.4 - 0.7329 = 0.6671 \text{ V} \quad [0.5]$$

$$\rightarrow i_{Cn} = I_S \exp(V_{BEN} / V_T) = (2 \times 10^{-15}) \exp(0.6671 / 0.026) = 0.2779 \text{ mA} \quad [1]$$

$$i_{Cn} = i_{Cp} + i_L \quad [0.5]$$

$$\text{Actual value of } i_{Cp} = i_{Cn} \hat{=} i_L = 0.2779 \text{ mA} \hat{=} (-3.5 \text{ mA}) \quad [1]$$

$$\rightarrow i_{Cp} = 3.7779 \text{ mA} \quad [0.5]$$

2<sup>nd</sup> iteration

$$V_{EBP} = 0.73494 \text{ V}$$

$$V_{BEN} = 0.66506 \text{ V}$$

$$i_{Cn} = 0.2570 \text{ mA}$$

$$i_{Cp} = 3.757 \text{ mA}$$

(d) Calculation of power dissipation:

$$P_{Qn} = i_{Cn} V_{CEn} \quad [1]$$

$$V_{CEn} = +V_{CC} \hat{=} v_O = +6 \hat{=} (-3.5) = 9.5 \text{ V} \quad [0.5]$$

$$\rightarrow P_{Qn} = (0.2779 \text{ mA})(9.5 \text{ V}) = 2.640 \text{ mW} \quad [0.5]$$

**Or**

$$P_{Qn} = (0.2570 \text{ mA})(9.5 \text{ V}) = 2.441 \text{ mW}$$

$$P_{Qp} = i_{Cp} V_{ECp} \quad [1]$$

$$V_{ECp} = v_O \hat{=} (-V_{CC}) = -3.5 - (-6) = 2.5 \text{ V} \quad [0.5]$$

$$\rightarrow P_{Qp} = (3.7779 \text{ mA})(2.5 \text{ V}) = 9.44475 \text{ mW} \quad [0.5]$$

**Or**

$$P_{Qp} = (3.757 \text{ mA})(2.5 \text{ V}) = 9.3925 \text{ mW}$$





(d)

$$v_2 = [R_4 / (R_3 + R_4)] v_I \quad [1]$$

$$= [(50k) / (50k + 25k)] v_I = [2/3] v_I \quad [0.5]$$

$$v_1 = v_2 = [2/3] v_I \quad [1]$$

$$v_O = [(1 + R_2 / R_1)] v_1 \quad [1]$$

$$= [(1 + 200k / 25k)] [2/3] v_I = 6 v_I \quad [0.5]$$

$$A_v = v_O / v_I = 6 \quad [1]$$

(e)

$$R_F / R_1 = 5 \quad \rightarrow R_F = 5 R_1 \quad [0.5]$$

and  $R_F / R_2 = 10 \quad \rightarrow R_F = 10 R_2 \quad [0.5]$

So, resistor  $R_2$  will be the **smallest** value. Set  $R_2 = 15 \text{ k}\Omega$ . [1]

$$\rightarrow R_F = 10 R_2 = 10 \times 15 \text{ k} = 150 \text{ k}\Omega \quad [0.5]$$

and  $R_1 = R_F / 4 = 150 \text{ k} / 4 = 30 \text{ k}\Omega \quad [0.5]$

$$R_N = R_1 \parallel R_2 = 30 \text{ k} \parallel 15 \text{ k} = 10 \text{ k}$$

$$1 + R_F / R_N = 1 + 150 \text{ k} / (10 \text{ k}) = 16$$

$$(1 + R_F / R_N)(R_P / R_A) = (16)(R_P / R_A) = 5 \quad [0.5]$$

and  $(1 + R_F / R_N)(R_P / R_B) = (16)(R_P / R_B) = 2 \quad [0.5]$

So,  $(R_A / R_B) = 2/5$ . [0.5]

Choose  $R_A = 80 \text{ k}\Omega$ , [1]

then  $R_B = 200 \text{ k}\Omega$  [1]

$$R_P = (2 R_B) / 16 = (5 R_A) / 16$$

$$\rightarrow R_P = 25 \text{ k}\Omega \quad [0.5]$$

$$R_P = R_A \parallel R_B \parallel R_C$$

$$\rightarrow R_C = 44.45 \text{ k}\Omega \quad [1]$$