

EEEE273 - Quiz 2 [Question Set 1]
 SEMESTER 2, ACADEMIC YEAR 2012/2013
 Date: 19 November 2012

Question:

Refer to **Figure 1**. Assume $\beta = 50$ and $V_{BE(on)} = 0.7 \text{ V}$ for all BJTs in the circuit. For $R_1 = 12 \text{ k}\Omega$ and $R_C = 10 \text{ k}\Omega$, find the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output at v_{C2}** . Write your answer as precise as possible, in 4 decimal points, with proper Units for the parameters. [10 marks]

Answer:

$$I_{REF} = (V^+ - V_{BE3} - V^-) / (R_1) \quad [2]$$

$$= (10 - 0.7 - (-10)) / (12k) = 1.6083 \text{ mA} \quad [1]$$

$$I_Q = I_{REF} / (1 + 2/\beta) \quad [2]$$

$$= 1.608\text{m} / (1 + 2/50) = 1.5464 \text{ mA} \quad [1]$$

$$A_d = (g_m R_C) / 2 = (I_Q R_C) / (4V_T) \quad [2]$$

$$g_m = I_Q / (2V_T) \quad [1]$$

$$= (1.5464\text{m}) / (2 \times 26\text{m}) = 29.7399 \text{ mA/V} \quad [1]$$

$$A_d = (29.7399\text{m} \times 10\text{k}) / (2) = 148.699 \text{ V/V} \quad [1]$$

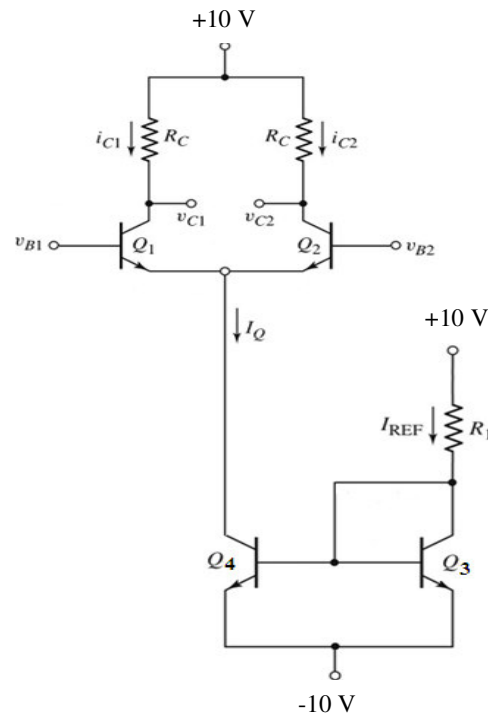


Figure 1

EEEE273 - Quiz 2 [Question Set 2]
 SEMESTER 2, ACADEMIC YEAR 2012/2013
 Date: 19 November 2012

Question:

Refer to **Figure 1**. Assume $\beta = 40$ and $V_{BE(on)} = 0.7 \text{ V}$ for all BJTs in the circuit. For $R_1 = 15 \text{ k}\Omega$ and $R_C = 12 \text{ k}\Omega$, find the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output at v_{C2}** . Write your answer as precise as possible, in 4 decimal points, with proper Units for the parameters. [10 marks]

Answer:

$$\begin{aligned}
 I_{REF} &= (V^+ - V_{BE3} - V^-) / (R_1) && [2] \\
 &= (10 - 0.7 - (-10)) / (15\text{k}) = 1.2867 \text{ mA} && [1] \\
 I_Q &= I_{REF} / (1 + 2/\beta) && [2] \\
 &= 1.2867\text{m} / (1 + 2/40) = 1.2254 \text{ mA} && [1] \\
 A_d &= (g_m R_C) / 2 = (I_Q R_C) / (4V_T) && [2] \\
 g_m &= I_Q / (2V_T) && [1] \\
 &= (1.2254\text{m}) / (2 \times 26\text{m}) = 23.5653 \text{ mA/V} && [1] \\
 A_d &= (23.5653\text{m} \times 12\text{k}) / (2) = 141.392 \text{ V/V} && [1]
 \end{aligned}$$

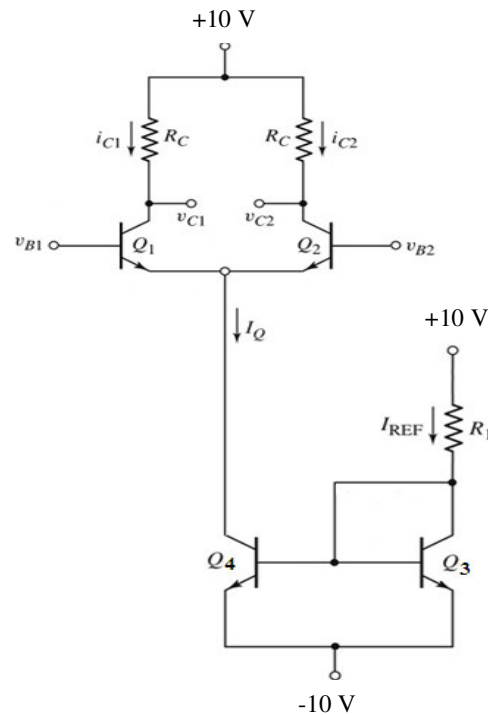


Figure 1

EEEE273 - Quiz 2 [Question Set 3]
 SEMESTER 2, ACADEMIC YEAR 2012/2013
 Date: 19 November 2012

Question:

Refer to **Figure 1**. Assume $\beta = 40$ and $V_{BE(on)} = 0.7 \text{ V}$ for all BJTs in the circuit. For $R_1 = 14 \text{ k}\Omega$ and $R_C = 15 \text{ k}\Omega$, find the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output at v_{C2}** . Write your answer as precise as possible, in 4 decimal points, with proper Units for the parameters. [10 marks]

Answer:

$$\begin{aligned}
 I_{REF} &= (V^+ - V_{BE3} - V^-) / (R_1) & [2] \\
 &= (10 - 0.7 - (-10)) / (14\text{k}) = 1.3786 \text{ mA} & [1] \\
 I_Q &= I_{REF} / (1 + 2/\beta) & [2] \\
 &= 1.3786\text{m} / (1 + 2/40) = 1.3129 \text{ mA} & [1] \\
 A_d &= (g_m R_C) / 2 = (I_Q R_C) / (4V_T) & [2] \\
 g_m &= I_Q / (2V_T) & [1] \\
 &= (1.3129\text{m}) / (2 \times 26\text{m}) = 25.2486 \text{ mA/V} & [1] \\
 A_d &= (25.2486\text{m} \times 15\text{k}) / (2) = 189.364 \text{ V/V} & [1]
 \end{aligned}$$

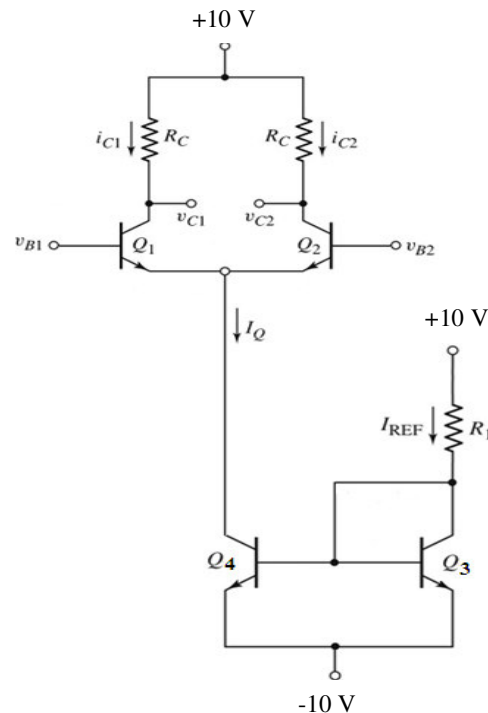


Figure 1

EEEE273 - Quiz 2 [Question Set 4]
 SEMESTER 2, ACADEMIC YEAR 2012/2013
 Date: 19 November 2012

Question:

Refer to **Figure 1**. Assume $\beta = 50$ and $V_{BE(on)} = 0.7 \text{ V}$ for all BJTs in the circuit. For $R_1 = 18 \text{ k}\Omega$ and $R_C = 12 \text{ k}\Omega$, find the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output at v_{C2}** . Write your answer as precise as possible, in 4 decimal points, with proper Units for the parameters. [10 marks]

Answer:

$$\begin{aligned}
 I_{REF} &= (V^+ - V_{BE3} - V^-) / (R_1) & [2] \\
 &= (10 - 0.7 - (-10)) / (18\text{k}) = 1.0722 \text{ mA} & [1] \\
 I_Q &= I_{REF} / (1 + 2/\beta) & [2] \\
 &= 1.0722\text{m} / (1 + 2/50) = 1.03098 \text{ mA} & [1] \\
 A_d &= (g_m R_C) / 2 = (I_Q R_C) / (4V_T) & [2] \\
 g_m &= I_Q / (2V_T) & [1] \\
 &= (1.03098\text{m}) / (2 \times 26\text{m}) = 19.8265 \text{ mA/V} & [1] \\
 A_d &= (19.8265\text{m} \times 12\text{k}) / (2) = 118.959 \text{ V/V} & [1]
 \end{aligned}$$

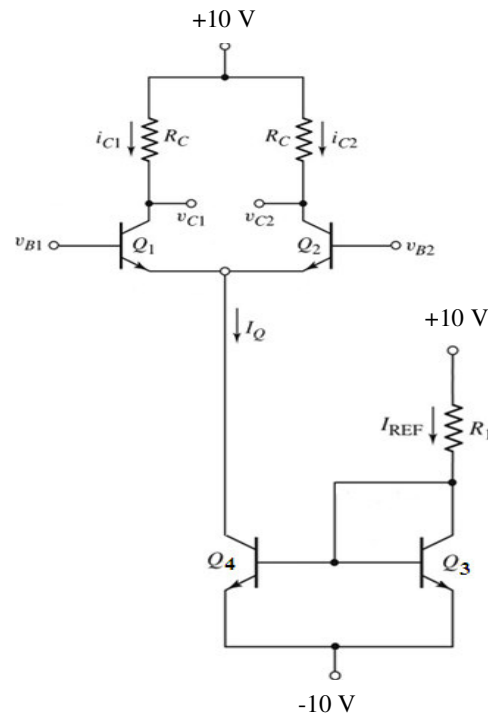


Figure 1