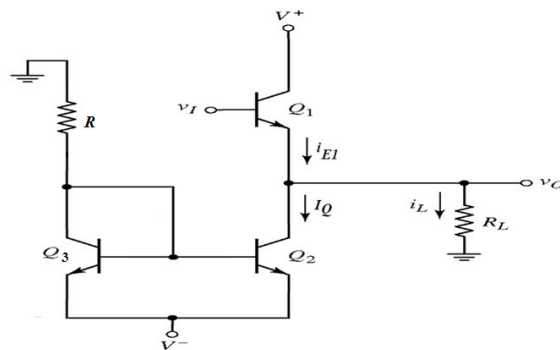


**Question:**

**Figure 1** shows a **class-A** emitter follower. The circuit parameters are  $V^+ = +12\text{ V}$ ,  $V^- = -12\text{ V}$ ,  $R = 1\text{ k}\Omega$ , and  $R_L = 330\ \Omega$ . The transistor parameters are  $V_{BE(\text{on})} = 0.7\text{ V}$  for all transistors,  $\beta = \infty$  for  $Q_1$ , and  $\beta = 50$  for  $Q_2$  and  $Q_3$ .

- (a) Find  $I_Q$ . [3 marks]  
 (b) For  $v_O = 0$ , find the power dissipated in the transistor  $Q_1$  and the power dissipated in the current source ( $Q_2$ ,  $Q_3$ , and  $R$ ). [5 marks]  
 (c) Determine the power conversion efficiency ( $\eta$ ) for a symmetrical sine-wave output voltage with a peak value of  $6\text{ V}$ . [2 marks]

**Write your answer using pen**, in 4 decimal points, with **proper Units** for the parameters.



**Figure 1**

**Answer:**

(a)  

$$I_R = (0 - V_{BE3(\text{on})} - V^-) / R = (0 - 0.7 - (-12)) / (1\text{k}) = 11.3\text{ mA} \quad [1, 0.5]$$

$$I_Q = I_R / (1 + 2/\beta) = (11.3\text{m}) / (1 + 2/50) = 10.865\text{ mA} \quad [1, 0.5]$$

(b)  

$$P_{DQ1} = V_{CE1} \times I_{C1} = (V^+ - v_O) \times I_{E1} = (V^+ - v_O) \times I_Q = (12 - 0) \times (10.865\text{m}) = 0.13038\text{ W} \quad [1.5]$$

$$P_{DCS} = P_{DQ2} + P_{DQ3} + P_{DR} = 0.13038\text{ W} + 0.13038\text{ W} + 0.1356\text{ W} = 0.39636\text{ W} \quad [0.5]$$

$$P_{DQ2} = V_{CE2} \times I_{C2} = (v_O - V^-) \times I_Q = (0 - (-12)) \times (10.865\text{m}) = 0.13038\text{ W} \quad [1]$$

$$P_{DQ3} + P_{DR} = (0 - V^-) \times I_R = (0 - (-12)) \times (11.3\text{m}) = 0.1356\text{ W} \quad [1]$$

$$P_{DCS} = 0.13038 + 0.1356 = 0.26598\text{ W} \quad [0.5]$$

(c)  
 Average power to load,  $P^*_L = V_p^2 / (2 R_L) = (6 \times 6) / (2 \times 330) = 0.05454\text{ W} \quad [0.5]$   
 Average power supplied,  $P^*_S = P_{DQ1} + P_{DCS} = 0.13038 + 0.26598 = 0.39636\text{ W} \quad [0.5]$   

$$\eta = (P^*_L / P^*_S) \times 100\% = (0.05454 / 0.39636) \times 100\% = 13.76\% \quad [1]$$


EEEE273 - Quiz 3 [Question Set 2]  
 SEMESTER 2, ACADEMIC YEAR 2012/2013  
 Date: 10 December 2012

**Question:**

**Figure 1** shows a **class-A** emitter follower. The circuit parameters are  $V^+ = +14\text{ V}$ ,  $V^- = -14\text{ V}$ ,  $R = 1\text{ k}\Omega$ , and  $R_L = 330\ \Omega$ . The transistor parameters are  $V_{BE(\text{on})} = 0.7\text{ V}$  for all transistors,  $\beta = \infty$  for  $Q_1$ , and  $\beta = 50$  for  $Q_2$  and  $Q_3$ .

- (a) Find  $I_Q$ . [3 marks]  
 (b) For  $v_O = 0$ , find the power dissipated in the transistor  $Q_1$  and the power dissipated in the current source ( $Q_2$ ,  $Q_3$ , and  $R$ ). [5 marks]  
 (c) Determine the power conversion efficiency ( $\eta$ ) for a symmetrical sine-wave output voltage with a peak value of  $6\text{ V}$ . [2 marks]

**Write your answer using pen**, in 4 decimal points, with **proper Units** for the parameters.

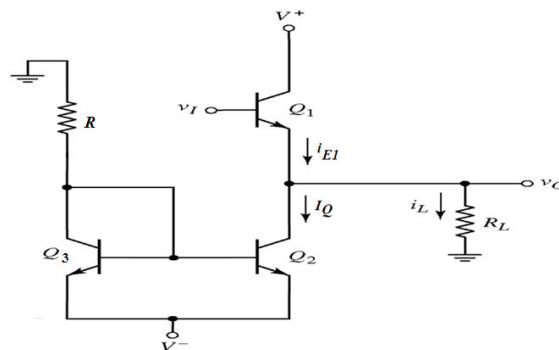

**Figure 1**

**Answer:**

(a)  

$$I_R = (0 - V_{BE3(\text{on})} - V^-) / R = (0 - 0.7 - (-14)) / (1\text{k}) = 13.3\text{ mA} \quad [1, 0.5]$$

$$I_Q = I_R / (1 + 2/\beta) = (13.3\text{m}) / (1 + 2/50) = 12.788\text{ mA} \quad [1, 0.5]$$

(b)  

$$P_{DQ1} = V_{CE1} \times I_{C1} = (V^+ - v_O) \times I_{E1} = (V^+ - v_O) \times I_Q = (14 - 0) \times (12.788\text{m}) = 0.17903\text{ W} \quad [1.5]$$

$$P_{DCS} = P_{DQ2} + P_{DQ3} + P_{DR} \quad [0.5]$$

$$P_{DQ2} = V_{CE2} \times I_{C2} = (v_O - V^-) \times I_Q = (0 - (-14)) \times (12.788\text{m}) = 0.17903\text{ W} \quad [1]$$

$$P_{DQ3} + P_{DR} = (0 - V^-) \times I_R = (0 - (-14)) \times (13.3\text{m}) = 0.1862\text{ W} \quad [1]$$

$$P_{DCS} = 0.17903 + 0.1862 = 0.36523\text{ W} \quad [0.5]$$

(c)  
 Average power to load,  $P^*_L = V_p^2 / (2 R_L) = (6 \times 6) / (2 \times 330) = 0.05454\text{ W} \quad [0.5]$   
 Average power supplied,  $P^*_S = P_{DQ1} + P_{DCS} = 0.17903 + 0.36523 = 0.54426\text{ W} \quad [0.5]$   

$$\eta = (P^*_L / P^*_S) \times 100\% = (0.05454 / 0.54426) \times 100\% = 10.02\% \quad [1]$$

EEEE273 - Quiz 3 [Question Set 3]  
 SEMESTER 2, ACADEMIC YEAR 2012/2013  
 Date: 10 December 2012

**Question:**

**Figure 1** shows a **class-A** emitter follower. The circuit parameters are  $V^+ = +12\text{ V}$ ,  $V^- = -12\text{ V}$ ,  $R = 1.2\text{ k}\Omega$ , and  $R_L = 330\ \Omega$ . The transistor parameters are  $V_{BE(\text{on})} = 0.7\text{ V}$  for all transistors,  $\beta = \infty$  for  $Q_1$ , and  $\beta = 50$  for  $Q_2$  and  $Q_3$ .

- (a) Find  $I_Q$ . [3 marks]  
 (b) For  $v_O = 0$ , find the power dissipated in the transistor  $Q_1$  and the power dissipated in the current source ( $Q_2$ ,  $Q_3$ , and  $R$ ). [5 marks]  
 (c) Determine the power conversion efficiency ( $\eta$ ) for a symmetrical sine-wave output voltage with a peak value of  $6\text{ V}$ . [2 marks]

Write your answer using pen, in 4 decimal points, with proper Units for the parameters.

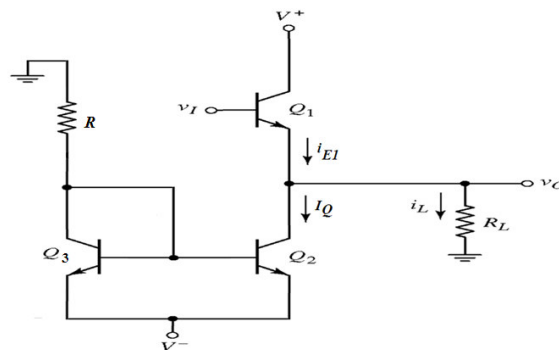


Figure 1

**Answer:**

(a)  

$$I_R = (0 - V_{BE3(\text{on})} - V^-) / R = (0 - 0.7 - (-12)) / (1.2\text{k}) = 9.4167\text{ mA} \quad [1, 0.5]$$

$$I_Q = I_R / (1 + 2/\beta) = (9.4167\text{m}) / (1 + 2/50) = 9.0544\text{ mA} \quad [1, 0.5]$$

(b)  

$$P_{DQ1} = V_{CE1} \times I_{C1} = (V^+ - v_O) \times I_{E1} = (V^+ - v_O) \times I_Q = (12 - 0) \times (9.0544\text{m}) = 0.10865\text{ W} \quad [1.5]$$

$$P_{DCS} = P_{DQ2} + P_{DQ3} + P_{DR} \quad [0.5]$$

$$P_{DQ2} = V_{CE2} \times I_{C2} = (v_O - V^-) \times I_Q = (0 - (-12)) \times (9.0544\text{m}) = 0.10865\text{ W} \quad [1]$$

$$P_{DQ3} + P_{DR} = (0 - V^-) \times I_R = (0 - (-12)) \times (9.4167\text{m}) = 0.1130\text{ W} \quad [1]$$

$$P_{DCS} = 0.10865 + 0.1130 = 0.22165\text{ W} \quad [0.5]$$

(c)  
 Average power to load,  $P^*_L = V_p^2 / (2 R_L) = (6 \times 6) / (2 \times 330) = 0.05454\text{ W} \quad [0.5]$   
 Average power supplied,  $P^*_S = P_{DQ1} + P_{DCS} = 0.10865 + 0.22165 = 0.3303\text{ W} \quad [0.5]$   

$$\eta = (P^*_L / P^*_S) \times 100\% = (0.05454 / 0.3303) \times 100\% = 16.51\% \quad [1]$$

**Question:**

**Figure 1** shows a **class-A** emitter follower. The circuit parameters are  $V^+ = +14\text{ V}$ ,  $V^- = -14\text{ V}$ ,  $R = 1.2\text{ k}\Omega$ , and  $R_L = 330\ \Omega$ . The transistor parameters are  $V_{BE(\text{on})} = 0.7\text{ V}$  for all transistors,  $\beta = \infty$  for  $Q_1$ , and  $\beta = 50$  for  $Q_2$  and  $Q_3$ .

- (a) Find  $I_Q$ . [3 marks]  
 (b) For  $v_O = 0$ , find the power dissipated in the transistor  $Q_1$  and the power dissipated in the current source ( $Q_2$ ,  $Q_3$ , and  $R$ ). [5 marks]  
 (c) Determine the power conversion efficiency ( $\eta$ ) for a symmetrical sine-wave output voltage with a peak value of  $6\text{ V}$ . [2 marks]

Write your answer using pen, in 4 decimal points, with proper Units for the parameters.

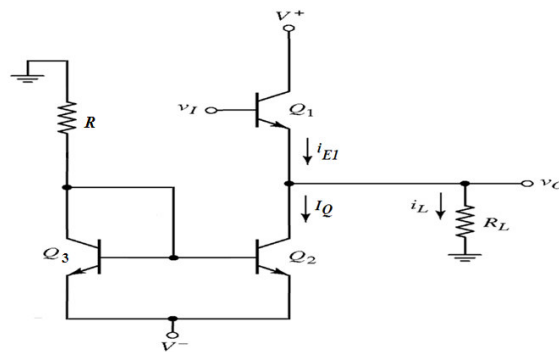


Figure 1

**Answer:**

(a)  
 $I_R = (0 - V_{BE3(\text{on})} - V^-) / R = (0 - 0.7 - (-14)) / (1.2\text{k}) = 11.083\text{ mA}$  [1, 0.5]  
 $I_Q = I_R / (1 + 2/\beta) = (11.083\text{m}) / (1 + 2/50) = 10.657\text{ mA}$  [1, 0.5]

(b)  
 $P_{DQ1} = V_{CE1} \times I_{C1} = (V^+ - v_O) \times I_{E1} = (V^+ - v_O) \times I_Q = (14 - 0) \times (10.657\text{m}) = 0.14919\text{ W}$  [1.5]  
 $P_{DCS} = P_{DQ2} + P_{DQ3} + P_{DR}$  [0.5]  
 $P_{DQ2} = V_{CE2} \times I_{C2} = (v_O - V^-) \times I_Q = (0 - (-14)) \times (10.657\text{m}) = 0.14919\text{ W}$  [1]  
 $P_{DQ3} + P_{DR} = (0 - V^-) \times I_R = (0 - (-14)) \times (11.083\text{m}) = 0.15516\text{ W}$  [1]  
 $P_{DCS} = 0.14919 + 0.15516 = 0.30435\text{ W}$  [0.5]

(c)  
 Average power to load,  $P^*_L = V_p^2 / (2 R_L) = (6 \times 6) / (2 \times 330) = 0.05454\text{ W}$  [0.5]  
 Average power supplied,  $P^*_S = P_{DQ1} + P_{DCS} = 0.14919 + 0.30435 = 0.45354\text{ W}$  [0.5]  
 $\eta = (P^*_L / P^*_S) \times 100\% = (0.05454 / 0.45354) \times 100\% = 12.02\%$  [1]