

**Question:**

Study the output stage circuit shown in **Figure 1** carefully. Let  $R_L = 1 \text{ k}\Omega$ ,  $V_{BB} = 1.42 \text{ V}$  and the reverse saturation current for the transistors,  $I_S = 2 \times 10^{-15} \text{ A}$ . Assume  $\beta \gg 1$ . For the case of the output voltage  $v_O = -3.8 \text{ V}$ :

- (a) Determine  $i_L$ ,  $i_{Cp}$ , and  $i_{Cn}$ . [6 marks]
- (b) Calculate the power dissipated in transistor  $Q_n$  and  $Q_p$ . [4 marks]

Write your answer using pen, in 4 decimal points, with proper Units for the parameters.

**Answer:**

(a)

$$v_O = -3.8 \text{ V} = i_L R_L \quad [0.5]$$

$$\Rightarrow i_L = v_O / R_L = (-3.8 \text{ V}) / (1 \text{ k}\Omega) = -3.8 \text{ mA} \quad [1]$$

Therefore,  $Q_p$  is conducting and  $Q_n$  is OFF.

Approximate value

$$|i_L| \approx i_{Cp} = I_S \exp(V_{EBP}/V_T) = 3.8 \text{ mA} \quad [0.5]$$

$$V_{EBP} = V_T \ln(i_{Cp}/I_S) = (26 \text{ m}) \ln(3.8 \text{ mA} / 2 \times 10^{-15}) = 0.73509 \text{ V} \quad [0.5]$$

$$\Rightarrow V_{BEN} = V_{BB} - V_{EBP} = 1.42 - 0.73509 = 0.68491 \text{ V} \quad [0.5]$$

$$\Rightarrow i_{Cn} = I_S \exp(V_{BEN}/V_T) = (2 \times 10^{-15}) \exp(0.68491/0.026) = \mathbf{0.55136 \text{ mA}} \quad [1]$$

$$i_{Cn} = i_{Cp} + i_L \quad [0.5]$$

Actual value of

$$\Rightarrow i_{Cp} = i_{Cn} - i_L = 0.55136 \text{ mA} - (-3.8 \text{ mA}) \quad [1]$$

$$\Rightarrow i_{Cp} = \mathbf{4.35136 \text{ mA}} \quad [0.5]$$

2<sup>nd</sup> iteration

$$V_{EBP} = 0.73862 \text{ V}$$

$$V_{BEN} = 0.68138 \text{ V}$$

$$i_{Cn} = \mathbf{0.48150 \text{ mA}}$$

$$i_{Cp} = \mathbf{4.28150 \text{ mA}}$$

(b) Power dissipation:

$$P_{Qn} = i_{Cn} V_{CEn} \quad [1]$$

$$V_{CEn} = +V_{CC} - v_O = +6 - (-3.8) = 9.8 \text{ V} \quad [0.5]$$

$$\Rightarrow P_{Qn} = (0.55136 \text{ mA})(9.8 \text{ V}) = \mathbf{5.40334 \text{ mW}} \quad [0.5]$$

$$\text{Or } P_{Qn} = (0.48150 \text{ mA})(9.8 \text{ V}) = \mathbf{4.71869 \text{ mW}} \quad [0.5]$$


$$P_{Qp} = i_{Cp} V_{ECP} \quad [1]$$

$$V_{ECP} = v_O - (-V_{CC}) = -3.8 - (-6) = 2.2 \text{ V} \quad [0.5]$$

$$\Rightarrow P_{Qp} = (4.35136 \text{ mA})(2.2 \text{ V}) = \mathbf{9.5730 \text{ mW}} \quad [0.5]$$

$$\text{Or } P_{Qp} = (4.28150 \text{ mA})(2.2 \text{ V}) = \mathbf{9.4193 \text{ mW}} \quad [0.5]$$

Note: Answer in red can be accepted.

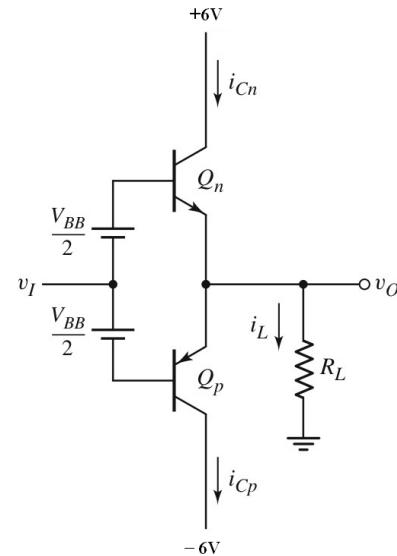

**Figure 1**

VT (V)	0.026
--------	-------

Pop Quiz 3	QS1	QS2	QS3	QS4
Vcc (V)	6	6	6	6
-Vcc (V)	-6	-6	-6	-6
Vbb (V)	1.420	1.420	1.380	1.380
I <sub>s</sub> (x10 <sup>-15</sup> A)	2.000	2.000	2.000	2.000
V <sub>o</sub> (V)	-3.8	-3.6	-3.8	-3.6
R <sub>L</sub> (kΩ)	1	1	1	1

$$I_L = V_o / R_L$$

$$i_{Cp} \approx I_L$$

$$V_{EBp} = VT \ln(i_{Cp}/I_s)$$

$$V_{BEn} = V_{bb} - V_{EBp}$$

$$i_{Cn1} = I_s \exp(V_{BEn}/VT)$$

$$i_{Cp1} = i_{Cn1} - I_L$$

$$V_{EBp1} = VT \ln(i_{Cp1}/I_s)$$

$$V_{BEn1} = V_{bb} - V_{EBp1}$$

$$i_{Cn2} = I_s \exp(V_{BEn1}/VT)$$

$$i_{Cp2} = i_{Cn2} - I_L$$

$$V_{CEn} = V_{cc} - V_o$$

$$P_{Qn1} = V_{CEn} * i_{Cn1}$$

$$P_{Qn2} = V_{CEn} * i_{Cn2}$$

$$V_{ECp} = V_o - (-V_{cc})$$

$$P_{Qp1} = V_{ECp} * i_{Cp1}$$

$$P_{Qp2} = V_{ECp} * i_{Cp2}$$

IL (mA)	-3.80000	-3.60000	-3.80000	-3.60000
i <sub>Cp</sub> (mA)	3.80000	3.60000	3.80000	3.60000
V <sub>EBp</sub> (V)	0.73509	0.73369	0.73509	0.73369
V <sub>BEn</sub> (V)	0.68491	0.68631	0.64491	0.64631
i <sub>Cn1</sub> (mA)	0.55136	0.58199	0.11838	0.12496
i <sub>Cp1</sub> (mA)	4.35136	4.18199	3.91838	3.72496
V <sub>EBp1</sub> (V)	0.73862	0.73759	0.73589	0.73458
V <sub>BEn1</sub> (V)	0.68138	0.68241	0.64411	0.64542
i <sub>Cn2</sub> (mA)	0.48150	0.50100	0.11481	0.12077
i <sub>Cp2</sub> (mA)	4.28150	4.10100	3.91481	3.72077
V <sub>CEn</sub> (V)	9.80	9.60	9.80	9.60
P <sub>Qn1</sub> (mW)	5.40334	5.58713	1.16016	1.19962
P <sub>Qn2</sub> (mW)	4.71869	4.80959	1.12511	1.15938
V <sub>ECp</sub> (V)	2.20	2.40	2.20	2.40
P <sub>Qp1</sub> (mW)	9.57300	10.03678	8.62044	8.93990
P <sub>Qp2</sub> (mW)	9.41930	9.84240	8.61258	8.92984