



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION**

SEMESTER 1 2013 / 2014 – MODEL ANSWER

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : September 2013

TIME : 3 hours

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **Six (6)** questions in **Ten (10)** pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided.
4. Write answer to different question on a **new page**.
5. For all calculations, assume that $V_T = 26 \text{ mV}$.
6. Use at least **4 significant numbers** in all calculations.

THIS QUESTION PAPER CONSISTS OF TEN (10) PRINTED PAGES INCLUDING THIS COVER PAGE.

Answer for Q1: [20 marks]

$$A_d = \frac{g_m R_C}{2} \quad \boxed{1}$$

$$g_m = \frac{I_C}{V_T} = \frac{I_Q}{2V_T} = \frac{1.5\text{m}}{2(26\text{m})} = 28.846 \text{ mA/V} \quad \boxed{1, 1, 0.5}$$


$$R_C = \frac{2A_d}{g_m} = \frac{2(150)}{28.846\text{m}} = 10.400 \text{ k}\Omega \quad \boxed{1, 1, 0.5}$$

$$I_Q = \frac{I_{REF}}{1 + 2/\beta} \quad \boxed{1}$$

$$I_{REF} = I_Q(1 + 2/\beta) = 1.5\text{m}(1 + 2/50) = 1.56 \text{ mA} \quad \boxed{1, 1, 0.5}$$

$$R_1 = \frac{V^+ - V_{BE(on)} - V^-}{I_{REF}} = \frac{10 - 0.7 - (-10)}{1.56\text{m}} = 12.372 \text{ k}\Omega \quad \boxed{1, 1, 0.5}$$

Total = 12 marks

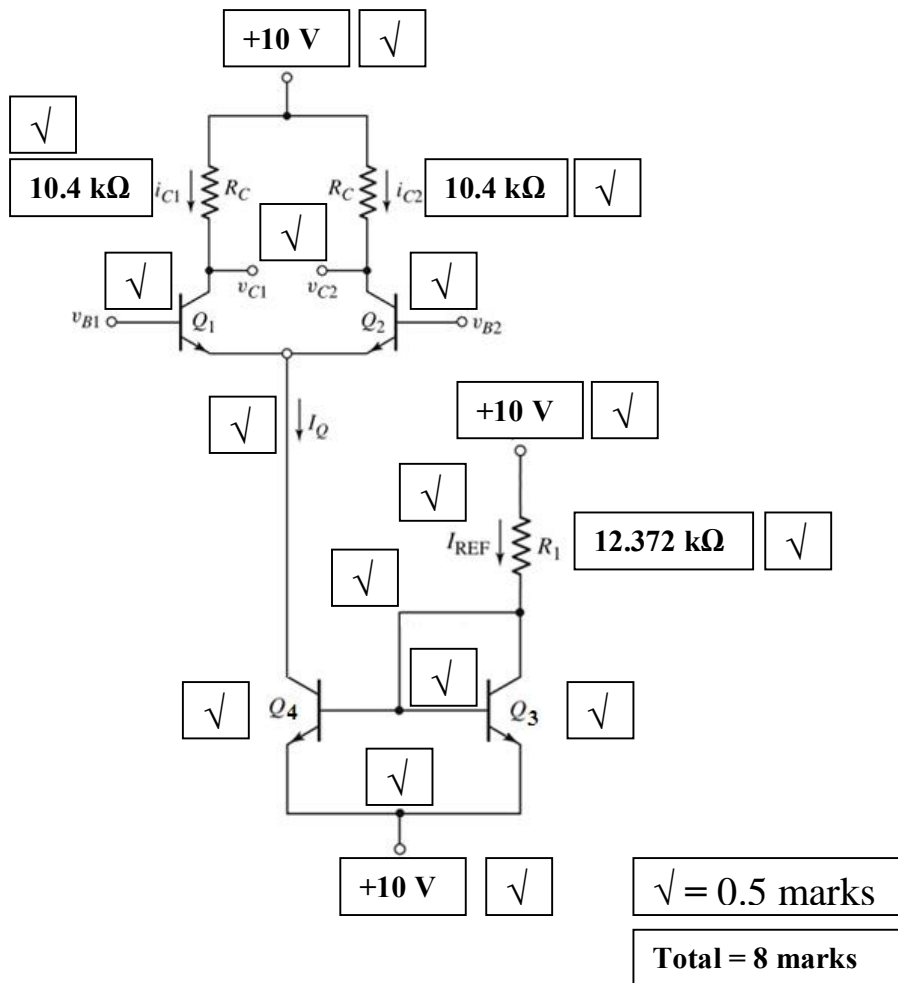

Answer for Q2: [15 marks]

Q2(a) [5 marks]

$$I_O = \frac{I_{CQ}}{2} = 0.09mA$$


0.5, 0.5

$$r_{O4} = \frac{V_{AP}}{I_O} = \frac{100}{0.09m} = 1.111M\Omega$$

0.5, 0.5

$$R_{OAL} = \beta r_{O4} = (150)(1.111M) = 166.7M\Omega$$

0.5, 0.5

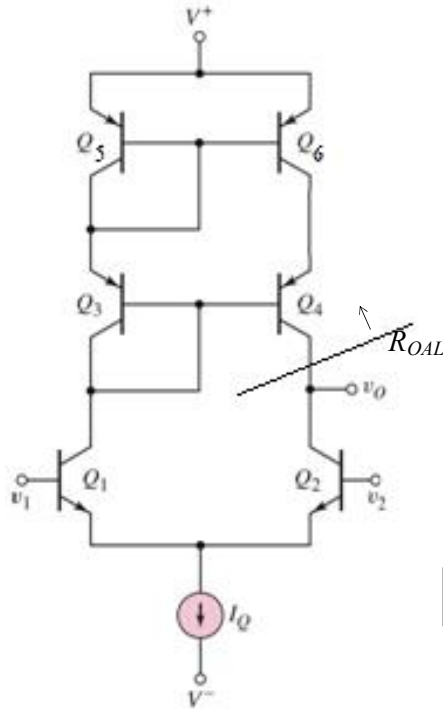

2

Q2(b) [6 marks]

$$v_O = (g_{m2}v_d)R_O$$

1

$$R_O = R_{OAL} \parallel r_{O2}$$

1

$$r_{O2} = \frac{V_{AN}}{I_O} = \frac{120}{0.09m} = 1.333M\Omega$$

0.5, 0.5

$$R_O = 166.7M \parallel 1.333M = 1.322M\Omega$$

0.5, 0.5

$$g_{m2} = \frac{I_O}{V_T} = \frac{0.09m}{0.026} = 3.462mA/V^2$$

0.5, 0.5

$$A_d = g_{m2}R_O = (3.462m)(1.322M) = 4578$$

0.5, 0.5

Q2(c) [4 marks]

$$v_O = A_d v_d = (4578)(5 \sin \omega t)mV = 22.89 \sin(\omega t)V$$

1, 0.5, 0.5

The total output resistance of the differential amplifier will be smaller resulting in smaller value for the small-signal voltage gain, A_d . The output voltage will be a lot smaller than 22.89 V.

2

Answer for Q3: [10 marks]

Q3(a) [3 marks]

- Class AB has less power dissipation than Class A (or Class AB has more power conversion efficiency than Class A) [1 mark]
 - since the output stage transistors are not continuously on. [0.5 mark]
- Class AB has removed the cross-over distortion of Class B [1 mark]
 - by providing a constant bias voltage V_{BB} across the output stage transistors. [0.5 mark]

Q3(b) [7 marks]

(i)

$$v_{O(\max)} = V^+ - V_{CE(\text{sat})} = 10 - 0.2 = 9.8 \text{ V}$$

1

1/2

$$I_Q = i_{L(\max)} = v_{O(\max)} / R_L = 9.8 / 1\text{k} = 9.8 \text{ mA}$$

1

1/2

(ii)

$$R = (0 - V_{BE} - (-10)) / I_Q = 9.3 / 9.8\text{m} = 949$$

1

1

(iii)

$$\overline{P_L} = \frac{1}{2} (i_L(\max))^2 R_L = \frac{1}{2} (9.8)^2 (1) \Rightarrow \overline{P_L} = 48.02 \text{ mW} \quad \boxed{1/2}$$

$$\overline{P_S} = I_Q (V^+ - V^-) + I_Q (0 - V^-) \quad \boxed{1/2}$$

$$= 9.8(20) + 9.8(10) \Rightarrow \overline{P_S} = 294 \text{ mW}$$

$$\eta = \frac{\overline{P_L}}{\overline{P_S}} = \frac{48.02}{294} \Rightarrow \eta = 16.3\%$$

1/2

1/2

Answer for Q4: [20 marks]

Calculating transistors aspect ratios:

$$A_v(\text{dB}) = 100 \text{ dB}$$

$$100 = 20 \log_{10}(A_v)$$

[2 marks]

So, $A_v = 100,000 \text{ V/V}$

[1 mark]

$$A_v = 100,000 = A_{d1} \times A_{v2}$$

[1 mark]

$$A_{d1} = g_{m1} (r_{o2} \parallel r_{o4})$$

[1 mark]

$$A_{v2} = g_{m7} (r_{o7} \parallel r_{o8})$$

[1 mark]

$$g_{m1} = 2 \text{ SQRT}[K_{p1} I_{D1}] = 2 \text{ SQRT}[(10\mu) (\text{W/L})_1 (5\text{m})]$$

$$g_{m1} = (0.4472\text{m}) \text{ SQRT}[(\text{W/L})_1]$$

[1 mark]

$$r_{o2} = 1/(\mu I_{D2}) = 1/(0.02 \times 5\text{m}) = 10 \text{ k}\acute{\text{a}}$$

[1 mark]

$$r_{o4} = 1/(n I_{D4}) = 1/(0.01 \times 5\text{m}) = 20 \text{ k}\acute{\text{a}}$$

[1 mark]

$$r_{o2} \parallel r_{o4} = 10\text{k} \parallel 20\text{k} = 6.67 \text{ k}\acute{\text{a}}$$

[1 mark]

$$g_{m7} = 2 \text{ SQRT}[K_{n7} I_{D7}] = 2 \text{ SQRT}[(20\mu) (\text{W/L})_7 (10\text{m})]$$

$$g_{m7} = (0.8944\text{m}) \text{ SQRT}[(\text{W/L})_7]$$

[1 mark]

$$r_{o8} = 1/(\mu I_{D8}) = 1/(0.02 \times 10\text{m}) = 5 \text{ k}\acute{\text{a}}$$

[1 mark]

$$r_{o7} = 1/(n I_{D7}) = 1/(0.01 \times 10\text{m}) = 10 \text{ k}\acute{\text{a}}$$

[1 mark]

$$r_{o7} \parallel r_{o8} = 5\text{k} \parallel 10\text{k} = 3.33 \text{ k}\acute{\text{a}}$$

[1 mark]

So, $A_v = 100,000 = A_{d1} \times A_{v2}$

$$= \{g_{m1} (r_{o2} \parallel r_{o4})\} \cdot \{g_{m7} (r_{o7} \parallel r_{o8})\}$$

$$= \{(0.4472\text{m}) \text{ SQRT}[(\text{W/L})_1] \cdot (6.67\text{k}\acute{\text{a}})\} \cdot \{(0.8944\text{m}) \text{ SQRT}[(\text{W/L})_7] \cdot (3.33 \text{ k}\acute{\text{a}})\}$$

$$= 8.88 \text{ SQRT}[(\text{W/L})_1] \text{ SQRT}[(\text{W/L})_7]$$

Since all transistor sizes are the same, $(\text{W/L})_1 = (\text{W/L})_7$

$$A_v = 100,000 = 8.88 (\text{W/L})_1$$

Thus, $(\text{W/L})_1 = 11,256 = (\text{W/L})_{2,3,4,7}$

[2 marks]

Calculating resistor Rset

$$R_{set} = (V^+ - V_{SG5} \acute{\text{o}} V) / I_{set}$$

[2 marks]

$$V_{SG5} = V_{SD5} + V_{TP} = 1.5 + 2 = 3.5 \text{ V}$$

[1 mark]

So, $R_{set} = (5 \acute{\text{o}} 3.5 \acute{\text{o}} (-5)) / 10\text{m} = 650 \acute{\text{a}}$

[1 mark]

Answer for Q5: [15 marks]

Q5(a) [5 marks]

$$V_{BE10} = V_T \ln\left(\frac{I_{C9}}{I_S}\right) = (0.026) \ln\left(\frac{10 \times 10^{-6}}{5 \times 10^{-16}}\right) = 0.6167V$$

1, 1, 0.5

$$R_4 = \frac{V_{BE11} - V_{BE10}}{I_{C9}} = \frac{0.65 - 0.6167}{10\mu} = 3.33k\Omega$$

1, 1, 0.5

Q5(b) [10 marks]

$$A_{d1} = \frac{v_{o1}}{v_d} = -g_m (r_{o4} \parallel R_{act1} \parallel R_{i2})$$

1

$$\Rightarrow A_{d1} = -\left(\frac{I_{CQ}}{V_T}\right) (r_{o4} \parallel R_{act1} \parallel R_{i2})$$

0.5

$$r_{o4} = \frac{V_{AP}}{I_{C4}} = \frac{50}{5\mu} = 10M\Omega$$

0.5, 0.5

$$R_{act1} = r_{o6} = \frac{V_{AN}}{I_{C6}} = \frac{50}{5\mu} = 10M\Omega$$

0.5, 0.5, 0.5

Where $I_{C6} = I_{C9}/2 = 5\mu A$

0.5

$$R_{i2} = r_{\pi16} + (1 + \beta_n)(r_{\pi17} \parallel R_9)$$

1

Where $r_{\pi16} = \beta_n V_T / I_{C16} = (200)(0.026)/13.2\mu = 394k\Omega$

0.5, 0.5

And $r_{\pi17} = \beta_n V_T / I_{C17} = (200)(0.026)/0.165m = 31.52k\Omega$

0.5, 0.5

$$R_{i2} = 394k + (201)(31.52k \parallel 50k) = 394k + 3886k = 4280k\Omega$$

0.5

$$A_{d1} = -\left(\frac{5\mu}{0.026}\right) (10M \parallel 10M \parallel 4280k) = -(0.1923m)(2306k) = -443.4$$

0.5, 0.5



Overall amplifier gain is $A_{d1} \times A_{v2} \times A_{v3}$ where A_{v3} is unity.

$$A_v = -(-443.4)(100)(1) = 44,340$$

0.5, 0.5

Answer for Q6: [20 marks]

Q6(a) [8 marks]

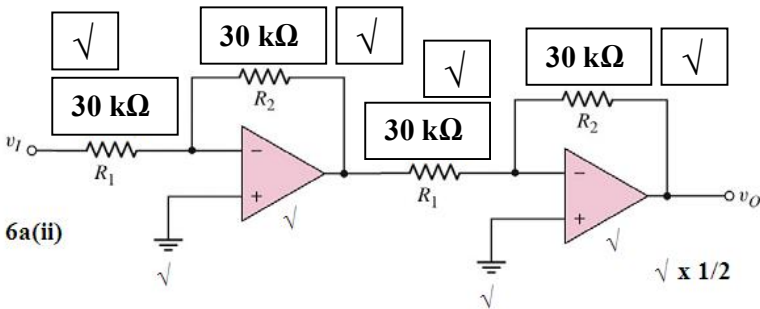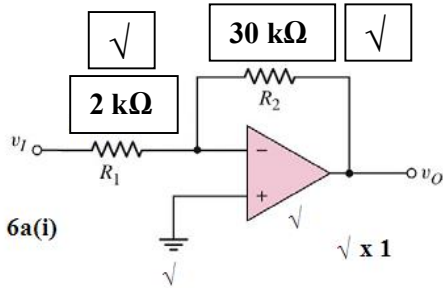

Q6(b) [4 marks]

$$v_O = \left(1 + \frac{R_2}{R_1} \right) v_I \quad \boxed{1}$$

$$A_v = 20 = \frac{v_O}{v_I} = \left(1 + \frac{R_2}{R_1} \right) \quad \boxed{1}$$

$$\frac{R_2}{R_1} = 19 \Rightarrow R_2 = 19R_1 \Rightarrow R_2 > R_1 \quad \boxed{0.5}$$

Select $R_1 = 15 \text{ k}\Omega$, then $R_2 = 285 \text{ k}\Omega$ $\boxed{1, 0.5}$

Q6(c) [8 marks]

$R_1 = 15 \text{ k}\Omega$, $R_2 = 90 \text{ k}\Omega$, $R_3 = 15 \text{ k}\Omega$, and $R_4 = 120 \text{ k}\Omega$

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_{I2} - \left(\frac{R_2}{R_1}\right) v_{I1}$$

$$v_O = \left(1 + \frac{90\text{k}}{15\text{k}}\right) \left(\frac{120\text{k}/15\text{k}}{1 + 120\text{k}/15\text{k}}\right) v_{I2} - \left(\frac{90\text{k}}{15\text{k}}\right) v_{I1}$$

1

$$v_O = (1 + 6) \left(\frac{8}{1 + 8}\right) v_{I2} - 6v_{I1}$$

1

$$v_O = 6.222v_{I2} - 6v_{I1} = 6.222\left(v_{cm} + \frac{v_d}{2}\right) - 6\left(v_{cm} - \frac{v_d}{2}\right)$$

1

$$v_O = 6.111v_d + 0.222v_{cm}$$

1

$$A_d = 6.111, \quad A_{cm} = 0.222$$

1, 1

$$CMRR = 20 \log_{10}[6.111/0.222] = 28.795 \text{ dB}$$

1, 1