



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION
SEMESTER 1 2013 / 2014**

PROGRAMME : **Bachelor of Electrical & Electronics Engineering (Honours)**
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : **EEEB273**

SUBJECT : **ELECTRONIC ANALYSIS AND DESIGN II**

DATE : **September 2013**

TIME : **3 hours**

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **Six (6)** questions in **Ten (10)** pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided.
4. Write answer to different question on a **new page**.
5. For all calculations, assume that $V_T = 26 \text{ mV}$.
6. Use at least **4 significant numbers** in all calculations.

THIS QUESTION PAPER CONSISTS OF TEN (10) PRINTED PAGES INCLUDING THIS COVER PAGE.

Question 1 [20 marks]

You are required **to design** a differential amplifier with passive load using NPN bipolar junction transistors (BJT).

The differential amplifier is biased by a **1.5 mA** constant current from a **2-transistor NPN BJT** current source. Power supplies of **+10 V** and **-10 V** are used to power the overall circuit.

Output of the differential amplifier is taken as **one-sided output** at one of its transistor. The differential-mode voltage gain (A_d) is **150 V/V**.

Available components for the design are:

- Matched NPN BJTs with $\beta = 50$, $V_{BE(on)} = 0.7 \text{ V}$, and $V_A = \infty$.
- Various resistors with precise values.

Design the differential amplifier described above, complete with its biasing circuit, and **draw and label clearly** the circuit diagram of your design. **Show clearly all calculations** related to the design, with the values as accurate as possible.

[20 marks]

Question 2 [15 marks]

As knowledge in electronic design and analysis advances, a differential amplifier circuit can be improved **to increase its gain by using active loads**. The BJT differential amplifier shown in **Figure 2** is biased by a **0.18 mA** constant current source (i.e. $I_Q = 0.18 \text{ mA}$). The differential amplifier uses a **BJT Cascode current source** made up of **PNP transistors** as the **active load**. The output voltage (v_O) of the differential amplifier is taken at v_{C2} . Information related to the transistor parameters are: $\beta = 150$, $V_{BE(\text{on})} = V_{EB(\text{on})} = 0.7 \text{ V}$, $V_{AN} = 120 \text{ V}$, and $V_{AP} = 100 \text{ V}$.

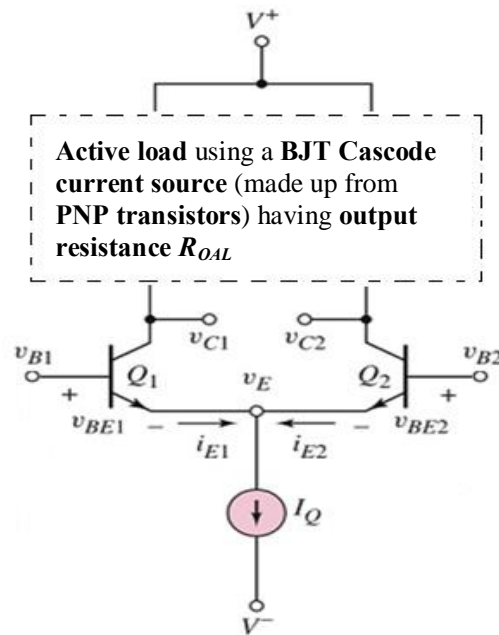


Figure 2

- (a) **Calculate** the output resistance of the **BJT Cascode current source (R_{OAL})** and then **sketch** the differential amplifier circuit incorporating the Cascode current source as the active load. [5 marks]
- (b) **Determine** the differential-mode voltage gain of the circuit, $A_d = v_O/v_d$. [6 marks]
- (c) **Determine** the output voltage of the circuit if a differential input $v_d = 5 \sin(\omega t) \text{ mV}$ is applied. **How** will this output different if we use a **two-transistor current source** (made up of **PNP transistors**) as the active load? [4 marks]

Question 3 [10 marks]

- (a) **Briefly describe** the advantage of **Class-AB** output stage as compared to the **Class-A** and **Class-B** output stages. [3 marks]
- (b) A **Class-A emitter follower** biased with a constant-current source is shown in **Figure 3**. The transistor parameters are: $\beta = 180$, $V_{BE} = 0.7 \text{ V}$, and $V_{CE(\text{sat})} = 0.2 \text{ V}$. Neglect base currents.
- (i) **Find** the value of I_Q . [3 marks]
- (ii) **Determine** the value of R that will produce the maximum possible output signal swing. [2 marks]
- (iii) **Calculate** the conversion efficiency, η . [2 marks]

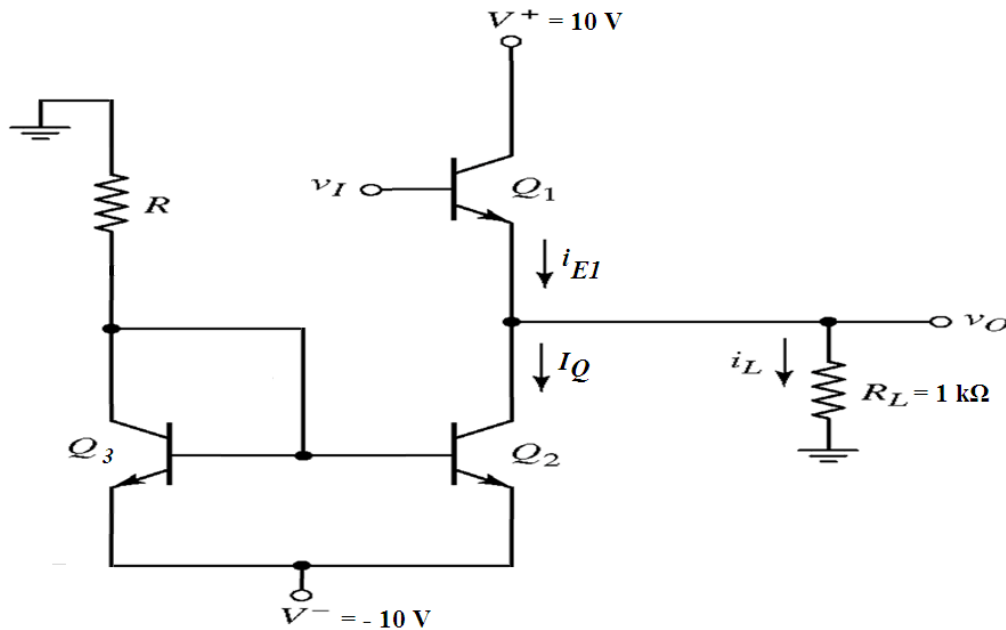


Figure 3

Question 4 [20 marks]

The **MC14573 CMOS op amp**, as shown in **Figure 4**, is used in a sensor circuit requiring a very high-degree of accuracy. The **open-loop gain** of this op amp is required to be **100 dB**. **Design** the circuit to achieve this.

Given: $V^+ = +5\text{ V}$, $V^- = -5\text{ V}$, and $I_{set} = 10\text{ mA}$ with $V_{SD5(sat)} = 1.5\text{ V}$.

The transistor parameters are: $|V_T| = 2\text{ V}$, $(1/2)\mu_n C_{ox} = 20\text{ }\mu\text{A/V}^2$, $(1/2)\mu_p C_{ox} = 10\text{ }\mu\text{A/V}^2$, $\lambda_n = 0.01\text{ V}^{-1}$, and $\lambda_p = 0.02\text{ V}^{-1}$.

The transistor **aspect ratios** are $(W/L)_{5,6,8} = 10$. Let the aspect ratios of **all other transistors** be the same.

[20 marks]

 


Figure 4

Question 5 [15 marks]

Consider the **standard 741 operational amplifier** circuit as in **Figure 5a**. The operational amplifier is supplied by $\pm 5\text{ V DC}$ voltage. The transistors have $\beta_n = 200$, $\beta_p = 50$, $V_{AN} = V_{AP} = 50\text{ V}$, $V_{BE(\text{on})} = V_{EB(\text{on})} = 0.65\text{ V}$ (**EXCEPT for V_{BE10}**), and the reverse saturation current $I_S = 5 \times 10^{-16}\text{ A}$. Neglect base current in your calculations. Let $I_{C16} = 13.2\ \mu\text{A}$ and $I_{C17} = 0.165\text{ mA}$.

- (a) Study the bias circuit **very carefully**. If the current $I_{C9} = 10\ \mu\text{A}$ and $I_{REF} = 0.22\text{ mA}$, **determine R_4** . [5 marks]

- (b) **Determine** the operational amplifier **overall differential mode voltage gain** if the resistor values for R_1 , R_2 and R_8 are changed to **0 (zero)**, and the small signal voltage gain of the gain stage $A_{v2} = -100$. You may use the ac equivalent circuits as in **Figure 5b** and **Figure 5c** to assist your calculations. [10 marks]

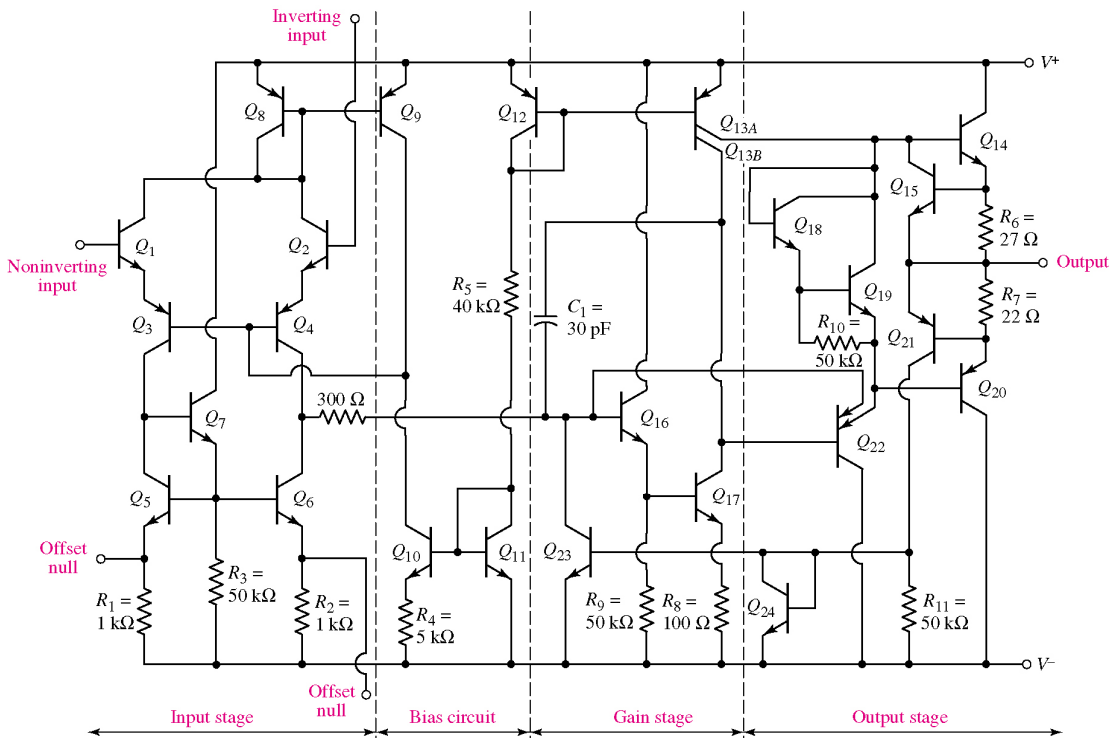


Figure 5a

 


Figure 5b

 


Figure 5c

Question 6 [20 marks]

(a) Using **feedback resistor** of **30 kΩ**, draw the following circuits using **inverting op-amp configuration**:

(i) An **inverting amplifier** with a closed-loop gain of **-15**. [4 marks]

(ii) A **voltage follower**. [4 marks]

(b) Consider the **non-inverting op-amp** shown in **Figure 6a**. Assume the op-amp is ideal. **Design** the circuit to produce a closed-loop gain of **20**, with the **minimum resistor value** in the circuit is to be **15 kΩ**. [4 marks]

 


Figure 6a

 


Figure 6b

(c) A general output equation for a difference amplifier shown in Figure 6b is

$$v_O = A_d v_d + A_{cm} v_{cm}$$

For the difference amplifier in Figure 6b, the circuit parameters are $R_1 = 15 \text{ k}\Omega$, $R_2 = 90 \text{ k}\Omega$, $R_3 = 15 \text{ k}\Omega$, and $R_4 = 120 \text{ k}\Omega$ and the output voltage (v_O) equation is as follows:

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_{I2} - \left(\frac{R_2}{R_1}\right) v_{I1}$$

where

$$v_{I1} = v_{cm} - \frac{v_d}{2}$$

and

$$v_{I2} = v_{cm} + \frac{v_d}{2}$$

Calculate A_d , A_{cm} , and the $CMRR$ in dB for the circuit.

[8 marks]

-END OF QUESTION PAPER-

APPENDIX

BASIC FORMULABJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{PNP}$$

$$i_C = \beta i_B = \alpha i_E$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$