

**Question:**

Study **Figure 1** carefully. Assume  $\beta = 30$ ,  $V_{BE(\text{on})} = 0.7 \text{ V}$ , and  $V_A = \infty$  for all BJTs in the circuit. For  $R_C = 2 \text{ k}\Omega$  and  $v_{B1} = v_{B2} = 0 \text{ V}$ , **determine** the value of  $R_1$  such that  $V_{CE1} = 2.5 \text{ V}$ . Write your answers as precise as possible, in 4 decimal points, with proper Units for the parameters.

[10 marks]

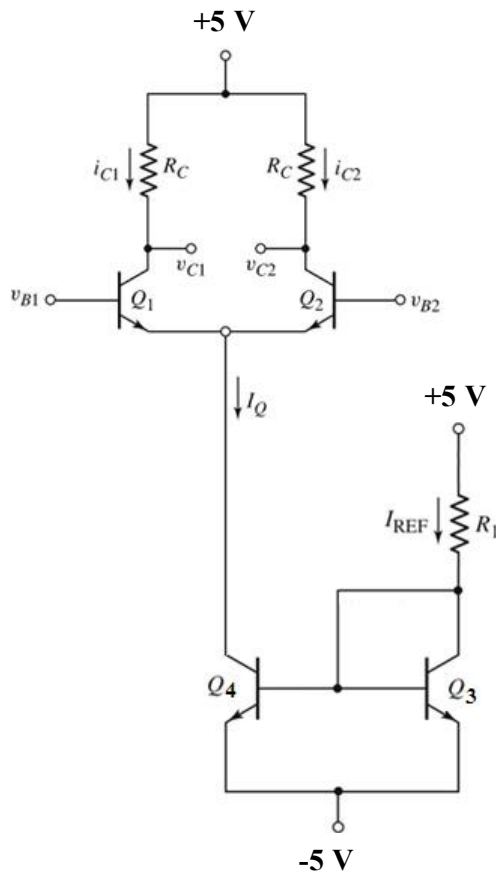


Figure 1

$$v_{C1} = v_{B1} - V_{BE1(\text{on})} + V_{CE1} \quad [1]$$

$$= 0 - 0.7 + 2.5 = 1.8 \text{ V} \quad [1]$$

$$v_{C1} = 5 - i_{C1} R_C \quad [1]$$

$$i_{C1} = (5 - v_{C1}) / R_C \quad [1]$$

$$= (5 - 1.8) / 2\text{k} = 1.6 \text{ mA} \quad [1]$$

When  $v_{B1} = v_{B2} = 0 \text{ V}$ :

$$i_{C2} = i_{C1} \quad [1]$$

$$I_Q = i_{C1} + i_{C2} = 3.2 \text{ mA} \quad [1]$$

$$I_{REF} = I_Q (1 + 2/\beta) \quad [1]$$

$$= (3.2\text{m})(1 + 2/30) = 3.4133 \text{ mA} \quad [1]$$

$$R_1 = (V^+ - V_{BE3(\text{on})} - V^-) / (I_{REF}) \quad [1]$$

$$= (5 - 0.7 - (-5)) / (3.4133 \text{ m}) = 2.7246 \text{ k}\Omega \quad [1]$$

$$g_m = \frac{I_{CQ}}{V_T}$$


$$r_o = \frac{V_A}{I_{CQ}}$$

**Answer:**

**Question:**

Study **Figure 1** carefully. Assume  $\beta = 40$ ,  $V_{BE(on)} = 0.7 \text{ V}$ , and  $V_A = \infty$  for all BJTs in the circuit. For  $R_C = 2 \text{ k}\Omega$  and  $v_{B1} = v_{B2} = 0 \text{ V}$ , **determine** the value of  $R_1$  such that  $V_{CE1} = 2.5 \text{ V}$ . Write your answers as precise as possible, in 4 decimal points, with proper Units for the parameters.

[10 marks]

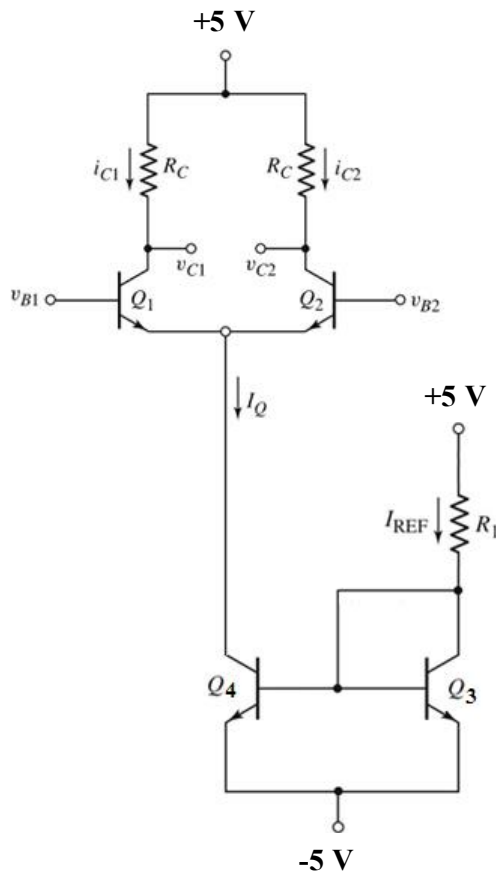

**Figure 1**

$$v_{C1} = v_{B1} - V_{BE1(on)} + V_{CE1} \quad [1]$$

$$= 0 - 0.7 + 2.5 = 1.8 \text{ V} \quad [1]$$

$$v_{C1} = 5 - i_{C1} R_C$$

$$i_{C1} = (5 - v_{C1}) / R_C \quad [1]$$

$$= (5 - 1.8) / 2\text{k} = 1.6 \text{ mA} \quad [1]$$

When  $v_{B1} = v_{B2} = 0 \text{ V}$ :

$$i_{C2} = i_{C1} \quad [1]$$

$$I_Q = i_{C1} + i_{C2} = 3.2 \text{ mA} \quad [1]$$

$$I_{REF} = I_Q (1 + 2/\beta) \quad [1]$$

$$= (3.2\text{m})(1 + 2/40) = 3.36 \text{ mA} \quad [1]$$

$$R_1 = (V^+ - V_{BE3(on)} - V^-) / (I_{REF}) \quad [1]$$

$$= (5 - 0.7 - (-5)) / (3.36 \text{ m}) = 2.7678 \text{ k}\Omega \quad [1]$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

**Answer:**

**Question:**

Study **Figure 1** carefully. Assume  $\beta = 40$ ,  $V_{BE(on)} = 0.7$  V, and  $V_A = \infty$  for all BJTs in the circuit. For  $R_C = 2.5$  k $\Omega$  and  $v_{B1} = v_{B2} = 0$  V, **determine** the value of  $R_1$  such that  $V_{CE1} = 2$  V. Write your answers as precise as possible, in 4 decimal points, with proper Units for the parameters.

[10 marks]

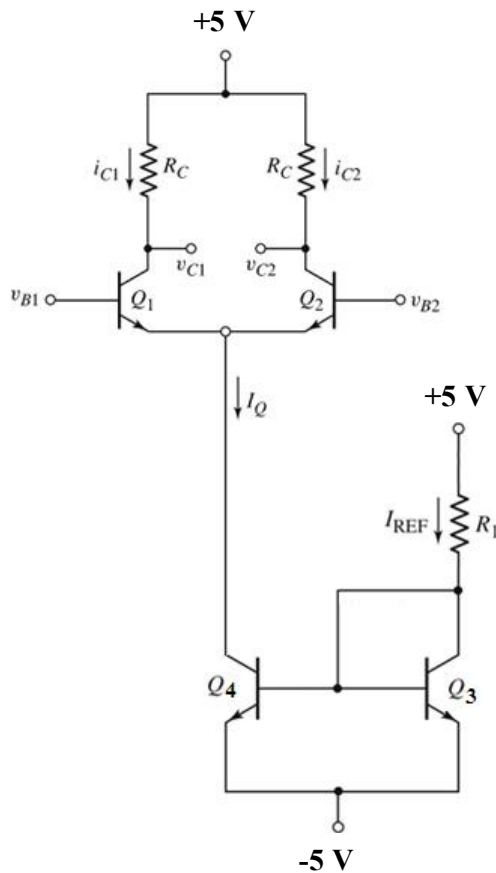


Figure 1

$$v_{C1} = v_{B1} - V_{BE1(on)} + V_{CE1} \quad [1]$$

$$= 0 - 0.7 + 2 = 1.3 \text{ V} \quad [1]$$

$$v_{C1} = 5 - i_{C1} R_C$$

$$i_{C1} = (5 - v_{C1}) / R_C \quad [1]$$

$$= (5 - 1.3) / 2.5k = 1.48 \text{ mA} \quad [1]$$

When  $v_{B1} = v_{B2} = 0$  V:

$$i_{C2} = i_{C1} \quad [1]$$

$$I_Q = i_{C1} + i_{C2} = 2.96 \text{ mA} \quad [1]$$

$$I_{REF} = I_Q (1 + 2/\beta) \quad [1]$$

$$= (2.96m)(1 + 2/40) = 3.108 \text{ mA} \quad [1]$$

$$R_1 = (V^+ - V_{BE3(on)} - V^-) / (I_{REF}) \quad [1]$$

$$= (5 - 0.7 - (-5)) / (3.108 \text{ m}) = 2.9922 \text{ k}\Omega \quad [1]$$

$$g_m = \frac{I_{CQ}}{V_T}$$


$$r_o = \frac{V_A}{I_{CQ}}$$

**Answer:**

**Question:**

Study **Figure 1** carefully. Assume  $\beta = 30$ ,  $V_{BE(on)} = 0.7$  V, and  $V_A = \infty$  for all BJTs in the circuit. For  $R_C = 2.5$  k $\Omega$  and  $v_{B1} = v_{B2} = 0$  V, **determine** the value of  $R_1$  such that  $V_{CE1} = 2$  V. Write your answers as precise as possible, in 4 decimal points, with proper Units for the parameters.

[10 marks]

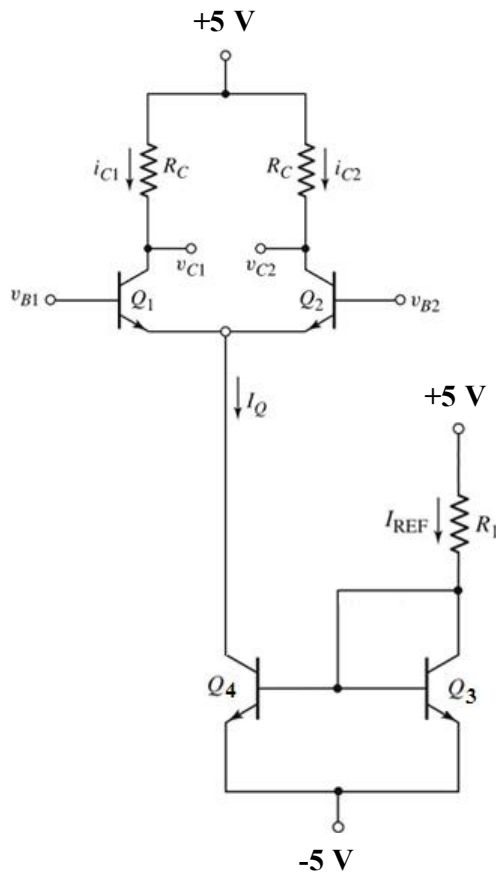

**Figure 1**

$$v_{C1} = v_{B1} - V_{BE1(on)} + V_{CE1} \quad [1]$$

$$= 0 - 0.7 + 2 = 1.3 \text{ V} \quad [1]$$

$$v_{C1} = 5 - i_{C1} R_C$$

$$i_{C1} = (5 - v_{C1}) / R_C \quad [1]$$

$$= (5 - 1.3) / 2.5k = 1.48 \text{ mA} \quad [1]$$

When  $v_{B1} = v_{B2} = 0$  V:

$$i_{C2} = i_{C1} \quad [1]$$

$$I_Q = i_{C1} + i_{C2} = 2.96 \text{ mA} \quad [1]$$

$$I_{REF} = I_Q (1 + 2/\beta) \quad [1]$$

$$= (2.96m)(1 + 2/30) = 3.1573 \text{ mA} \quad [1]$$

$$R_1 = (V^+ - V_{BE3(on)} - V^-) / (I_{REF}) \quad [1]$$

$$= (5 - 0.7 - (-5)) / (3.1573 \text{ m}) = 2.9455 \text{ k}\Omega \quad [1]$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

**Answer:**