

EEEE273 - Quiz 4
 SEMESTER 1, ACADEMIC YEAR 2013/2014
 Date: 2 September 2013 Time: 15 minutes

Question:

Refer to Figure 1.

- (a) Derive the relationship (formula) between v_I and v_O in terms of R_1 and R_2 . [6 marks]
 (b) Calculate v_O when $R_1 = 50 \text{ k}\Omega$, $R_2 = 200 \text{ k}\Omega$ and $v_I = 0.5 \text{ V}$. [4 marks]

Show clearly all calculations in order to get full marks.

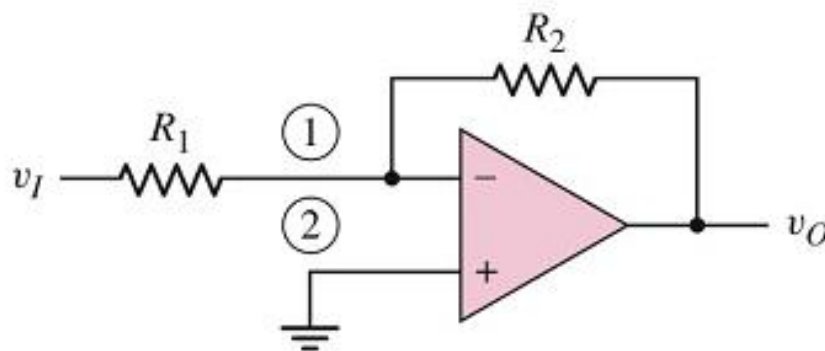


Figure 1

Answer:

- (a)
 $v_1 \cong v_2 = 0$ [1]
 $i_1 = (v_I - v_1) / R_1 = v_I / R_1$ [2]
 $i_1 = i_2$ [0.5]
 $v_O = v_1 - i_2 R_2 = 0 - (v_I / R_1) R_2$ [2]
 $v_O = - (R_2 / R_1) v_I$ [0.5]
- (b)
 $v_O = - (R_2 / R_1) v_I$ [2]
 $= - (200\text{k} / 50\text{k})(0.5\text{V}) = -2 \text{ V}$ [2]

EEEE273 - Quiz 4
 SEMESTER 1, ACADEMIC YEAR 2013/2014
 Date: 2 September 2013 Time: 15 minutes

Question:

Refer to Figure 1.

(c) **Derive** the relationship (formula) between v_I and v_O in terms of R_1 and R_2 . [6 marks]

(d) **Calculate** v_I when $R_1 = 50 \text{ k}\Omega$, $R_2 = 180 \text{ k}\Omega$ and $v_O = 2.5 \text{ V}$. [4 marks]

Show clearly all calculations in order to get full marks.

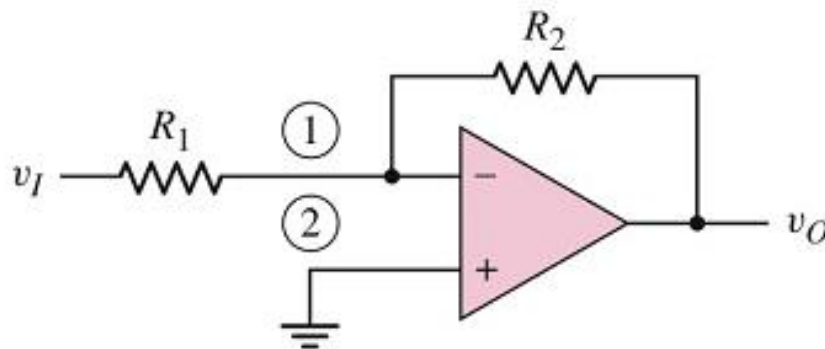


Figure 1

Answer:

(a)

$$v_1 \cong v_2 = 0 \quad [1]$$

$$i_1 = (v_I - v_1) / R_1 = v_I / R_1 \quad [2]$$

$$i_1 = i_2 \quad [0.5]$$

$$v_O = v_1 - i_2 R_2 = 0 - (v_I / R_1) R_2 \quad [2]$$

$$v_O = - (R_2 / R_1) v_I \quad [0.5]$$

(b)

$$v_I = - (R_1 / R_2) v_O \quad [2]$$

$$= - (50\text{k} / 180\text{k})(2.5\text{V}) = -0.6944 \text{ V} \quad [2]$$

Name: **Dr JBO**

Student ID Number: **Model Answer**

Section:

Lecturer: **Dr. Jamaludin Bin Omar**

EEEE273 - Quiz 4
SEMESTER 1, ACADEMIC YEAR 2013/2014
Date: 2 September 2013 Time: 15 minutes

Question:

Refer to Figure 1.

(e) **Derive** the relationship (formula) between v_I and v_O in terms of R_1 and R_2 . **[6 marks]**

(f) **Calculate** R_1 when $R_2 = 150 \text{ k}\Omega$, $v_I = -0.5 \text{ V}$ and $v_O = 2.5 \text{ V}$. **[4 marks]**

Show clearly all calculations in order to get full marks.

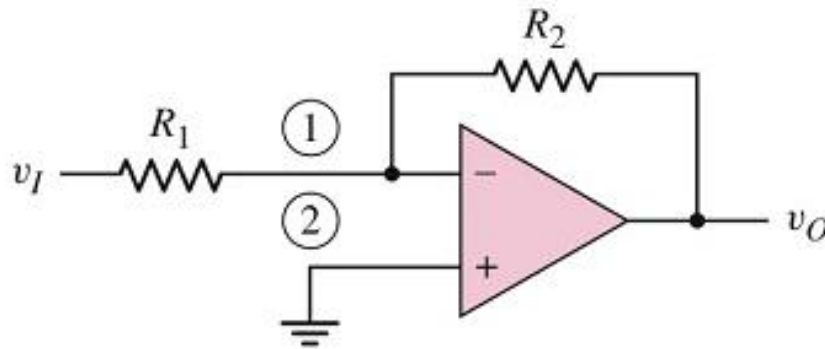


Figure 1

Answer:

(a)

$$v_1 \cong v_2 = 0 \quad [1]$$

$$i_1 = (v_I - v_1) / R_1 = v_I / R_1 \quad [2]$$

$$i_1 = i_2 \quad [0.5]$$

$$v_O = v_1 - i_2 R_2 = 0 - (v_I / R_1) R_2 \quad [2]$$

$$v_O = - (R_2 / R_1) v_I \quad [0.5]$$

(b)

$$R_1 = - (R_2 v_I) / v_O \quad [2]$$

$$= - (150\text{k} \times (-0.5)) / (2.5\text{V}) = 30 \text{ k}\Omega \quad [2]$$

EEEE273 - Quiz 4
 SEMESTER 1, ACADEMIC YEAR 2013/2014
 Date: 2 September 2013 Time: 15 minutes

Question:

Refer to Figure 1.

(g) **Derive** the relationship (formula) between v_I and v_O in terms of R_1 and R_2 . [6 marks]

(h) **Calculate** R_2 when $R_1 = 50 \text{ k}\Omega$, $v_I = -0.6 \text{ V}$ and $v_O = 3.8 \text{ V}$. [4 marks]

Show clearly all calculations in order to get full marks.

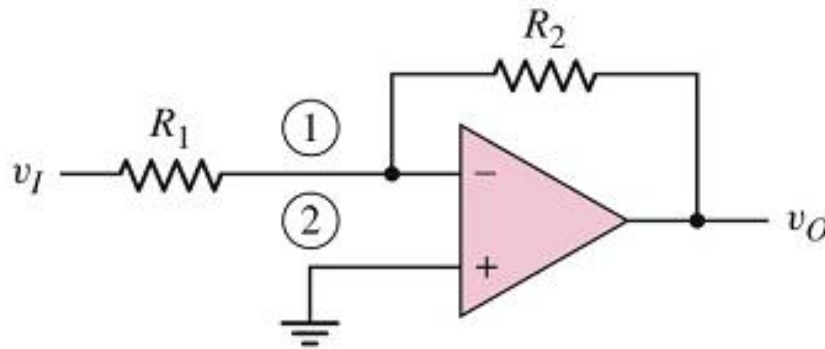


Figure 1

Answer:

(a)

$v_1 \cong v_2 = 0$	[1]
$i_1 = (v_I - v_1) / R_1 = v_I / R_1$	[2]
$i_1 = i_2$	[0.5]
$v_O = v_1 - i_2 R_2 = 0 - (v_I / R_1) R_2$	[2]
$v_O = - (R_2 / R_1) v_I$	[0.5]

(b)

$R_2 = - (R_1 v_O) / v_I$	[2]
$= - (50\text{k} \times 3.8\text{V}) / (-0.6\text{V}) = 316.67 \text{ k}\Omega$	[2]