

EEEE273 - Quiz 4
SEMESTER 1, ACADEMIC YEAR 2013/2014
Date: 2 September 2013 Time: 15 minutes

Question:

Refer to Figure 1.

(a) **Derive** the relationship (formula) between v_I and v_O in terms of R_1 and R_2 . **[6 marks]**

(b) **Calculate** v_O when $R_1 = 50 \text{ k}\Omega$, $R_2 = 200 \text{ k}\Omega$ and $v_I = 0.5 \text{ V}$. **[4 marks]**

Show clearly all calculations in order to get full marks.

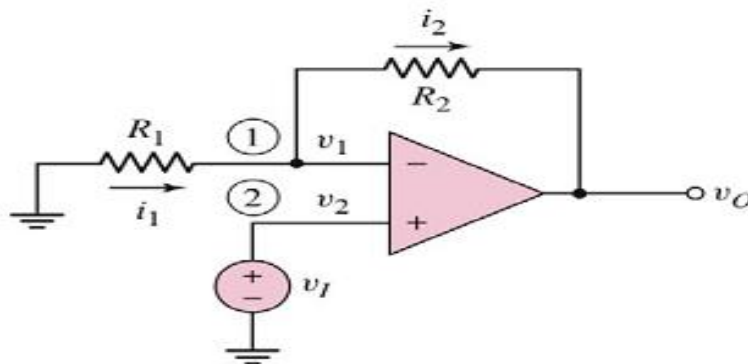


Figure 1

Answer:

(a)

$$v_1 \cong v_2 = v_I \quad [1]$$

$$i_1 = (0 - v_1) / R_1 = -v_I / R_1 \quad [2]$$

$$i_1 = i_2 \quad [0.5]$$

$$v_O = v_1 - i_2 R_2 = v_I - (-v_I / R_1) R_2 \quad [2]$$

$$v_O = (1 + R_2 / R_1) v_I \quad [0.5]$$

(b)

$$v_O = (1 + R_2 / R_1) v_I \quad [2]$$

$$= (1 + 200\text{k} / 50\text{k})(0.5\text{V}) = 2.5 \text{ V} \quad [2]$$

EEEE273 - Quiz 4
SEMESTER 1, ACADEMIC YEAR 2013/2014
Date: 2 September 2013 Time: 15 minutes

Question:

Refer to Figure 1.

(c) **Derive** the relationship (formula) between v_I and v_O in terms of R_1 and R_2 . [6 marks]

(d) **Calculate** v_I when $R_1 = 50 \text{ k}\Omega$, $R_2 = 180 \text{ k}\Omega$ and $v_O = 2.5 \text{ V}$. [4 marks]

Show clearly all calculations in order to get full marks.

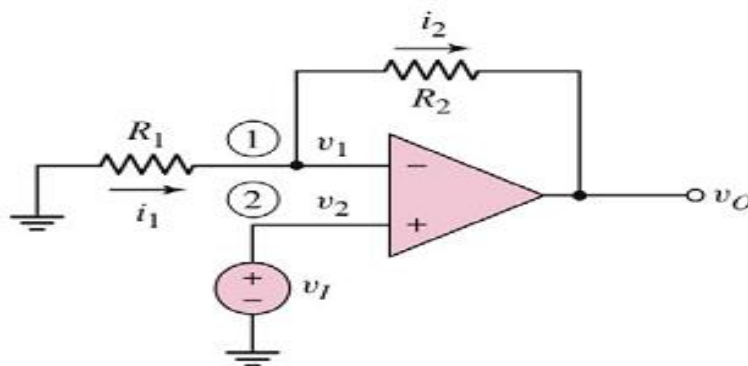


Figure 1

Answer:

(a)

$$v_1 \cong v_2 = v_I \quad [1]$$

$$i_1 = (0 - v_1) / R_1 = -v_I / R_1 \quad [2]$$

$$i_1 = i_2 \quad [0.5]$$

$$v_O = v_1 - i_2 R_2 = v_I - (-v_I / R_1) R_2 \quad [2]$$

$$v_O = (1 + R_2 / R_1) v_I \quad [0.5]$$

(b)

$$v_I = v_O / (1 + R_2 / R_1) \quad [2]$$

$$= 2.5\text{V} / (1 + 180\text{k} / 50\text{k}) = 0.54347 \text{ V} \quad [2]$$

EEEE273 - Quiz 4
 SEMESTER 1, ACADEMIC YEAR 2013/2014
 Date: 2 September 2013 Time: 15 minutes

Question:

Refer to Figure 1.

(e) **Derive** the relationship (formula) between v_I and v_O in terms of R_1 and R_2 . **[6 marks]**

(f) **Calculate** R_1 when $R_2 = 150 \text{ k}\Omega$, $v_I = +0.5 \text{ V}$ and $v_O = 2.5 \text{ V}$. **[4 marks]**

Show clearly all calculations in order to get full marks.

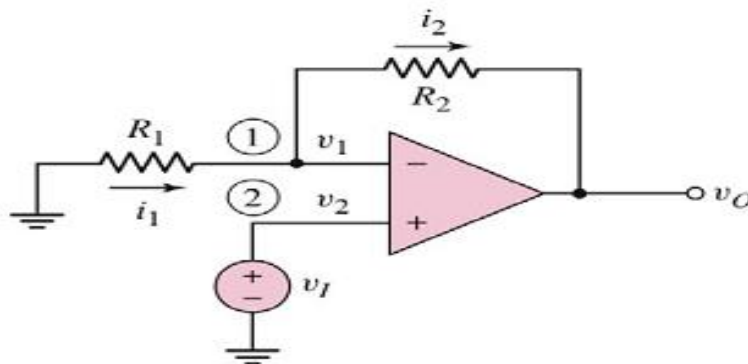


Figure 1

Answer:

(a)

$$v_1 \cong v_2 = v_I \quad [1]$$

$$i_1 = (0 - v_1) / R_1 = -v_I / R_1 \quad [2]$$

$$i_1 = i_2 \quad [0.5]$$

$$v_O = v_1 - i_2 R_2 = v_I - (-v_I / R_1) R_2 \quad [2]$$

$$v_O = (1 + R_2 / R_1) v_I \quad [0.5]$$

(b)

$$R_1 = R_2 / (v_O / v_I - 1) \quad [2]$$

$$= 150\text{k} / (2.5/0.5 - 1) = 37.5 \text{ k}\Omega \quad [2]$$

EEEE273 - Quiz 4
 SEMESTER 1, ACADEMIC YEAR 2013/2014
 Date: 2 September 2013 Time: 15 minutes

Question:

Refer to Figure 1.

(g) **Derive** the relationship (formula) between v_I and v_O in terms of R_1 and R_2 . [6 marks]

(h) **Calculate** R_2 when $R_1 = 50 \text{ k}\Omega$, $v_I = +0.6 \text{ V}$ and $v_O = 3.8 \text{ V}$. [4 marks]

Show clearly all calculations in order to get full marks.

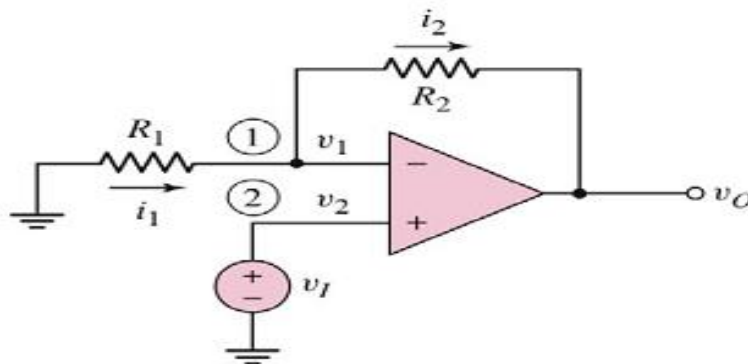


Figure 1

Answer:

(a)

$$v_1 \cong v_2 = v_I \quad [1]$$

$$i_1 = (0 - v_1) / R_1 = -v_I / R_1 \quad [2]$$

$$i_1 = i_2 \quad [0.5]$$

$$v_O = v_1 - i_2 R_2 = v_I - (-v_I / R_1) R_2 \quad [2]$$

$$v_O = (1 + R_2 / R_1) v_I \quad [0.5]$$

(b)

$$R_2 = R_1 (v_O / v_I - 1) \quad [2]$$

$$= 50 \text{ k} (3.8 / 0.6 - 1) = 266.667 \text{ k}\Omega \quad [2]$$