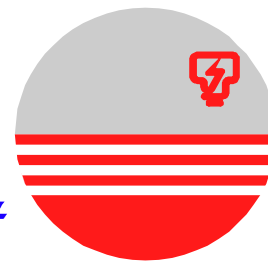


Name:
Student ID Number:
Section: 01/02/03/04 A/B
Lecturer: Dr Jamaludin /Dr Azni Wati
/Dr Fazrena Azlee

**UNIVERSITI
TENAGA
NASIONAL**



College of Engineering
Department of Electronics and Communication Engineering

Test 2 – **MODEL ANSWER**

SEMESTER 1, ACADEMIC YEAR 2013/2014

Subject Code : **EEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **22 August 2013**
Time Allowed : **1½ hours**

Instructions to the candidates:

1. Write your Name and Student ID number. Circle your section number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**
5. For BJT, use $V_T = 26 \text{ mV}$ where appropriate.
6. Use at least **4 significant numbers** in all calculations.

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!



Question No.	1	2	3	Total
Marks				

FORMULA FOR TRANSISTORS

BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n \cdot W}{2 \cdot L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p \cdot W}{2 \cdot L}$$

; Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$


$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

Question 1 [40 marks]

Figure 1 shows a MOSFET differential amplifier circuit biased with constant current source I_Q . It is given that $V^+ = 10\text{ V}$, $V^- = -10\text{ V}$, and $I_Q = 0.2\text{ mA}$.

Also, the NMOS transistor parameters are: $V_{TN} = 1\text{ V}$, $k'_n = 100\text{ }\mu\text{A/V}^2$ and $\lambda_n = 0.01\text{ V}^{-1}$, and the PMOS transistor parameters are: $V_{TP} = -1\text{ V}$, $k'_p = 80\text{ }\mu\text{A/V}^2$ and $\lambda_p = 0.015\text{ V}^{-1}$.

- State the function of each transistor M_1 to M_6 in the **Figure 1**. [10 marks]
- Calculate the differential gain of the circuit if given: $(W/L)_{1-2} = 5$, $(W/L)_{3-6} = 10$. [20 marks]
- Calculate the *CMRR* (dB) if $A_{cm} = -0.003$. [10 marks]

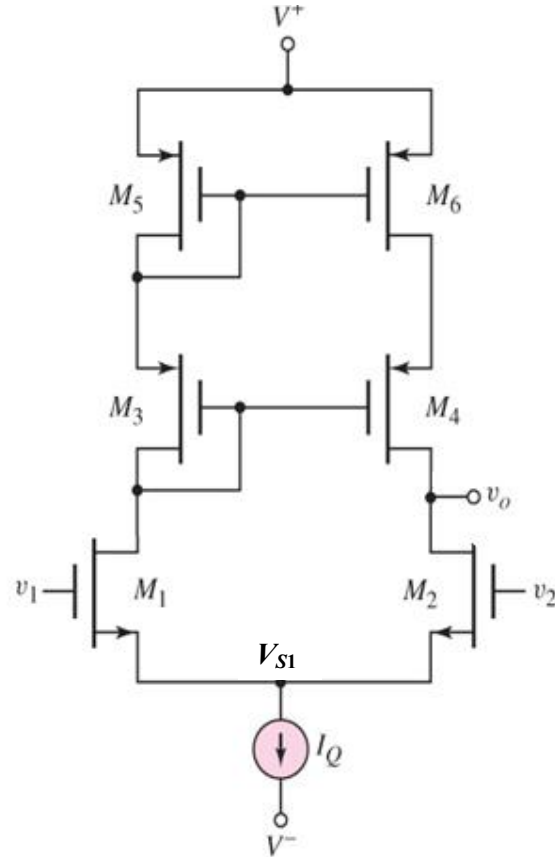Answers for Question 1**Figure 1**

Answers for Question 1 (Cont.)**Question 1: Solution**

- a) State the function of each transistor M1 to M6 in Figure 1. [10 marks]
- M_1 & M_2 : differential-pair, common-emitter amplifier [4 marks]
 - M_3 to M_6 : cascode current mirror [2 marks], active load [4 marks]
- b) Calculate the differential gain of the circuit if given: $(W/L)_{1-2}=5$, $(W/L)_{3-6}=10$ [20 marks]

$$A_d = g_{m1}(r_{O2} \parallel R_{O4}) [4marks]$$

$$g_{m1} = 2\sqrt{K_{n1}I_{D1}} = 2\sqrt{0.5(100\mu)(5)(0.1m)} = 0.316 \text{ mA/V} [2marks]$$

$$r_{O2} = 1/(\lambda_n I_{D2}) = 1/(0.01 \times 0.1m) = 1M\Omega [2marks]$$

$$R_{O4Cascode} = g_{m4}r_{O4}r_{O6} [4marks]$$

$$g_{m4} = 2\sqrt{K_{p4}I_{D4}} = 2\sqrt{0.5(80\mu)(10)(0.1m)} = 0.4 \text{ mA/V} [2marks]$$

$$r_{O4} = 1/(\lambda_p I_{D4}) = 1/(0.015 \times 0.1m) = 667k\Omega [2marks]$$

$$r_{O6} = r_{O4} = 667k\Omega [1mark]$$

$$R_{O4Cascode} = (0.4m)(667k)(667k) = 178M\Omega [1mark]$$

$$A_d = (0.316m)(1M \parallel 178M) = 312.8V/V [2marks]$$

- c) Calculate the CMRR (dB) if $A_{cm} = -0.003$. [10 marks]

$$CMRR = |A_d/A_{cm}| = |312.8/-0.003| = 104.27k \quad [4 \text{ marks}]$$


$$CMRR(\text{dB}) = 20 \log(|A_d/A_{cm}|) = 20 \log(104.27k) \quad [4 \text{ marks}]$$

$$= 100.3 \text{ dB} \quad [2 \text{ marks}]$$

Question 2 [20 marks]

The Class AB output stage is shown in **Figure 2**, with $V_{CC} = 10\text{ V}$, $I_{CQ} = 2\text{ mA}$, and $R_L = 100\ \Omega$. Assume Q_n and Q_p to be matched, with $I_S = 3 \times 10^{-13}\text{ A}$.

- a) Determine V_{BB} . [4 marks]
- b) For $v_O = 6\text{ V}$,
- Find the values of i_L , i_{Cn} , i_{Cp} , v_{BE_n} , and v_{BE_p} . [10 marks]
 - Calculate the power dissipated in Q_n and Q_p . [6 marks]

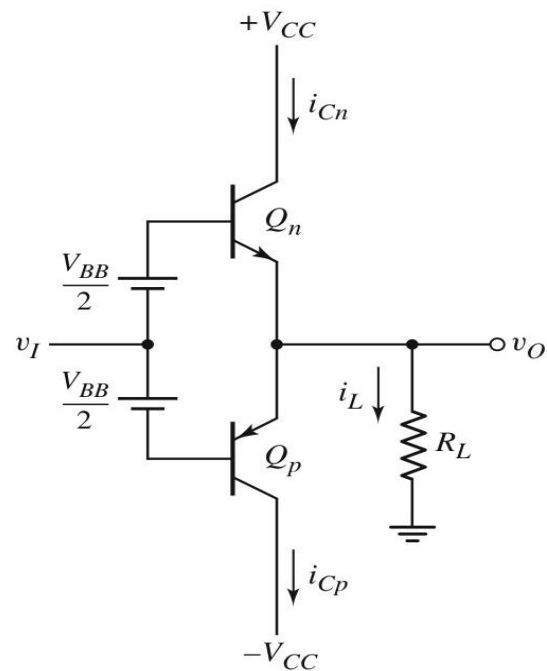Answers for Question 2**Figure 2**

Answers for Question 2 (Cont.)**Question 2: Solution**

a) Determine V_{BB} [4marks]

$$I_{CQ} = i_{Cn} = i_{Cp} \text{ when } v_{BE n} = v_{BE p} = V_{BB}/2 \quad [2 \text{ marks}]$$

$$V_{BB}/2 = V_T \ln(I_{CQ} / I_S) = (26\text{m}) \ln(2\text{m} / 3 \times 10^{-13}) = 0.588 \text{ V}$$

$$V_{BB} = 2 \times 0.588 = 1.176 \text{ V} \quad [2 \text{ marks}]$$

b) For $v_o = 6 \text{ V}$,

i. Find the values of i_L , i_{Cn} , i_{Cp} , $v_{BE n}$, and $v_{BE p}$. [10 marks]

$$i_L = v_o / R_L = 6 / 100 = 60 \text{ mA} \quad [2 \text{ marks}]$$

1st iteration:

$$i_{Cn} \approx i_L = 60 \text{ mA} \quad [1 \text{ mark}]$$

$$v_{BE n} = V_T \ln(i_{Cn} / I_S) = (26\text{m}) \ln(60\text{m} / 3 \times 10^{-13}) = 0.677 \text{ V} \quad [2 \text{ marks}]$$

$$v_{EB p} = V_{BB} - v_{BE n} = 1.176 - 0.677 = 0.499 \text{ V} \quad [2 \text{ marks}]$$

$$i_{Cp} = I_S \exp(v_{EB p} / V_T) = (3 \times 10^{-13}) \exp(0.499/26\text{m}) = 0.0649 \text{ mA} \quad [2 \text{ marks}]$$

Recalculate i_{Cn} :

$$i_{Cn} = i_L + i_{Cp} = 60\text{m} + 0.0649\text{m} = 60.065 \text{ mA} \quad [1 \text{ mark}]$$

ii. Calculate the power dissipated in Q_n and Q_p . [6 marks]

$$P_{Qn} = V_{CE n} \times i_{Cn} \quad [1 \text{ mark}]$$

$$V_{CE n} = V_{CC} - v_o = 10 - 6 = 4 \text{ V} \quad [1 \text{ mark}]$$

$$P_{Qn} = 4 \times 60.065\text{m} = 240.26 \text{ mW} \quad [1 \text{ mark}]$$

$$P_{Qp} = V_{EC p} \times i_{Cp} \quad [1 \text{ mark}]$$

$$V_{EC p} = v_o - (-V_{CC}) = 6 - (-10) = 16 \text{ V} \quad [1 \text{ mark}]$$

$$P_{Qp} = 16 \times 0.0649\text{m} = 1.038 \text{ mW} \quad [1 \text{ mark}]$$

Question 3 [40 marks]

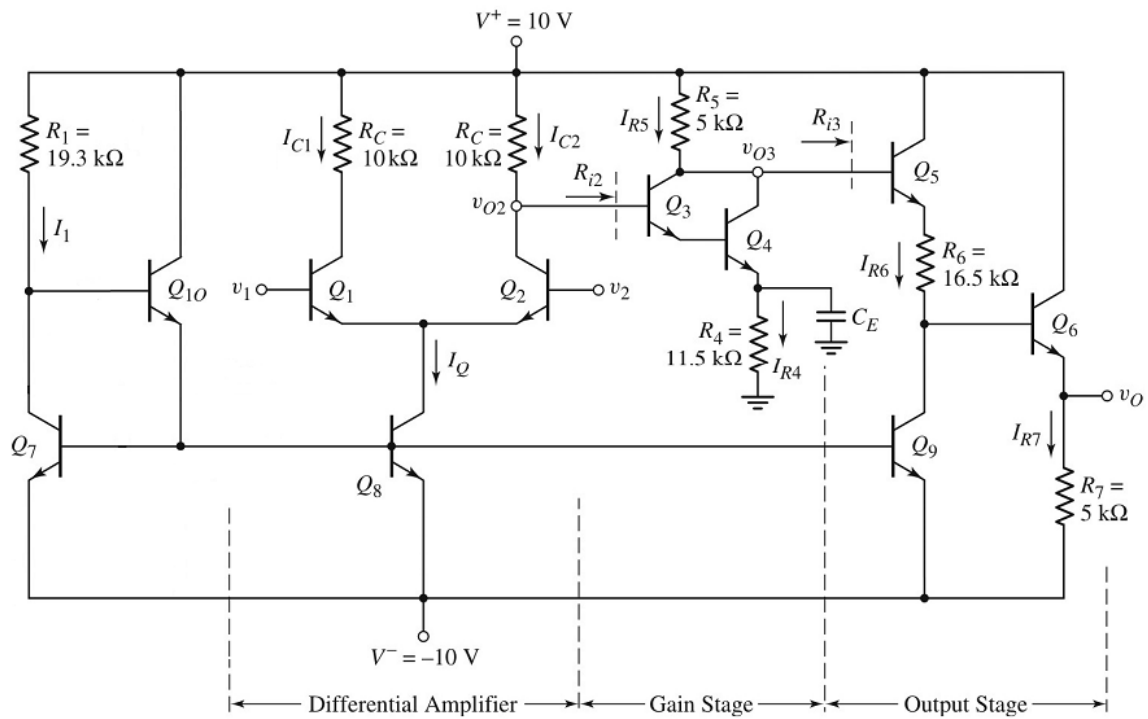


Figure 3

Figure 3 shows a design for a simple bipolar op-amp. The biasing for amplifiers in the circuit is provided by **three-transistor current sources**. The measured current through R_6 is **0.42 mA**. Study the figure carefully. **Neglect base currents**. Assume $V_{BE(\text{on})} = 0.7\text{ V}$ for all transistors.

Calculate I_1 , I_Q , I_{C2} , v_{O2} , v_{O3} , and v_O . Show all your calculation clearly in order to get full marks. [40 marks]

Answers for Question 3

Answers for Question 3 (Cont.)

$$I_1 = (V^+ - V_{BE10} - V_{BE7} - V^-) / (R_1) \quad [4]$$

$$= (10 - 0.7 - 0.7 - (-10)) / (19.3k) = 0.9637 \text{ mA} \quad [2]$$

$$\text{Neglect base current, } I_Q = I_1 = 0.9637 \text{ mA} \quad [3]$$

$$I_{C2} = I_Q / 2 = 0.4818 \text{ mA} \quad [3]$$

$$v_{O2} = V^+ - I_{C2} R_C = 10 - (0.4818\text{m})(10k) = 5.182 \text{ V} \quad [5]$$

$$I_{R4} = (v_{O2} - 2 V_{BE(\text{on})}) / (R_4) \quad [4]$$

$$= (5.182 - 1.4) / (11.5k) = 0.3288 \text{ mA} \quad [3]$$

$$I_{R5} \approx I_{R4} \text{ (neglecting base currents)} = 0.3288 \text{ mA} \quad [3]$$

$$v_{O3} = V^+ - I_{R5} R_5 = 10 - (0.3288\text{m})(5k) = 8.356 \text{ V} \quad [4]$$

$$I_{R7} = (v_{O3} - 2V_{BE(\text{on})} - I_{R6} R_6 + 10) / (R_7) \quad [3]$$

$$= (8.356 - 1.4) - (0.42\text{m})(16.5k) + 10 / (5k) = 2.005 \text{ mA} \quad [2]$$

$$v_O = -10 + I_{R7} R_7 = -10 + (2.005\text{m})(5k) = 0.026 \text{ V} \quad [4]$$