



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION
SEMESTER 2 2013 / 2014**

PROGRAMME : **Bachelor of Electrical & Electronics Engineering (Honours)**
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : **EEEB273**

SUBJECT : **ELECTRONIC ANALYSIS AND DESIGN II**

DATE : **January 2014**

TIME : **3 hours**


INSTRUCTIONS TO CANDIDATES:

1. This paper contains **Six (6)** questions in **Ten (10)** pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided.
4. Write answer to different question on a **new page**.
5. For all calculations, assume that $V_T = 26 \text{ mV}$.
6. Use at least **4 significant numbers** in all calculations.

MODEL ANSWERS

THIS QUESTION PAPER CONSISTS OF TEN (10) PRINTED PAGES INCLUDING THIS COVER PAGE.

Question 1 [20 marks]

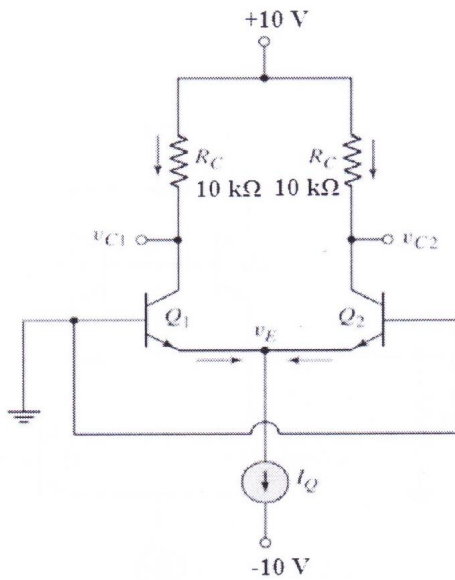


Sketch and label of complete figure [5 marks]

- As $V_{C1} = V_{C2} = 4 \text{ V}$, and $I_Q = 1.2 \text{ mA}$,
 Using KVL rule, $V^+ - I_{C1}R_C = V_{C1} = 4 \text{ V}$ [4]
 $I_Q = I_{C1} + I_{C2} = 1.2 \text{ mA}$ [2]
 $\Rightarrow I_{C1} = I_{C2} = 1.2\text{m}/2 = 0.6 \text{ mA}$ [2]
 Substituting I_{C1} , $(10) - (0.6)R_C = 4 \Rightarrow R_C = 10 \text{ k}\Omega$ [2]
- Assuming that $v_{B1} = v_{B2} = 0 \text{ V}$ [1]
 $v_{cm} = (v_{B1} + v_{B2})/2 = 0 \text{ V}$ [1]
 $v_d = v_{B1} - v_{B2} = 0 \text{ V}$ [1]
- $V_E = v_{B1} \text{ ó } V_{BE(\text{on})} = 0 - 0.7 = -0.7 \text{ V}$ [2]

Question 2 [15 marks]

(a)

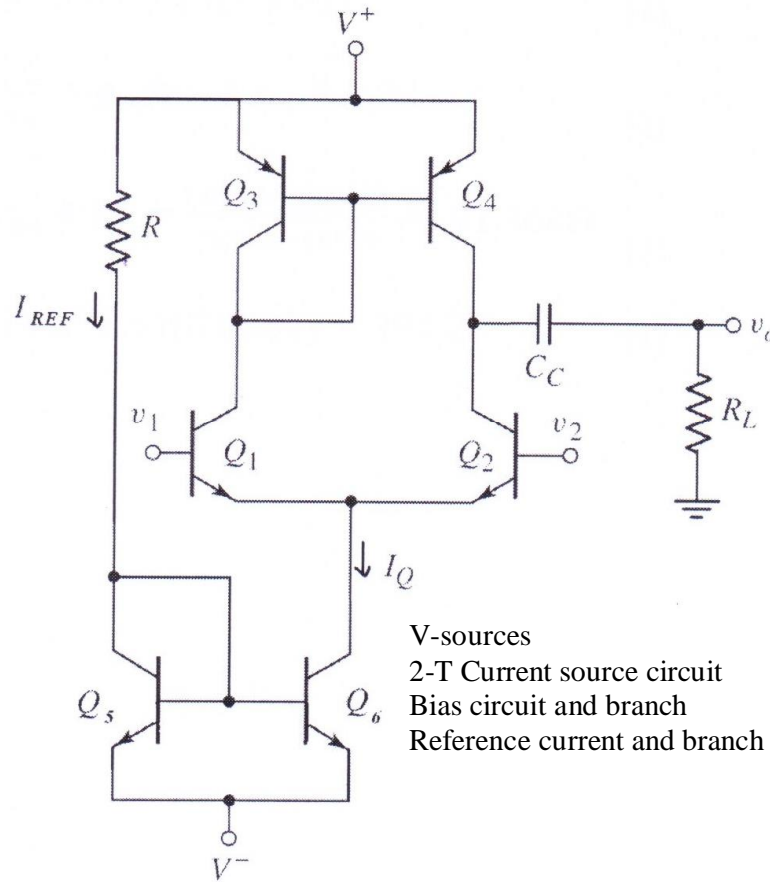

- V-sources [1 mark]
- 2-T Current source circuit [2 marks]
- Bias circuit and branch [1 mark]
- Reference current and branch [1 mark]

(b) The equation used is $v_o = g_m v_d (r_{o2} || r_{o4})$

$$A_d = \frac{v_o}{v_d} = g_m (r_{o2} || r_{o4}) \quad [1 \text{ mark}]$$

$$g_m = \frac{I_Q/2}{V_T} = \frac{0.25\text{m}/2}{0.026} = 4.808 \text{ mA/V} \quad [1 \text{ mark}]$$

$$r_{o2} = \frac{V_{AN}}{I_Q/2} = \frac{120}{0.125\text{m}} = 960 \text{ k}\Omega \quad [1 \text{ mark}]$$

$$r_{o4} = \frac{V_{AP}}{I_Q/2} = \frac{100}{0.125\text{m}} = 800 \text{ k}\Omega \quad [1 \text{ mark}]$$

$$(r_{o2} || r_{o4}) = \frac{(960\text{k})(800\text{k})}{(960 + 800)\text{k}} \Rightarrow 436.4 \text{ k}\Omega \quad [1 \text{ mark}]$$

∴ Substituting for the terms,

$$A_d = \frac{v_o}{v_d} = (4.808 m)(436.4 k) = 2098 \quad [1 \text{ mark}]$$

(c) $v_o = g_m v_d (r_{o2} || r_{o4} || R_L)$ is used. [1 mark]

$$A_d = \frac{v_o}{v_d} = g_m (r_{o2} || r_{o4} || R_L) \quad [1 \text{ mark}]$$

$$(r_{o2} || r_{o4} || R_L) \Rightarrow \frac{(436.4k)(100)k}{(436.4 + 100)k} = 81.36 k\Omega \quad [1 \text{ mark}]$$

$$A_d = (4.808m)(81.36k) = 391.2 \quad [1 \text{ mark}]$$

Question 3 [10 marks]

- (a) From voltage transfer characteristics of complementary push-pull output stage in Class B, both transistors are cut off and v_O is 0 in the dead band portion. [1.5marks]

A not perfect sinusoidal signal means that crossover distortion is produced by the dead band region. [1.5marks]

(b) (i) $i_{Cn} = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \Rightarrow V_{BE} = V_T \ln\left(\frac{i_{Cn}}{I_S}\right) = (0.026) \ln\left(\frac{10^{-3}}{2 \times 10^{-15}}\right) = 0.7004 \text{ V}$ [1 mark]
 $V_{BB} = 2V_{BE} = 1.40077 \text{ V}$ [1 mark]

(ii) For $v_o = -3.5 \text{ V}$, $i_{Cp} \cong \frac{3.5}{1} = 3.5 \text{ mA} \cong i_L$ [0.5 mark]
 $v_{EB} = (0.026) \ln\left(\frac{3.5 \times 10^{-3}}{2 \times 10^{-15}}\right) = 0.732957 \text{ V}$ [0.5 mark]
 $v_{BE} = 1.40077 - 0.732957 = 0.66781 \text{ V}$ [0.5 mark]
 $i_{Cn} = (2 \times 10^{-15}) \exp\left(\frac{0.66781}{0.026}\right) \Rightarrow i_{Cn} = 0.2857 \text{ mA}$ [0.5 mark]

Then $i_{Cp} \cong 0.2857 + 3.5 = 3.7857 \text{ mA}$
 $v_{EB} = (0.026) \ln\left(\frac{3.7857 \times 10^{-3}}{2 \times 10^{-15}}\right) = 0.734997 \text{ V}$
 $v_{BE} = 1.40077 - 0.734997 = 0.66577 \text{ V}$ [0.5 mark]
 $i_{Cn} = (2 \times 10^{-15}) \exp\left(\frac{0.66577}{0.026}\right) \Rightarrow i_{Cn} = 0.2642 \text{ mA}$
 $i_{Cp} = 3.5 + 0.2642 = 3.764 \text{ mA}$
 $v_I = v_o - v_{EB} + \frac{V_{BB}}{2} = -3.5 - 0.735 + 0.7004 = -3.535 \text{ V}$ [0.5 mark]

- (iii) The power dissipated in R_L ,
 $P_{RL} = i_L^2 R_L = (3.5)^2 (1k) = 12.25 \text{ mW}$ [2 marks]

Question 4 [20 marks]

(i)

$$\begin{aligned}
 I_{D3} &= (k'_p/2)(W/L)_3(V_{SG3} + V_{TP})^2 \\
 150\mu &= (40\mu/2)(50)(V_{SG3} - 0.4)^2 && [1] \\
 V_{SG3} &= \mathbf{0.7873 \text{ V}} && [0.5] \\
 R_{D1} &= V_{SG3} / I_{D1} = V_{SG3} / (I_Q/2) && [1] \\
 &= 0.7873 / (200\mu/2) && = \mathbf{7.87 \text{ k}\Omega} && [0.5]
 \end{aligned}$$

$$\begin{aligned}
 I_{D4} &= (k'_n/2)(W/L)_4(V_{GS4} - V_{TN})^2 \\
 200\mu &= (100\mu/2)(40)(V_{GS4} - 0.4)^2 && [1] \\
 V_{GS4} &= \mathbf{0.7162 \text{ V}} && [0.5] \\
 V_{G4} &= V_O + V_{GS4} = 0 + 0.7162 && = \mathbf{0.7162 \text{ V}} && [1] \\
 R_{D2} &= (V_{G4} - (V)) / I_{D3} && [1] \\
 &= (0.7162 - (-3.5)) / (150\mu) && = \mathbf{28.108 \text{ k}\Omega} && [0.5]
 \end{aligned}$$

$$\begin{aligned}
 R_S &= (V_O - (V)) / I_{D4} && [1] \\
 &= (0 - (-3.5)) / (200\mu) && = \mathbf{17.5 \text{ k}\Omega} && [1]
 \end{aligned}$$

(ii)

$$\begin{aligned}
 A_{d1} &= (g_{m1} R_{D1})/2 && [1] \\
 g_{m1} &= 2 \text{ SQRT}[(k'_n/2)(W/L)_1(I_Q/2)] && [1] \\
 &= 2 \text{ SQRT}[(100\mu/2)(20)(200\mu/2)] && = \mathbf{0.6325 \text{ mA/V}} && [1] \\
 A_{d1} &= ((0.6325\text{m})(7.87\text{k}))/2 && = \mathbf{2.49 \text{ V/V}} && [1]
 \end{aligned}$$

(iii)

$$\begin{aligned}
 A_2 &= -g_{m3} R_{D2} && [0.5] \\
 g_{m3} &= 2 \text{ SQRT}[(k'_p/2)(W/L)_3(I_{D3})] && [1] \\
 &= 2 \text{ SQRT}[(40\mu/2)(50)(150\mu)] && = \mathbf{0.7746 \text{ mA/V}} && [0.5] \\
 A_2 &= -(0.7746\text{m})(28.108\text{k}) && = \mathbf{-21.772 \text{ V/V}} && [1]
 \end{aligned}$$

(iv)

$$\begin{aligned}
 A_3 &= \mathbf{1} && (\text{assume}) && [1] \\
 A_v &= A_{d1} \times A_2 \times A_3 && [2] \\
 &= (2.49) \times (-21.772) \times (1) && = \mathbf{-47.8 \text{ V/V}} && [1]
 \end{aligned}$$

Question 5 [15 marks]

$$R_{i2} = r_{\pi16} + (1 + \beta_n)R'_E \quad [1]$$

$$R'_E = R_9 \parallel [r_{\pi17} + (1 + \beta_n)R_8] \quad [1]$$

$$r_{\pi17} = \frac{\beta_n V_T}{I_{C17}} = \frac{(200)(0.026)}{0.54\text{mA}} = 9.63 \text{ k}\Omega \quad [1]$$

$$\Rightarrow R'_E = 50\text{k} \parallel [9.63\text{k} + (1 + 200)(0.1\text{k})] = 18.6 \text{ k}\Omega \quad [0.5]$$

$$r_{\pi16} = \frac{\beta_n V_T}{I_{C16}} = \frac{(200)(0.026)}{15.8} = 329 \text{ k}\Omega \quad [1]$$

$$\Rightarrow R_{i2} = 329\text{k} + (201)(18.6\text{k}) = 4.07 \text{ M}\Omega \quad [0.5]$$

$$R_{i3} = r_{\pi22} + (1 + \beta_p)[R_{19} \parallel R_{20}]$$

$$r_{\pi22} = \frac{\beta_p V_T}{I_{C13A}} = \frac{(50)(0.026)}{0.18\text{mA}} = 7.22 \text{ k}\Omega \quad [1]$$

$$r_{\pi20} = \frac{\beta_p V_T}{I_{C20}} = \frac{(50)(0.026)}{0.138\text{mA}} = 9.42 \text{ k}\Omega \quad [1]$$

$$R_{20} = r_{\pi20} + (1 + \beta_p)R_L$$

$$R_{20} = 9.42\text{k} + (51)(2\text{k}) \cong 111 \text{ k}\Omega \quad [1]$$

$$R_{19} = r_{o13A} = \frac{V_A}{I_{C13A}} = \frac{50}{0.18\text{mA}} = 278 \text{ k}\Omega \quad [1]$$

$$\Rightarrow R_{i3} = 7.22\text{k} + (51)[278\text{k} \parallel 111\text{k}] = 4.05 \text{ M}\Omega \quad [1]$$

$$R_{o17} \cong r_{o17} = \frac{V_A}{I_{C17}} = \frac{50}{0.54\text{mA}} = 92.6 \text{ k}\Omega \quad [1]$$

$$R_{act2} = r_{o13B} = \frac{V_A}{I_{C13B}} = \frac{50}{0.54\text{mA}} = 92.6 \text{ k}\Omega \quad [1]$$

$$A_{v2} = \frac{-\beta_n(1 + \beta_n)R_9(R_{act2} \parallel R_{i3} \parallel R_{o17})}{R_{i2}\{R_9 + [r_{\pi17} + (1 + \beta_n)R_8]\}}$$


$$A_{v2} = \frac{-(200)(201)(50\text{k})(92.6\text{k} \parallel 4.05\text{M} \parallel 92.6\text{k})}{4.07\text{M}\{50\text{k} + [9.63\text{k} + (201)(0.1\text{k})]\}} \quad [2]$$

$$A_{v2} = -285 \quad [1]$$


Question 6 [20 marks]

(a) Can state and draw 3 of the following applications:


Summing amplifier [1]

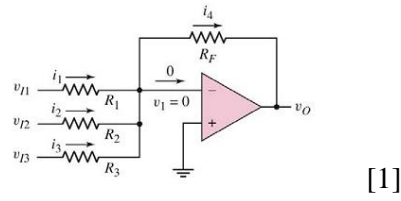


Current to voltage converter [1]

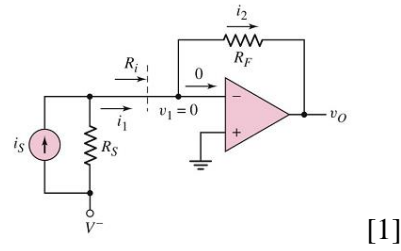


Voltage to current converter [1]

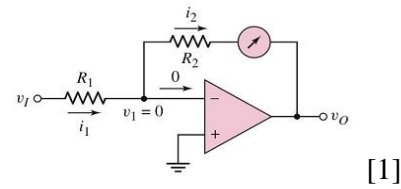


Difference amplifier [1]

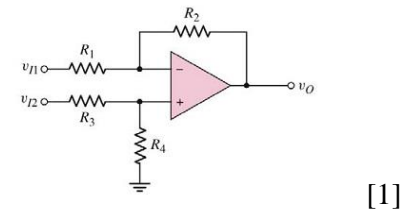


Instrumentation amplifier [1]

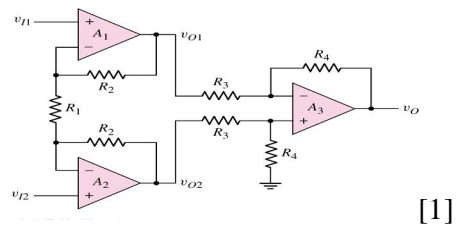


Integrator [1]

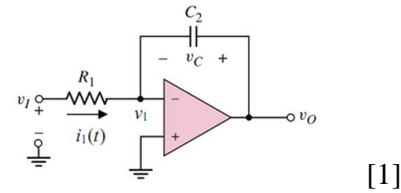

Differentiator [1]

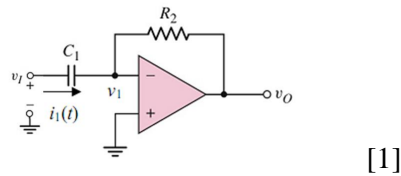

(b)

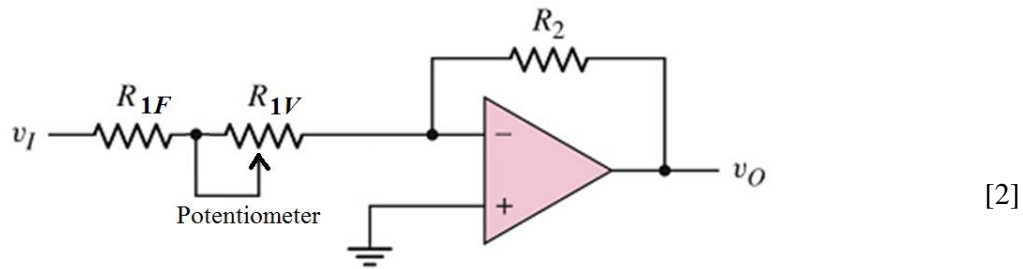

[2]

$$A_v = -R_2 / (R_{1F} + R_{1V}) \quad [1]$$

$R_2 = 200 \text{ k}$. R_{1F} is a constant value resistor.

R_{1V} is a potentiometer. Gain is maximum, i.e. -25, when $R_{1V} = 0$.

$$A_{v1} = -25 = -R_2 / (R_{1F} + R_{1V}) = -200\text{k} / (R_{1F} + 0) \quad [2]$$

$$R_{1F} = 8 \text{ k} \quad [0.5]$$

$$A_{v2} = -10 = -R_2 / (R_{1F} + R_{1V}) = -200\text{k} / (8\text{k} + R_{1V}) \quad [2]$$

$$R_{1V} = 12 \text{ k} \quad [0.5]$$

(c)

$$i_1 = \frac{v_{I1} - v_{I2}}{R_1} = \frac{(0.60 - 0.30 \sin \omega t) - (0.60 + 0.30 \sin \omega t)}{20\text{k}} \quad [1]$$

$$\Rightarrow i_1 = \frac{-0.60 \sin \omega t}{20\text{k}} = -0.030 \sin \omega t \text{ (mA)} \quad [0.5]$$

$$v_{O1} = i_1 R_2 + v_{I1} = (-0.030 \sin \omega t \text{ (mA)})(115\text{k}) + (0.60 - 0.30 \sin \omega t \text{ (V)}) \quad [1]$$

$$\Rightarrow v_{O1} = 0.60 - 3.75 \sin \omega t \text{ (V)} \quad [0.5]$$

$$v_{O2} = -i_1 R_2 + v_{I2} = -(-0.030 \sin \omega t \text{ (mA)})(115\text{k}) + (0.60 + 0.30 \sin \omega t \text{ (V)}) \quad [1]$$

$$\Rightarrow v_{O2} = 0.60 + 3.75 \sin \omega t \text{ (V)} \quad [0.5]$$

$$v_O = (R_4 / R_3)(v_{O2} - v_{O1}) = (200\text{k} / 50\text{k})[(0.60 + 3.75 \sin \omega t) - (0.60 - 3.75 \sin \omega t)] \quad [1]$$

$$\Rightarrow v_O = (200\text{k} / 50\text{k})(7.5 \sin \omega t) = 30 \sin \omega t \text{ (V)} \quad [0.5]$$

Other solution :

$$v_{O1} = (1 + R_2 / R_1)v_{I1} - (R_2 / R_1)v_{I2} = 0.60 - 3.75 \sin \omega t \text{ (V)} \quad [2]$$

$$v_{O2} = (1 + R_2 / R_1)v_{I2} - (R_2 / R_1)v_{I1} = 0.60 + 3.75 \sin \omega t \text{ (V)} \quad [2]$$

$$v_O = (R_4 / R_3)(1 + 2R_2 / R_1)(v_{I2} - v_{I1}) = 30 \sin \omega t \text{ (V)} \quad [2]$$