



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION
SEMESTER 2 2013 / 2014**

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : January 2014

TIME : 3 hours

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **Six (6)** questions in **Nine (9)** pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided. Use **pen** to write your answer.
4. Write answer to different question on a **new page**.
5. For all calculations, assume that $V_T = 26 \text{ mV}$.

THIS QUESTION PAPER CONSISTS OF NINE (9) PRINTED PAGES INCLUDING THIS COVER PAGE.

Question 1 [20 marks]

You are required to design a differential amplifier with passive load using **NPN bipolar junction transistors (BJT)** with the following specifications. You **DO NOT** need to design the biasing circuit for the differential amplifier.

Two-transistor NPN BJT current source is biasing a **1.2 mA** constant current. The circuit parameters are power supplies of **+10 V** and **-10 V**. The voltages measured at v_{C1} and v_{C2} of the differential amplifier are **4 Volts**.

The transistors parameters are matched NPN BJTs with $\beta = 50$, $V_{BE(\text{on})} = 0.7 \text{ V}$, and $V_A = \infty$, and various resistors with precise values are made available.

Design the differential amplifier described above with its biasing circuit. **Draw and label** the circuit diagram of your design clearly. **Show all calculations** and values as accurate as possible with regard to the design. Based on your assumption for the design, **calculate** the values for v_d , v_{cm} , and V_E (i.e. voltage at a point where emitters for both transistors in the differential amplifier are connected).

[20 marks]

Question 2 [15 marks]

Figure 2 shows a basic differential amplifier. A two-transistor current source is used to bias a constant current source of **0.25 mA** (Note: $I_Q = 0.25 \text{ mA}$). The differential amplifier is using a **pair of PNP transistors as its active load**. The output voltage, v_O , of the differential amplifier is taken as v_{C2} .

The transistors parameters are: $\beta = 150$, $V_{BE(\text{on})} = V_{EB(\text{on})} = 0.7 \text{ V}$, $V_{AN} = 120 \text{ V}$, and $V_{AP} = 100 \text{ V}$.

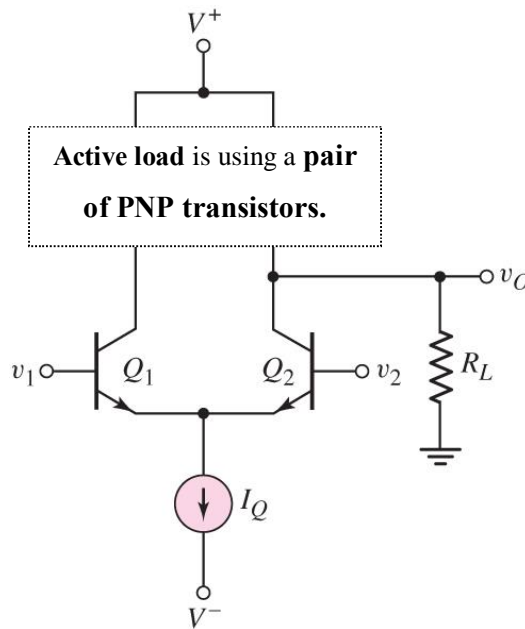


Figure 2

- (a) **Draw** a complete differential amplifier circuit including the pair of PNP transistors as active load and the two-transistor current source as biasing circuit.

[5 marks]

- (b) **Determine** the differential-mode voltage gain of the circuit, $A_d = v_O/v_d$.

[6 marks]

- (c) **Calculate** the differential-mode voltage gain if the load resistance, R_L , is **100 k Ω** .

[4 marks]

Question 3 [10 marks]

- (a) **Describe** the operation of a **class-B** output stage by means of crossover distortion. [3 marks]
- (b) A **class-AB** output stage with BJTs is shown in **Figure 3**. Reverse saturation current for each transistor is $I_S = 2 \times 10^{-15}$ A.
- (i) **Find** V_{BB} when $v_I = 0$, as such producing $i_{Cn} = i_{Cp} = 1$ mA. [2 marks]
- (ii) **Calculate** i_{Cn} , i_{Cp} , and v_I to obtain $v_O = -3.5$ V. [3 marks]
- (iii) **Calculate** the power dissipated in R_L . [2 marks]

 


Figure 3

Question 4 [20 marks]

A MOSFET op-amp circuit as shown in **Figure 4** is biased with $I_Q = 200 \mu\text{A}$. The transistor parameters are $k'_n = 100 \mu\text{A}/\text{V}^2$, $k'_p = 40 \mu\text{A}/\text{V}^2$, $V_{TN} = 0.4 \text{ V}$, $V_{TP} = -0.4 \text{ V}$, and $\lambda_n = \lambda_p = 0$. The transistor aspect ratios are $(W/L)_1 = (W/L)_2 = 20$, $(W/L)_3 = 50$, and $(W/L)_4 = 40$.

- (i) **Design** the circuit such that $I_{D3} = 150 \mu\text{A}$, $I_{D4} = 200 \mu\text{A}$, and $v_o = 0$ for $v_1 = v_2 = 0 \text{ V}$. [9 marks]
- (ii) **Find** the differential voltage gain (A_d) of the differential amplifier in the circuit. [4 marks]
- (iii) **Determine** the voltage gain for the gain stage (A_2), **made up by transistor M_3** , in the circuit. A_2 can be calculated using $A_2 = -g_{m3} R_{D2}$. [3 marks]
- (iv) **Calculate** the overall small-signal voltage gain (A_v) of the multi-stage amplifier circuit. You may assume value for the voltage gain of the output stage (A_3) **made up by transistor M_4** . [4 marks]

 


Figure 4

Question 5 [15 marks]

Consider a **standard 741 operational amplifier** (op-amp) circuit as shown in **Figure 5a**. Study **Figure 5a** carefully and observe the values for resistors in the circuit. Load resistance connected to the Output of the 741 op-amp is $R_L = 2 \text{ k}\Omega$. The op-amp is supplied by $\pm 15 \text{ V DC}$ voltages.

The transistors have $\beta_n = 200$, $\beta_p = 50$, $V_{AN} = V_{AP} = 50 \text{ V}$, $V_{BE(\text{on})} = V_{EB(\text{on})} = 0.6 \text{ V}$, and the reverse saturation current $I_S = 5 \times 10^{-16} \text{ A}$.

From **DC analysis**, bias currents for selected transistors are $I_{C13A} = 0.18 \text{ mA}$, $I_{C13B} = 0.54 \text{ mA}$, $I_{C16} = 15.8 \mu\text{A}$, $I_{C17} = 0.54 \text{ mA}$, $I_{C20} = 0.138 \text{ mA}$, and $I_{C22} = 0.18 \text{ mA}$.

Figure 5b shows the AC equivalent circuit for the gain stage of the 741 op-amp. **Figure 5c** shows the AC equivalent circuit for the output stage of the 741 op-amp, which is used to determine R_{i3} in the **Figure 5b**.

With analysis, the voltage gain for the gain stage (A_{v2}) of the 741 op-amp can be calculated using the following formula:

$$A_{v2} = \frac{v_{o2}}{v_{o1}} = \frac{-\beta_n (1 + \beta_n) R_9 (R_{act2} \parallel R_{i3} \parallel R_{o17})}{R_{i2} \{R_9 + [r_{\pi 17} + (1 + \beta_n) R_8]\}}$$

Where: $R_{act2} = r_{o13B}$

$$R_{i3} = r_{\pi 22} + (1 + \beta_p) [R_{19} \parallel R_{20}]$$

$$R_{19} \cong R_{13A} = r_{o13A}$$

$$R_{20} = r_{\pi 20} + (1 + \beta_p) R_L$$

Calculate the voltage gain for the gain stage (A_{v2}) of the 741 op-amp. Neglect base current in your calculations.

[15 marks]

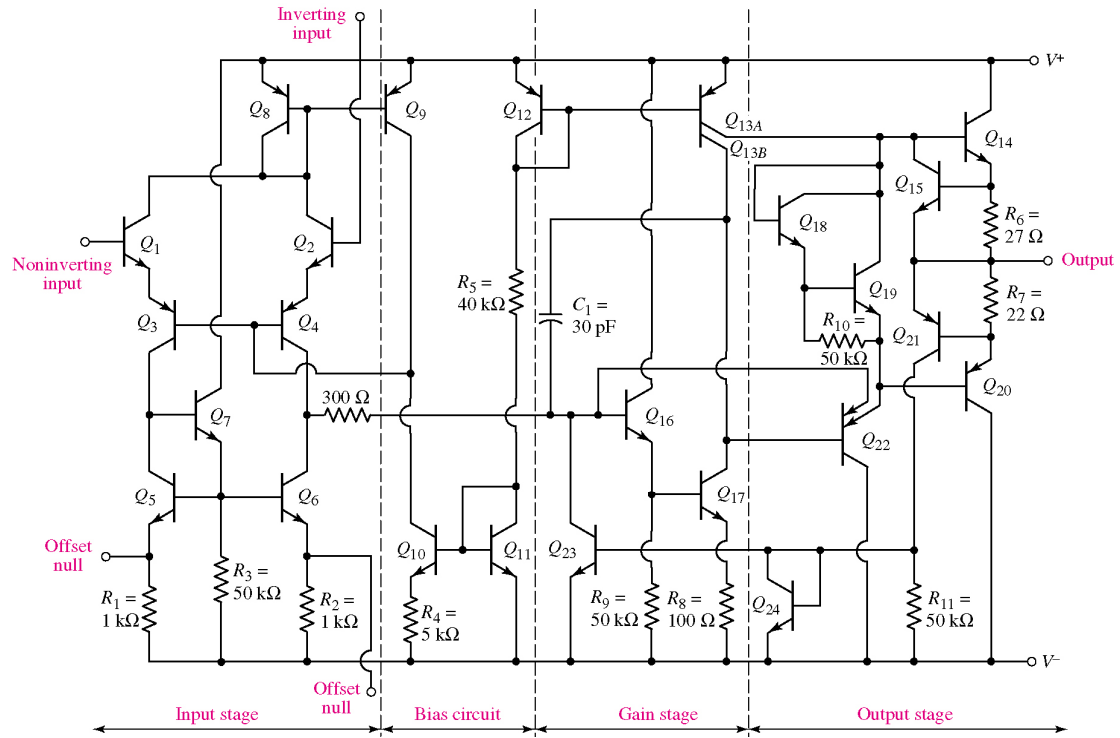


Figure 5a

 


Figure 5b

 


Figure 5c

Question 6 [20 marks]

(a) **EXCEPT** for standard inverting and non-inverting amplifier circuits using op-amp, **state three (3) other applications using the op-amp** and **sketch** those three (3) other op-amp based circuits. You are required to sketch the circuit to include all external components connected to the op-amp, in order for the overall circuit to function its intended application.

[6 marks]

(b) With a feedback resistor of 200 kΩ, **design** an amplifier using op-amp with a **closed-loop gain** which can be **varied between -10 to -25** using a **potentiometer**. **Draw clearly** your circuit design.

[6 marks]

(c) For the instrumentation amplifier shown in **Figure 6**, the circuit parameters are $R_1 = 20 \text{ k}\Omega$, $R_2 = 115 \text{ k}\Omega$, $R_3 = 50 \text{ k}\Omega$, and $R_4 = 200 \text{ k}\Omega$. For input signals of $v_{I1} = 0.60 - 0.30 \sin \omega t \text{ (V)}$ and $v_{I2} = 0.60 + 0.30 \sin \omega t \text{ (V)}$, **determine** v_{O1} , v_{O2} , and v_O .

[8 marks]

 


Figure 6

-END OF QUESTION PAPER-

APPENDIX

BASIC FORMULABJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{PNP}$$

$$i_C = \beta i_B = \alpha i_E$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$