

Question:

Refer to Figure 1.

(a) **Show** that the gain for the circuit is given by: **[6 marks]**

$$A_V = \frac{v_O}{v_I} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right)$$

(b) **Calculate** A_V when $R_1 = 50 \text{ k}\Omega$, $R_2 = 200 \text{ k}\Omega$, $R_3 = 40 \text{ k}\Omega$, and $R_4 = 20 \text{ k}\Omega$. **[4 marks]**

Show clearly all calculations in order to get full marks.

(a)

$$v_O = \left(1 + \frac{R_2}{R_1}\right) v_1 \quad [1]$$

$$v_1 = v_2 = \frac{R_4}{R_3 + R_4} v_I = \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_I \quad [2]$$

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_I \quad [2]$$

$$A_V = \frac{v_O}{v_I} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) \quad [1]$$

(b)

$$A_V = \frac{v_O}{v_I} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) \quad [1]$$

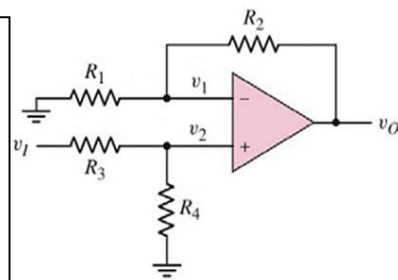
$$A_V = \left(1 + \frac{200k}{50k}\right) \left(\frac{20k / 40k}{1 + 20k / 40k}\right) = 1.67 \text{ V/V} \quad [2, 1]$$


Figure 1

EEEE273 - Quiz 4
 SEMESTER 2, ACADEMIC YEAR 2013/2014
 Date: 15 January 2014 Time: 15 minutes

Question:

Refer to Figure 1.

(c) **Show** that the output for the circuit is given by:

[6 marks]

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_I$$

(d) Calculate v_O when $R_1 = 50 \text{ k}\Omega$, $R_2 = 200 \text{ k}\Omega$, $R_3 = 20 \text{ k}\Omega$, $R_4 = 40 \text{ k}\Omega$, and $v_I = 0.01 \text{ V}$.

[4 marks]

Show clearly all calculations in order to get full marks.

(a)

$$v_O = \left(1 + \frac{R_2}{R_1}\right) v_1 \quad [1]$$

$$v_1 = v_2 = \frac{R_4}{R_3 + R_4} v_I = \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_I \quad [1, 2]$$

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_I \quad [2]$$

(b)

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_I \quad [1]$$

$$v_O = \left(1 + \frac{200k}{50k}\right) \left(\frac{40k / 20k}{1 + 40k / 20k}\right) 0.01 = 0.033 \text{ V} \quad [2, 1]$$

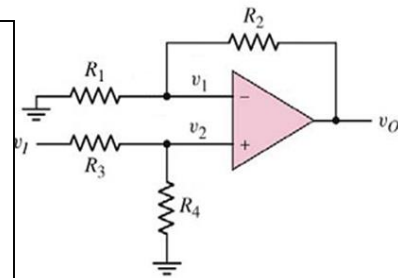


Figure 1

EEEE273 - Quiz 4
 SEMESTER 2, ACADEMIC YEAR 2013/2014
 Date: 15 January 2014 Time: 15 minutes

Question:

Refer to Figure 1.

(e) Show that the gain for the circuit is given by:

[6 marks]

$$A_V = \frac{v_O}{v_I} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right)$$

(f) Calculate v_O when $R_1 = 50 \text{ k}\Omega$, $R_2 = 200 \text{ k}\Omega$, $R_3 = 40 \text{ k}\Omega$, $R_4 = 20 \text{ k}\Omega$, and $v_I = -0.05 \text{ V}$.

[4 marks]

Show clearly all calculations in order to get full marks.

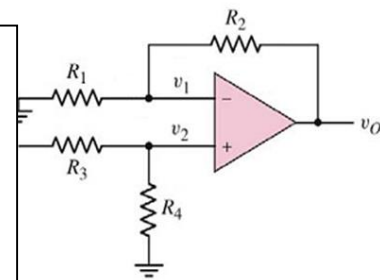


Figure 1

(a)

$$v_O = \left(1 + \frac{R_2}{R_1}\right) v_1 \quad [1]$$

$$v_1 = v_2 = \frac{R_4}{R_3 + R_4} v_I = \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_I \quad [2]$$

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_I \quad [2]$$

$$A_V = \frac{v_O}{v_I} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) \quad [1]$$

(b)

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_I \quad [1]$$

$$v_O = \left(1 + \frac{200k}{50k}\right) \left(\frac{20k / 40k}{1 + 20k / 40k}\right) (-0.05) = -0.083 \text{ V} \quad [2, 1]$$

Question:

Refer to Figure 1.

(g) **Show** that the output for the circuit is given by:

[6 marks]

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_I$$

(h) **Calculate** v_I when $R_1 = 50 \text{ k}\Omega$, $R_2 = 200 \text{ k}\Omega$, $R_3 = 40 \text{ k}\Omega$, $R_4 = 20 \text{ k}\Omega$, and $v_O = -2.35 \text{ V}$.

[4 marks]

Show clearly all calculations in order to get full marks.

(a)

$$v_O = \left(1 + \frac{R_2}{R_1}\right) v_1 \quad [1]$$

$$v_1 = v_2 = \frac{R_4}{R_3 + R_4} v_I = \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_I \quad [1, 2]$$

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_I \quad [2]$$

(b)

$$v_I = v_O / \left(\left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right)\right) \quad [1]$$

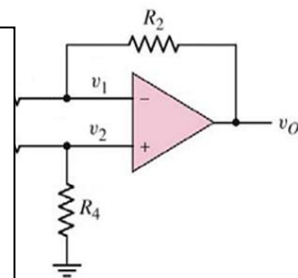
$$v_I = (-2.35) / \left(\left(1 + \frac{200k}{50k}\right) \left(\frac{20k/40k}{1 + 20k/40k}\right)\right) = -1.41 \text{ V} \quad [2, 1]$$


Figure 1