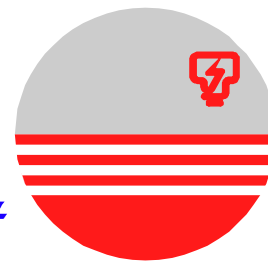


Name:
Student ID Number:
Section: 01/02/03 A/B
Lecturer: Dr Jamaludin /Mdm Jehana

**UNIVERSITI
TENAGA
NASIONAL**



College of Engineering
Department of Electronics and Communication Engineering

Test 1 - MODEL ANSWERS

SEMESTER 2, ACADEMIC YEAR 2013/2014

Subject Code : **EEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **14 November 2013**
Time Allowed : **1 hour 15 minutes**

Instructions to the candidates:

1. Write your Name and Student ID number. Circle your section number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**
5. For BJT, use $V_T = 26 \text{ mV}$ where appropriate.
6. Use at least **4 significant numbers** in all calculations.

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!



Question No.	1	2	Total
Marks			

FORMULA FOR TRANSISTORS

BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{PNP}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

; Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

Question 1 [65 marks]

You are assigned to analyze the following BJT current sources: **Three-transistor current source, Wilson current source, and Cascode current source**. All NPN transistors in the given current sources are matched. The transistor parameters are: $\beta = 50$, $V_{BE(on)} = 0.6 \text{ V}$, and $V_A = 150 \text{ V}$. The circuit parameters for the current sources are: $V^+ = 12 \text{ V}$, $V^- = -12 \text{ V}$, and $R_1 = 30 \text{ k}\Omega$.

- (a) Calculate reference current (I_{REF}), output current (I_O), and output resistance (R_O) for every BJT current source given above. Show clearly all calculations and do not forget to put proper Units for I_{REF} , I_O , and R_O . [45 marks]
- (b) Based on the value of R_O , which current source has the most stable I_O ? Give a reason for your answer. [5 marks]
- (c) What is the percent change in I_O as the output voltage of a particular current source changes by +3 V? [15 marks]

Answers for Question 1

Q1(a)

Three-transistor current source	Wilson current source	Cascode current source
$I_{REF} = (V^+ - 2 V_{BE} - V^-)/R_1$ $= (12 - 2 \times 0.6 - (-12))/(30\text{k})$ $= 0.76 \text{ mA}$ [2, 2, 1]	$I_{REF} = (V^+ - 2 V_{BE} - V^-)/R_1$ $= (12 - 2 \times 0.6 - (-12))/(30\text{k})$ $= 0.76 \text{ mA}$ [2, 2, 1]	$I_{REF} = (V^+ - 2 V_{BE} - V^-)/R_1$ $= (12 - 2 \times 0.6 - (-12))/(30\text{k})$ $= 0.76 \text{ mA}$ [2, 2, 1]
$I_O = I_{REF}/(1 + 2/(\beta(1+\beta)))$ $= (0.76\text{m})/(1+2/(50 \times 51))$ $= 0.7594 \text{ mA}$ [2, 2, 1]	$I_O = I_{REF}/(1 + 2/(\beta(2+\beta)))$ $= (0.76\text{m})/(1+2/(50 \times 52))$ $= 0.7594 \text{ mA}$ [2, 2, 1]	$I_O = I_{REF}/(1 + 4/\beta)$ $= (0.76\text{m})/(1+4/50)$ $= 0.7037 \text{ mA}$ [2, 2, 1]
$r_{O2} = V_A / I_O$ $= 150/(0.7594\text{m})$ $= 197.524 \text{ k}\Omega$ $R_O = r_{O2}$ $= 197.524 \text{ k}\Omega$ [1, 1, 1, 1, 1]	$r_{O3} = V_A / I_O$ $= 150/(0.7594\text{m})$ $= 197.524 \text{ k}\Omega$ $R_O = (\beta r_{O3})/2$ $= (50 \times 197.524\text{k})/2$ $= 4.9381 \text{ M}\Omega$ [1, 1, 1, 1, 1]	$r_{O4} = V_A / I_O$ $= 150/(0.7037\text{m})$ $= 213.159 \text{ k}\Omega$ $R_O = \beta r_{O4}$ $= 50 \times 206.89\text{k}$ $= 10.6579 \text{ M}\Omega$ [1, 1, 1, 1, 1]

[5 marks each box, Total 45 marks]

Answers for Question 1 (Cont.)**Q1(b)**

Cascode current source. [3]

Because with highest value for R_o makes change in I_o to be smallest and I_o most stable. [2]

Q1(c)

Three-transistor current source	Wilson current source	Cascode current source
$R_o = \Delta V_o / \Delta I_o$ $\Delta I_o = \Delta V_o / R_o$ $= (3)/(197.524k)$ $= 15.188 \text{ uA}$ $\% \Delta I_o = (\Delta I_o / I_o) \times 100\%$ $= (15.188\text{u}/0.7594\text{m}) \times 100\%$ $= 2 \%$ [1, 1, 1, 1, 1]	$R_o = \Delta V_o / \Delta I_o$ $\Delta I_o = \Delta V_o / R_o$ $= (3)/(4.9381M)$ $= 0.6075 \text{ uA}$ $\% \Delta I_o = (\Delta I_o / I_o) \times 100\%$ $= (0.6075\text{u}/0.7594\text{m}) \times 100\%$ $= 0.0799 \%$ [1, 1, 1, 1, 1]	$R_o = \Delta V_o / \Delta I_o$ $\Delta I_o = \Delta V_o / R_o$ $= (3)/(10.6579M)$ $= 0.2814 \text{ uA}$ $\% \Delta I_o = (\Delta I_o / I_o) \times 100\%$ $= (0.2814\text{u}/0.7037\text{m}) \times 100\%$ $= 0.0399 \%$ [1, 1, 1, 1, 1]

Question 2 [35 marks]

For a MOSFET current source circuit shown in **Figure 1**, transistor parameters are $V_{TN} = 0.7 \text{ V}$, $k'_n = 70 \mu\text{A/V}^2$, and $\lambda = 0.015 \text{ V}^{-1}$. The transistor aspect ratios are $(W/L)_1 = 20$, $(W/L)_2 = 12.5$, and $(W/L)_3 = 3$.

- (a) Determine V_{GS1} , V_{GS3} , I_{REF} , I_O , and V_{DS2} [25 marks]
- (b) Find I_O at $V_{DS2} = 2.5 \text{ V}$ [10 marks]

Answers for Question 2

(a)

$$I_{REF} = I_{D1} = \frac{k'_n}{2} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{TN})^2$$

$$I_{REF} = \frac{70\mu}{2} (20) (V_{GS1} - 0.7)^2$$

$$I_{REF} = I_{D3} = \frac{k'_n}{2} \left(\frac{W}{L} \right)_3 (V_{GS3} - V_{TN})^2$$

$$I_{REF} = \frac{70\mu}{2} (3) (V_{GS3} - 0.7)^2$$

$$V_{GS1} + V_{GS3} = V^+ - V^- = 5 - (-5) = 10 \text{ V}$$

$$V_{GS3} = 10 - V_{GS1}$$

$$20(V_{GS1} - 0.7)^2 = 3(10 - V_{GS1} - 0.7)^2$$

Solve the equation clearly to find

$$V_{GS1} = 3.1 \text{ V} \quad [2]$$

$$V_{GS3} = 10 - V_{GS1} = 10 - 3.1 = 6.9 \text{ V} \quad [1]$$

$$I_{REF} = I_{D1} = \frac{70\mu}{2} (20) (3.1 - 0.7)^2 = 4.032 \text{ mA} \quad [3]$$

$$V_{GS2} = V_{GS1} = 3.1 \text{ V} \quad [2]$$

$$I_O = I_{D2} = \frac{k'_n}{2} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{TN})^2 \quad [2]$$

$$I_O = \frac{70\mu}{2} (12.5) (3.1 - 0.7)^2 = 2.520 \text{ mA} \quad [3]$$

$$V_{DS2} = V_{DS1} = V_{GS1} = 3.1 \text{ V} \quad [2]$$

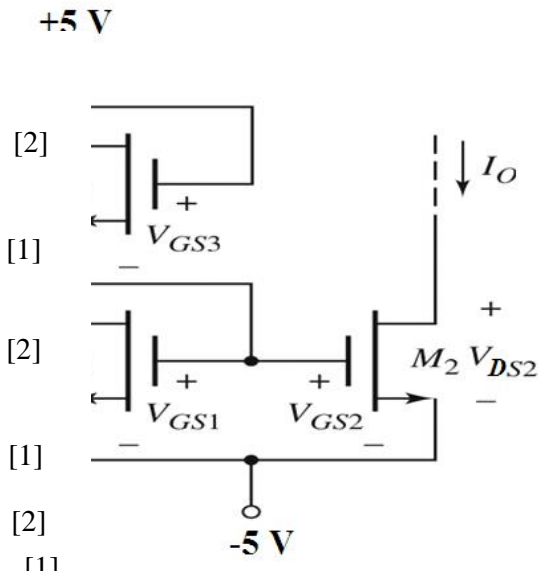


Figure 1

Answers for Question 2 (Cont.)

(b)

From part (a)

$$I_O = 2.520 \text{ mA at } V_{DS2} = 3.1 \text{ V} \quad [1]$$

$$R_O = 1/(\lambda I_O) = 1/(0.015 \times 2.520\text{m}) = 26.455 \text{ k}\Omega \quad [2, 1, 1]$$

At $V_{DS2} = 2.5 \text{ V}$,

$$\Delta I_O = V_{DS2}/R_O = (2.5 - 3.1)/R_O = -0.0226 \text{ mA} \quad [1, 1, 1]$$

$$\rightarrow I_O = 2.520\text{m} + (-0.0226\text{m}) = 2.4974 \text{ mA} \quad [2]$$